
ECE 428 Programmable ASIC Design

FPGA Microprocessor

Part 1


Haibo Wang
ECE Department
Southern Illinois University
Carbondale, IL 62901

Microprocessor *v.s.* ASIC

- ❑ For a given function, we can implement it by using a general purpose microprocessor or by designing an ASIC

Microprocessor	ASIC
<ul style="list-style-type: none">1. General purpose2. Flexible and easy to update by loading new software3. Typically, the performance is not optimized for a given task	<ul style="list-style-type: none">1. Application specific2. Less flexible and almost impossible to Update unless the ASIC contains programmable circuits3. Normally, optimal performance


How Does A Microprocessor Work?

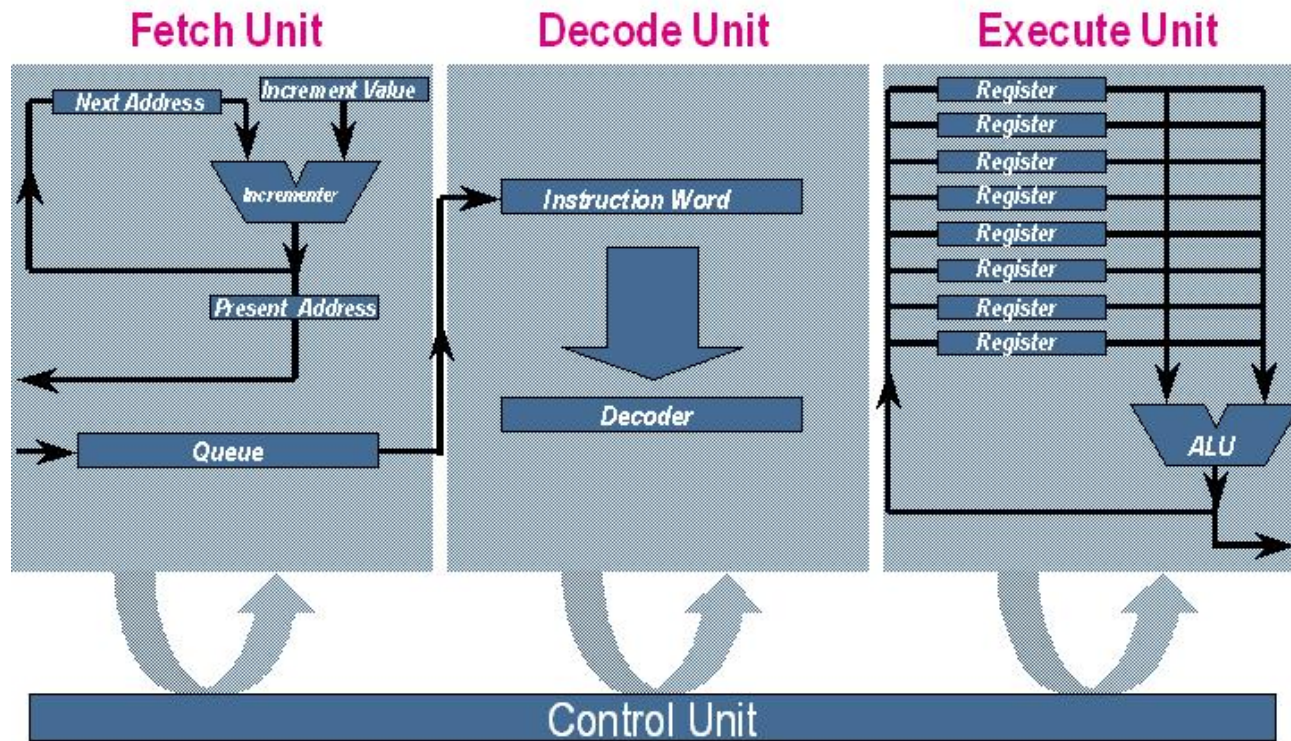

- ☐ First, an instruction is fetched into the microprocessor
- ☐ Second, the instruction is decoded for execution
- ☐ Finally, the instruction is executed.


Advantages of FPGA Microprocessors

 - ❑ The architecture of FPGA microprocessor can be easily modified to achieve optimal performance for a given application.
- ❑ Example: calculate $Y = A \cdot X^2 + B \cdot X + C$



FPGA

 
$t1 \leftarrow x$
 $t2 \leftarrow A \times t1$
 $t2 \leftarrow t2 + B$
 $t2 \leftarrow t2 \times t1$
 $y \leftarrow t2 + C$




General purpose microprocessor

Introduction to GNOME Microprocessor

 Data : 4 bits
 Instruction : 8 bits
 Data RAM : 16 X 4
 Instr. RAM : 128 X 8



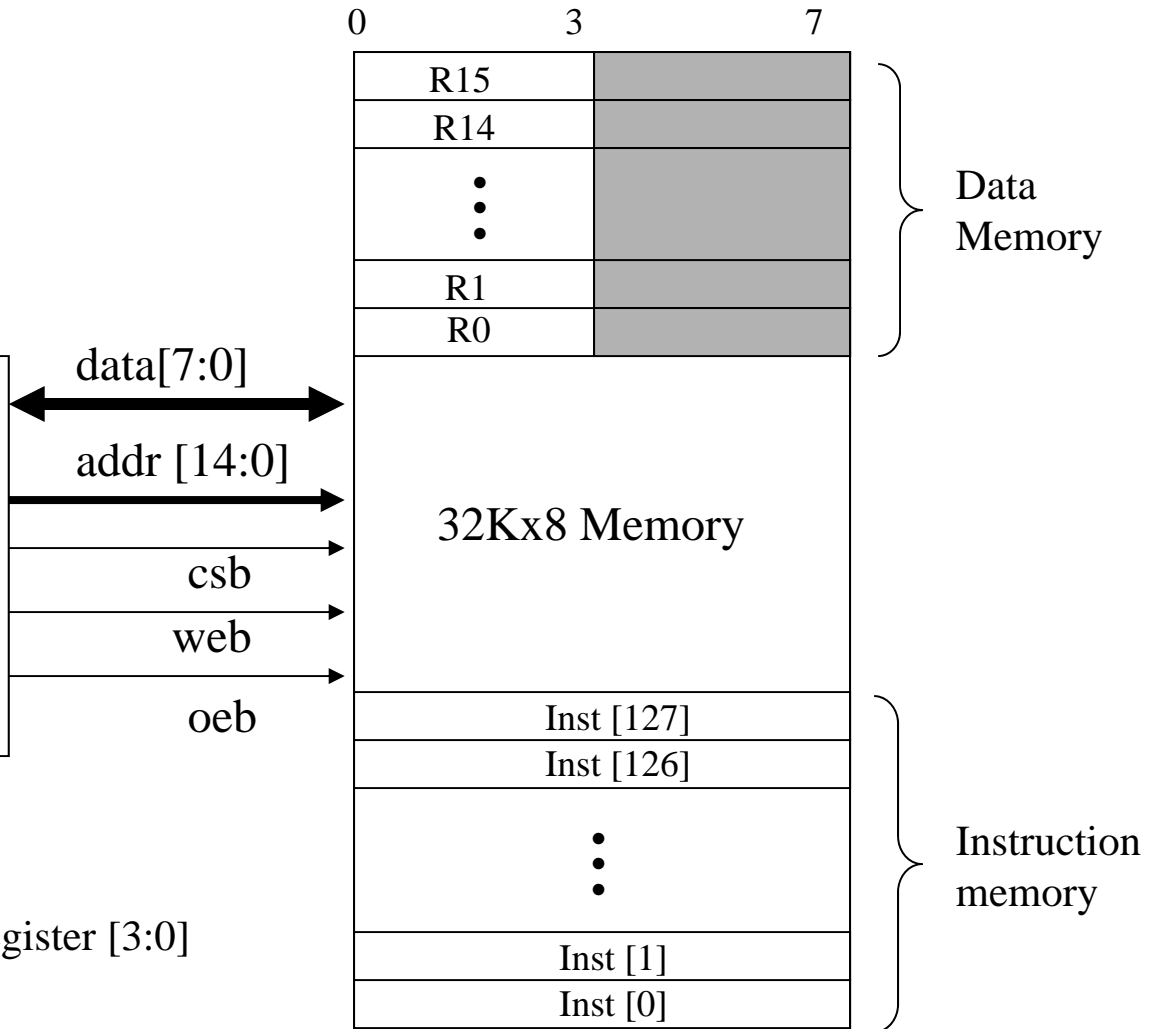C : Carry flag
 Z : Zero flag
 ACC : Accumulator Register [3:0]



Instructions of GNOME Microprocessor

Mnemonic	Operation	Description
load Rd	$ACC \leftarrow Rd$	Load the accumulator with the contents of the memory location whose address is d.
loadi d	$ACC \leftarrow d$	Load the accumulator with the immediate data d
store Rd	$Rd \leftarrow ACC$	Store the value in the accumulator into RAM location Rd.
add Rd	$ACC \leftarrow ACC + Rd + C$	Add the content of RAM location Rd and the C flag to the Accumulator.
addi d	$ACC \leftarrow ACC + d + C$	Add the value d and the C flag to the accumulator.
xor Rd	$ACC \leftarrow ACC \otimes Rd$	EXCLUSIVE-OR the content of RAM location Rd with the Accumulator.
test Rd	$Z \leftarrow ACC \bullet Rd$	AND the contents of RAM location Rd with the accumulator, but do not store the results in the accumulator. Instead, set the Z flag if the result is 0, otherwise clear the Z flag.


Instructions of GNOME Microprocessor

Mnemoni c	Operation	Description
clear_c	$C \leftarrow 0$	Clear the C flag to zero.
set_c	$C \leftarrow 1$	Set the C flag to one.
skipc	$PC \leftarrow PC+1+C$	If $C=1$, skip the next instruction by incrementing the program counter by two instead of one. Otherwise, execute the next instruction
skipz	$PC \leftarrow PC+1+Z$	If $Z=1$, skip the next instruction by incrementing the program counter by two instead of one. Otherwise, execute the next instruction
jump a	$PC \leftarrow a$	Jump to program address a and execute instructions from address a. a is an address in the range [0..127]


Instruction Encoding

❑ Instruction Format

 
- Fixed length instructions (8 bits)
- Each instruction can have one or zero operand



clear_c set_c

 

 load Rd, loadi d, store Rd, add Rd, addi d,
xor Rd, xori d, test Rd, testi d




jump a


Instruction Encoding

Mnemonic	Encoding	Comment
load Rd	0 1 0 0 $d_3 d_2 d_1 d_0$	$d_3 d_2 d_1 d_0$ is the address of RAM location
loadi d	0 0 0 1 $d_3 d_2 d_1 d_0$	$d_3 d_2 d_1 d_0$ is the immediate data
store Rd	0 0 1 1 $d_3 d_2 d_1 d_0$	$d_3 d_2 d_1 d_0$ is the address of RAM location
add Rd	0 1 0 1 $d_3 d_2 d_1 d_0$	$d_3 d_2 d_1 d_0$ is the address of RAM location
addi d	0 0 1 0 $d_3 d_2 d_1 d_0$	$d_3 d_2 d_1 d_0$ is the immediate data
xor Rd	0 1 1 0 $d_3 d_2 d_1 d_0$	$d_3 d_2 d_1 d_0$ is the address of RAM location
test Rd	0 1 1 1 $d_3 d_2 d_1 d_0$	$d_3 d_2 d_1 d_0$ is the address of RAM location
clear_c	0 0 0 0 0 0 0 0	
set_c	0 0 0 0 0 0 0 1	
skipc	0 0 0 0 0 0 1 0	
skipz	0 0 0 0 0 0 1 1	
jump a	1 $a_6 a_5 a_4 a_3 a_2 a_1 a_0$	$a_6 a_5 a_4 a_3 a_2 a_1 a_0$ is the new instruction address

Operation of GNOME Microprocessor

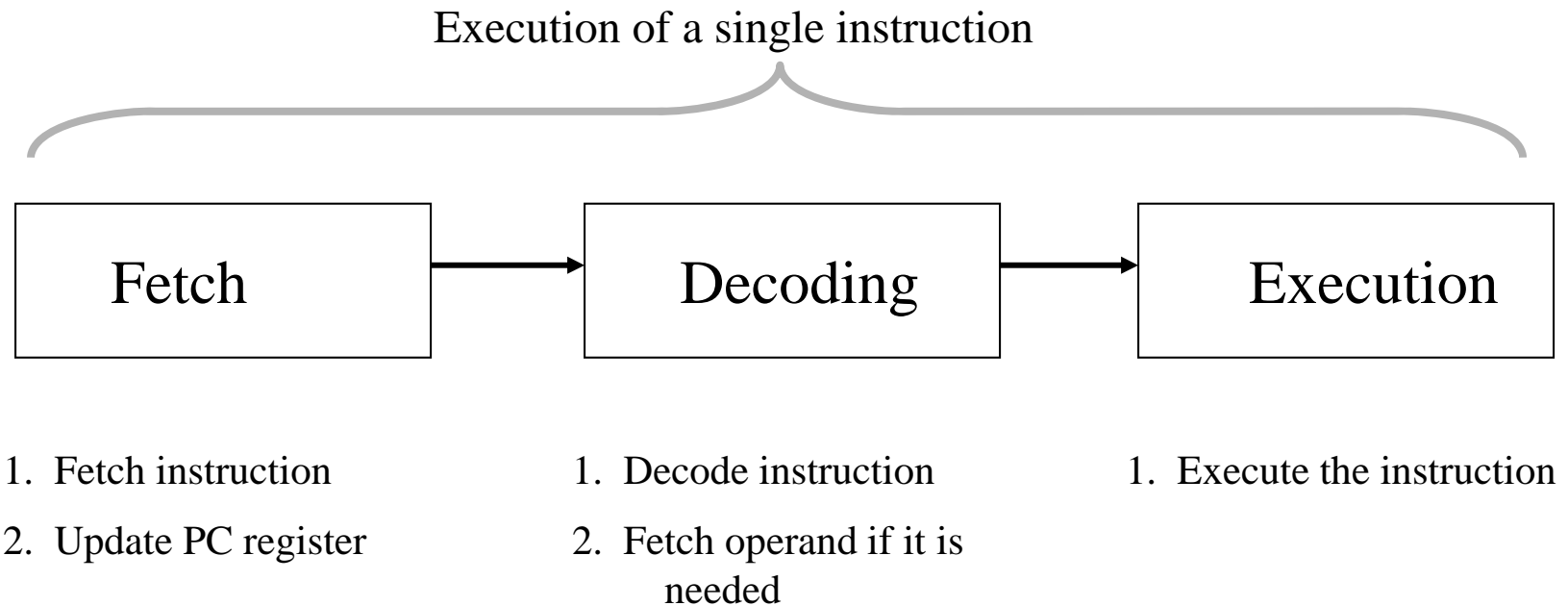


GNOME Block Diagram

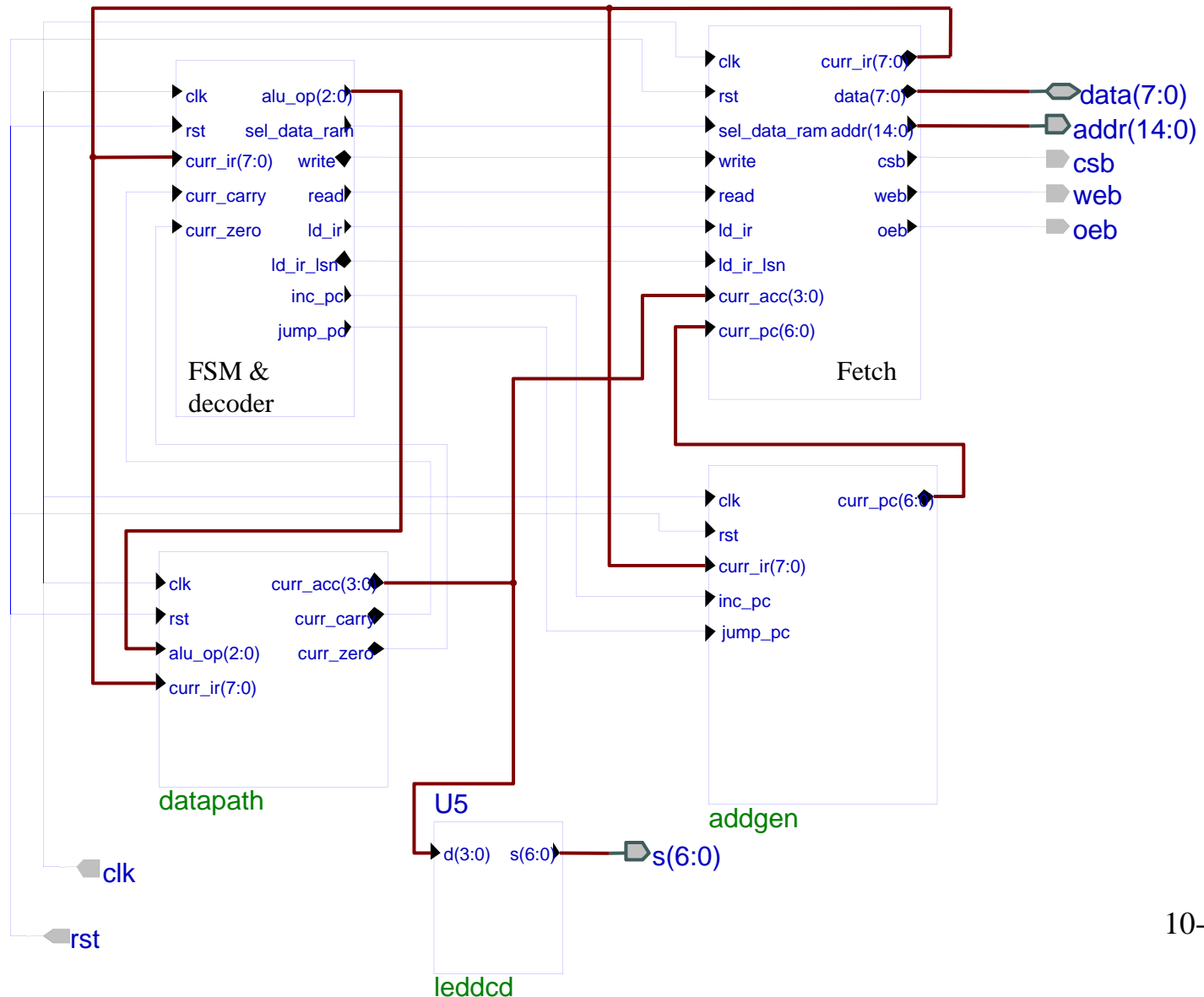


Address Generation

- ❑ If $\text{inc_pc} = 1$, the adder output goes to the input of the register (for normal instruction address update and skipz and skipc instructions).
- ❑ If $\text{jump_pc} = 1$, curr_ir goes to the input of the register (for jump instruction)
- ❑ If $\text{jump_pc} = 0$ and $\text{inc_pc} = 0$, the output of the register goes to the input of the register.
- ❑ It is prohibited to have $\text{jump_pc} = 1$ and $\text{inc_pc} = 1$ at the same time.
- ❑ After reset, $\text{curr_pc} = 0$. Thus, the microprocessor fetches the first instruction from address 000000


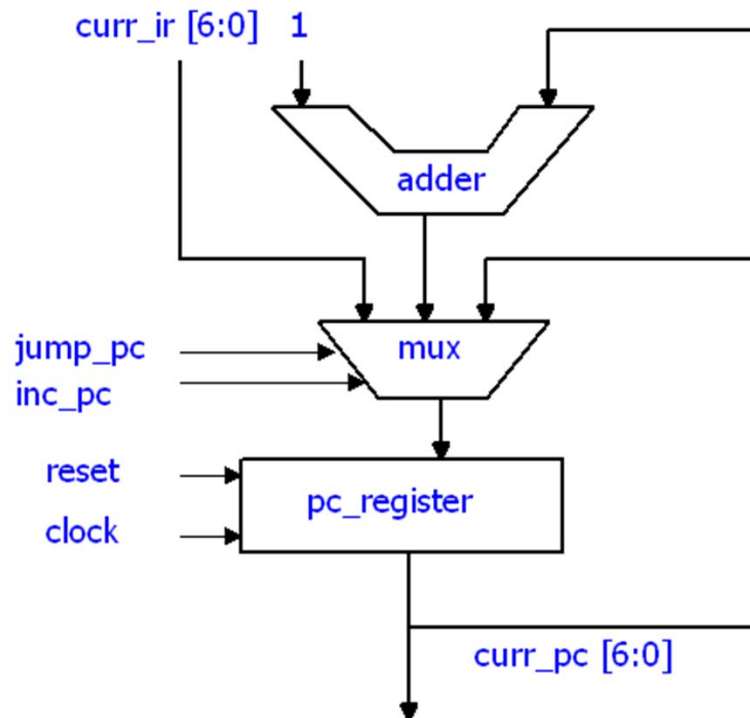


Instruction Latch & Data Bus Circuits

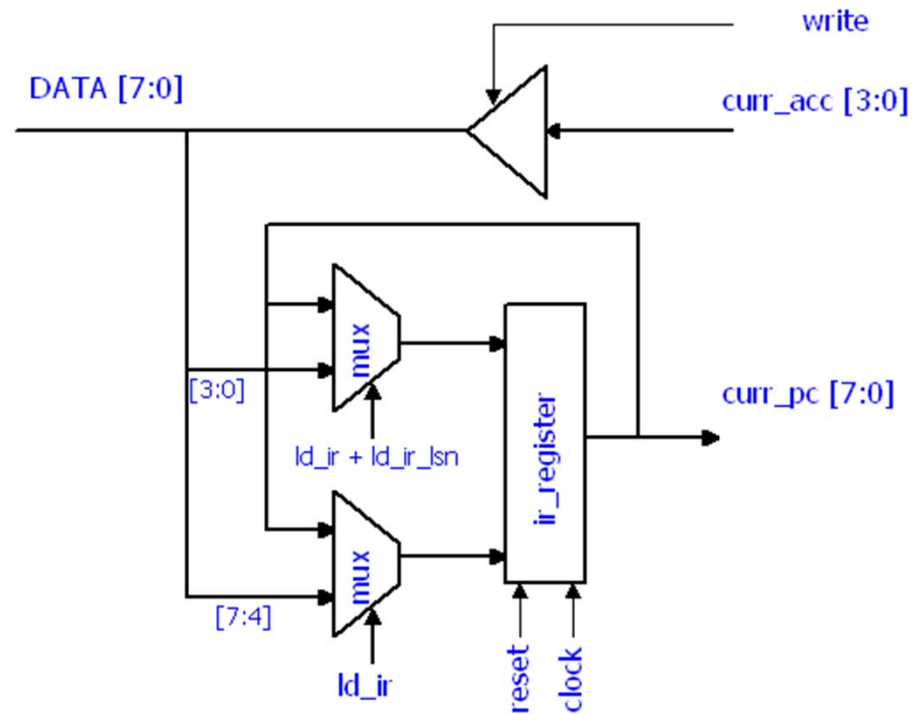- ❑ For write operation (store rd), the write buffer is on and data on curr_acc are written into memory. During other time, the write buffer is off (high impedance output)
- ❑ To fetch an instruction, both muxs pass the data on the data bus to the instruction register
- ❑ To fetch data from data RAM, only the least significant mux passes the data on the data bus to the instruction register



Control & decoding Unit

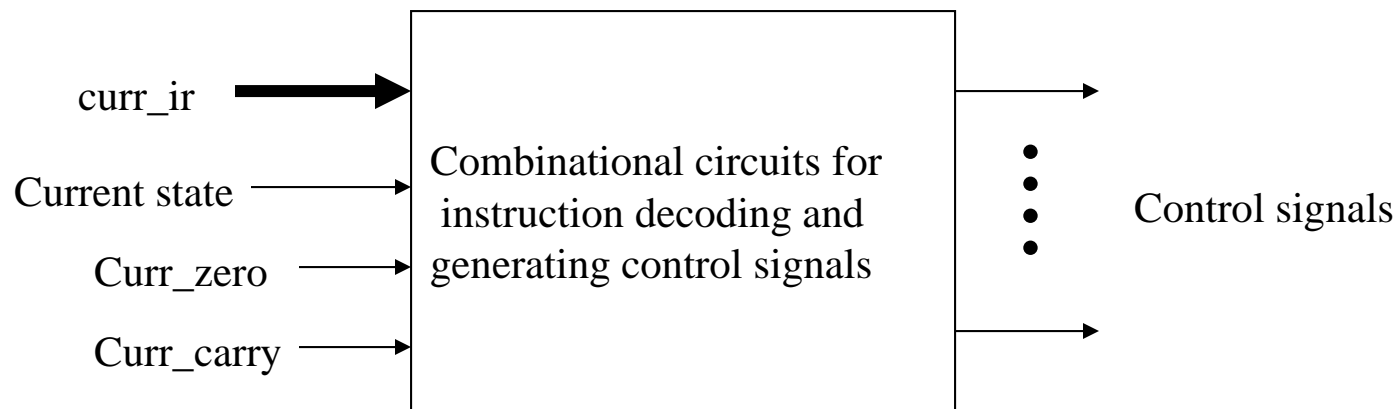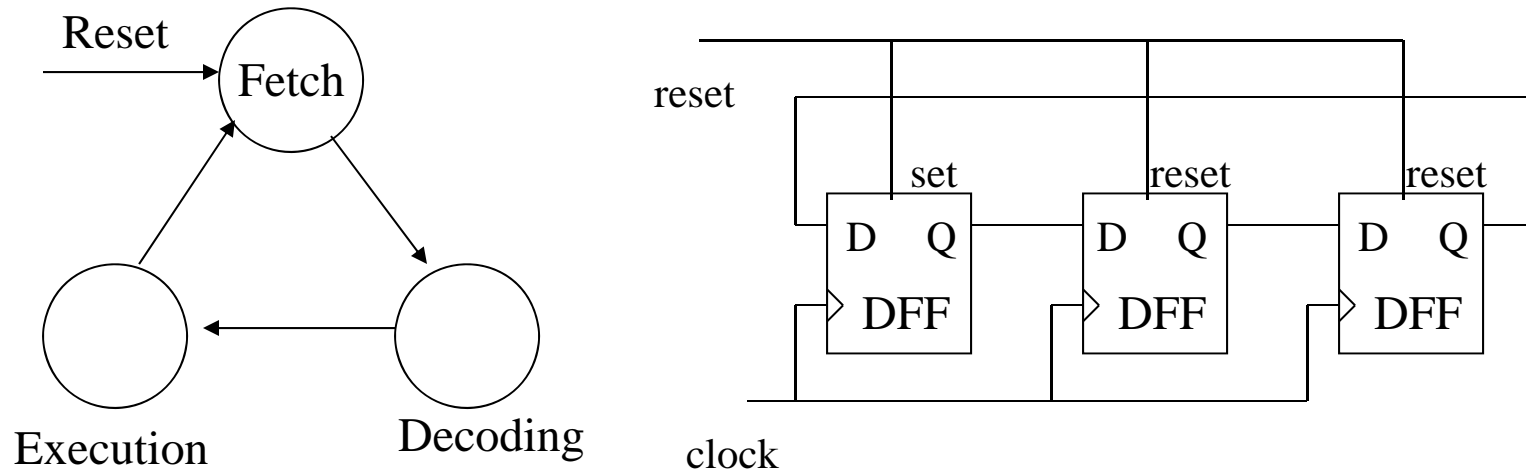

Control & decoding Unit

❑ Example: how generate control signal write


— write signal should be driven to high to enable the write buffer during the execution state of *store rd* instructions

$$\text{write} = \text{exe_state} \mathbf{AND} \text{store_instruction}$$

1. Signal exe_state is high when GNOME is during execution states
2. Signal store_instruction is high if the current instruction is *store rd*

Execution Unit

❑ Accumulator-Based Architecture

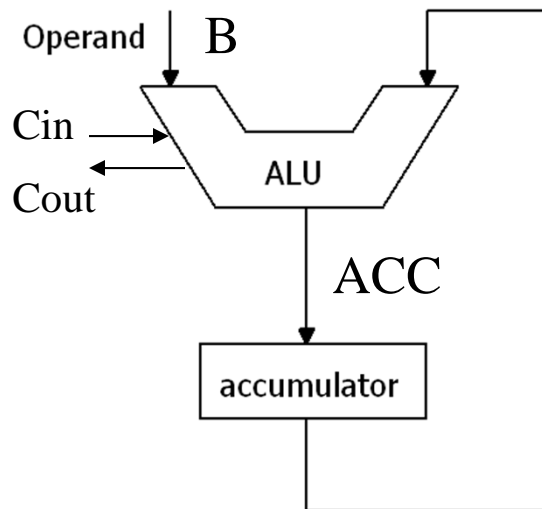


- For operations with two operands, one operand is accumulator.
- The execution result is store in accumulator

❑ ALU operations

Name	Operation	Encoding
PASS	$ACC \leftarrow B$	0 0 1
ADD	$ACC \leftarrow ACC + B + Cin$	0 1 0
XOR	$ACC \leftarrow ACC \otimes B$	0 1 1
AND	Zero flag = $ACC \cdot B$	1 0 0
SET_C	Set carry flag	1 0 1
CLR_C	Clear carry flag	1 1 0


ALU Circuit

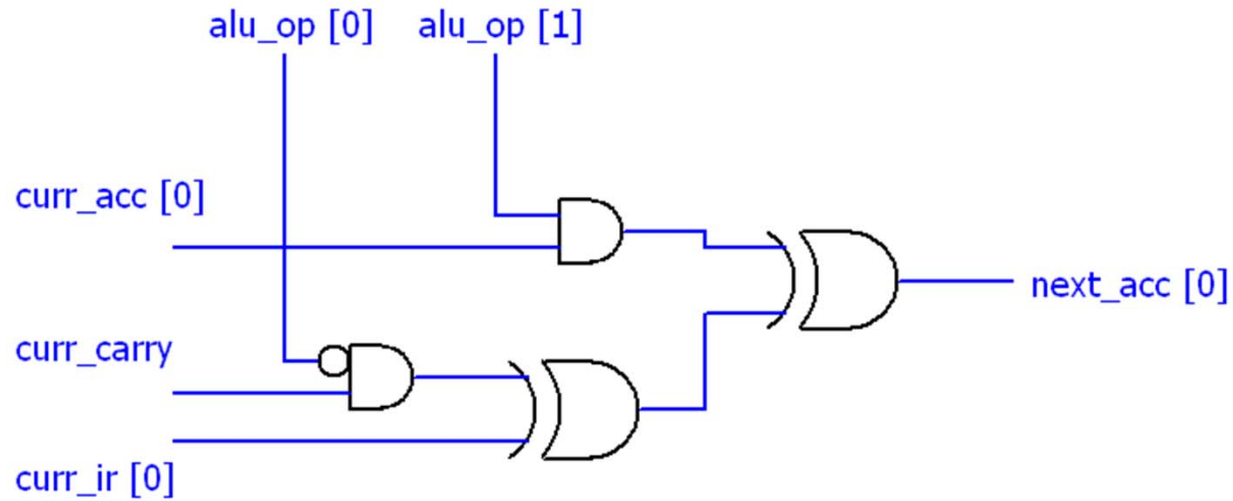

alu_op[1]	alu_op[0]	Operation
0	1	PASS
1	1	XOR
1	0	ADD*

* Extra circuits are needed for carry generation

Complete ALU Circuit

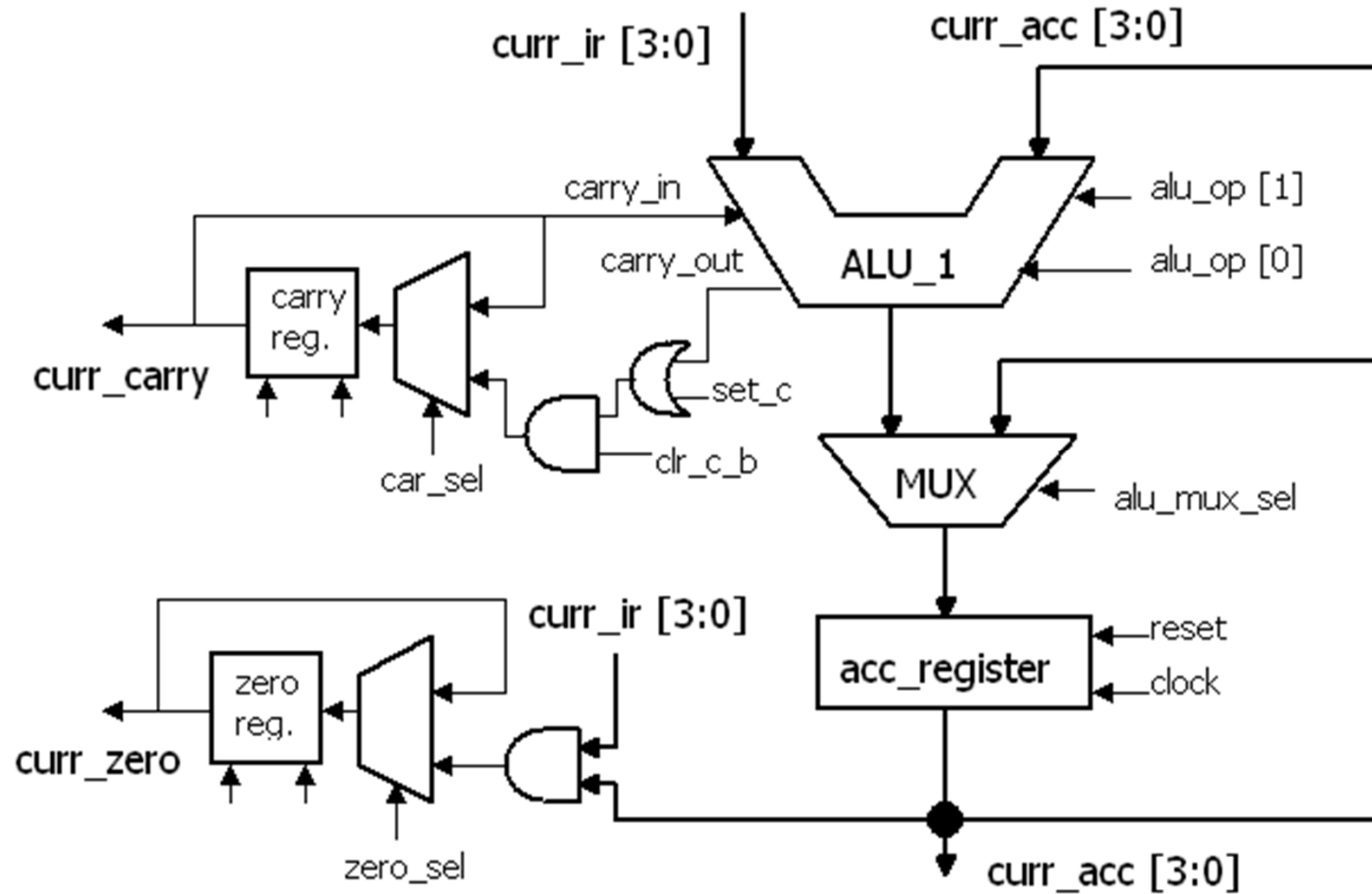

Programming GNOME Processor

❑ Example: writing a program to calculate $48H + 29H$

Instructions		Machine code
Loadi	8	18H
Store	R0	30H
Loadi	4	14H
Store	R1	31H
Loadi	9	19H
Store	R2	32H
Loadi	2	12H
Store	R3	33H
Clear_c		00H
Load	R0	40H
Add	R2	52H
Store	R4	34H
Load	R1	41H
Add	R3	53H
Store	R5	35H

Put Everything Together

