

---

*ECE 428 Programmable ASIC Design*


# Fundamentals of Digital IC Design

Haibo Wang  
ECE Department  
Southern Illinois University  
Carbondale, IL 62901


# Semiconductor Devices

---


## ❑ Bipolar Transistors:

 
 
## ❑ Junction Field Effect Transistor (JFET):



 
## ❑ Metal-Oxide-Semiconductor (MOS) Devices:




# CMOS Process

## ❑ Cross-Section Diagram

 

## ❑ Layout

 

Source from <http://infopad.eecs.berkeley.edu/~icdesign>  
For a great tour of IC fabrication process, see  
<http://www.fullman.com/semiconductors/semiconductors.html>

# Digital Signals and Basic Logic Gates

---

## □ Digital signal values

True	1	High Voltage (e.g. 5V) <sub>12</sub>
False	0	Low Voltage (e.g. 0V)

## □ Basic logic gates

1. Inverter       $X \longrightarrow \text{Inverter} \longrightarrow Y = \overline{X}$

X	Y	Truth Table of an inverter
1	0	
0	1	


2. AND       $\begin{matrix} X \\ Y \end{matrix} \longrightarrow \text{AND} \longrightarrow Z = X \bullet Y$

X	Y	Z	Truth Table of an AND gate
0	0	0	
0	1	0	
1	0	0	
1	1	1	

3. NAND       $\begin{matrix} X \\ Y \end{matrix} \longrightarrow \text{NAND} \longrightarrow Z = \overline{X \bullet Y}$

# Basic Logic Gates


4. OR

 


X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

Truth Table of  
an OR gate

5. NOR

 


4. XOR

 

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0


Truth Table of  
an XOR gate

5. XNOR

 



# Basic Logic Gates

## □ Tri-state Buffer

 


C	I	O
1	X	Z
0	0	0
0	1	1

Truth table of a tri-state buffer

  

# Gate Delay Definition


---

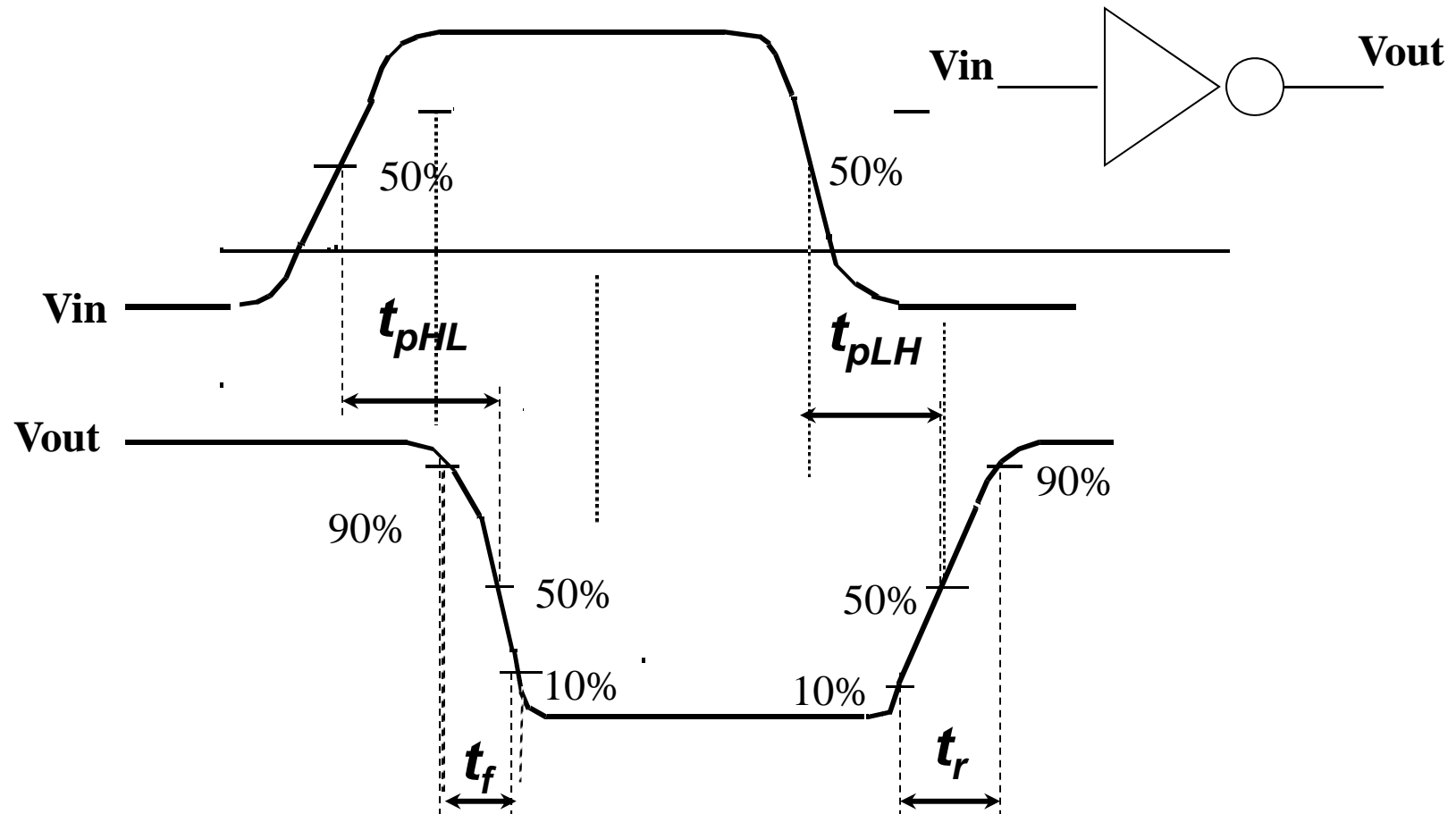

# Sequential Logic Circuits


---

## □ D latch

 

- When CLK=1, Q always reflects the signal value at input D
- If CLK=0, Q stores the last D value which appears at D just before CLK falls to 0

## □ D Flip-flop

 



- D flip-flop will not change its output values unless there is a negative edge event at CLK input (CLK switches from logic 1 to 0).
- When a negative edge appears at CLK input, D Flip-flop updates Q to the current D value




# Timing Parameters for D Flip-Flops

---


## ❑ Clock-Q Delay

  

## ❑ Setup Time

 


## ❑ Hold time

 

 
# Decoder Circuits

- ❑ A decoder circuit uniquely selects one of its outputs according to its input signals



- ❑ 2-to-4 decoder implementation



X	Y	Z1	Z2	Z3	Z4
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

 

# Decoder Circuit
  
## ❑ 3-to-8 decoder implementation


- Assume that we have 2-to-4 decoders available as standard components
- When CS is low (0), all the outputs of the decoder are low (0)




# Sequential Logic Circuits

## □ Counter

### ➤ Basic binary counter

 

### ➤ Synchronous counter

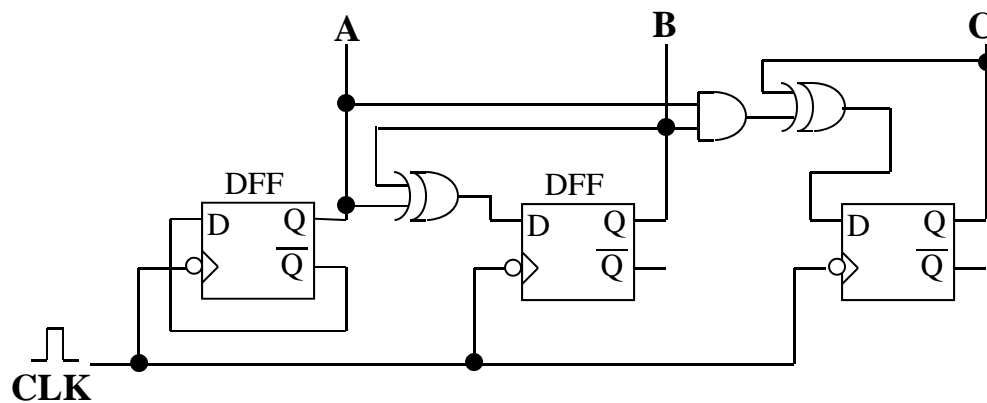


Clk	C	B	A
Init.	0	0	0
⌊	0	0	1
⌊	0	1	0
⌊	0	1	1
⌊	1	0	0
⌊	1	0	1
⌊	1	1	0
⌊	1	1	1


# Sequential Logic Circuits

## □ frequency divider

- Divide clock frequency by 4

 


- Divide clock frequency by 3

 


# Sequential Logic Circuits
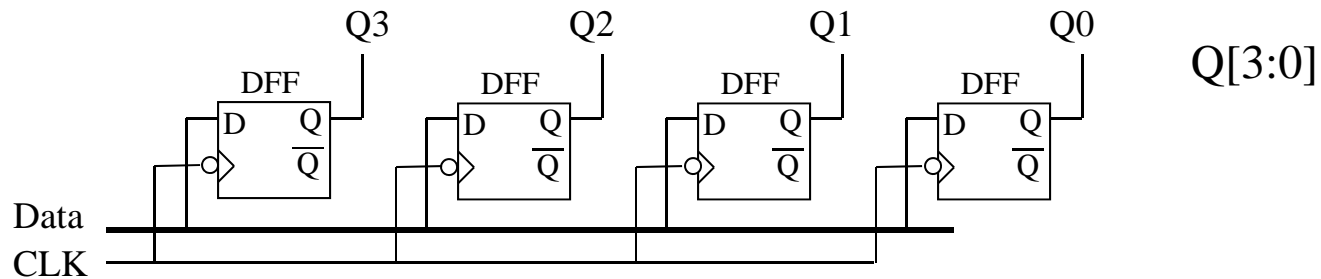
## ❑ Register

- A row of storage elements (e.g. D flip-flops)





## ❑ Shift register

 

CLK	Q3	Q2	Q1	Q0
Init.	1	0	1	0
$\nearrow$	0	1	0	1
$\nearrow$	0	0	1	0
$\nearrow$	0	0	0	1
$\nearrow$	0	0	0	0



# Major Parasitic Effects in Digital ICs

## ❑ Ideal Circuit

  

**No delay!**


## ❑ Real Circuit

  

**Significant delay!**


# Power Consumption of CMOS Gates

## ❑ Dynamic Power Consumption

 

$$P_{Dynamic} = 0.5 \cdot C \cdot V_{DD}^2 \cdot f$$

## ❑ Short-Circuit Power Consumption

 



$$P_{SC} = \int I_{sc}(t) V dt$$

## ❑ Leakage Power Consumption




# Transistor Sizing


---

  

Driver Size

 


Driver Size

 

Driver Size

# Design Constraints for Digital ICs

---

 

## ☐ Delay (speed) constraints

— For example, the delay from Vin1 to Vout1 should be smaller than 10 ns; the clock frequency should be greater 100MHz

## ☐ Power constraints

## ☐ Area constraints

# How to Find Circuits Complying with Design Constraints


---

Full-custom approach	Standard-cell based approach Gate-array approach FPGA approach
<ol style="list-style-type: none"><li>1. It heavily depends on designers' expertise.</li><li>2. Finding a proper circuit implementation can be very time consuming.</li><li>3. Very creative circuit implementations can be achieved.</li></ol>	<ol style="list-style-type: none"><li>1. These approaches heavily use design automation techniques to search circuits complying with constraints.</li><li>2. They are time saving approaches.</li><li>3. These approaches require pre-developed technology libraries.</li><li>4. The quality of the final implementation depends on algorithms and libraries used in the search.</li></ol>

# Example: How to Search a Proper Circuit Implementation in FPGA Design Flow

---

## ❑ FPGA Design Flow

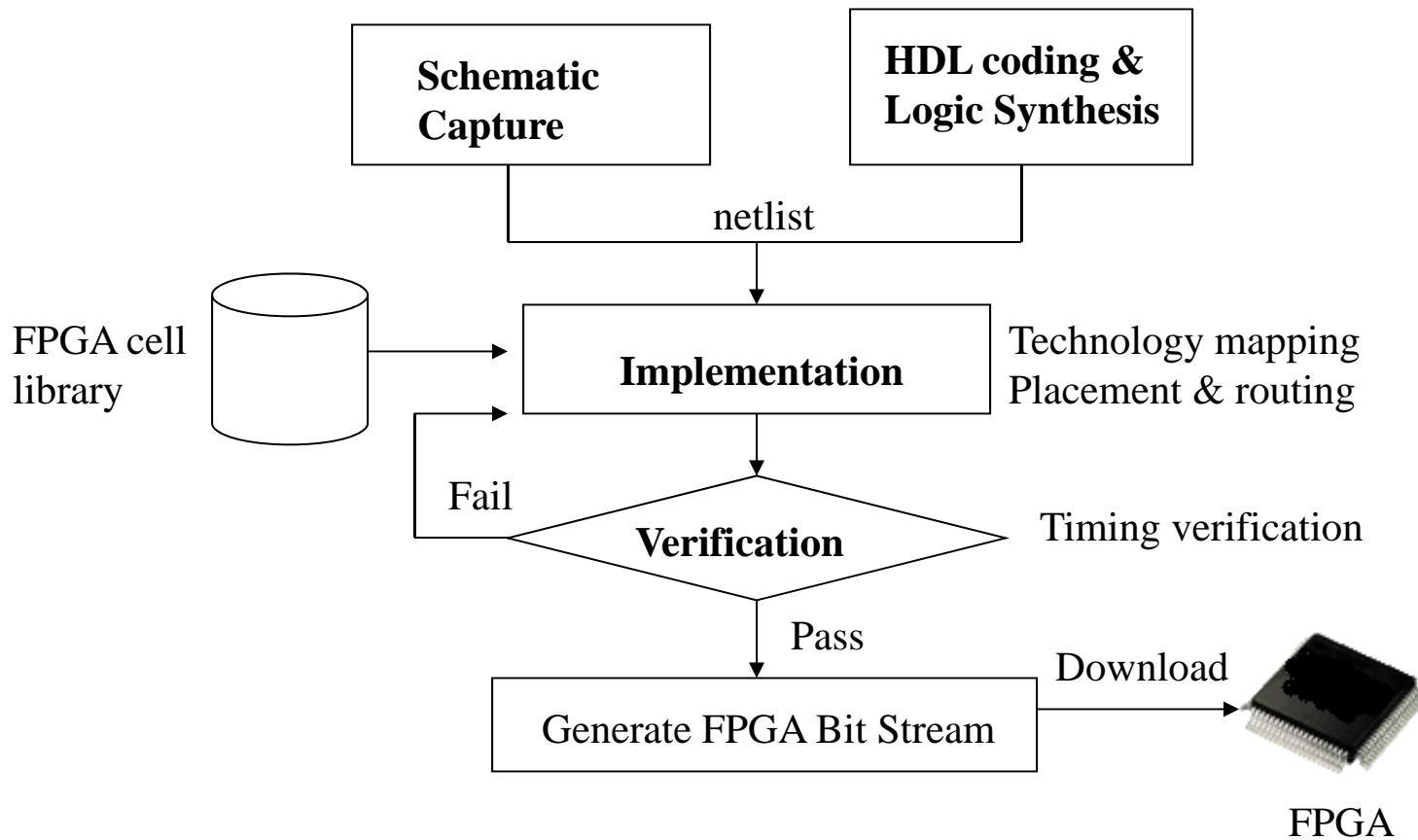


# Example: How to Search a Proper Circuit Implementation in FPGA Design Flow

---
 
## ❑ Given Logic Function

- This circuit is either from schematic capture or from logic synthesis



## ❑ FPGA Library Components

- The library contains five components
- Three inverters at size 1, 3, 5
- Two two-input NAND gates at size 1 and 3


## ❑ Design Constraints

- The maximum delay between an input and an output should not exceed 5 ns
 
# Example: How to Search a Proper Circuit Implementation in FPGA Design Flow


---

- ❑ Step 1: Use the available logic gates to implement the given function.  
(Technology Mapping)



- ❑ Step 2: Select proper size for each gate used in the above circuit.  
(Gate Sizing)

 - After this step, the circuit can be simulated to verify that it complies with timing constraints.
- In the simulation, the parasitic capacitance and resistance on interconnects are estimated  
(Estimated wire load)




# Example: How to Search a Proper Circuit Implementation in FPGA Design Flow

---

- ❑ Step 3: Determine where to place these gates and how to connect them (Placement & Routing).

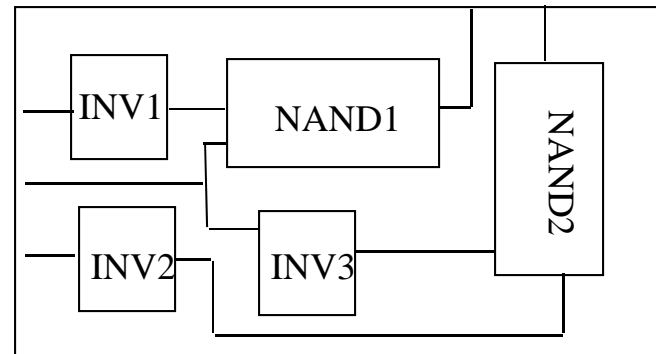- Some algorithms first place the components and then route the interconnects.
- Some algorithms perform the placement and routing simultaneously



- Steps 1, 2, and 3 are included in the implementation phase of the FPGA design Flow

- ❑ Step 4: Perform post-layout simulation to verify that the generated circuit complies with timing constraints

- Since detail information of each interconnect is available, the circuit can be simulated with accurate wire load.
- The process that writes the accurate wire load into the circuit netlist is called back annotation

# What Information Should Be Stored in FPGA Library

---


- ☐ Logic function
- ☐ Timing (delay) information
- ☐ Power consumption information
- ☐ Silicon area
- ☐ Layout information
- ☐ Placement & routing constraints
- ☐ ....
- ☐ ....


 
# Example: How to Store Delay Information

---

- Normally, the delay of gate is proportional to the load on its output



$$\text{Delay} = D_0 + K * \text{Load}$$

So, we can store two parameters ( $D_0$  and  $K$ ) for each gate to model its delay property.

# Binary Number System

---

## ❑ Converting binary numbers to decimal numbers

Binary		Decimal
--------	--	---------

1011	→	$1*2^3 + 0*2^2 + 1*2^1 + 1*2^0$	= 11
------	---	---------------------------------	------

0111	→	$0*2^3 + 1*2^2 + 1*2^1 + 1*2^0$	= 7
------	---	---------------------------------	-----

## ❑ Converting binary numbers to hexadecimal numbers


1 1 1 1	0 1 0 1	1 0 1 0	0 0 1 1
↓	↓	↓	↓
F	5	A	3

# Binary Addition


## ➤ Example

$$\begin{array}{r} 0101 \\ + 1001 \\ \hline 1110 \end{array}$$

## ➤ A single-bit full adder

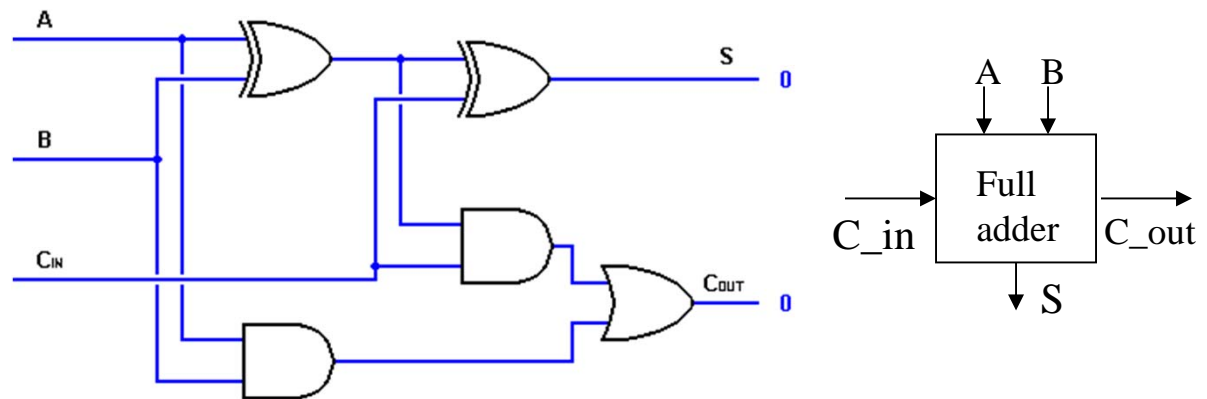

## ➤ 4-bit adder

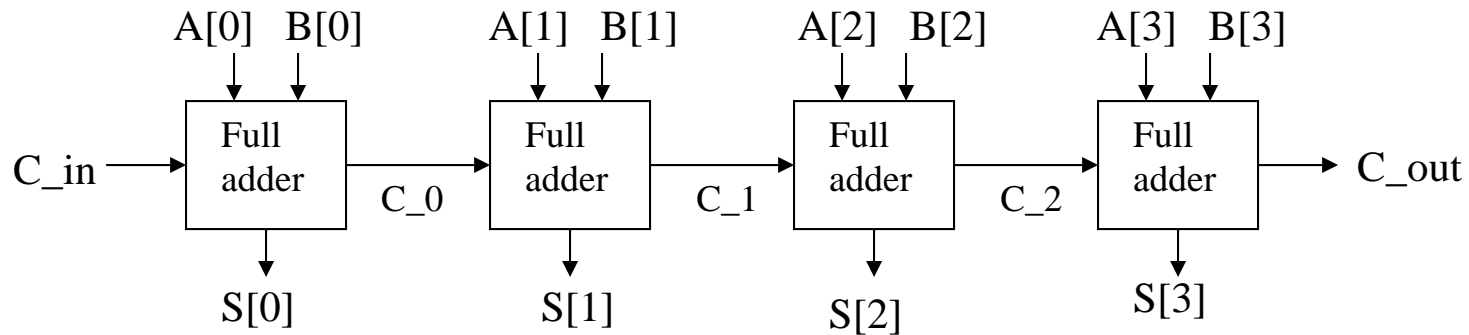

# Handling Negative numbers

## ❑ Signed magnitude

- The left-most bit is a sign bit  
0 indicates positive a number and  
1 indicates negative a number

Signed magnitude			Decimal
0	0	0	0
0	0	1	1
0	1	0	2
0	1	1	3
1	0	0	0
1	0	1	-1
1	1	0	-2
1	1	1	-3

## ❑ One's complement

- For positive number A, it is represented as usual binary number
- For negative number -A, its representation is obtained by flipping the bits of the binary representation of A

1's complement			Decimal
0	0	0	0
0	0	1	1
0	1	0	2
0	1	1	3
1	1	1	0
1	1	0	-1
1	0	1	-2
1	0	0	-3

# Handling Negative numbers

## ❑ Two's complement

- For positive number A, it is the same as the one's complement
- For negative number A, add one to the one's complement representation

2's complement			Decimal
0	0	0	0
0	0	1	1
0	1	0	2
0	1	1	3
1	1	1	-1
1	1	0	-2
1	0	1	-3
1	0	0	-4

- ❑ By using two's complement number representation, minus operations can be performed by adders

$$\begin{array}{r}
 3 \\
 \hline
 1 \\
 \hline
 2
 \end{array}
 \Rightarrow
 \begin{array}{r}
 \phantom{+} 0 \ 1 \ 1 \\
 + \phantom{+} 1 \ 1 \ 1 \\
 \hline
 1 \ 0 \ 1 \ 0 \\
 \hline
 2
 \end{array}$$

Overflow Ignore

$$\begin{array}{r}
 2 \\
 \hline
 3 \\
 \hline
 -1
 \end{array}
 \Rightarrow
 \begin{array}{r}
 \phantom{+} 0 \ 1 \ 0 \\
 + \phantom{+} 1 \ 0 \ 1 \\
 \hline
 1 \ 1 \ 1 \\
 \hline
 -1
 \end{array}$$