

ET 438a
Continuous and Digital Control Systems

Homework

The output of an inverting OP AMP circuit must have an error of no more than $\pm 3\%$. The input voltage has an error of $\pm 1.75\%$. What is the maximum tolerance that the resistors in the circuit can have without exceeding the output error limit? Assume that the tolerance of the resistors will be the same.