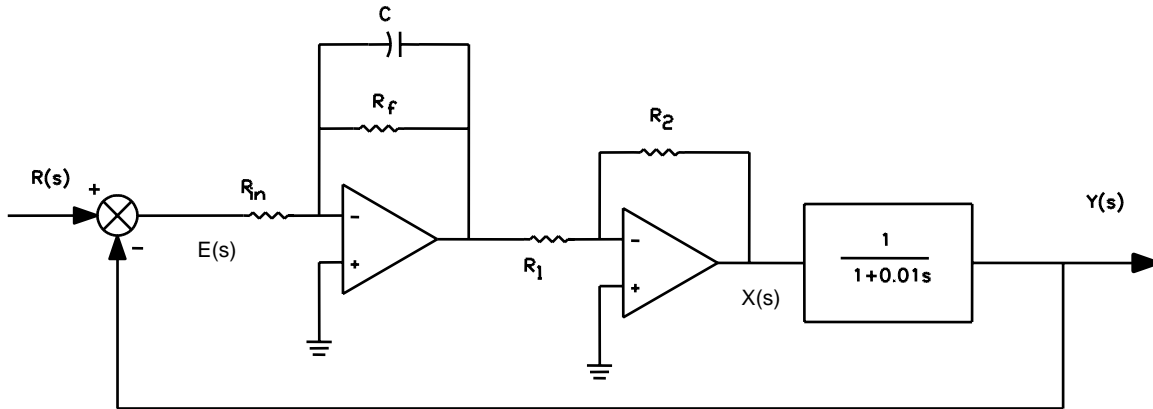


ET438a
Practical Integrator and differentiator Circuits
Homework


1. Practical integrator circuits in control

- a) Find the transfer function, $X(s)/E(s)$, of the practical integrator circuit in the control system diagram below.
- b.) Find the closed loop transfer function of the system $Y(s)/R(s)$.
 $R_{in} = 10k\Omega$ $R_f = 50 k\Omega$ $C = 1\mu F$ $R_1 = 100k\Omega$ $R_2 = 100k\Omega$



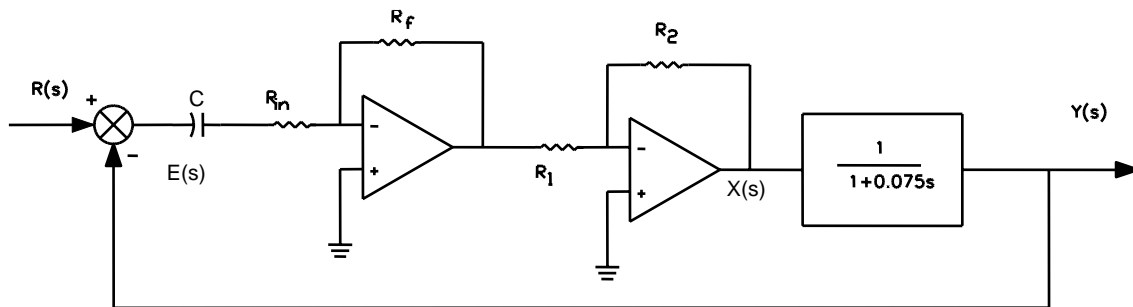2. Practical differentiator circuits in control

- a.) Find the transfer function, $X(s)/E(s)$ of the practical differentiator circuit including the inverting amplifier.
- b.) Find the closed loop transfer function of the the system $Y(s)/R(s)$.



$R_f = 10k\Omega$ $R_{in} = 12k\Omega$ $C = 2.5 \mu F$ $R_1 = 100k\Omega$ $R_2 = 220k\Omega$