

ET 438a
Continuous and Digital Control

Use the generalized gain formula and the Laplace impedance concept to find the output voltage v_o in terms of the input v_i for the circuit below. Assume that v_i and v_o are arbitrary functions of time.

