

ET438a
Electric Circuit Modelling

Write the equations that completely describe the operation of the bridge circuit in the figure below using

a.) mesh equations

