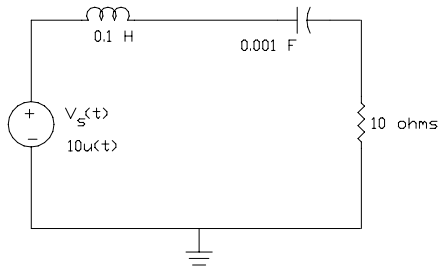


ET 438a  
Continuous and Digital Control  
Laplace Transform of Dynamic Systems

- 1.) Write the integro-differential equation that describes the loop current response of the circuit below and then convert it to an algebraic equation using the Laplace transform.



- 2.) Write the Laplace formula that describes the velocity response of the system below to the force  $F(t) = 5\sin(0.1t)$

