

ET 438a  
Transfer Functions and Block Diagrams

Find the transfer function and draw a block diagram for each of the circuits shown below.

