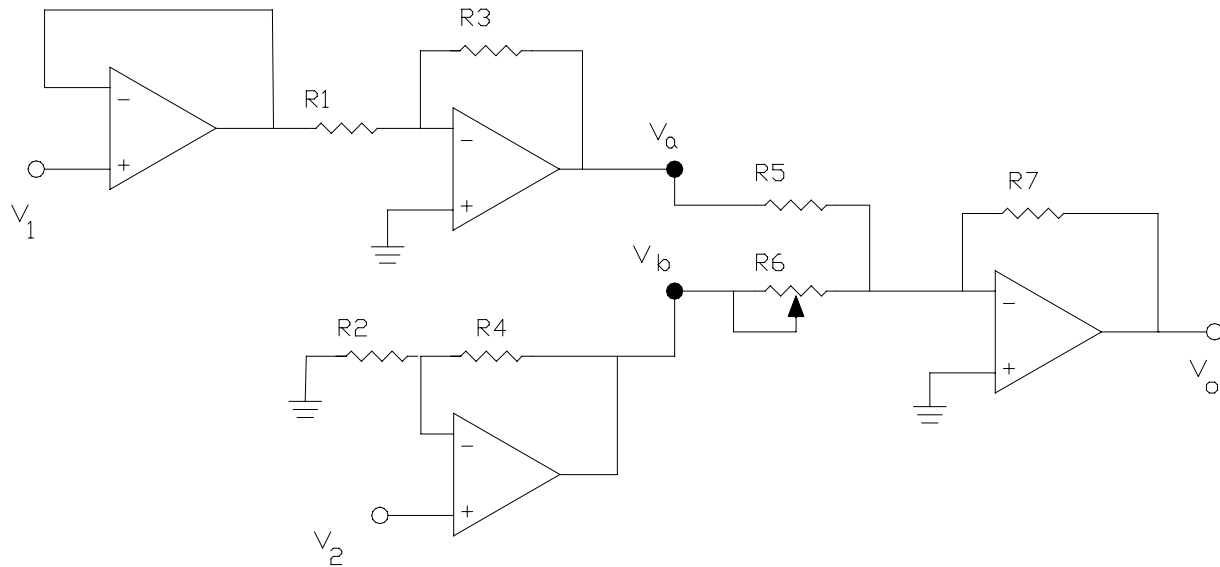


ET 438a
Continuous and Digital Control

Homework



For the circuit above the resistor values are:

$R_1 = 470 \text{ k}\Omega$ $R_2 = 10 \text{ k}\Omega$ $R_3 = 100 \text{ k}\Omega$
 $R_4 = 8.2 \text{ k}\Omega$ $R_5 = 82 \text{ k}\Omega$ $R_6 = \text{set to } 187 \text{ k}\Omega$
 $R_7 = 270 \text{ k}\Omega$

The values of input voltage are: $V_1 = +3 \text{ Vdc}$
 $V_2 = -0.10 \text{ Vdc}$

Find the values of V_a , V_b and V_o for the circuit