

# Lesson 16: Basic Control Modes

ET 438a Automatic Control Systems Technology

lesson16et438a.pptx

1

## Learning Objectives

After this presentation you will be able to:

- Describe the common control modes used in analog control systems
- List the characteristics of common control modes
- Write the time, Laplace and transfer functions of common control modes
- Identify the Bode plots of common control modes
- Design OP AMP circuits that realize theoretical control mode performance.

lesson16et438a.pptx

2

## Control Modes-Proportional Control Action

Process characteristics for optimum results:

- 1) Small process capacitance
- 2) Rapid load changes

**Limitations:** Small steady-state error may require high gain to achieve acceptable error levels

### Mathematical representations

Time function:  $v = K_p \cdot e + v_o$

Where:  $e$  = time domain error signal

$K_p$  = proportional gain

$v_o$  = controller output with  $e=0$

$v$  = controller time domain output

Laplace function:  $V(s) = K_p \cdot E(s)$

Note: Initial condition  $v_o=0$  on Laplace function


Transfer function:  $\frac{V(s)}{E(s)} = K_p$

lesson16et438a.pptx

3
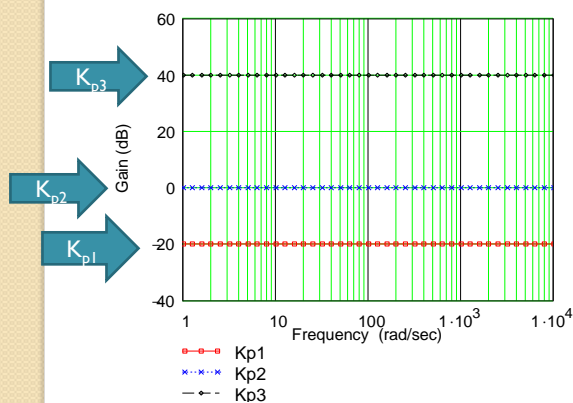
## Proportional Control Frequency Response

Bode plots of three values of  $K_p$ :  $K_{p1}=0.1$ ,  $K_{p2}=1$ , and  $K_{p3}=100$



**Note:** gain is independent of frequency.

### Practical realization:

Non-inverting OP AMP circuit


lesson16et438a.pptx

4

# Motor Speed Control

**Example 16-1:** Determine the effect of applying proportional control to the block diagram shown below. The motor produces the following results with the control loop open:

$T_{L1} = 0.05 \text{ N-m}$	$T_{L2} = 0.075 \text{ N-m}$ (50% increase in load)
$V_T = 19.24 \text{ Vdc}$	$V_T = 19.24$
$I_{a1} = 1.033 \text{ A}$	$I_{a2} = 1.45 \text{ A}$
$\omega_1 = 300 \text{ rad/sec}$	$\omega_2 = 291.7 \text{ rad/sec}$

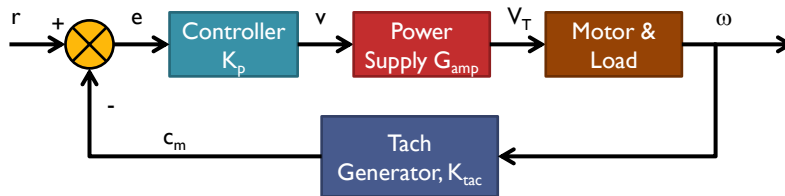

lesson16et438a.pptx


5

# Motor Speed Control

## Motor Parameters:

$T_f = 0.012 \text{ N-m}$	$R_a = 1.2 \text{ ohms}$
$K_T = 0.06 \text{ N-m/A}$	$K_{tac} = 0.11 \text{ V-sec/rad}$
$K_e = 0.06 \text{ V-sec/rad}$	$K_p G_{amp} = 10 \text{ V/V}$

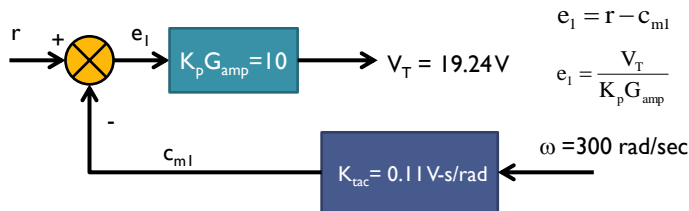**Solution:** Find the error produced and the setpoint value, r. Then write equations around control loop.



$$e_1 = r - c_{m1}$$

$$e_1 = \frac{V_T}{K_p G_{amp}}$$

$$c_{m1} = K_{tac} \cdot \omega = (0.11 \text{ V-s/rad}) \cdot (300 \text{ rad/s}) = 33 \text{ V}$$

lesson16et438a.pptx

6

## Example 16-1 Solution (2)

Combine equations

$$e_1 = r - c_{m1}$$

$$e_1 = \frac{V_T}{K_p G_{amp}} \Rightarrow \frac{V_T}{K_p G_{amp}} = r - c_{m1} \Rightarrow \frac{V_T}{K_p G_{amp}} + c_{m1} = r$$

Substitute values  $\frac{19.24 \text{ V}}{10 \text{ V/V}} + 33 \text{ V} = 34.924 \text{ V}$

Simplify  $r = 34.924 \text{ V}$

Compute error  $e_1 = r - c_{m1}$

Substitute values  $e_1 = 34.924 - 33.0 \text{ V}$

Simplify  $e_1 = 1.924 \text{ V}$

The initial setpoint value of  $r=34.924\text{V}$  with an error of  $1.924\text{V}$  at a speed of  $300 \text{ rad/s}$  and  $T_{L1}=0.05 \text{ N-m}$

lesson16et438a.pptx

7

## Example 16-1 Solution (3)

When torque increase to  $T_{L2}=0.075 \text{ N-m}$  new  $V_T$  is defined by...

$$V_{T2} = (r - c_{m2}) \cdot K_p \cdot G_{amp}$$

Substitute in Tachometer formula

$$V_{T2} = (r - K_{tac} \cdot \omega_2) \cdot K_p \cdot G_{amp}$$

Since setpoint,  $r$  does not change error must change due to measured speed change.

Motor equations  $V_{T2} = I_{a2} \cdot R_a + e_{b2}$

$$e_b = K_e \cdot \omega_m$$

Combine these equations to get:

$$V_{T2} = I_{a2} \cdot R_a + K_e \cdot \omega_2$$

Need two equations to find both  $V_{T2}$  and  $\omega_{m2}$ .

lesson16et438a.pptx

8

## Example 16-1 Solution (4)

Substitute in know values and simplify equation to get first relationship.

$$r_1 = 34.924 \text{ V} \quad K_p G_{\text{amp}} = 10 \quad K_{\text{tac}} = 0.11 \text{ V-s/rad}$$

$$V_{T2} = (r - K_{\text{tac}} \cdot \omega_2) \cdot K_p \cdot G_{\text{amp}}$$

$$V_{T2} = (34.924 - 0.11 \cdot \omega_2) \cdot 10$$

$$V_{T2} = 349.24 - 1.1 \cdot \omega_2 \quad (1)$$

← Equation 1

Now use the motor armature circuit equation and the armature current for  $T_{L2} = 0.075 \text{ N-m}$  to find second independent equation.

$$I_{a2} = 1.45 \text{ A} \quad K_e = 0.06 \text{ V-s/rad} \quad R_a = 1.2 \text{ ohms}$$

$$V_{T2} = I_{a2} \cdot R_a + K_e \cdot \omega_2$$

$$V_{T2} = (1.45 \text{ A}) \cdot (1.2 \Omega) + (0.06 \text{ V-s/rad}) \cdot \omega_2$$

$$V_{T2} = 1.74 + 0.06 \cdot \omega_2 \quad (2)$$

← Equation 2

lesson16et438a.pptx

9

## Example 16-1 Solution (5)

Place equations (1) and 2) into standard form and solve simultaneously using software or calculator.

$$V_{T2} = 349.24 - 1.1 \cdot \omega_2$$

$$V_{T2} + 1.1 \cdot \omega_2 = 349.24 \quad (1)$$

$$V_{T2} = 1.74 + 0.06 \cdot \omega_2$$

$$V_{T2} - 0.06 \cdot \omega_2 = 1.74 \quad (2)$$

$$V_{T2} = 19.71 \text{ V} \quad \omega_2 = 299.6 \text{ rad/sec}$$

← Answers

Now compute the error signal from the new tachometer output voltage  $c_{m2}$ .

$$c_{m2} = K_{\text{tac}} \cdot \omega_2$$

$$c_{m2} = (0.11 \text{ V-s/rad}) \cdot (299.6 \text{ rad/sec}) = 32.956 \text{ V}$$

$$e_2 = (r - c_{m2}) = 34.924 - 32.956 = 1.968 \text{ V}$$

Error increases  $e_2 > e_1$   $1.968 > 1.924 \text{ V}$  to rebalance system

lesson16et438a.pptx

10

## Example 16-1 Solution (6)

Now determine the percentage speed changes for open loop and feedback control. Setpoint,  $r=300$  rad/sec

### Open loop speed change

$$\left[ \frac{\omega_r - \omega_l}{\omega_r} \right] \cdot 100\% = \%SE \quad (SE = \text{speed error})$$

$$\left[ \frac{300 - 291.7}{300} \right] \cdot 100\% = \%SE$$

$$2.77\% = \%SE$$

Answers

### Feedback loop speed change

$$\left[ \frac{300 - 299.6}{300} \right] \cdot 100\% = \%SE$$

$$0.143\% = \%SE$$

Answers

Feedback reduces speed error by factor of 19.35

lesson16et438a.pptx

11

## Integral Control Mode

Integral Mode characteristics:

- 1) Output is integral of error over time
- 2) Drives steady-state error to zero
- 3) Adds pole to transfer function at  $s=0$  (infinite gain to constant)
- 4) Integrators tend to make systems less stable

### Equations

Time:  $v(t) = K_I \cdot \int_0^t e(t) dt + v_0$

Where  $K_I$  = integral gain constant

Laplace:  $V(s) = K_I \cdot \left[ \frac{1}{s} \right] \cdot E(s)$


Transfer Function:  $\frac{V(s)}{E(s)} = K_I \cdot \left[ \frac{1}{s} \right]$

lesson16et438a.pptx

12

## OP AMP Realizations of Integral Control

Ideal OP AMP Integrator

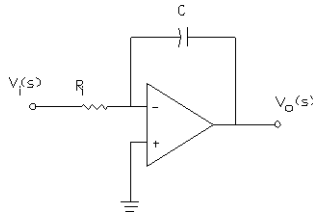


Transfer Function

$$\frac{V_o(s)}{V_i(s)} = \frac{-1}{R_i \cdot C} \cdot \left[ \frac{1}{s} \right] \quad K_I = \frac{-1}{R_i \cdot C}$$

One pole at  $s=0$

Practical OP AMP Integrator

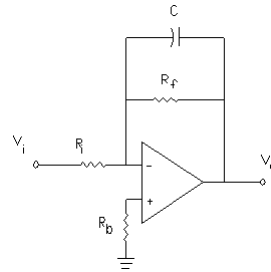

Transfer Function

$$\frac{V_o(s)}{V_i(s)} = \left[ \frac{-R_f}{R_i} \right] \left[ \frac{1}{1 + R_f \cdot C \cdot s} \right]$$

One pole at  $s = -1/R_f \cdot C$

lesson16et438a.pptx

13

## Bode Plots of Integrator Circuits

Substitute  $j\omega$  for  $s$  and find the magnitude and phase shift of the transfer function for different values of  $\omega$ .

Ideal Integrator

$$G(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{-1}{R_i \cdot C \cdot j\omega}$$

Practical Integrator

$$G(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \left[ \frac{-R_f}{R_i} \right] \left[ \frac{1}{1 + R_f \cdot C \cdot j\omega} \right]$$

Take magnitude and phase shift of each of these functions using rules of complex numbers.

$$z = a + jb$$

Magnitude of  $z$ :  $z = |z|$

$$|z| = \sqrt{a^2 + b^2} = \sqrt{\text{Re}(z)^2 + \text{Im}(z)^2}$$

Scale for dB  $\text{dB} = 20 \cdot \log(|G(j\omega)|)$

Phase Shift

$$\phi = \tan^{-1} \left[ \frac{b}{a} \right] = \tan^{-1} \left[ \frac{\text{Im}(z)}{\text{Re}(z)} \right]$$

lesson16et438a.pptx

14

## Bode Plots of Integrator Circuits

### Practical Integrator Circuit

$$G(j\omega) = \left[ \frac{-R_f}{R_i} \right] \left[ \frac{1}{1 + R_f \cdot C \cdot j\omega} \right]$$

Taking magnitude gives

$$|G(j\omega)| = \left[ \frac{-R_f}{R_i} \right] \left[ \frac{1}{\sqrt{1 + R_f^2 \cdot C^2 \cdot \omega^2}} \right]$$

$$\text{dB} = 20 \cdot \log(|G(j\omega)|)$$

Phase Shift gives

$$\phi(\omega) = 180 - \tan^{-1}[R_f \cdot C \cdot \omega]$$

180 degree phase shift is from inverting configurations

### Ideal Integrator Circuit

Magnitude gives

$$|G(j\omega)| = \frac{1}{R_i \cdot C} \quad \text{dB} = 20 \cdot \log(|G(j\omega)|)$$

Phase shift

$$\frac{1}{j} = -j = -90^\circ \quad \phi = 180^\circ - 90^\circ = 90^\circ \quad \text{Contant value}$$

lesson16et438a.pptx

15

## Integrator Bode Plots Using MatLAB

$$G(j\omega) = \left[ \frac{-R_f}{R_i} \right] \left[ \frac{1}{1 + R_f \cdot C \cdot j\omega} \right]$$

$$G(j\omega) = \frac{-1}{R_i \cdot C \cdot j\omega}$$

Use MatLAB script to generate Bode plots and transfer function.

Define parameters:  $R_i = 10 \text{ k}\Omega$ ,  $R_f = 100 \text{ k}\Omega$ ,  $C = 0.01 \text{ }\mu\text{F}$

### MatLAB Script

```
ri=input('Enter value of input resistance: ');
c=input('Enter value of capacitance: ');
rf=input('Enter value of feedback resistance: ');

% compute transfer function model parameters for
% practical integrator

tau=rf*c;
ki=-rf./ri;
```

Input  
statement

Comments  
begin with  
%

lesson16et438a.pptx

16



## Integrator Bode Plots Using MatLAB

### MatLAB Script (Continued)

```
% compute parameter for ideal integrator
tau I = ri*c;
```

```
% build transfer functions
% denominator form is a l*s^2+a2s+a3
```

```
Av=tf([ki],[tau I])
AvI=tf([-I],[tauI 0])
```

```
%plot both on the same graphs
bode(Av,AvI);
```


Create  
transfer  
functions

Plot both  
graphs on  
same figure

lesson16et438a.pptx

17

## Integrator Bode Plots Using MatLAB

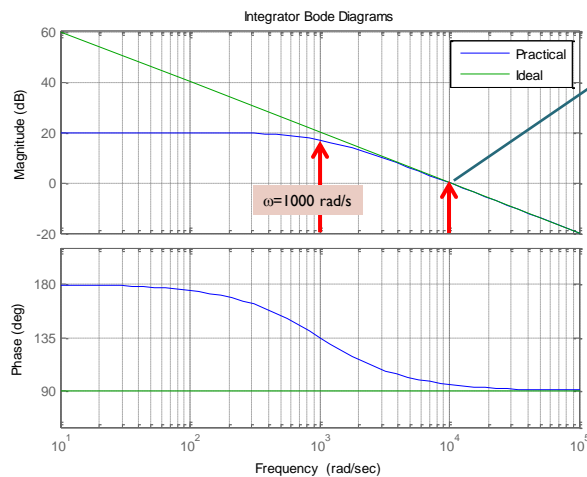


lesson16et438a.pptx

18
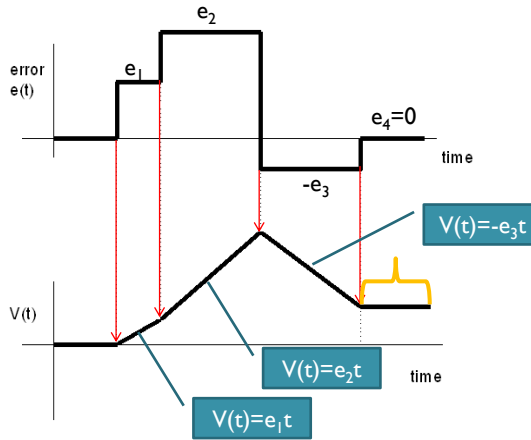
## Integral Action on Time Varying Error Signals

Integral of constant, k, is line with slope k.



Integrator produces a linearly increasing output for constant error input

Negative error causes decreasing output

Zero error maintains last output value


lesson16et438a.pptx

19
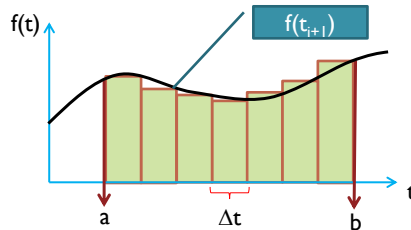
## Estimating Integrator Output

From Calculus, integral is sum of area below a function plot

$$\int_a^b f(t) dt \approx \sum_{i=0}^n (f(t_{i+1})) \cdot \Delta t \quad \text{Where } \Delta t = t_{i+1} - t_i = \frac{b-a}{n}$$



For linear error plots, integral is the sum of the areas of linear segments. Use triangle, trapezoid, and rectangle formulas to approximate output

lesson16et438a.pptx

20

## Integrator Output

**Example 16-2:** An ideal integrator has a gain of  $K_I = 0.1 \text{ V/s}$ . Its initial output is  $v = 1.5 \text{ V}$ . Determine the integrator outputs if the error has step increases given by the table below.


Error Magnitude (V)	Time Interval
$e(t) = 0$	$0 \leq t \leq 1$ seconds
$e(t) = 2.5$	$1 < t \leq 2$ seconds
$e(t) = 4$	$2 < t \leq 3$ seconds
$e(t) = 0$	$3 < t \leq 4$ seconds
$e(t) = -1.5$	$4 < t \leq 5$ seconds

lesson16et438a.pptx

21
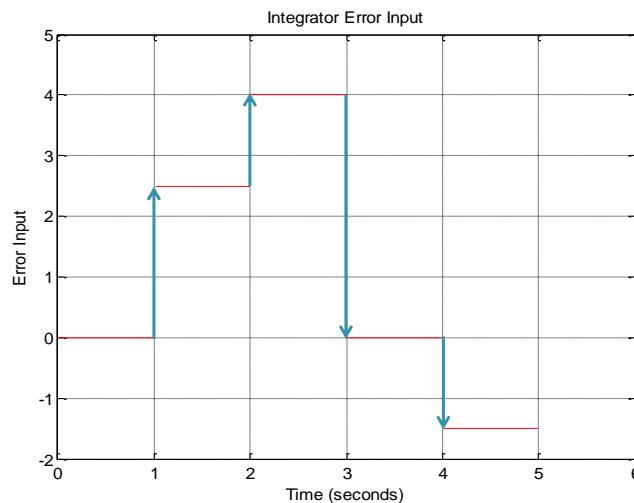
## Example 16-2 Solution (1)

Plot the error function that is input to the integrator




lesson16et438a.pptx

22
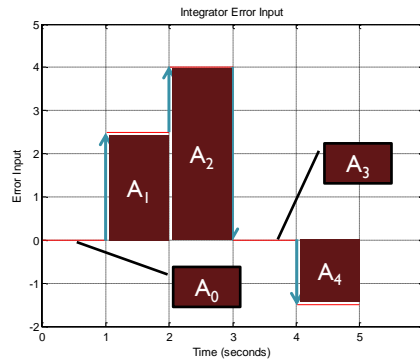
## Example 16-2 Solution (1)

Use the approximate formula to find the error at the end of each interval

$$v_i = K_I \cdot \sum_{i=0}^n e_i \cdot \Delta t \quad \text{Where } \Delta t = 1 \quad n = 5$$



$$V_0 = 1.5$$

$$A_0 = K_I \cdot \Delta t \cdot e_0 = 0.1(1)(0) = 0$$

$$V_1 = 1.5 + A_0 = 1.5 + 0 = 1.5$$

$$A_1 = K_I \cdot \Delta t \cdot e_1 = 0.1(1)(2.5) = 0.25$$

$$V_2 = 1.5 + A_1 = 1.5 + 0.25 = 1.75$$

$$A_2 = K_I \cdot \Delta t \cdot e_2 = 0.1(1)(4) = 0.40$$

$$V_3 = 1.75 + A_2 = 1.75 + 0.40 = 2.15$$

$$A_3 = K_I \cdot \Delta t \cdot e_3 = 0.1(1)(0) = 0$$

$$V_4 = 2.15 + A_3 = 2.15 + 0.0 = 2.15$$

$$A_4 = K_I \cdot \Delta t \cdot e_4 = 0.1(1)(-1.5) = -0.15$$


$$V_5 = 2.15 + A_4 = 2.15 + (-0.15) = 2.00$$

lesson16et438a.pptx

23

## Example 16-2 Solution (2)

Integrator output plot

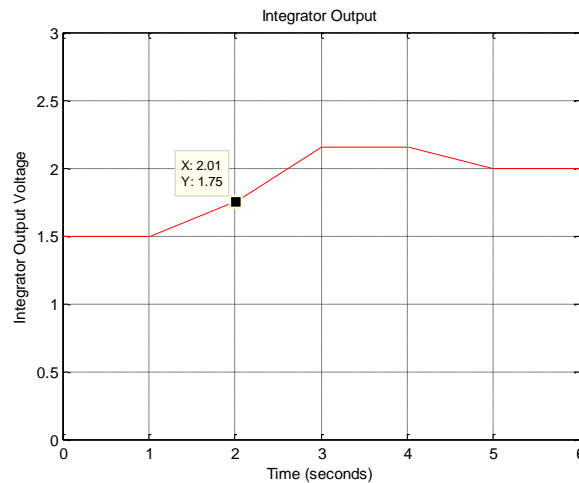

lesson16et438a.pptx

24

## Derivative Control Mode

Derivative Control Characteristics:

- 1) Produces output only when error is changing
- 2) Output is proportional to rate of change in error
- 3) Derivative control never used alone
- 4) Used with proportional and/or integral modes
- 5) Anticipates error by observing the rate of change

lesson16et438a.pptx

25

## Derivative Mode Equations

Time Equation: 
$$v(t) = K_d \cdot \frac{de(t)}{dt}$$

Laplace Equation: 
$$V(s) = K_d \cdot s \cdot E(s)$$

Transfer Function Equation: 
$$\frac{V(s)}{E(s)} = K_d \cdot s$$


Differentiators are high-pass filters to sinusoidal signals. They increase sensitivity to rapid error changes when added to controllers.

lesson16et438a.pptx

26

## OP AMP Realizations of Differentiators

Ideal OP AMP Differentiator

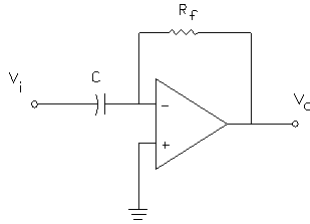


Transfer Function

$$\frac{V_o(s)}{V_i(s)} = -R_f \cdot C \cdot s$$

Introduces one zero at  $s=0$

Practical OP AMP Differentiator

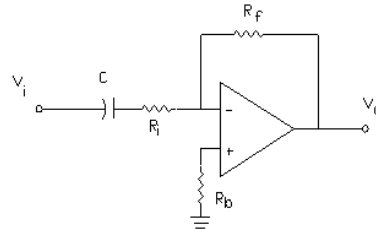

Transfer Function

$$\frac{V_o(s)}{V_i(s)} = \frac{-R_f \cdot C \cdot s}{1 + R_i \cdot C \cdot s}$$

Introduces: zero at  $s=0$   
pole at  $s=-1/R_i \cdot C$

lesson16et438a.pptx

27

## Bode Plots of Differentiators

Ideal Differentiator Equations

$$G(j\omega) = \frac{V_o(s)}{V_i(s)} = -R_f \cdot C \cdot j\omega$$

$$|G(j\omega)| = R_f \cdot C \cdot \omega$$

$$\text{dB} = 20 \cdot \log[|G(j\omega)|]$$

$$\phi = 90^\circ \quad \text{Constant over all } \omega$$

Practical Differentiator Equations

$$G(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{-R_f \cdot C \cdot j\omega}{1 + R_i \cdot C \cdot j\omega}$$

$$|G(j\omega)| = \frac{R_f \cdot C \cdot \omega}{\sqrt{1 + R_i^2 \cdot C^2 \cdot \omega^2}}$$

$$\text{dB} = 20 \cdot \log[|G(j\omega)|]$$

$$\phi = 270^\circ - \tan^{-1}(R_i \cdot C \cdot \omega)$$


Use MatLAB script to generate Bode plots and transfer function.

Define parameters:  $R_i = 10 \text{ k}\Omega$ ,  $R_f = 100 \text{ k}\Omega$ ,  $C = 0.01 \text{ }\mu\text{F}$

lesson16et438a.pptx

28

## Bode Plots of Differentiators

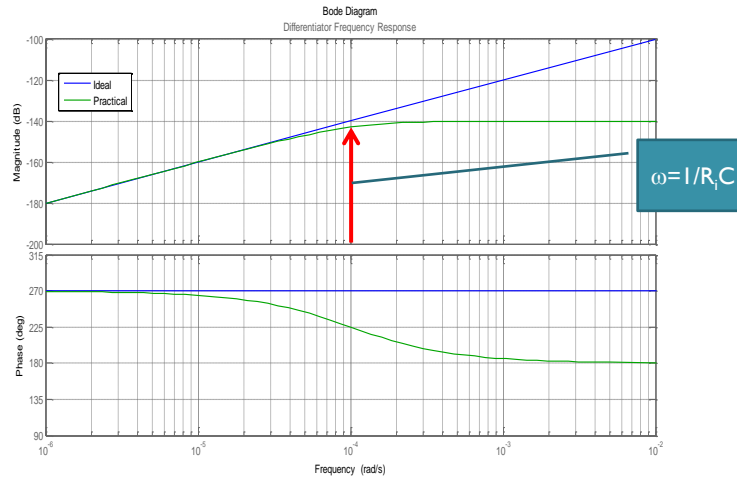

lesson16et438a.pptx

29

ET 438a Automatic Control Systems Technology

## END LESSON 16: BASIC CONTROL MODES

lesson16et438a.pptx

30