

Lesson 3: Operational Amplifier Circuits in Analog Control

ET 438a
Automatic Control Systems Technology

lesson3et438a.pptx

1

After this presentation you will be able to:

- List the characteristics of an ideal Operational Amplifier (OP AMP) circuit.
- Identify and utilize fundamental OP AMP circuits to amplify and signals.
- Use OP AMP circuits to reduce inter-stage loading effects in sensor circuits.
- Average sensor signals using OP AMP circuits.

LEARNING OBJECTIVES

lesson3et438a.pptx

2

The diagram shows an ideal operational amplifier (OP AMP) model. It features an inverting terminal (-) and a non-inverting terminal (+). The input impedance is labeled as Z_{in} and is described as infinite. The output impedance is labeled as Z_{out} and is zero. The voltage gain is labeled as A_v and is infinite. The output voltage is V_o and is equal to the input voltage V_d when $V_d = 0$. The input current I_{in} is zero due to the infinite input impedance.

INVERTING TERMINAL (-)

NON-INVERTING TERMINAL (+)

Characteristics:

- $Z_{out} = 0$
Zero output resistance
- No offset voltage,
 $V_o = 0$ with $V_d = 0$
- Infinite voltage gain,
 A_v
- Bandwidth Infinite
Gain constant for all f
- Instant recovery
from saturation
- $I_{in} = 0$ due to
infinite Z_{in}

Ideal OP AMP Characteristics

lesson3et438a.pptx 3

OP AMPs are voltage amplifiers designed originally for use in analog computers

OP AMPs are direct coupled (dc) amplifiers that amplify both ac and dc signals simultaneously. Requires bipolar supplies.

The schematic symbol for a non-ideal OP AMP shows two inputs: V_1 (inverting input, -) and V_2 (non-inverting input, +). The output is V_o . The supply rails are labeled $+V$ and $-V$.

Characteristics:

- $V_1 > 0, V_o < 0$
- $V_2 > 0, V_o > 0$


Schematic symbol for non-ideal OP AMP

Two inputs: V_1 = inverting input
 V_2 = non inverting input

Non-Ideal OP AMPs

lesson3et438a.pptx 4


Inverting Voltage Amplifier

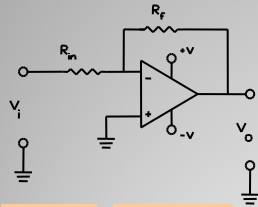

$$A_v = \frac{-R_f}{R_{in}} \quad V_o = V_i \left(\frac{-R_f}{R_{in}} \right)$$

V_o Limited by saturation
Large A_v causes $V_o = \pm V$

Non-Inverting Voltage Amplifier

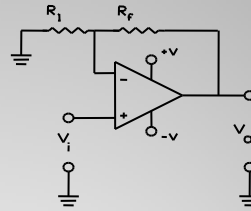

$$A_v = \left(1 + \frac{R_f}{R_{in}} \right) \quad V_o = V_i \left(1 + \frac{R_f}{R_{in}} \right)$$


$R_{in} = R_{in}$ of OP AMP
 A_v has minimum value of 1

Fundamental OP AMP Circuits

lesson3et438a.pptx

5

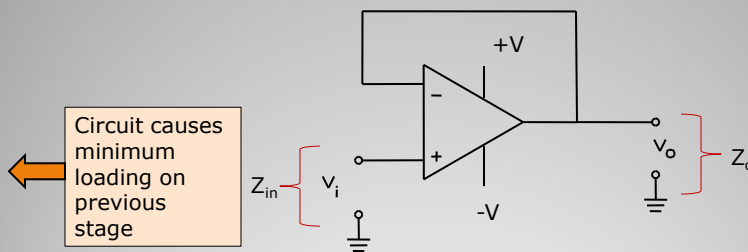Voltage follower (Impedance buffer) circuit used to reduce circuit loading. (Has a high Z_{in} and low Z_{out})



Circuit causes minimum loading on previous stage

Characteristics

Practical Circuit (LM741)

$$A_v = 1$$

$$Z_{in} = 1 \text{ M}\Omega$$

$$Z_o = 10 \Omega$$

Ideal

$$A_v = 1$$

$$Z_{in} = \text{infinite}$$


$$Z_o = 0$$

Voltage Follower Circuit

lesson3et438a.pptx

6

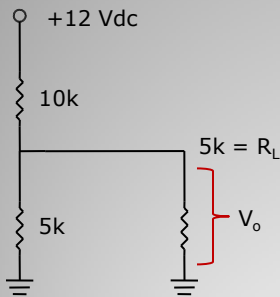Voltage divider formula only valid for infinite load resistance



Find V_o under load

No load V_o

$$V_o = \left(\frac{5 \text{ k}\Omega}{5 \text{ k}\Omega + 10 \text{ k}\Omega} \right) \cdot 12 \text{ V}$$

$$V_o = 4.0 \text{ V}$$

With load resistor

$$R_L \parallel 5 \text{ k}\Omega = 5 \text{ k}\Omega \parallel 5 \text{ k}\Omega = 2.5 \text{ k}\Omega$$


$$V_{oL} = \left(\frac{2.5 \text{ k}\Omega}{2.5 \text{ k}\Omega + 10 \text{ k}\Omega} \right) \cdot 12 \text{ V} = 2.4 \text{ V} \quad \leftarrow \text{ANS}$$

Example 3-1 Buffered Voltage Divider Circuit

lesson3et438a.pptx

7

Add impedance buffer

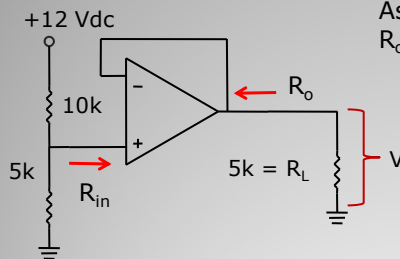

Find V_o with load and OP AMP buffer
Assume LM741 with $R_i = 1 \text{ M}\Omega$ and $R_o = 10 \Omega$ $A_v = 1$ so $V_{in} = V_o$

With load resistor

$$R_L \parallel 1 \text{ M}\Omega = 5 \text{ k}\Omega \parallel 1 \text{ M}\Omega = R_{eq}$$

$$R_{eq} = \frac{1 \text{ M}\Omega \cdot 5 \text{ k}\Omega}{1 \text{ M}\Omega + 5 \text{ k}\Omega} = 4975 \Omega$$

$$V_{in} = \left(\frac{4975 \Omega}{4975 \Omega + 10 \text{ k}\Omega} \right) \cdot 12 \text{ V} = 3.987 \text{ V}$$

$$V_{in} = V_o = 3.987 \text{ V} \quad \leftarrow \text{ANS}$$


Example 3-1 Buffered Voltage Divider Circuit (1)

lesson3et438a.pptx

8

Inverting Summing Amplifier

Find total output using superposition

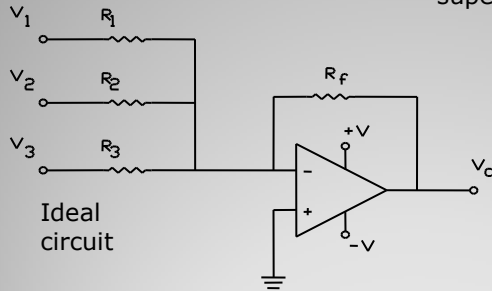

$$\text{Gain } v_1 \quad \frac{-R_f}{R_1}$$

$$\text{Gain } v_2 \quad \frac{-R_f}{R_2}$$

$$\text{Gain } v_3 \quad \frac{-R_f}{R_3}$$

Total output $V_0 = -R_f \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$


Output is inverted sum of v_1 , v_2 , and v_3

Electronic Addition and Subtraction

lesson3et438a.pptx

9

Improved circuit (non-ideal OP AMP)

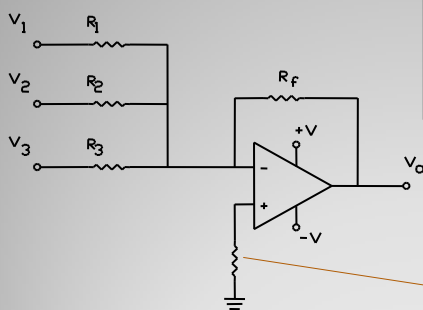

Practical OP AMP chips require bias currents to operate. Unequal R values at each input cause voltage differences that produce output errors.

Bias compensation R


$$R_c = R_1 \parallel R_2 \parallel R_3 \parallel R_f$$

Electronic Addition and Subtraction

lesson3et438a.pptx

10

Non-inverting Summing Amp

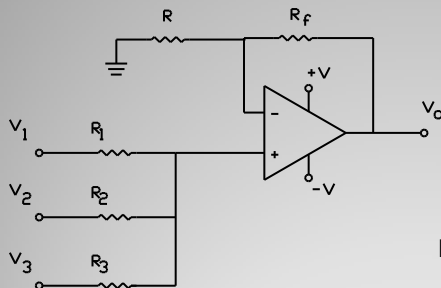

Assuming $R_1 = R_2 = R_3$

$$v_o = \left(1 + \frac{R_f}{R}\right) \left(\frac{v_1 + v_2 + v_3}{3}\right)$$

For any number, n , inputs.


$$v_o = \left(1 + \frac{R_f}{R}\right) \left(\frac{v_1 + v_2 + \dots + v_n}{n}\right) \quad n \text{ input average}$$

Assuming $R_1 = R_2 = R_3 = \dots = R_n$

Electronic Addition and Subtraction

lesson3et438a.pptx

11

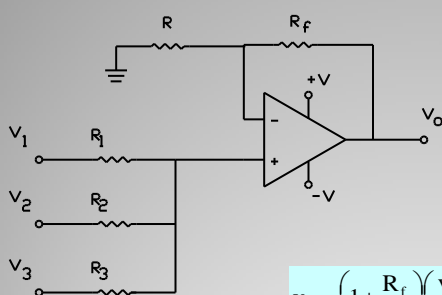

For circuit shown $n=3$

$R_1 = R_2 = R_3 = 56k$

$R_f = 9k$ $R = 1k$

$V_1 = 0.5 \text{ Vdc}$

$V_2 = 0.37 \text{ Vdc}$

$V_3 = 0.8 \text{ Vdc}$ Find V_o

$$v_o = \left(1 + \frac{R_f}{R}\right) \left(\frac{v_1 + v_2 + v_3}{3}\right)$$


$$v_o = \left(1 + \frac{9k}{1k}\right) \left(\frac{0.5 + 0.37 + 0.8}{3}\right) = 5.5667 \quad \leftarrow \text{ANS}$$

Example 3-2 Non-inverting Averager

lesson3et438a.pptx

12

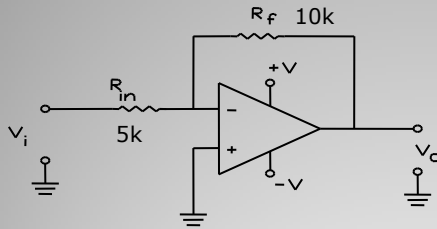For the circuit shown find V_o with $V_{in} = 2 \text{ Vdc}$



$$V_o = \frac{-R_f}{R_{in}} V_i$$

$$V_o = \frac{-10k\Omega}{5k\Omega} V_i$$

$$V_o = -2V_i \quad V_i = 2.0$$

$$V_o = -2(2.0V) = \boxed{-4 \text{ Vdc}}$$

LET $R_f = 5k\Omega$ Find A_V and V_o for $V_i = 2.0$

$$A_V = \frac{-R_f}{R_i} = \frac{-5k\Omega}{5k\Omega} = \boxed{-1} \text{ Inverting voltage follower}$$


$$V_{in} = 2.0 \text{ Vdc}$$

$$V_o = (-1)(2 \text{ Vdc}) = \boxed{-2.0 \text{ Vdc}}$$

Example 3-3: Inverting Amplifier

lesson3et438a.pptx

13

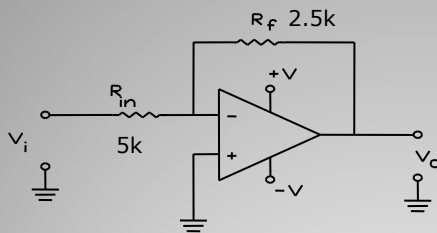

Let $R_f = 2.5 \text{ k}\Omega$ and find A_V and V_o for $V_i = 2.0 \text{ Vdc}$

$$A_V = \frac{-R_f}{R_{in}} = \frac{-2.5k\Omega}{5k\Omega} = -0.5$$

Reduces input voltage

$$V_o = A_V V_i = -0.5(2.0V) = -1Vdc$$


Output is smaller than input. Circuit divides input by 2
($0.5 = \frac{1}{2}$)

Example 3-3: Solution (2)

lesson3et438a.pptx

14

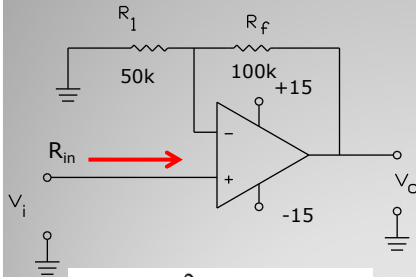Find V_o and A_v given values of R and $V_i = -1$ Vdc. Assume non-ideal OP AMP with power supply values of ± 15 Vdc



$$V_o = V_i \left(1 + \frac{R_f}{R_1}\right) = V_i \left(1 + \frac{100k\Omega}{50k\Omega}\right)$$

$$V_o = -1(3) = -3 \text{ Vdc}$$

No sign change

$$A_v = \left(1 + \frac{R_f}{R_1}\right) = 1 + \frac{100k\Omega}{50k\Omega}$$


$$A_v = 1 + 2 = 3$$

Note: R_{in} of non-inverting OP AMP is infinite (Ideally). Circuit will not load previous stage significantly

Example 3-4 Non-Inverting Amp (1)

lesson3et438a.pptx

15

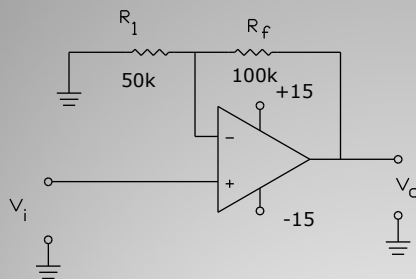

V_{in} rises to 6 Vdc. What is V_o ? Assume a non-ideal OP AMP with given power supply values of ± 15 Vdc

$$V_o = A_v V_i = 3(6) = 18 \text{ Vdc}$$

This value can't be achieved since the OP AMP saturates between 13-15 Vdc. Power supplies limit output. Ac signals distorted (clipping)

Example 3-4 Solution (2)

lesson3et438a.pptx

16

Find V_o given $v_1 = 0.2$ Vdc $v_2 = 0.1$ Vdc
 $v_3 = -0.1$ Vdc

$$V_o = -R_f \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

$$V_o = -\frac{R_f}{R_1} V_1 - \frac{R_f}{R_2} V_2 - \frac{R_f}{R_3} V_3$$

$$V_o = \frac{-100k}{25k} V_1 + \frac{-100k}{15k} V_2 + \frac{-100k}{10k} V_3$$

$$V_o = -4(0.20) - 6.667(0.1) - 10(-0.1)$$

Gains

$$V_o = -0.8 - 0.6667 + 1.0 \text{ Vdc}$$

$$V_o = -0.4667 \text{ Vdc}$$

Example 3-5 Inverting Summing Amplifier


lesson3et438a.pptx 17

Letting R_1 , R_2 and R_3 be potentiometers produces an audio mixer

When $R_1=R_2=R_3$ Output voltage is the average of the input values

Summing Amplifier Applications

lesson3et438a.pptx 18

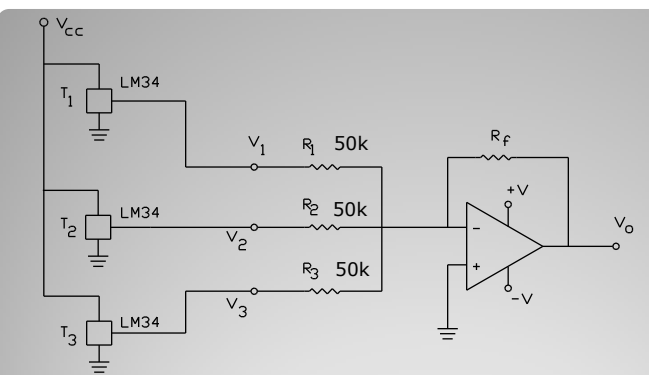

LM34 - temperature sensors. Gain = 10 mV/F
 $T_1 = 50\text{ F}$ $T_2 = 45\text{ F}$ $T_3 = 40\text{ F}$

Average the temperature using a gain of -1 and -5. Find the value of R_f and V_o for each gain value.

Example 3-6: Averaging Sensor Signals

lesson3et438a.pptx 19

To average let $R_1=R_2=R_3=50\text{ k}\Omega$

Summing equation
$$V_o = -R_f \left(\frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_3}{R_3} \right)$$

Since $R_1=R_2=R_3$
$$V_o = -R_f \left(\frac{v_1}{R_1} + \frac{v_2}{R_1} + \frac{v_3}{R_1} \right) = -\left(\frac{R_f}{R_1} \right) (v_1 + v_2 + v_3)$$

Find relationship for average with 3 inputs and gain of -1

$$V_{\text{ave}} = -1 \cdot \left[\frac{v_1 + v_2 + v_3}{3} \right]$$

$$V_o = V_{\text{ave}} = -\left(\frac{R_f}{R_1} \right) (v_1 + v_2 + v_3) = -\left(\frac{1}{3} \right) (v_1 + v_2 + v_3)$$

Example 3-6 Solution (1)

lesson3et438a.pptx 20

Complete Algebra to
find value of R_f

$$-\left(\frac{R_f}{R_1}\right) = -\left(\frac{1}{3}\right)$$

$$R_f = \frac{R_1}{3}$$

Make equation more general by letting n be the number of inputs and A_v be the desired gain factor.

$$V_o = -R_f \left(\frac{v_1}{R_1} + \frac{v_2}{R_1} \dots + \frac{v_n}{R_1} \right) = -\left(\frac{R_f}{R_1}\right) (v_1 + v_2 \dots + v_n)$$

$$V_{ave} = -A_v \cdot \left[\frac{v_1 + v_2 \dots + v_n}{n} \right]$$

Example 3-6 Solution (2)

lesson3et438a.pptx

21

Equate the OP AMP output and the average formula

$$V_o = V_{ave} = -\left(\frac{R_f}{R_1}\right) (\cancel{v_1 + v_2 \dots + v_n}) = -\left(\frac{A_v}{n}\right) (\cancel{v_1 + v_2 \dots + v_n})$$

$$-\left(\frac{R_f}{R_1}\right) = -\left(\frac{A_v}{n}\right)$$

$$R_f = \frac{A_v \cdot R_1}{n}$$

Use this formula

Find sensor output voltages using temperature and gain value

$$T_1 = 50^\circ \text{ F} \quad V_1 = (10 \text{ mV/F})(50^\circ \text{ F}) = 0.5 \text{ V}$$

$$T_2 = 45^\circ \text{ F} \quad V_2 = (10 \text{ mV/F})(45^\circ \text{ F}) = 0.45 \text{ V}$$

$$T_3 = 40^\circ \text{ F} \quad V_3 = (10 \text{ mV/F})(40^\circ \text{ F}) = 0.40 \text{ V}$$

Example 3-6 Solution (3)

lesson3et438a.pptx

22

Find R_f and V_o for a gain of -1 and $R_1=50 \text{ k}\Omega$, $n=3$

$$R_f = \frac{A_v \cdot R_1}{n} = \frac{1 \cdot 50,000 \Omega}{3} = 16,670 \Omega$$

← ANS

$$-\left(\frac{R_f}{R_1}\right)(v_1 + v_2 + v_3) = -\left(\frac{16.67\text{k}}{50\text{k}}\right)(0.50 + 0.45 + 0.40) = -0.45 \text{ V}$$

← ANS

Use average formula to check output

$$V_{\text{ave}} = -1 \cdot \left(\frac{0.50 + 0.45 + 0.40}{3}\right) = -0.45$$

Checks

Example 3-6 Solution (4)

lesson3et438a.pptx

23

Find R_f and V_o for a gain of -5 and $R_1=50 \text{ k}\Omega$, $n=3$

$$R_f = \frac{A_v \cdot R_1}{n} = \frac{5 \cdot 50,000 \Omega}{3} = 83,330 \Omega$$

← ANS

$$V_o = -\left(\frac{R_f}{R_1}\right)(v_1 + v_2 + v_3) = -\left(\frac{83.33\text{k}}{50\text{k}}\right)(0.50 + 0.45 + 0.40) = -2.25 \text{ V}$$

← ANS

$$V_{\text{ave}} = -5 \cdot \left(\frac{0.50 + 0.45 + 0.40}{3}\right) = -2.25$$

Note: both values of R_f are not standard values. Use potentiometer and closest standard value then calibrate circuit to get desired output



Example 3-6 Solution (5)

lesson3et438a.pptx

24

Differential Voltage Amplifier Circuit

Input/output Formula

$$V_o = \left(\frac{R_2 + R_1}{R_4 + R_3} \right) \cdot \left(\frac{R_4}{R_1} \right) \cdot V_2 - \left(\frac{R_2}{R_1} \right) \cdot V_1$$

To simplify let
 $R_1 = R_3 \quad R_2 = R_4$

$$V_o = \left(\frac{R_2}{R_1} \right) (V_2 - V_1)$$

Amplifiers the difference between + - terminals

Differential Voltage Amplifier

lesson3et438a.pptx 25

Can use voltage differential amp to generate an error signal


Block diagram

Measured value
 m
 r
 setpoint
 error

$e = r - m$

Differential Amplifier Applications

lesson3et438a.pptx 26

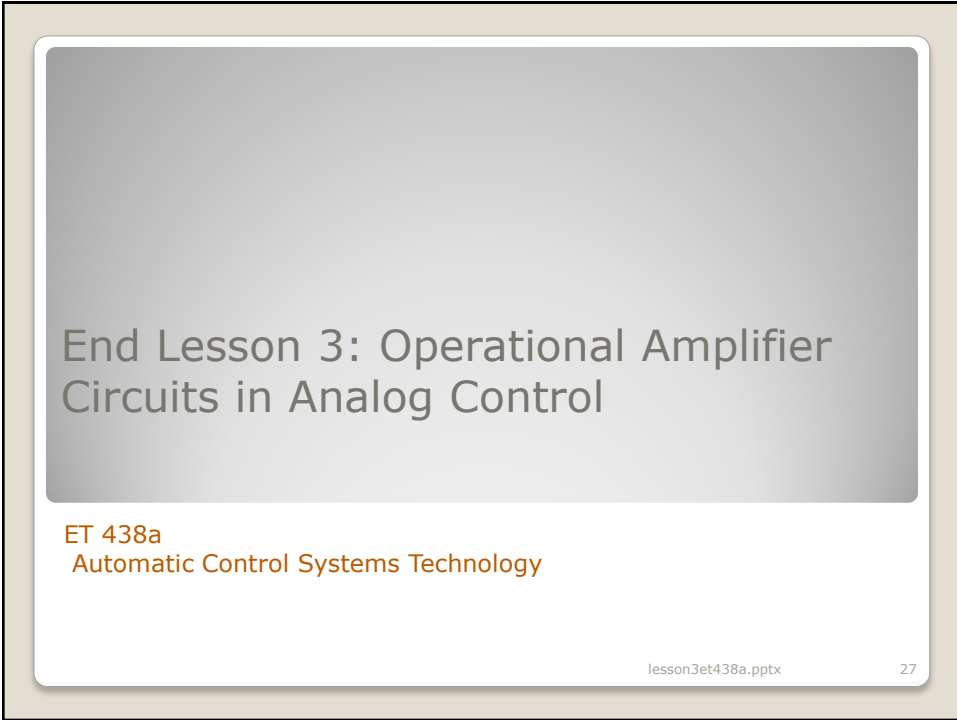

End Lesson 3: Operational Amplifier
Circuits in Analog Control

ET 438a
Automatic Control Systems Technology

lesson3et438a.pptx 27