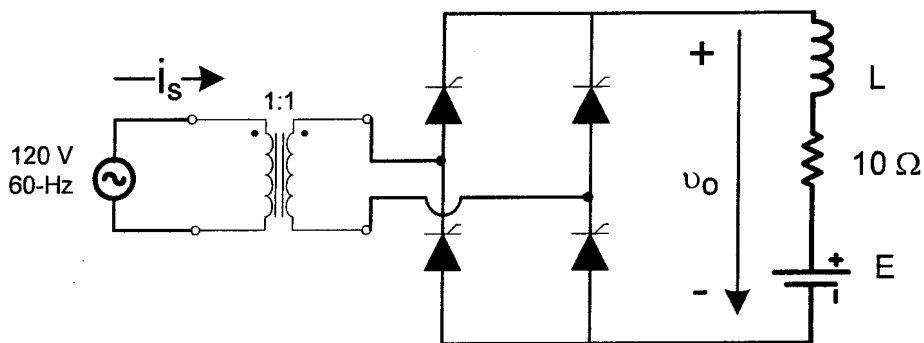


ECE 483/583 POWER ELECTRONICS

EXAM 1 (Closed books and notes, cheat sheet)

Problem 1 (50 points, assesses DO7,11): Consider the thyristor rectifier below.


- $E=0$ V and $L=0$ H. Draw the output voltage, v_o and the input current i_s , if the firing delay angle $\alpha=0^\circ$. Calculate the average value of v_o . Show the key values on the graph (10 points).
- $E=0$ V and $L=0$ H. Draw the output voltage, v_o and the input current i_s , if the firing delay angle $\alpha=90^\circ$. Calculate the average value of v_o . Show the key values on the graph (10 points).
- $E=50$ V and $L=\infty$. Draw the output voltage, v_o and the input current i_s , if the firing delay angle $\alpha=30^\circ$. Calculate the average value of v_o . Show the key values on the graph. Then find, the rms value of i_s ,
the rms value of the fundamental (60-Hz) component of i_s ,
the rms of the 3rd and 5th harmonics and the harmonic factor of i_s ,
also calculate the displacement factor, power factor and the input real and reactive powers (30 points).



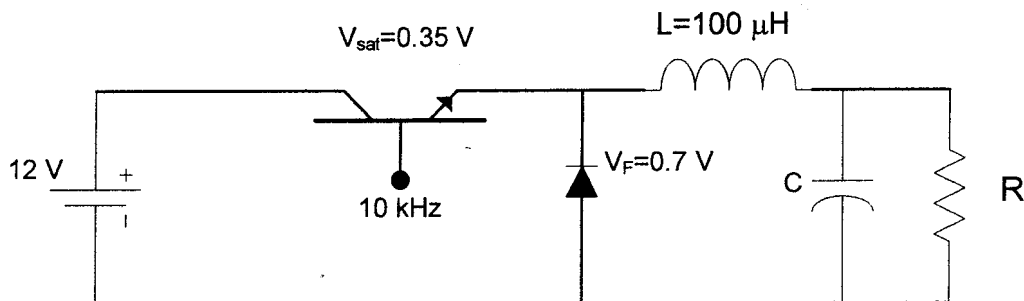Problem 2 (50 points, assesses DO7,8): Consider the buck regulator below. The desired output voltage is 9 V. The maximum output current is 8 A.


- Find the average, rms and peak values of the switch current.
- Find the value of the output capacitor to limit the output ripple to ± 1 V.
- Find the efficiency of the converter.
- If the minimum load current is 1 A, what is the critical value of the output inductor to maintain continuous conduction?

Provide proper figures and waveform plots to demonstrate your calculations.



SOLUTIONS

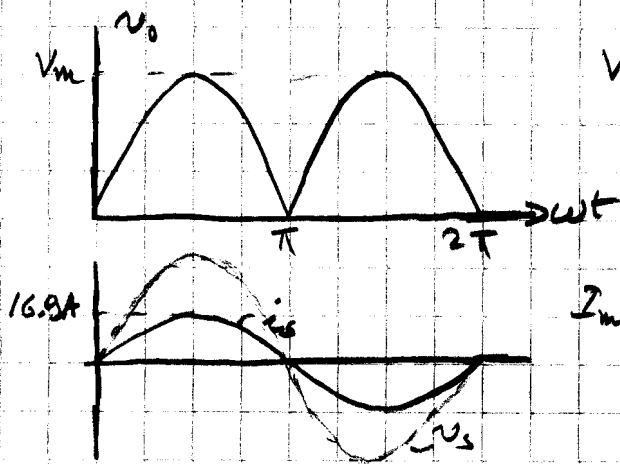P1.a: $\alpha = 0, E = 0V, L = 0H$ (purely resistive load)




$$V_m = \sqrt{2} \times 120 = 169.7V$$

$$V_{o,av} = \frac{2}{\pi} V_m = \underline{108.03V}$$

$$I_m = \frac{V_m}{R} = \underline{16.97A}$$

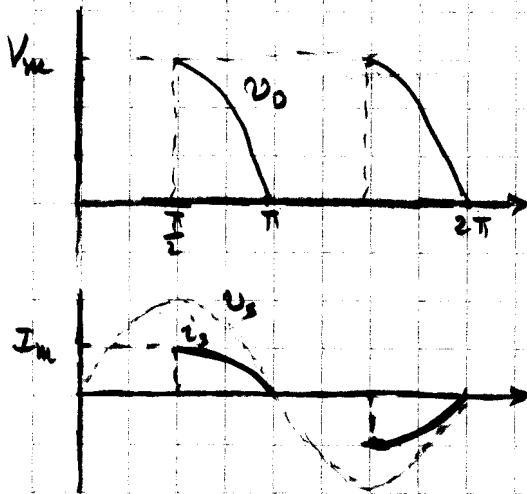
1.b: $\alpha = 90^\circ, E = 0V, L = 0H$ (purely resistive load) Discontinuous cond.



$$V_{o,av} = \frac{V_m}{\pi} (1 + \cos \alpha) = \frac{V_m}{\pi} = \underline{54.02V}$$

$$I_m = \frac{V_m}{R} = \underline{16.97A}$$

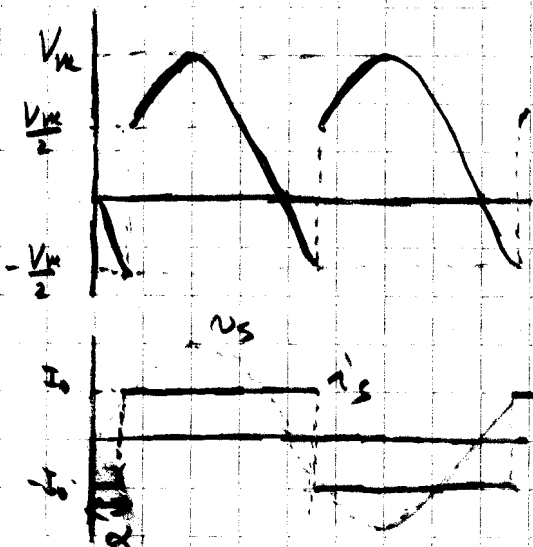1.c: $\alpha = 30^\circ, E = 50V, L = \infty$ (ripple free) Continuous cond.



$$V_{o,av} = \frac{2V_m}{\pi} \cos \alpha = \underline{93.56V}$$

$$I_{o,av} = \frac{V_{o,av} - E}{R} = \underline{4.35A}$$

$$I_{s,rms} = I_o = \underline{4.35A}$$

$$I_{s1,rms} = \frac{2\sqrt{2}}{\pi} I_o = \underline{3.02A}$$

$$I_{s2,rms} = \frac{2\sqrt{2}}{3\pi} I_o = \frac{I_{s1,rms}}{3} = 1.31A$$

$$I_{s3,rms} = I_{s1}/5 = 0.784A$$

$$P_{in} = V_s I_{s,rms} \cos \alpha = \underline{407.37W}$$

$$Q_{in} = V_s I_{s1,rms} \sin \alpha = \underline{235.2VAR}$$

$$HF = \frac{\sqrt{I_{s1,rms}^2 - I_o^2}}{I_{s1,rms}} = 48.1\%$$

$$PF = \frac{V_s I_{s1,rms} \cos \alpha}{V_m I_{s1,rms}} = 0.78 \text{ lag}$$

$$\cos \alpha = 0.866 = DF \text{ (lag)}$$


P. 2

a. Duty cycle: Assume continuous cond.

$$V_{LON} = 12 - 0.35 - 9 = 2.65V, \quad V_{LOP} = -0.7 - 9 = -9.7V$$

$$V_{LON} k T_s = |V_{LOP}| (1 - k) T_s \Rightarrow 2.65k = 9.7(1 - k) \Rightarrow \underline{k = 0.785}$$

Inductor current

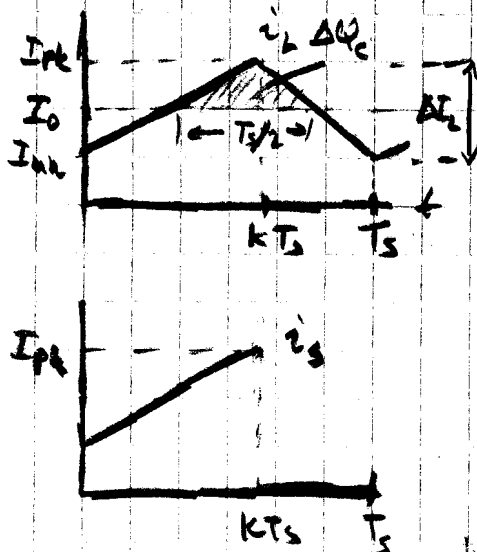

$$I_{L,av} = I_0 = 8A \text{ (at max. output current)}$$

$$\Delta I_L = \frac{V_{LON} k T_s}{L} = \frac{V_{LON} k}{L f_s} = \frac{2.65V \times 0.785}{100\mu H \times 100kHz} = \underline{\underline{2.08A}}$$

Therefore

$$I_{pk} = I_0 + \frac{\Delta I_L}{2} = \underline{\underline{9.04A}}, \text{ peak switch current}$$

$$I_{min} = I_0 - \frac{\Delta I_L}{2} = \underline{\underline{6.96A}}$$

$$I_{s,av} = k I_{L,av} = \underline{\underline{6.28A}}$$

$$I_{s,rms} = \sqrt{k} \cdot I_{L,rms}, \text{ but } I_{L,rms} \approx \sqrt{I_0^2 + \left(\frac{\Delta I_L}{2k}\right)^2} = \underline{\underline{8.034A}}$$

(Also, $I_{L,rms} \approx I_0$ acceptable)

$$\text{And } I_{s,rms} = \underline{\underline{7.12A}}$$

b. Capacitor charge:

$$\Delta Q_c = \frac{1}{2} \left(\frac{\Delta I_L}{2} \right) \frac{T_s}{2} =$$


$$= \frac{1}{8} \frac{\Delta I_L}{f_s} = 26 \mu C$$

and

$$C \geq \frac{\Delta Q_c}{\Delta V_0} = \frac{26 \mu C}{2V} = \underline{\underline{13 \mu F}} \text{ and } C_{min} = \underline{\underline{13 \mu F}}$$

c. $P_{in} = V_{in} \times I_{s,av} = 12V \times 6.28A = 75.36W$, $P_{out} = 9 \times 8 = 72W$, or $\eta = 95.5\%$.

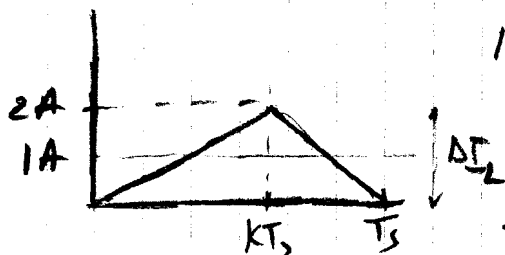d. Duty cycle remains same, $\underline{k = 0.785}$



In cont. cond. $I_{L,av} = I_0 = 1A$. From the figure

$$\Delta I_L = 2A. \text{ But } \Delta I_L = \frac{V_{LON} k T_s}{L} \Rightarrow L = \frac{V_{LON} k}{\Delta I_L f_s}$$

To sustain cont. cond

$$L \geq \frac{V_{LON} k}{\Delta I_L f_s} = \frac{2.65 \times 0.785}{2 \times 100kHz} = \underline{\underline{10.4 \mu H}}$$