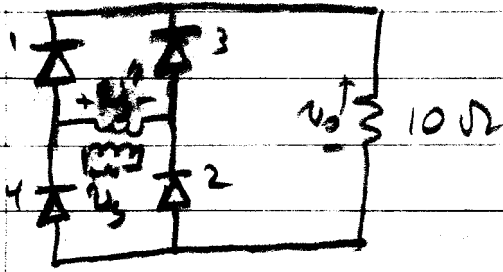


3.7

$$v_s'' = V_m'' \sin \omega t$$



CALCULATIONS

$$V_{o,av} = \frac{2V_m}{\pi} \Rightarrow V_m'' = \frac{\pi}{2} V_{o,av} = \underline{628.32 \text{ V}}$$

$$I_{o,av} = \frac{V_{o,av}}{R} = 40.0 \text{ A}$$

$$V_{o,rms} = V_s'' = \frac{628.32}{\sqrt{2}} = 444.3 \text{ V}$$

$$I_{o,rms} = \frac{V_{o,rms}}{R} = 44.4 \text{ A}$$

DIODE RATING

$V_{MR} = 628.3 \text{ V}$, repetitive reverse peak voltage

$I_{D,PK} = V_m''/R = 628 \text{ A}$, peak repetitive current

$I_{D,AV} = I_{o,AV}/2 = 20 \text{ A}$, Average current

$I_{D,RMS} = \frac{I_{o,rms}}{\sqrt{2}} = 31.4 \text{ A}$, RMS current

TRANSFORMER


$$V_s'' = 444.3 \text{ V} \quad \text{rms V}$$

$$I_s'' = 44.4 \text{ A} \quad \text{rms I}$$

$$VA = V_s'' I_s'' = 19682 \text{ VA}$$


2.12

20 V_{rms}
60 Hz

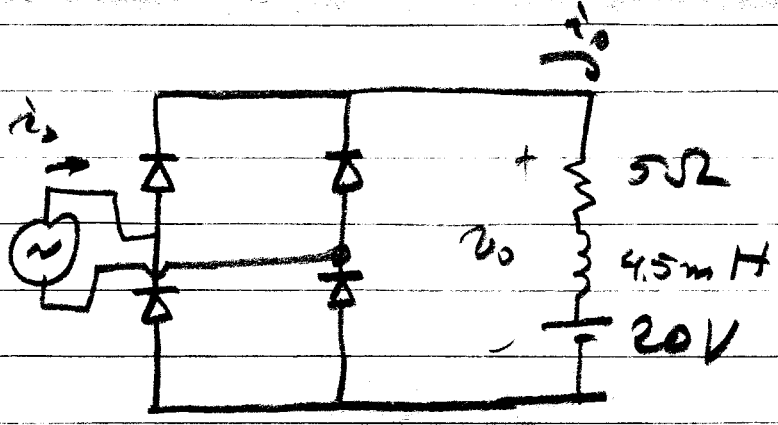

Assume $V_D = 0V$

$V_m = \sqrt{2} V_s = 169.7 V$

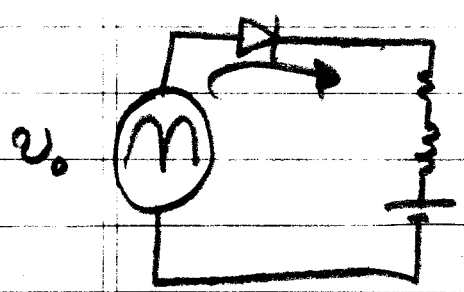

For continuous conduction v_o is a rectified v_s , or
 $v_o = V_m |\sin \omega t|$, using π


— part a —
(1) F.S.

$$v_o(t) = \frac{2V_m}{\pi} - \frac{4V_m}{\pi} \sum_{n=2,4,\dots} \frac{1}{(n-1)(n+1)} \cos n \omega t$$

using π first two terms ($n=2, 4$)


$$v_o(t) = 108.03 - 216.1 \left(\frac{1}{3} \cos 2\omega t + \frac{1}{15} \cos 4\omega t \right)$$
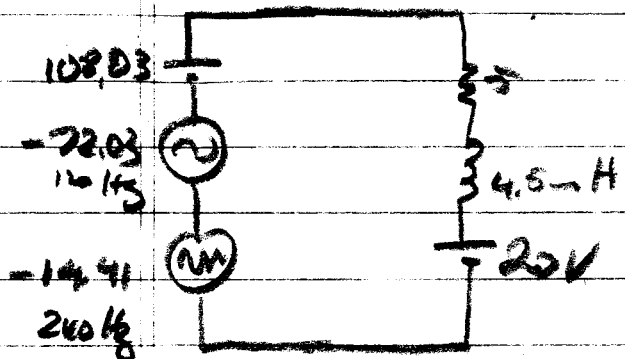
$$= 108.03 - 72.03 \cos 2\omega t - 14.41 \cos 4\omega t$$




Apply frequency
superposition

(a) $f = 0 \text{ Hz}$

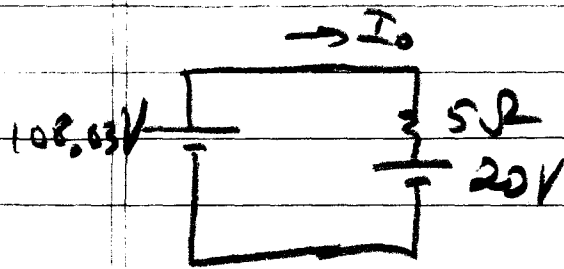


$$I_0 = \frac{108.03 - 20}{5} = 17.6 \text{ A}$$

(b) $f = 120 \text{ Hz}$

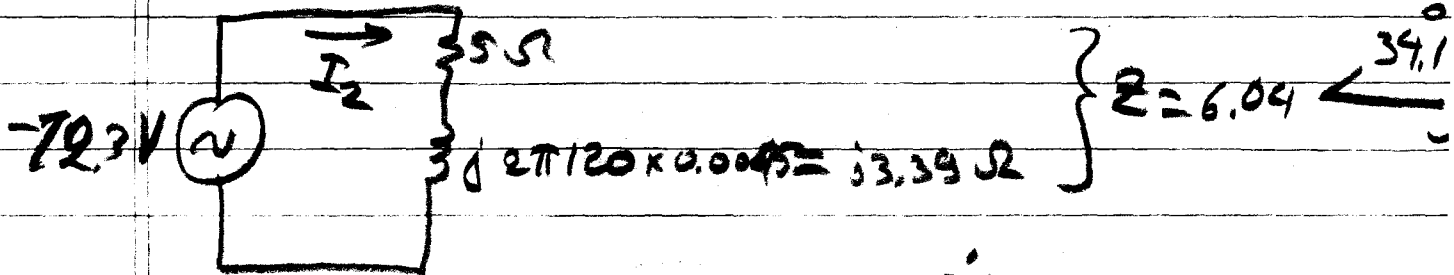

$$\bar{I}_2 = \frac{-72.3 \text{ V}}{6.03 \angle 34.1^\circ} = 12 \angle 145.9^\circ \text{ A} \text{ or } -12 \angle -34.1^\circ$$

(c) $f = 240 \text{ Hz}$

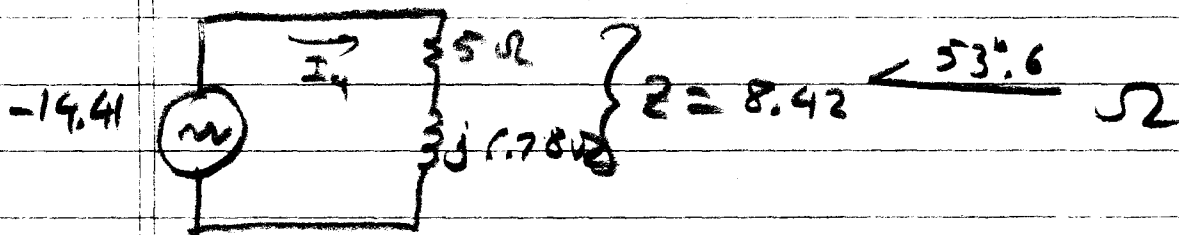

$$\bar{I}_3 = \frac{-14.4}{8.42 \angle 53.6^\circ} = 1.71 \angle 126.4^\circ \text{ A} \text{ or } -1.71 \angle -53.6^\circ$$

AND

$$i_0 \approx 17.6 \text{ A} - 12 \cos(2\omega t - 34.1^\circ) - 1.71 \cos(4\omega t - 53.6^\circ)$$

$$\text{at } \omega t = 0, \quad i_0 = 17.6 - 12 \cos(-34.1^\circ) - 1.71 \cos(53.6^\circ) = 6.55 \text{ A}$$





(2) Average diode current

$$I_{D,AV} = \frac{I_{0,AV}}{2} = 8.8 \text{ A}$$

(3) rms diode current $I_{D,rms} = \frac{I_{0,rms}}{\sqrt{2}}$, but $I_{0,rms} \approx \sqrt{17.6^2 + 12^2} = 21.1 \text{ A}$ $\rightarrow I_{D,rms} = 14.8 \text{ A}$

3,21

(a)

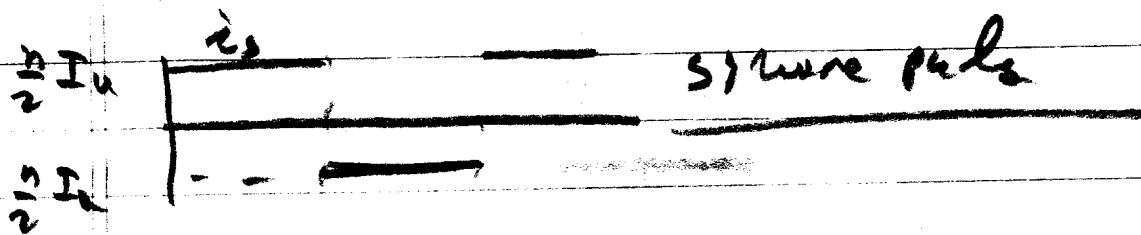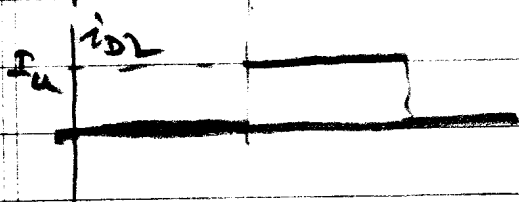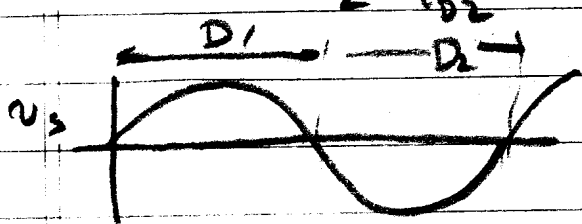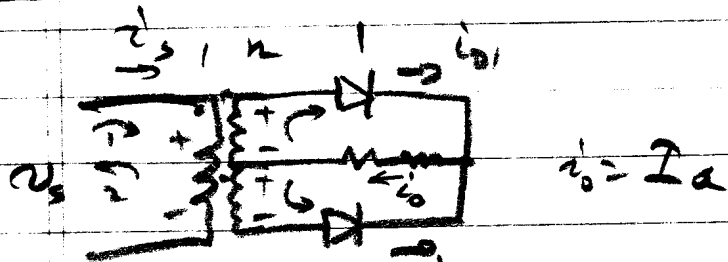

(b)

$i_o = \sum_{n=1,3,5} b_n \sin n\omega t$ only odd harmonics are sin because of odd symm.



$$b_n = \frac{1}{\pi} \int_0^{2\pi} i_o \sin n\omega t d\omega t = \frac{2}{\pi} \int_0^{\pi} I_a \sin n\omega t d\omega t =$$

$$= \frac{2I_a}{n\pi} (-\cos n\omega t) \Big|_0^{\pi} = \frac{2I_a}{n\pi} (1 - \cos n\pi) \quad n=1,3,5$$

$$\cos n\pi = -1 \Rightarrow b_n = \frac{4I_a}{n\pi} \quad \text{and}$$

$$i_o = \frac{4I_a}{\pi} \cos \omega t + \frac{4I_a}{\pi} \sum \frac{1}{n} \cos n\omega t$$

Prob 10.7

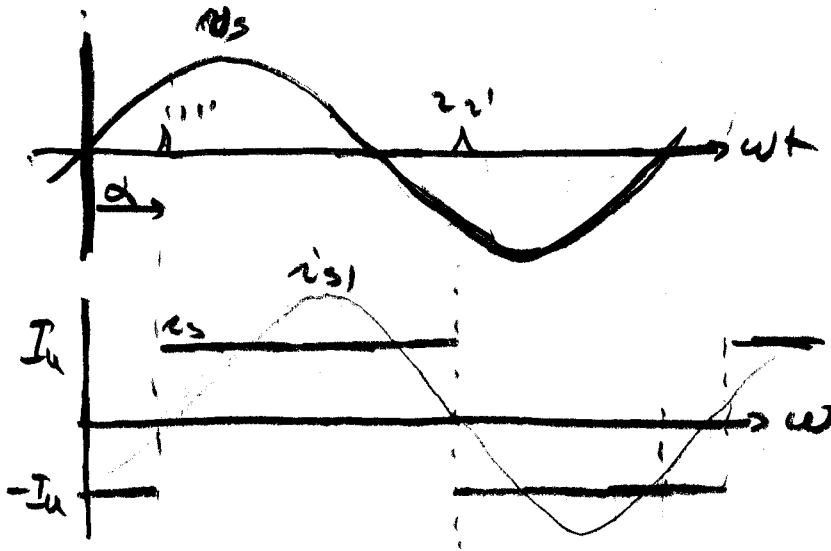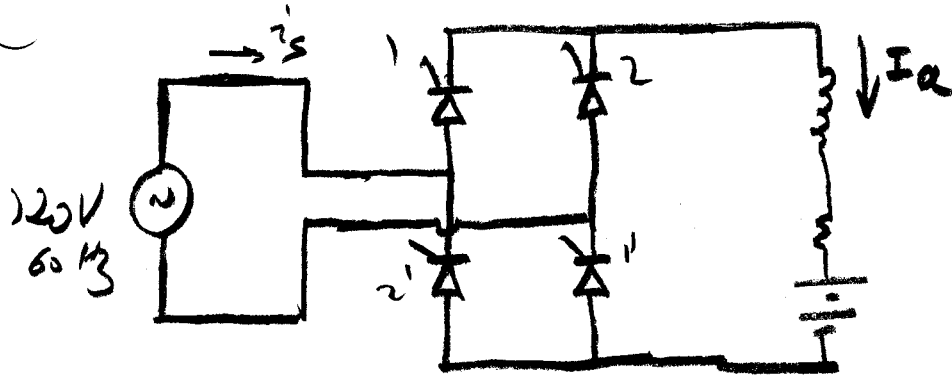

$$i_s = \frac{4I_a}{\pi} \sin(\omega t - \alpha) + \frac{4I_a}{\pi} \sum_{n=3,5}^{\infty} \frac{1}{n} \sin(n\omega t - n\alpha)$$

(a) RMS value of i_s , $I_s = I_a$


Fund. $i_{s1} = \frac{4I_a}{\pi} \sin(\omega t - \alpha)$, Fund. rms, $I_{s1} = \frac{2\sqrt{2}}{\pi} I_a = 0.9 I_a$

HF = $\frac{\sqrt{I_a^2 - 0.9^2 I_a^2}}{0.9 I_a} = 0.48$ (48%)

(b) DF = $\cos \alpha = \cos \frac{\pi}{3} = 0.5$

(c) pf = $\frac{V_s I_{s1} \cos \alpha}{V_s I_s} = \frac{I_{s1}}{I_s} \cos \alpha = \frac{0.9 I_a}{I_a} \cos \alpha = 0.9 \cos \alpha = 0.45$ lag

Prob 10.8

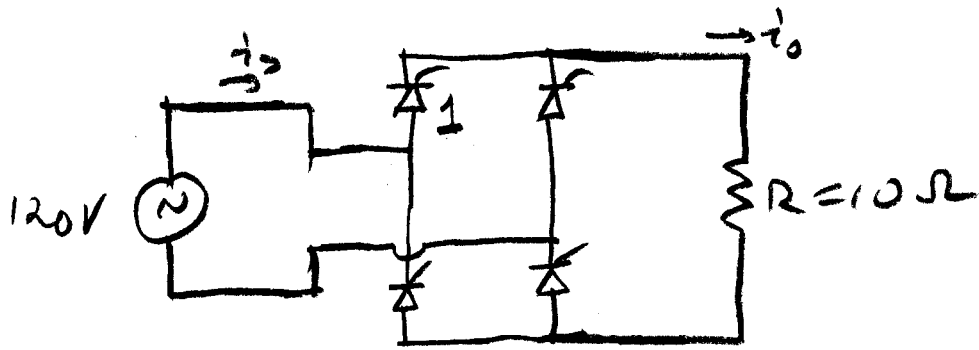

$$V_m = \sqrt{2} 120 = 169.7 \text{ V}$$

$$(a) V_{o,av,max} = \frac{2V_m}{\pi} = 108.03 \Rightarrow$$

$V_{o,av} = 25\% \cdot 108.03 = 27 \text{ V}$. but $V_{o,av} = \frac{2V_m}{\pi} \cos \alpha$ for a resistive load w/ large inductance.

$$\text{Thus } \cos \alpha = \frac{\pi \times 27}{2V_m} = 0.25 \Rightarrow \underline{\alpha = 75^\circ.5}$$

$$(b) i_o = \frac{V_{o,av}}{10} = \frac{27}{10} = 2.7 \text{ A const. (no ripple)}$$

$$i_s = \frac{2.7}{10} \cdot \sin \omega t = \frac{4 \times 10^{-8}}{\pi} \sum_{n=1,3,\dots} \frac{\sin(n\omega t - n\alpha)}{n}$$

$$I_s = 10.8 \text{ A (rms)}$$

$$I_{s1} = \frac{2V_m}{\pi} \times \frac{2.7}{10} = \frac{2.93}{10} \text{ A (fund. rms)}$$


(c) Thyristor current:

$$I_{T1,av} = \frac{10.8}{2} = 5.4 \text{ A (conducts } \frac{1}{2} \text{ periods)}$$

$$I_{T1,rms} = \frac{10.8}{\sqrt{2}} = 7.64 \text{ A}$$

$$(d) \text{ pf} = \frac{V_s I_{s1} \cos \alpha}{V_s I_s} = \frac{I_o}{I_s} \cos \alpha = 0.9 \cos \alpha = \underline{\underline{0.225 \text{ lag}}}$$


5.9

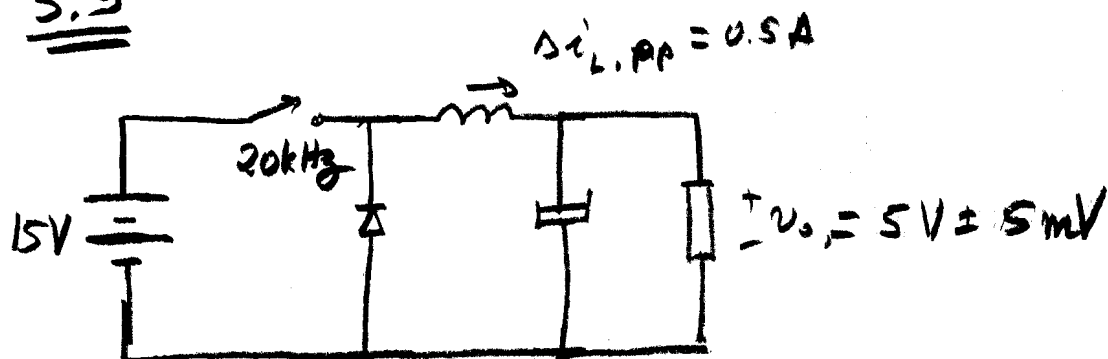

Assume $V_{sat} = V_F = 0$ (since not given)

(a) $k = \frac{V_{o,av}}{V_s} = \frac{5}{15} = \underline{\underline{0.33}}$

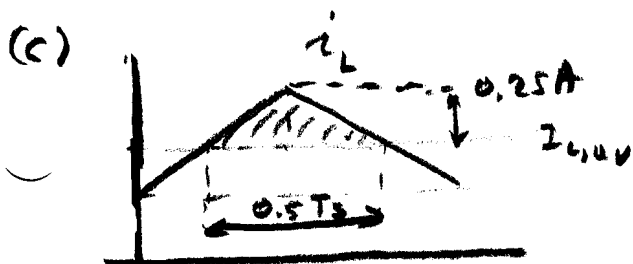(b) $\Delta I_L = \frac{V_s - V_{o,av}}{L} k T_s \Rightarrow L = \frac{V_s - V_{o,av}}{\Delta I_L f_s} k = \frac{10 \cdot k}{0.5 \cdot 20k} = \underline{\underline{333 \mu H}}$




Capacitor charge variation

$\Delta Q = \frac{1}{2} \left(\frac{\Delta I_L}{2} \right) 0.5 T_s = 3.125 \mu C$

Therefore $C = \Delta Q / \Delta V_o = 3.125 \mu C / 20mV = \underline{\underline{312.5 \mu F}}$

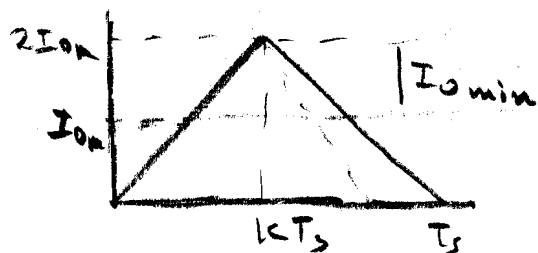(d) The critical value of ΔI_L for cont. cond. is

$\Delta I_L = 2 I_{o,min}$, $I_{o,min}$ is the minimum expected load current




Thus $L_{cr} = \frac{V_s - V_{o,av}}{2 I_{o,min} f_s} k$

Also $\Delta Q_{cr} = \frac{1}{2} I_{o,min} \frac{k T_s}{2} = \frac{1}{4} \frac{k I_{o,min}}{f_s}$ and

$C_{cr} = \frac{\Delta Q_{cr}}{\Delta V_o} = \frac{1}{4} \frac{k I_{o,min}}{f_s \Delta V_o}$

5.10

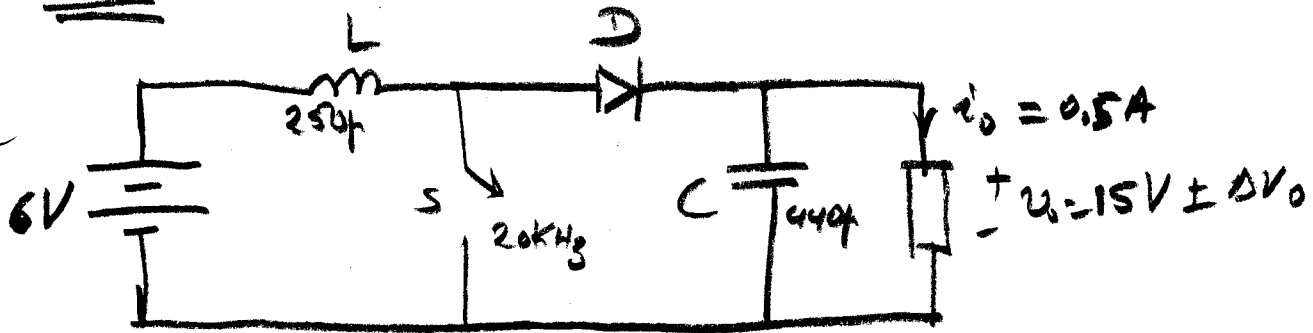


Assume $V_{sat} = V_F = 0$

(a) For cont. cond. $V_o = \frac{V_s}{1-k} \Rightarrow 1-k = \frac{V_s}{V_o} = 0.4$ and $k = 0.6$

(b) $\Delta I_L = \frac{V_s k T_s}{L} = \frac{V_s k}{L f_s} = \underline{\underline{0.72 A}}$

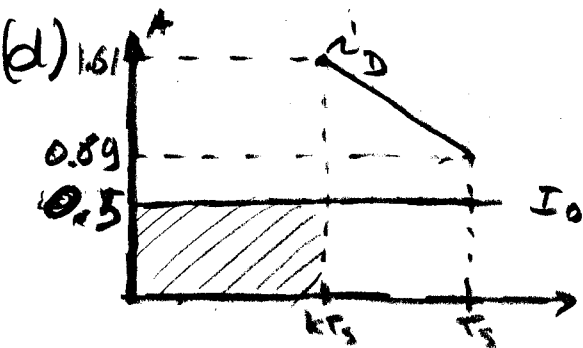(c) $I_{Lpk} = I_{Lav} + \frac{\Delta I_L}{2}$, but in cont. cond $I_{Lav} = \frac{I_o}{1-k} = \frac{0.5A}{0.4} = 1.25A$

Thus, $I_{Lpk} = 1.25 + \frac{0.72}{2} = \underline{\underline{1.61 A}}$ (Also, $I_{Lmin} = 0.89 A$)



Capacitor charge


$\Delta Q = I_o \cdot k T_s = 15 \mu C$

Therefore, $\Delta V_o = \frac{\Delta Q}{C} = \underline{\underline{34.1 mV}}$

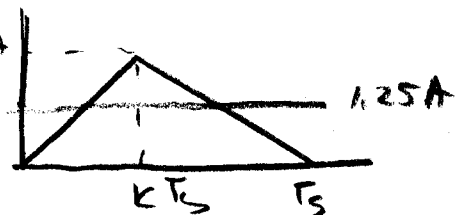
(e) The critical L is found by letting $I_{Lmin} = 0$ or

$\Delta I_{Lcr} = 2 I_{L,av} = 2 \times 1.25 A = 2.5 A$

and $L_{cr} = \frac{V_s k T_s}{\Delta I_{Lcr}} = 72 \mu H$




ΔQ_{cr}

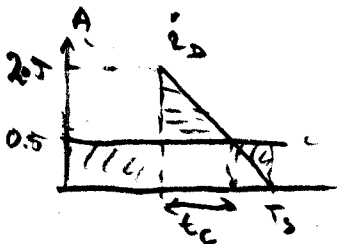

$\frac{t_c}{2.5-0.5} = \frac{(1-k)T_s}{2.5} \Rightarrow t_c = 16 \mu s$ and $\Delta Q_{cr} = 16 \mu C$

$C_{cr} = \Delta Q_{cr} / \Delta V_o = 469 \mu F$ ($\Delta V_o = 34.1 mV$)


5.11

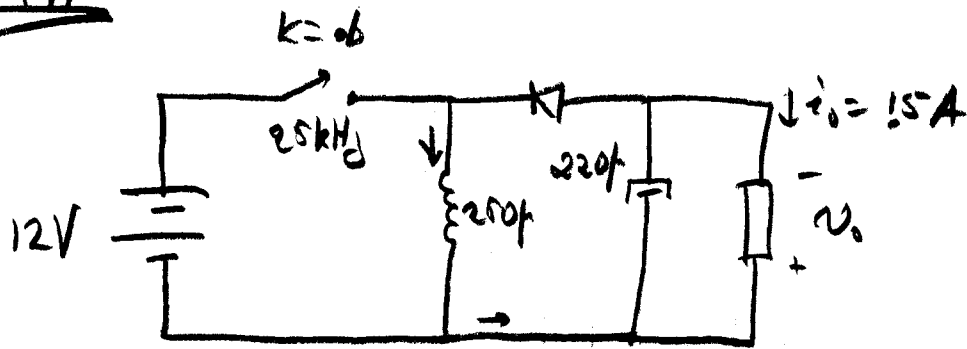

$$V_{out} = V_c = 0$$

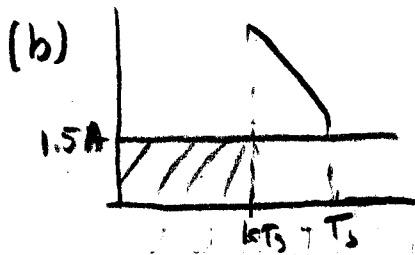(a) Assume const. cond.

$$V_{o,av} = \frac{k}{1-k} V_s = \underline{\underline{18V}}$$



$$\Delta Q = I_o k T_s = \frac{I_o k}{f_s} = \frac{0.6 \times 1.5}{25k} = 36 \mu C$$

$$\Delta V_o = \frac{\Delta Q}{C} = \underline{\underline{163 mV}}$$


(c)
$$\Delta I_L = \frac{V_s k T_s}{L_f} = \frac{V_s k}{L f_s} = \underline{\underline{1.152 A}}$$

(d)
$$I_{L,av} = \frac{I_o}{1-k} = 3.75 A, \quad I_{L,MIN} = 3.75 - \frac{1.152}{2} = 3.174 A$$

$$I_{L,MAX} = 3.75 + \frac{1.152}{2} = \underline{\underline{4.326 A}}$$

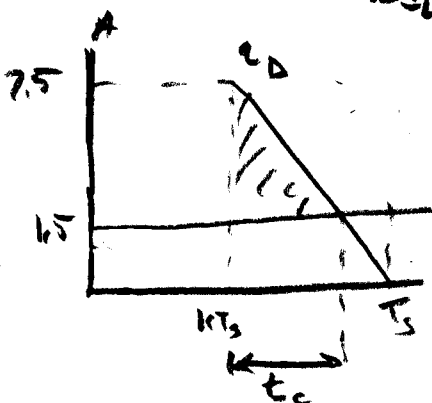(e)
$$\Delta I_{L,cr} = 2 I_{L,av} = 7.5 A$$

and
$$L_{cr} = \frac{V_s k T_s}{\Delta I_{L,cr}} = \underline{\underline{38.4 \mu H}}$$



$$\frac{t_c}{7.5 - 1.5} = \frac{(1-k)T_s}{2.5} \Rightarrow t_c = \frac{6(1-k)}{7.5 f_s} = 12.8 \mu s$$

$$\Delta Q_{cr} = \frac{1}{2} (7.5 - 1.5) t_c = 38.4 \mu C$$

assume $\Delta V_o = 163 mV \Rightarrow C_{cr} = \frac{\Delta Q_{cr}}{\Delta V_o} = \underline{\underline{236 \mu F}}$