

Lesson 16: Computing Resistive Starter Values

ET 332a

Dc Motors, Generators and Energy Conversion Devices

Lesson 16 332a.pptx

1

Learning Objectives

After this presentation you will be able to:


- Identify and utilize formulas for computing the values of resistance in a step resistive dc motor starter
- Work an example using the formulas
- Find individual resistor values based on the computations

Lesson 16 332a.pptx

2

Sizing Resistors in Step Resistor Starter

Three step resistive starter

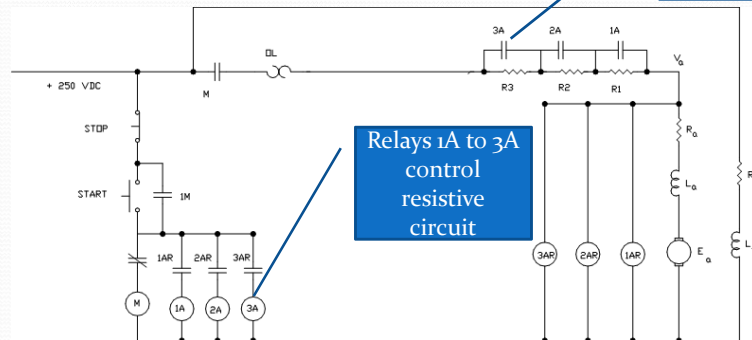

Relays 1AR to 3AR pickup based on motor terminal voltage, V_a

Lesson 16 332a.pptx

3

Sizing Resistors in Step Resistor Starter

Resistive starter equations

Current level determines the size of resistors. Set based on percentage of rated current allowed into machine during startup.

Compute starter R at step n.

$$R_{Tn} = \left[\frac{V_T - E_a}{\left[\frac{\%I}{100} \right] \cdot I_{rated}} \right] - R_a$$

Where:

V_T = motor terminal voltage

R_a = total armature resistance

R_{Tn} = total starter R at step n

I_{rated} = rated motor current

$\%I$ = percentage of rated allowed

E_a = induced internal voltage

Compute induced internal voltage at step n.

$$E_a = V_T - I_a (R_a + R_{Tn})$$

Compute relay n pick-up voltage at step n.


$$V_a = V_T - I_a (R_{Tn})$$

Repeat for all n steps of starter

Lesson 16 332a.pptx


4

Example 16-1: Sizing Starter Resistors

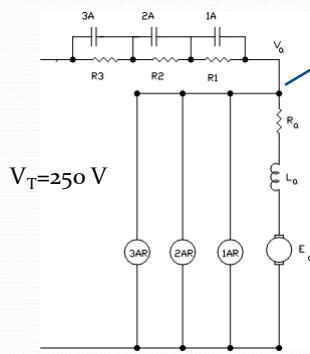

Example 16-1: Dc motor has terminal voltage of 250 Vdc and rated current of 125 A. The total armature resistance is 0.15 ohms Find values of R1-R3 and pick-up voltage \$V_a\$ for relays 1AR to 3AR to limit current to 200% of rated. Relays 1AR-3AR should activate when the armature current reaches rated motor current at each stage.

Example 16-1 Solution (1)

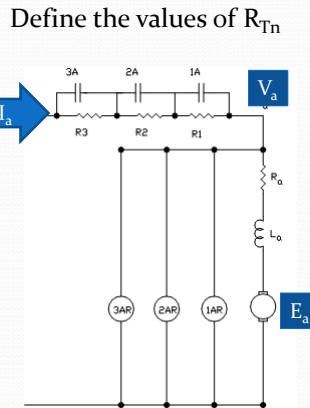

Define the values of \$R_{Tn}\$

$$R_{T1} = R_1 + R_2 + R_3$$

$$R_{T2} = R_2 + R_3$$

$$R_{T3} = R_3$$

Basic operational theory: \$I_a\$ produces torque that Accelerates armature causing \$E_a\$ to increase. Relays 1AR-3AR short out R's as \$V_a\$ increases

Stage 1 %I = 200% \$R_a = 0.15 \Omega\$
 $V_T = 250V$
 $I_{rated} = 125A$
 $n = 0 \quad E_a = 0$

$$R_{T1} = \left[\frac{V_T - E_a}{\left[\frac{200}{100} \right] I_{rated}} \right] - R_a \Omega$$

Example 16-1 Solution (2)

$$R_{T1} = \left[\frac{250 - 0}{\left[\frac{200\%}{100} \right] 125A} \right] - 0.15 \Omega$$

$$R_{T1} = \frac{250V}{250A} - 0.15 \Omega$$

$$R_{T1} = 1 \Omega - 0.15 \Omega = 0.85 \Omega$$

Find V_{a1} and E_a drop at 125 A due to the starting R's in the circuit

$$V_{a1} = V_T - R_{T1} I_{rated}$$

$$V_{a1} = 250V - 0.85 \Omega (125A) = 193.75V$$

$$E_{a1} = 250 - (125A)(0.85 \Omega + 0.15 \Omega) = 125V$$

$$E_{a1} = 125V$$

answer

Voltage setting
1AR

Lesson 16 332a.pptx

7

Example 16-1 Solution (3)

Stage 2

Compute stage 2 values with 1AR closed. Use $E_{a1} = 125V$

$$R_{T2} = \left[\frac{V_T - E_{a1}}{\left[\frac{200\%}{100} \right] I_{rated}} \right] - R_a$$

$$R_{T2} = \left[\frac{250V - 125V}{\left[\frac{200\%}{100} \right] (125)} \right] - 0.15 \Omega$$

$$R_{T2} = \left[\frac{125V}{250A} \right] - 0.15 \Omega$$

$$R_{T2} = 0.35 \Omega$$

$$V_{a2} = V_T - I_{rated} (R_{T2})$$

$$V_{a2} = 250V - 125A (0.35)$$

$$V_{a2} = 206.25V$$

2AR VOLTAGE SETTING

answer

$$E_{a2} = V_T - I_{rated} (R_{T2} + R_a)$$

$$E_{a2} = 250V - (125A)(0.35 + 0.15 \Omega)$$

$$E_{a2} = 187.5V$$

Lesson 16 332a.pptx

8

Example 16-1 Solution (4)

Stage 3

1AR and 2AR are closed. Use $E_{a2} = 187.5 \text{ V}$

$$R_{T3} = \left[\frac{V_T - E_{a2}}{\left[\frac{\%I}{100} \right] I_{\text{rated}}} \right] - R_a$$

$$R_{T3} = \left[\frac{250 - 187.5 \text{ V}}{\left(\frac{200\%}{100} \right) (25 \text{ A})} \right] - 0.15 \Omega$$

$$R_{T3} = \frac{62.5 \text{ V}}{250 \text{ A}} = 0.15 \Omega$$

$$R_{T2} = 0.25 - 0.15 \Omega$$

$$R_{T2} = 0.1 \Omega$$

Compute the last relay pick up voltages

$$V_{a3} = V_T - I_{\text{rated}} R_{T3}$$

$$V_{a3} = 250 \text{ V} - (25 \text{ A})(0.15 \Omega)$$

$$V_{a3} = 237.5 \text{ V}$$


← answer

Lesson 16 332a.pptx

9

Example 16-1 Solution (5)

Compute the individual resistor values

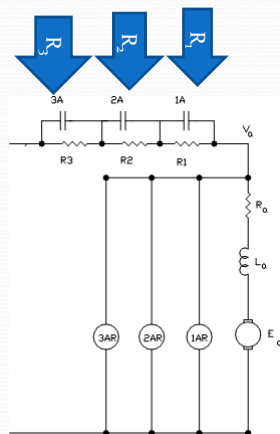

$$R_1 = R_{T1} - R_{T2}$$

$$R_1 = 0.85 \Omega - 0.35 \Omega$$

$$R_1 = 0.5 \Omega$$

$$R_2 = R_{T2} - R_{T3}$$

$$R_2 = 0.35 \Omega - 0.15 \Omega$$

$$R_2 = 0.25 \Omega$$

$$R_3 = R_{T3}$$

$$R_3 = 0.1 \Omega$$

Lesson 16 332a.pptx

10

End Lesson 16

ET 332a

Dc Motors, Generators and Energy Conversion Devices