

Lesson 18: Series Motor Torque–Speed Characteristics

ET 332a
Dc Motors, Generators and Energy Conversion
Devices

Lesson 18 332a.pptx

1

Learning Objectives

- Use series dc motor model and equations to determine motor speed at different load levels
- Identify the torque–speed characteristic of a series dc motor
- Explain how a series dc motor can develop large starting torques

Lesson 18 332a.pptx

2

Series Dc Motor Example: Torque-Speed Characteristic

Example 18-1


A 550 V, 25 HP series connected 800 rpm dc motor draws 38 A at rated output. The total armature circuit resistance excluding the series field coil is 0.117 ohms. The series field resistance is 0.125 ohms.

- determine the developed torque supplied by the motor when it operates at rated output.
- determine the motor speed when the developed torque is reduced by 50% from rated
- repeat (b) with 75% reduction from rated
- plot the torque-speed curve for the motor. Can it be considered a constant speed machine?

Lesson 18 332a.pptx

3

Example 18-1 Solution (1)

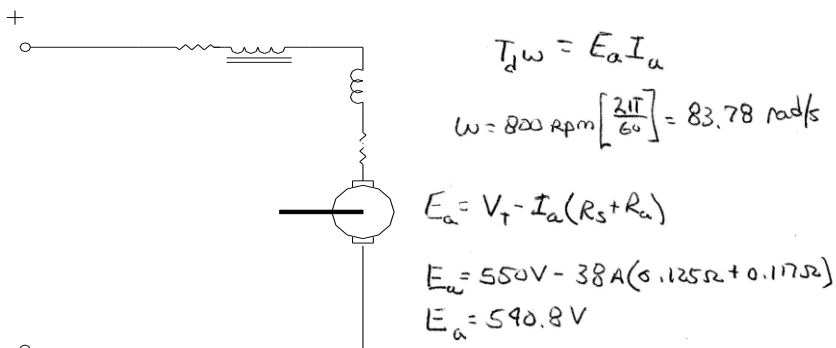

$E_a I_a = P_e = P_{em}$ electromechanical power developed in armature

Lesson 17 332a.pptx

4

Example 18-1 Solution (2)

$$E_a I_a = (540.8 \text{ V})(38 \text{ A}) = 20,550 \text{ W}$$

$$T_D = \frac{E_a I_a}{\omega} = \frac{(540.8 \text{ V})(38 \text{ A})}{83.78 \text{ rad/s}} = \boxed{245.3 \text{ N-m}} \text{ Ans}$$

Part b.) 50% developed torque. Compute 50% torque speed value

$$T_{D50} = T_D \left(\frac{50\%}{100\%} \right) \quad T_D = 245.3 \text{ N-m from above}$$

$$T_{D50} = 245.3 - 0.5(245.3)$$

$$T_{D50} = 122.65 \text{ N-m}$$

Lesson 17 332a.pptx

5

Example 18-1 Solution (3)

$$\text{Torque} \propto I_a^2$$

$$\frac{T_D}{T_{D50}} = \frac{k_T I_a^2}{k_T I_{a1}^2} \Rightarrow \frac{T_D}{T_{D50}} = \frac{I_a^2}{I_{a1}^2} \Rightarrow \sqrt{\frac{T_D}{T_{D50}}} = \frac{I_a}{I_{a1}}$$

I_{a50} = Armature current at 50% rated torque

To find speed

$$\frac{n_1}{n_2} = \frac{\frac{E_{a1}}{\Phi_{p1} k_G}}{\frac{E_{a2}}{\Phi_{p2} k_G}} \quad \frac{n_1}{n_2} = \left[\frac{E_{a1}}{E_{a2}} \right] \left[\frac{\Phi_{p2}}{\Phi_{p1}} \right] \quad \Phi_{p2} \text{ reduced by reduction in } I_a$$

$n_1 = 800 \text{ RPM}$ from problem statement

Lesson 17 332a.pptx

6

Example 18-1 Solution (4)

Find I_{a50}

$$I_{a50} = \sqrt{\frac{T_D}{T_{D50}}}$$

$$(38A) \sqrt{\frac{1}{\frac{295.3 \text{ N}\cdot\text{m}}{122.65 \text{ N}\cdot\text{m}}}} = I_{a50}$$

$$I_{a50} = 26.87A$$

In linear region of magnetization curve
 Φ_p is proportional to I_a
 $I_f = I_a$ in series connection so...

$$\frac{\Phi_{p1}}{\Phi_{p2}} = \frac{I_{a1}}{I_{a2}}$$

Lesson 17 332a.pptx

7

Example 18-1 Solution (5)

$$E_{a2} = V_T - I_{a50} (R_{a12} + R_s)$$

$$E_{a2} = 550V - 26.87A(0.117 + 0.125\Omega)$$

$$E_{a2} = 543.5V$$

$$E_{a1} = 540.8 \text{ from Part a}$$

$$n_2 = \left[\frac{\Phi_{p1}}{\Phi_{p2}} \right] \left[\frac{E_{a2}}{E_{a1}} \right] n_1 \quad \frac{\Phi_{p1}}{\Phi_{p2}} = \frac{38A}{26.87A} = 1.414$$

$$n_2 = 1.414 \left[\frac{543.5V}{540.8V} \right] (800 \text{ Rpm})$$

$$n_2 = 1137 \text{ Rpm}$$

Answer

Lesson 17 332a.pptx

8

Example 18-1 Solution (6)

Part c.) 75% developed torque. Compute 75% torque speed value

From previous equations

$$\sqrt{\frac{T_D}{T_{D75}}} = \frac{I_a}{I_{a75}} \Rightarrow I_{a75} = I_a \left[\sqrt{\frac{T_D}{T_{D75}}} \right]$$

$$T_{D75} = 0.75 [T_D]$$

$$I_{a75} = (38A) \left[\sqrt{\frac{245.3 \text{ N}\cdot\text{m}}{61.325 \text{ N}\cdot\text{m}}} \right] \quad I_{a75} = 19A$$

$$T_{D75} = 0.75(245.3 \text{ N}\cdot\text{m})$$

$$T_{D75} = 61.325 \text{ N}\cdot\text{m}$$

Lesson 17 332a.pptx

9

Example 18-1 Solution (7)

Determine new value of E_a and flux ratio

$$\frac{\Phi_{p1}}{\Phi_{p2}} = \frac{I_{a1}}{I_{a2}} = \frac{38A}{19A} = 2.0$$

$$E_{a2} = V_T - I_{a2}(R_s + R_{a2})$$

$$E_{a2} = 550V - 19A(0.117 + 0.125\Omega)$$

$$E_{a2} = 545.4V$$

$$E_{a1} = 540.8V \text{ part a)}$$

Speed at 75% load

$$n_2 = \left[\frac{\Phi_{p1}}{\Phi_{p2}} \right] \left[\frac{E_{a2}}{E_{a1}} \right] n_1 \quad n_2 = 2.0 \left[\frac{545.4V}{540.8V} \right] (800 \text{ rpm})$$


$$n_2 = 1614 \text{ rpm}$$

Answer

Lesson 17 332a.pptx

10

Series Motor Torque-Speed Characteristic

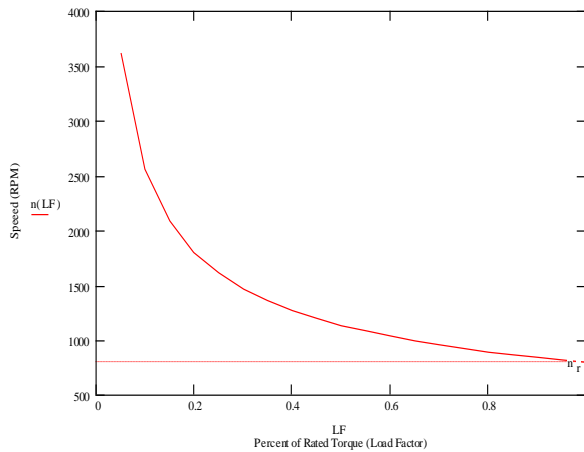

Rated speed is 800 rpm.
At no load, the speed will increase exponentially and destroy the machine. (Last point plotted was at 5% rated load)

MathCAD equations

$$I_L(LF) := I_a \cdot \frac{1}{\sqrt{\frac{1}{LF}}}$$

$$n(LF) := \frac{I_a}{I_L(LF)} \cdot \frac{V_T - I_L(LF) \cdot (R_s + R_a)}{V_T - I_a \cdot (R_s + R_a)} \cdot n_r$$

Vary value of LF to generate curve

Lesson 18 332a.pptx

11

Starting Series Connected Dc Motors

Series motors develop extremely high starting torques

Under locked rotor conditions $E_a = 0$ so...

$$I_{as} = \frac{V_T}{R_{acir} + R_s}$$

$$T_D = k_T \cdot I_a^2$$

Where I_{as} = starting armature current
 R_s = series field resistance
 R_{acir} = total armature resistance
 T_D = developed torque
 k_T = motor torque constant
 V_T = terminal voltage

Since $R_{acir} + R_s \ll 1$ then $I_{as} \gg I_a$ when operating at rated speed

Lesson 18 332a.pptx

12

Series Motor Starting Example

Example 18-2: Using the values from the previous example, find the series motor starting currents and starting torque of the machine from that example. Assume linear magnetization curves

$$V_T = 550\text{V} \quad R_{acir} + R_s = 0.117\Omega + 0.125\Omega \\ R_{acir} + R_s = 0.242\Omega$$

$$I_{as} = \frac{550\text{V}}{0.242\Omega} = 2273\text{A} \quad \text{Wow!}$$

Find the developed starting torque. Find k_T from rated conditions.

In previous example
 $T_D = 245.3\text{ N}\cdot\text{m}$
 $I_a = 38\text{ A}$

$$T_D = k_T I_a^2 \\ \frac{T_D}{I_a^2} = k_T$$

$$\frac{245.3\text{ N}\cdot\text{m}}{(38\text{ A})^2} = k_T \\ 0.1698\text{ N}\cdot\text{m}/\text{A}^2$$

Example 18-2 Solution (2)

T_{Ds} = starting developed torque

$$T_{Ds} = k_T I_{as}^2$$

$$T_{Ds} = (0.1698\text{ N}\cdot\text{m}/\text{A}^2) (2273\text{ A})^2$$

$$T_{Ds} = 877,066\text{ N}\cdot\text{m} \quad \text{Wow!}$$

Saturation limits torque to lower value since flux is not proportional to armature current for large values of current.

End Lesson 18

» ET 332a
Dc Motors, Generators and
Energy Conversion Devices