

ET 332a
Dc Motors, Generators and Energy Conversion Devices

Lesson 9: Power Balance and Efficiency in Dc Generators

1


Learning Objectives

After this presentation you will be able to:

- Identify the sources of power loss in separately excited dc generators and compute their values
- Balance the input and output power of a separately excited dc generator.
- Compute generator efficiency
- Explain how changing generator load affects efficiency
- Explain how the generator/motor and motor generator transition takes place in dc machines

2

Power Balance for Dc Generators

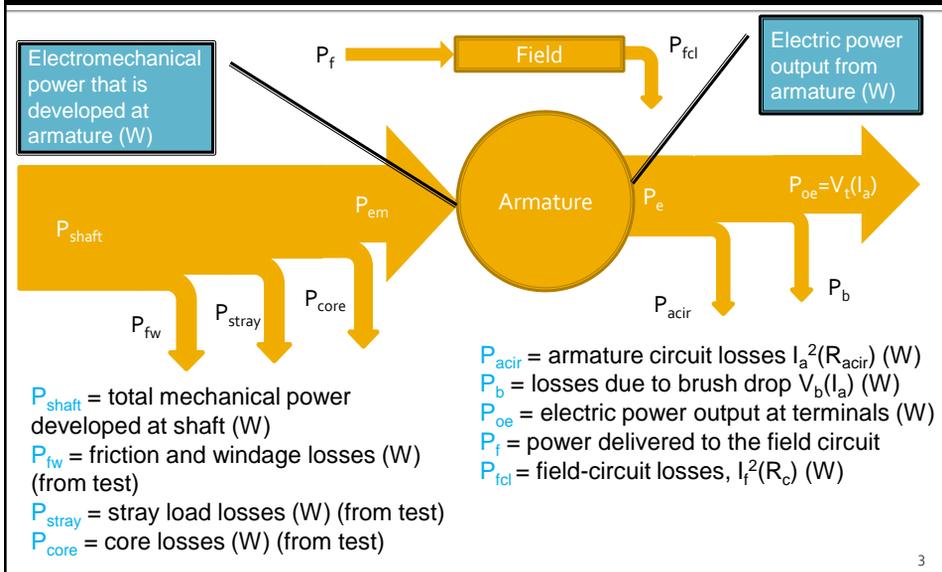

Power Balance in Armature

Electric power developed at the armature is equal to the electromechanical power delivered from the shaft.

$$P_{em} = P_e$$

$$T \cdot \omega = E_a \cdot I_a$$

To find P_e , add electrical losses to output electric power, P_{oe}

$$P_e = P_{oe} + P_{acir} + P_b$$


In terms of armature circuit variables the above is:

$$P_e = V_t \cdot I_a + I_a^2 \cdot R_{acir} + V_b \cdot I_a$$

Where $V_b = 0.5$ for metal-graphite brushes
 $= 2.0$ for electrographitic and graphite brushes

Power Balance in Armature

On mechanical side of generator:

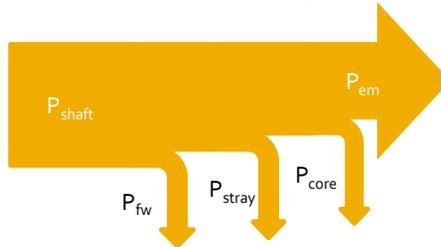

Find shaft power input by equating P_e and P_{em} and then adding mechanical losses

$$P_{\text{shaft}} = P_{\text{em}} + P_{\text{fw}} + P_{\text{stray}} + P_{\text{core}}$$

Find electromechanical power in armature by subtracting mechanical losses from shaft power

$$P_{\text{em}} = P_{\text{shaft}} - P_{\text{fw}} - P_{\text{stray}} - P_{\text{core}}$$

5

Machine Efficiency

Ratio of output power to input power determines efficiency of dc generator

Mathematically $\eta = \frac{P_{\text{out}}}{P_{\text{in}}} \cdot 100\%$ or $\eta = \frac{P_{\text{out}}}{P_{\text{out}} + P_{\text{losses}}} \cdot 100\%$

Where: η = machine efficiency
 P_{out} = machine output power
 P_{in} = machine input power
 P_{losses} = total mechanical and electrical losses

For generator operation :

$$P_{\text{out}} = P_{\text{oe}} = V_t \cdot I_a$$

$$P_{\text{in}} = P_{\text{shaft}}$$

Units must be the same
(Watts or HP)

6


Efficiency Example

Example: A 25 kW, 120 V, 1800 rpm separately excited generator is delivering rated current. The stray losses of the generator are found from test to be 1.5% of the rated output. The total core, friction, and windage losses are 2.0% of rated output. $R_{acir} = 0.0280 \Omega$ Neglect the losses of the field circuit. Assume graphite brushes.

- Find the power in HP that the prime mover must develop at rated speed to drive the generator
- Find the efficiency of the machine operating at rated load.
- Find the efficiency of the machine when operating at 0% 25%, 50% and 75% of rated output. Assume that rated terminal voltage is maintained at the generator output as the load varies.
- Plot the % efficiency vs the % load and comment on the result

7

Efficiency Example Solution

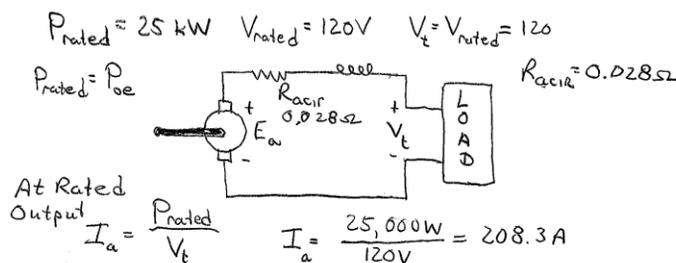

Find losses due to Brushes and armature R

$$P_{acir} = I_a^2 R_{acir} = (208.3)^2 (0.028 \Omega) = 1214.9 \text{ W}$$

$$P_b = V_b I_a = 2 (208.3) = 416.6 \text{ W}$$

$$P_e = P_{oe} + P_{acir} + P_b = 25,000 \text{ W} + 1214.9 \text{ W} + 416.6 \text{ W} = 26,631.5 \text{ W}$$

8

Example Solution Continued

Remember $P_e = P_{em}$ in armature

Add mechanical losses $P_{em} = P_e$

$$P_{mech} = P_{em} + P_{fw} + P_{stray} + P_{core}$$

$$P_{stray} = \frac{1.5\%}{100\%}(25,000) = 375 \text{ W} \quad P_{core} + P_{fw} = \frac{2.0\%}{100\%}(25,000) = 500 \text{ W}$$

$$P_{mech} = 26,631.5 + 375 + 500 \text{ W} = 27,506.3 \text{ Watt}$$

$$a) P_{HP} = \frac{27,506.3 \text{ W}}{746 \text{ W/HP}} = \underline{\underline{36.87 \text{ HP ANS}}}$$

Now compute the efficiency at full load

$$b.) \eta = \frac{P_{out}}{P_{in}} \times 100\% = \frac{P_{oe}}{P_{mech}} \times 100\% = \frac{25,000 \text{ W}}{27,506.3 \text{ W}} \times 100\% = \underline{\underline{90.89\%}}$$

9

Efficiency Example: 0% Output

Compute the efficiency at 0% output power

at 0% Load $I_a = 0$ So $P_{acir} = 0$ $R_{acir} = 0$ ARMATURE LOSSES

$$P_b = 2I_a = 2(0) = 0 \text{ brush losses}$$

$$P_{oe} = 0 \quad V_t I_a = 0$$

Mechanical losses Still Present $P_{rated} = 25,000 \text{ W}$

$$2.0\% \text{ Rated } P_{fw} + P_{core} = 25,000(0.02) = 500 \text{ W}$$

$$1.5\% \text{ Rated } P_{stray} = 25,000(0.015) = 375 \text{ W}$$

Electrical Output of Armature

$$P_e = P_{oe} + P_b + P_{acir} = \underline{\underline{0 \text{ watts}}}$$

$$P_{em} = P_e = 0$$

10

Efficiency Example: 0% Output

Total Mechanical Power Developed is power necessary to overcome mechanical losses.

$$P_{\text{Mechloss}} = P_{fw} + P_{\text{stray}} + P_{\text{core}}$$

$$P_{\text{Mechloss}} = 500 + 375 \text{ W} = \underline{\underline{875 \text{ W}}}$$

Shaft power required of prime mover to overcome mechanical losses

$$P_{\text{HP}} = \frac{875 \text{ W}}{746 \text{ W/HP}} = \underline{\underline{1.173 \text{ HP}}}$$

Now compute the efficiency with 0% output

$$\% \eta = \frac{P_{\text{oe}}}{P_{\text{mech}}} \times 100\% = \frac{0}{875 \text{ W}} \times 100\% = \underline{\underline{0\%}}$$

11

Efficiency Example 25, 50, 75%

Now compute the efficiencies for the other load levels

$$\text{At 25\% Rated Load } P_{\text{oe}} = \frac{25\%}{100\%} (25,000) = 6250 \text{ W}$$

$$I_a = \frac{P_{\text{oe}}}{V_t} \quad V_t = 120 \text{ V} \quad I_a = \frac{6250 \text{ W}}{120 \text{ V}} = 52.08 \text{ A}$$

$$P_{\text{acir}} = I_a^2 R_{\text{acir}} = (52.08 \text{ A})^2 (0.028 \Omega) = 75.95 \text{ W}$$

$$P_b = 2(I_a) = 2(52.08 \text{ A}) = 104.16 \text{ W}$$

$$\text{From previous calculations } P_{fw} + P_{\text{core}} = \underline{500 \text{ W}} \quad P_{\text{stray}} = \underline{375 \text{ W}}$$

12

Efficiency Example 25, 50, 75%

Electric power developed

$$P_e = P_{oe} + P_{acir} + P_b$$

$$P_e = 6250 + 75.95 + 104.16 \text{ W}$$

$$P_e = \underline{\underline{6430.11 \text{ watts}}}$$

$P_{em} = P_e$
Armature mechanical
power = armature
electric power.

$$P_{mech} = P_{em} + P_{stray} + P_{fw} + P_{core}$$

$$P_{mech} = 6430.11 + 375 + 500 \text{ W} = \underline{\underline{7305.11 \text{ W}}}$$

Prime mover required horsepower

$$P_{HP} = \frac{P_{mech}}{746 \text{ W/HP}} = \frac{7305.11 \text{ W}}{746 \text{ W/HP}} = \underline{\underline{9.79 \text{ HP}}}$$

$$\eta = \frac{P_{oe}}{P_{mech}} \times 100\% = \frac{6250 \text{ W}}{7305.11} \times 100\%$$

$$\eta = \underline{\underline{85.56\%}}$$

13

Efficiency Example 50, 75%

Now compute efficiencies for 50 and 75% loading

At 50% And 75% Rated load

$$P_{oe50} = \frac{50\%}{100\%} 25,000 = \underline{\underline{12,500 \text{ W}}} \quad I_{a50} = \frac{P_{oe50}}{V_t} = \frac{12,500}{120} = \underline{\underline{104.2 \text{ A}}}$$

$$P_{oe75} = \frac{75\%}{100\%} 25,000 = \underline{\underline{18,750 \text{ W}}} \quad I_{a75} = \frac{P_{oe75}}{V_t} = \frac{18,750}{120} = \underline{\underline{156.25 \text{ A}}}$$

Power Loss at 50 and 75% Rated

$$P_{b50} = 2(104.2 \text{ A}) = \underline{\underline{208.3 \text{ W}}} \quad P_{acir50} = (104.2)^2 (0.028) = \underline{\underline{304.01 \text{ W}}}$$

$$P_{b75} = 2(156.25 \text{ A}) = \underline{\underline{312.5 \text{ W}}} \quad P_{acir75} = (156.25)^2 (0.028) = \underline{\underline{683.6 \text{ W}}}$$

Finally compute the total power losses for 50 and 75% load

14

Efficiency Example 50, 75%

Electric power values in armature

$$P_{e_{50}} = 12,500 + 208.3 + 304.1 \text{ W} \quad P_{e_{75}} = 18,750 + 312.5 + 683.6 \text{ W}$$

$$P_{e_{50}} = \underline{13012.4 \text{ W}} \quad P_{e_{75}} = \underline{19,746.1 \text{ W}}$$

Add fixed losses between armature and shaft to get the required shaft power

$$P_{\text{shaft}50} = 13012.4 + 875 \text{ W} \quad P_{\text{shaft}75} = 19746.1 + 875 \text{ W}$$

$$P_{\text{shaft}50} = 13887.4 \text{ W} \quad P_{\text{shaft}75} = 20,621.1 \text{ W}$$

Prime mover Hp 50% Prime mover Hp 75%

$$P_{\text{HP}} = \frac{13887.4 \text{ W}}{746 \text{ W/HP}} = \underline{\underline{18.62 \text{ HP}}} \quad P_{\text{HP}} = \frac{20,621.1 \text{ W}}{746 \text{ W/HP}} = \underline{\underline{27.64 \text{ HP}}}$$

15

Compute Efficiencies at 50 and 75%

$$\eta_{50} = \frac{12500 \text{ W}}{13887.4 \text{ W}} \times 100\% \quad \eta_{75} = \frac{18750 \text{ W}}{20621.1 \text{ W}} \times 100\%$$

$$\eta_{50} = 90.00\% \quad \eta_{75} = 90.93\%$$


Power losses related to I_a are called **load losses** since they relate to the generator loading

Maximum efficiency occurs when the **fixed losses equal the load losses**.

16


Plot of Efficiency vs Percent Rated Load

Typical Efficiency curve

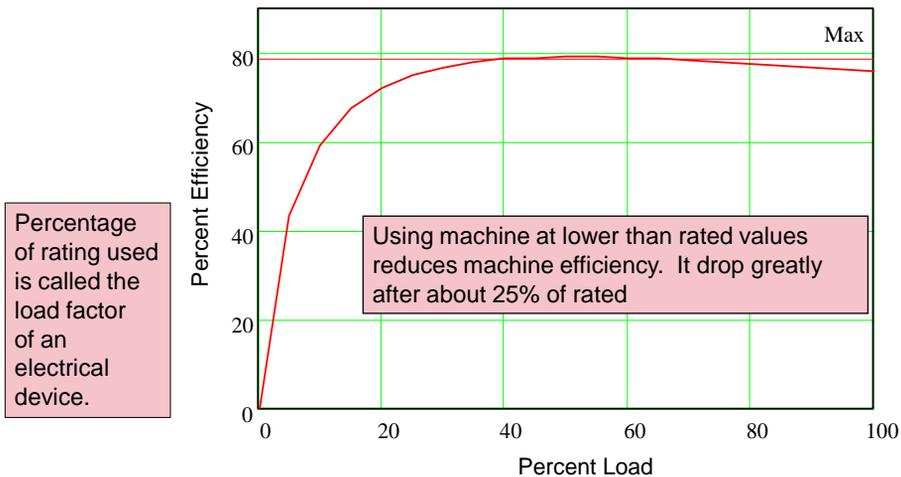

17

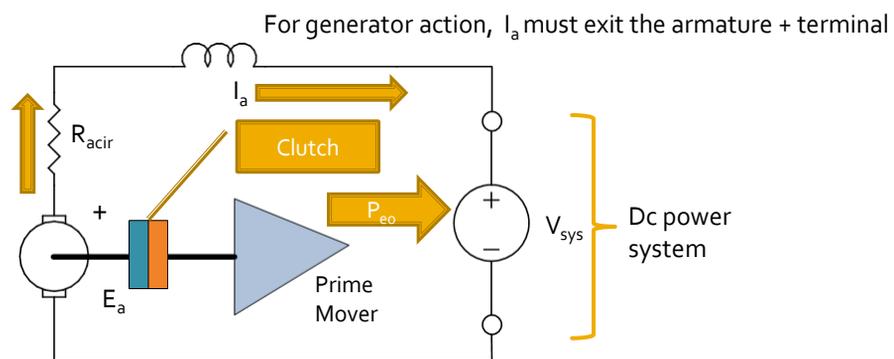Generator-to-Motor and Motor-to-Generator Transitions




If $E_a > V_{sys}$, then I_a leaves the machine for generator action and power is delivered to system

If $E_a = V_{sys}$, then $I_a = 0$ a power is delivered to system but generator action

18

Generator-to-Motor and Motor-to-Generator Transitions

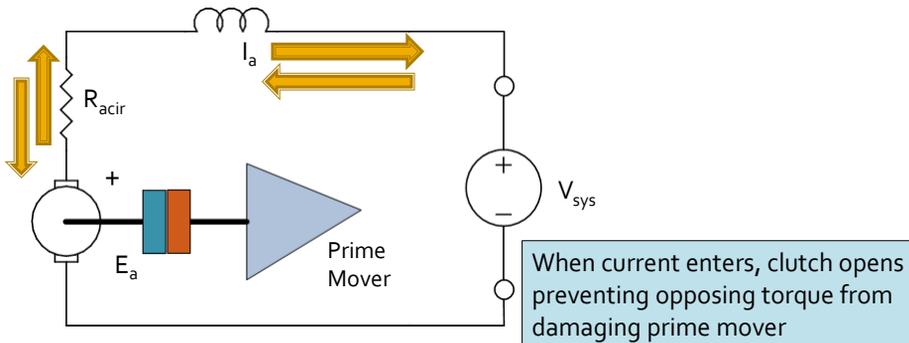For motor action, current must enter the positive terminal of the machine: $V_{sys} > E_a$



Mechanical power delivered to load depends on the needs of the load. With no mechanical power load, the electric power drawn is only that necessary to overcome electrical and mechanical losses

19

End Lesson 9: Power Balance and Efficiency in Dc Generators

ET 332a

Dc Motors, Generators and Energy Conversion Devices

20