

ET 332b  
3 Phase System Homework

For the circuit given below, compute:

- a.) the magnitude of line-to-neutral voltage
- b.) the magnitude of the line current and the phase current
- c.) the total apparent power absorbed in the circuit
- d.) the power factor for the circuit

