## ET 332b

## Three-Phase Power Calculations

A 480 V line-to-line 60 Hz 3-phase power system supplies three loads:

- 1.) A 3-phase delta connected induction motor that has a line current of 200 A at a power factor of 70% lagging.
- 2.) A 3-phase delta connected 100 hp induction motor. This motor is operating at 80% of its rated power output and has an efficiency of 92% and a power factor of 0.80 lagging.
- 3.) A delta connected resistive heater that draws 50 kW from the 3-phase supply.

For this system:

- a.) Find the total P Q, S and power factor for the combined loads
- b.) Find the per phase voltage rating and value of capacitance for a delta connected capacitor bank that is used to correct the power factor of the combined loads to 0.95 lagging.
- c.) Find the magnitude of line current for the total connected load when:
  - 1.) power factor is that computed in part a
  - 2.) power factor is corrected to 0.95