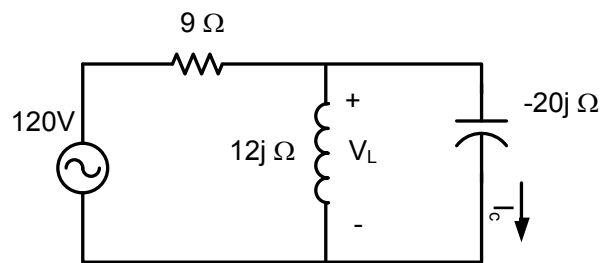


ET 332B
Per Unit Homework Problems

- 1.) A single phase 60 Hz control voltage transformer is rated at 500 VA, 480-120 volts. It has a total winding impedance in terms of the secondary side of $0.125 + 0.355j$ ohms. Compute the per unit winding impedance of the transformer based on the transformer power rating and the rated secondary voltage.
- 2.) Refer the impedance give in problem 1 to the primary side. Repeat problem 1 using the rated primary voltage as the voltage base. Compare and comment on the results of the two calculations.
- 3.) A 10 kVA, 2400-120 volt transformer has a percent winding impedance of $1.25 + 2.5j\%$ based on transformer power and voltage ratings.
 - a.) Find the winding impedance in ohms based on the rated transformer primary voltage.
 - b.) Find the winding impedance in ohms based on the rated transformer secondary voltage.
- 4.) The circuit shown below has a base voltage of 120 Vac and a base power of 1000 VA.
 - a.) Find the per unit current phasor, I_C , flowing through the capacitor.
 - b.) Find the per unit voltage drop phasor, V_L , across the inductor.
 - c.) Convert the per unit values from parts a and b into capacitor current in amps and the inductor voltage in volts.



- 5.) The system below has a base voltage of 240V and a base power of 25 kVA find the source voltage (in actual volts) required to maintain 1 p.u. voltage on the load with the indicated current flowing.

