

Lesson 12: Parallel Transformers and Autotransformers

ET 332b Ac Motors, Generators and Power Systems

Lesson 12_et332b.pptx


Lesson 12_et332b.pptx

Learning Objectives

After this presentation you will be able to:

- Explain what causes circulating currents in parallel and compute its value.
- Compute the load division between parallel transformers.
- Explain how autotransformers operate
- Make calculation using ideal autotransformer model

Parallel Operation of Transformers

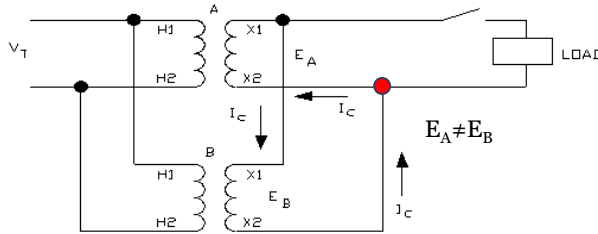

Currents circulate between A and B based on the voltage difference and transformer impedance even with no load


$$I_c = \frac{E_A - E_B}{Z_A + Z_B}$$

When voltage ratios are not equal, currents circulate between the windings of each transformer without a load connected. Circulating currents reduce the load capacity of transformer

Where: E_A = operating voltage of transformer A
 E_B = operating voltage of transformer B
 Z_A = series impedance of A
 Z_B = series impedance of B

Capacity Loss Due to Circulating Currents

Find effects using superposition

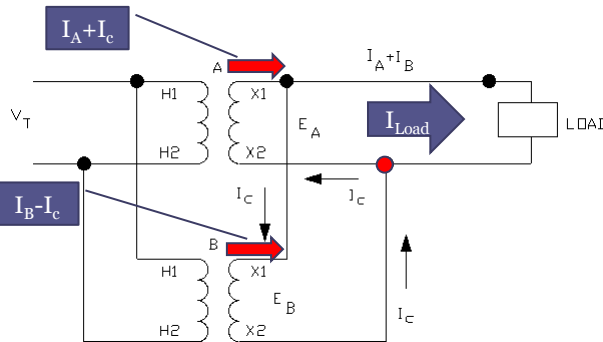

Transformer A current

$$I_{TA} = I_A + I_c$$

Transformer B current

$$I_{TB} = I_B - I_c$$

I_c driven by $E_A - E_B$

Adding circulating current to transformer A increases total current in winding. Not seen in load current. Can cause overload

Circulating Current Example

Example 12-1: Two 100 kVA single phase transformer operated in parallel.

Nameplate data:

Transformer	V-ratio	%R	%X
A	2300-460	1.36	3.50
B	2300-450	1.40	3.32

Find I_c magnitude and I_c as percent of transformer secondary ratings

Example 12-1 Solution (1)

Use per unit method – $V_{base} =$ secondary voltage

$$V_b = 460 \text{ V}$$

$$V_{TxA} = \frac{V_R}{V_{bA}} = \frac{460 \text{ V}}{460 \text{ V}} = 1.0 \text{ p.u.}$$

$$V_{TxB} = \frac{V_R}{V_{bB}} = \frac{450 \text{ V}}{460 \text{ V}} = 0.9783 \text{ p.u.}$$

Find $Z_A + Z_B$ in p.u.

$$\bar{Z}_A = 1.36 + 3.50j \text{ \%}/100\%$$

$$\bar{Z}_B = 1.40 + 3.32j \text{ \%}/100\%$$

$$\bar{Z}_A = 0.0136 + 0.035j \text{ p.u.}$$

$$\bar{Z}_B = 0.0140 + 0.0332j \text{ p.u.}$$

$$\bar{Z}_A + \bar{Z}_B = (0.0136 + 0.035j) + (0.0140 + 0.0332j) \text{ p.u.}$$

$$\bar{Z}_A + \bar{Z}_B = 0.0276 + 0.0682j \text{ p.u.}$$

$$\bar{Z}_A + \bar{Z}_B = 0.07357 \angle 67.92^\circ \text{ p.u.}$$

Example 12-1 Solution (2)

Use formula

$$\bar{I}_c = \frac{\bar{V}_{TXA} - \bar{V}_{TXB}}{\bar{Z}_A + \bar{Z}_B}$$

$$\bar{I}_c = \frac{(1.0 - 0.9783) / \angle 0^\circ \text{ p.u.}}{0.07357 / \angle 67.97^\circ \text{ p.u.}}$$

$$\bar{I}_c = 0.2955 / \angle -67.97^\circ \text{ p.u.}$$

Convert per unit to percent

$$\% \bar{I}_c = 0.2955 / \angle -67.97^\circ (100\%)$$

$$\% \bar{I}_c = 29.55 / \angle -67.97^\circ \%$$

Ans

29.55% of Transformer A's capacity is consumed by I_c .

Now convert this to amps using a base current


$$I_{base} = \frac{S_{base}}{V_{base}} = \frac{100,000 \text{ VA}}{460 \text{ V}}$$

$$I_{base} = 217.4 \text{ A}$$

$$\bar{I}_{cact} = \bar{I}_c I_{base} \quad \bar{I}_{cact} = 0.2955 / \angle -67.97^\circ (217.4 \text{ A}) = 64.35 / \angle -67.97^\circ$$

Load Division Between Parallel Transformers

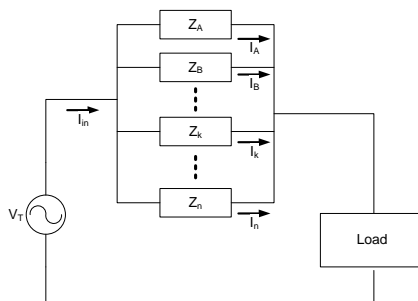When turns ratios are equal, the load current divides following the winding impedance of the transformers. More current flows through the lowest impedance.



Circuit model

All Transformer Z's and Load Z referred to the same side of transformer or all per unit (%) quantities

$$Y_A = \frac{1}{Z_A}, \quad Y_B = \frac{1}{Z_B} \dots Y_k = \frac{1}{Z_k} \dots Y_n = \frac{1}{Z_n}$$

Use current divider rule

$$Y_p = Y_A + Y_B + \dots Y_k + \dots Y_n$$

$$I_k = I_{in} \cdot \left(\frac{Y_k}{Y_p} \right) \quad \text{Finds the current in the } k^{\text{th}} \text{ transformer}$$

Parallel Transformer Example

Example 12-2: A 100 kVA transformer is to be paralleled with a 200 kVA transformer. Each transformer has rated voltages of 4160 - 240 V. Their percent impedances based on the ratings of each are:

$$Z\% = 1.64 + 3.16j \quad \% \quad 100 \text{ kVA}$$

$$Z\% = 1.10 + 4.03j \quad \% \quad 200 \text{ kVA}$$

- Find:
- rated high side current of each transformer
 - % of total bank current drawn by each transformer
 - maximum bank load that can be handled without overloading either transformer

Example 12-2 Solution (1)

- a) Rated current of both transformers

$$I_{\text{ratedA}} = \frac{S_{\text{rated}}}{V_{\text{rated}}} = \frac{100,000 \text{ VA}}{4160 \text{ V}} = 24.04 \text{ A} \quad \text{Transformer A: 100 kVA}$$

$$I_{\text{ratedB}} = \frac{200,000}{4160 \text{ V}} = 48.08 \text{ A} \quad \text{Transformer B: 200 kVA}$$

- b) Percent current drawn by each transformer

Convert %Z to actual ohms. Need base impedances

$$Z_{\text{baseA}} = \frac{(V_{\text{baseA}})^2}{S_{\text{baseA}}} = \frac{(4160 \text{ V})^2}{100,000 \text{ VA}} = 173.1 \Omega$$

$$Z_{\text{baseB}} = \frac{(V_{\text{baseB}})^2}{S_{\text{baseB}}} = \frac{(4160 \text{ V})^2}{200,000 \text{ VA}} = 86.53 \Omega$$

Example 12-2 Solution (2)

P.u.

$$\bar{Z}_A = 0.0169 + j0.0316$$

$$\bar{Z}_A = 0.0356 / 62.6^\circ \text{ p.u.}$$

$$\bar{Z}_B = 0.011 + j0.0403$$

$$\bar{Z}_B = 0.0418 / 74.7^\circ \text{ p.u.}$$

Convert p.u. to ohms

$$\bar{Z}_A = Z_{\text{base}} \bar{Z}_A = (173.1 \Omega) (0.0356 / 62.6^\circ)$$

$$\bar{Z}_A = 6.161 / 62.6^\circ \Omega$$

$$\bar{Z}_B = Z_{\text{base}} \bar{Z}_B = (86.53 \Omega) (0.0418 / 74.7^\circ)$$

$$\bar{Z}_B = 3.617 / 74.7^\circ \Omega$$

Example 12-2 Solution (3)

Find the admittance

$$Y_P = \frac{1}{\bar{Z}_A} + \frac{1}{\bar{Z}_B}$$

$$Y_P = \frac{1}{6.161 / 62.7^\circ} + \frac{1}{3.615 / 74.7^\circ}$$

$$Y_P = 0.1623 / -62.7^\circ + 0.2766 / -74.7^\circ \text{ S}$$


$$Y_P = (0.0749 - j0.1442) + (0.0788 - j0.2668) \text{ S}$$

$$Y_P = 0.1474 - j0.411 \text{ S}$$

$$Y_P = 0.4366 / -70.3^\circ \text{ S Total admittance.}$$

Now use current divide rule to find flows through each transformer.

Example 12-2 Solution (4)

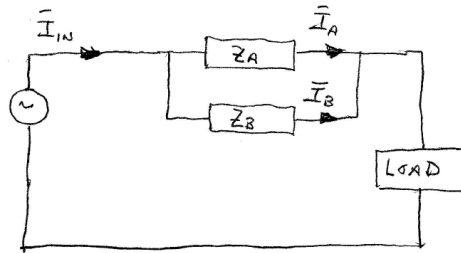

Find I_A and I_B in terms of I_{in}

$$\bar{V}_A = \frac{1}{Z_A} = 0.1623 \angle -62.7^\circ \text{ S}$$

$$\bar{V}_B = \frac{1}{Z_B} = 0.2766 \angle -74.7^\circ \text{ S}$$

$$|\bar{I}_A| = |\bar{I}_{in}| \frac{|\bar{V}_A|}{|\bar{V}_P|} \quad |\bar{I}_A| = I_{in} \left[\frac{0.1623 \angle -62.7^\circ}{0.4366 \angle -70.3^\circ} \right] \quad I_A = I_{in} \cdot 0.3717$$

$$|\bar{I}_B| = |\bar{I}_{in}| \frac{|\bar{V}_B|}{|\bar{V}_P|} \quad |\bar{I}_B| = I_{in} \left[\frac{0.2766 \angle -74.7^\circ}{0.4366 \angle -70.3^\circ} \right] \quad I_B = I_{in} \cdot 0.6335$$

Example 12-2 Solution (5)

Transformer A carries 37.17% of the total load

$$I_A = I_{in} \cdot 0.3717$$

Transformer B carries 63.35% of the total load

$$I_B = I_{in} \cdot 0.6335$$

c) Find the maximum load of the parallel transformers without an overload

Let $I_A = I_{\text{rated}A} = 24.04 \text{ A}$ and compute I_{in} using relationships above. Then find flow through other transformer

$$I_A = 0.3717 I_{in} \quad \frac{I_A}{0.3717} = I_{in} \quad \frac{24.04}{0.3717} = I_{in} \quad 64.68 \text{ A} = I_{in}$$

Example 12-2 Solution (6)

$$I_B = 0.6335 I_{IN}$$

$$I_B = 0.6335 (69.68 \text{ A})$$

$$I_B = 40.97 \text{ A}$$

TX B not
overloaded
 $I_{\text{ratedB}} = 48.08$

Let $I_B = I_{\text{ratedB}} = 48.08 \text{ A}$. Find I_{in} and then compute the flow in transformer A

$$I_B = 0.6335 I_{IN}$$

$$\frac{I_B}{0.6335} = I_{IN} \quad \frac{48.08 \text{ A}}{0.6335} = I_{IN} \quad 75.9 \text{ A} = I_{IN}$$

Example 12-2 Solution (7)

$$I_A = 0.3717 I_{IN}$$

$$I_A > I_{\text{rated A}}$$

$$I_A = 0.3717 (75.9 \text{ A})$$

$$28.2 > 29.04 \text{ A}$$

$$I_A = 28.2 \text{ A}$$

$$\text{Max load, } I_{\text{in}} = 64.68 \text{ A}$$

Find bank power

$$S_{\text{BANK}} = V_{\text{rated}} I_{IN}$$

$$V_{\text{rated}} = 4160 \text{ V}$$

$$I_{IN} = 64.68 \text{ A}$$


$$S_{\text{BANK}} = (4160 \text{ V})(64.68 \text{ A})$$

$$S_{\text{BANK}} = 269,069 \text{ VA}$$

$$\approx 269 \text{ kVA}$$

Autotransformers

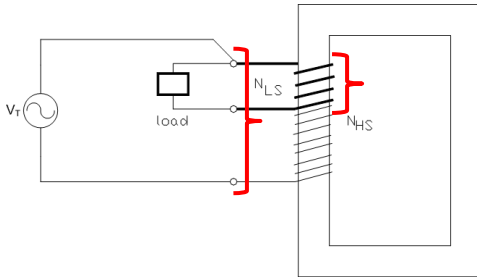Autotransformers use a single tapped coil to change voltage levels and current levels – They provide **no electrical isolation**



N_{LS} = number of turns
"embraced" by low side
 N_{HS} = number of turns on high side

Polarity of induced voltages determined by direction of current and winding wraps.

If $N_{LS} = 20$ and $N_{HS} = 80$


$$a = \frac{N_{HS}}{N_{LS}} = \frac{V_{HS}}{V_{LS}}$$

$$a = \frac{80}{20} = 4 \quad V_{HS} = 120 \text{ V} \quad \text{so} \quad V_{LS} = \frac{V_{HS}}{a} = \frac{120}{4} = 30 \text{ V}$$

Step-down action

Autotransformers: Step-Down Operation

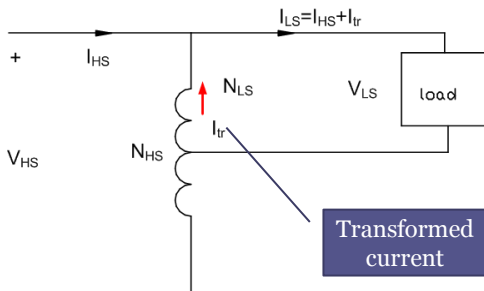Some load is transferred via conduction from one side to the other and some is transferred by transformer action



Like two winding transformers

$$S_{HS} = S_{LS}$$

$$V_{HS} \cdot I_{HS} = V_{LS} \cdot I_{LS}$$

I_{tr} = the current from transformer action

Low side current must increase to maintain power balance so:


$$I_{LS} = I_{HS} + I_{tr}$$

Autotransformer connected in step-down mode. Note direction of I_{tr}

Autotransformer Current Ratio and Step-Up Operation

Current ratio of autotransformer $\frac{I_{HS}}{I_{LS}} = \frac{1}{a}$ Where $a = \frac{N_{HS}}{N_{LS}}$

Autotransformer In Step-up Mode

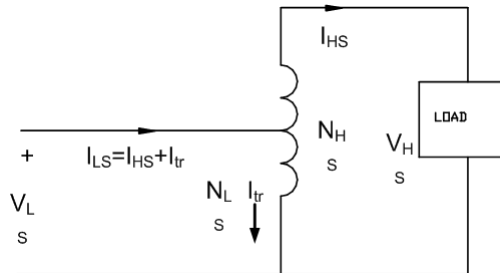


Coils in these diagrams are series aiding (induced voltages add)

Note: direction of I_{tr} reversed to maintain power balance

Autotransformers from Two-Winding Transformers

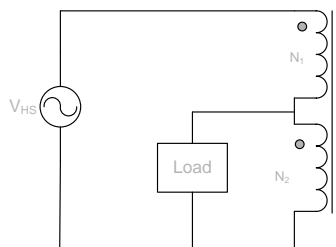Autotransformer action can be obtained by proper connection of two winding transformer coils



For step-down mode

$$N_{HS} = N_1 + N_2$$

$$N_{LS} = N_2$$


$$a = \frac{N_{HS}}{N_{LS}} = \frac{N_1 + N_2}{N_2} = \frac{V_{HS}}{V_{LS}}$$

Where: N_1 = number of turns in primary (HV)

N_2 = number of turns in secondary (LV)

Autotransformers from Two-Winding Transformers

Step-Down Connections

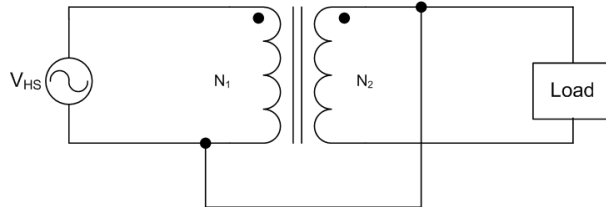

Find V_{LS} with $V_{HS}=120$ V, $N_1=500$ and $N_2=100$

$$a = \frac{N_{HS}}{N_{LS}} = \frac{N_1 + N_2}{N_2} = \frac{V_{HS}}{V_{LS}} \quad a = \frac{500 + 100}{100} = 6 \quad a = \frac{V_{HS}}{V_{LS}} \text{ Where } V_{HS} = 120 \text{ V}$$

$$V_{LS} = \frac{V_{HS}}{a} = \frac{120 \text{ V}}{6} = 20 \text{ V}$$


Autotransformer Example

Example 12-3: 400 turn autotransformer operating at a 25% tap supplies a 4.8 kVA load at 0.85 lagging P.F. $V_{HS} = 2400$ V

Find:

- a) load current b) incoming line current c) I_{tr} d) apparent power transformed and conducted

Example 12-3 Solution (1)

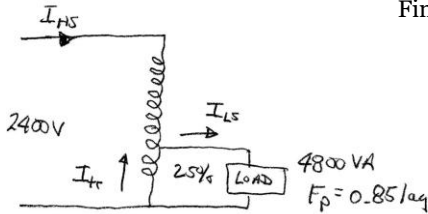

Find turns ratio

$$N_{HS} = 460 \text{ t} \quad N_{LS} = 0.25(N_{HS})$$

$$N_{LS} = 0.25(460 \text{ t})$$

$$N_{LS} = 100 \text{ t}$$

$$a = \frac{N_{HS}}{N_{LS}} = \frac{460 \text{ t}}{100 \text{ t}} = 4$$

Find secondary voltage

$$\frac{V_{HS}}{V_{LS}} = a \quad V_{HS} = a V_{LS}$$

$$\frac{V_{HS}}{a} = V_{LS} \quad \frac{2400 \text{ V}}{4} = 600 \text{ V}$$

a) Find I_{LS}

$$S_{\text{load}} = 4800 \text{ VA} \quad V_{LS} = 600 \text{ V}$$

$$I_L = \frac{S_{\text{load}}}{V_{LS}} \quad I_L = \frac{4800 \text{ VA}}{600 \text{ V}}$$

$$I_L = 8 \text{ A} \quad \leftarrow \text{Ans}$$

Example 12-3 Solution (2)

b) Find high-side current

Current must decrease to maintain power balance

$$I_{HS} + I_{tr} = I_{LS}$$

$$\frac{I_{HS}}{I_{LS}} = \frac{1}{a} \Rightarrow I_{HS} = \frac{1}{a} I_{LS} \quad I_{LS} = I_L = 8 \text{ A} \quad I_{HS} = \frac{1}{4}(8 \text{ A}) = 2 \text{ A}$$

c) Find transformed current

$$I_{tr} = I_{LS} - I_{HS} \quad I_{tr} = 8 - 2 \text{ A}$$

$$I_{tr} = 6 \text{ A} \quad \leftarrow \text{Ans}$$

d) Find transformed and conducted apparent powers

$$S_{tr} = V_{LS} I_{tr} \quad S_{tr} = 600 \text{ V}(6 \text{ A}) = 3600 \text{ VA} \quad \leftarrow \text{Ans}$$

$$S_{\text{cond}} = V_{LS} I_{HS} \quad S_{\text{cond}} = 600 \text{ V}(2) = 1200 \text{ VA} \quad \leftarrow \text{Ans}$$

End Lesson 12: Parallel Transformers and Autotransformers

ET 332b Ac Motors, Generators and Power Systems