

ET 332b
Ac Motors, Generators and Power Systems

LESSON 13 INDUCTION MOTOR MODEL EXAMPLE

1

LEARNING OBJECTIVES

After this presentation you will be able to:

- Draw the per phase circuit model of an induction motor
- Correctly place motor parameters on the circuit model
- Reduce the circuit model and solve for stator and rotor currents
- Compute the motor power and losses
- Compute motor torques

2

Lesson13_et332b.pptx

Example 13-1: A 60 Hz, 15 HP, 460 V, 4-pole wye connected induction spins a mechanical load at 1778 RPM. The motor parameters given in ohms referred to the stator are:

$$\begin{aligned} R_1 &= 0.18 & R_2 &= 0.20 \\ X_1 &= 1.15 & X_2 &= 1.23 \\ X_M &= 40 & R_{fe} &= 317 \end{aligned}$$


Total mechanical power losses (friction, windage and stray) are 170 W
Find: a.) the motor slip; b.) the motor line current; c.) the apparent power the motor draws from the system; d.) active power drawn by the motor; e.) motor power factor; f.) total electric power losses of motor; g.) shaft power and torque; h.) efficiency

Use per phase circuit model and circuit analysis to find these quantities

3

Lesson13_et332b.pptx

EXAMPLE 13-1 SOLUTION (1)

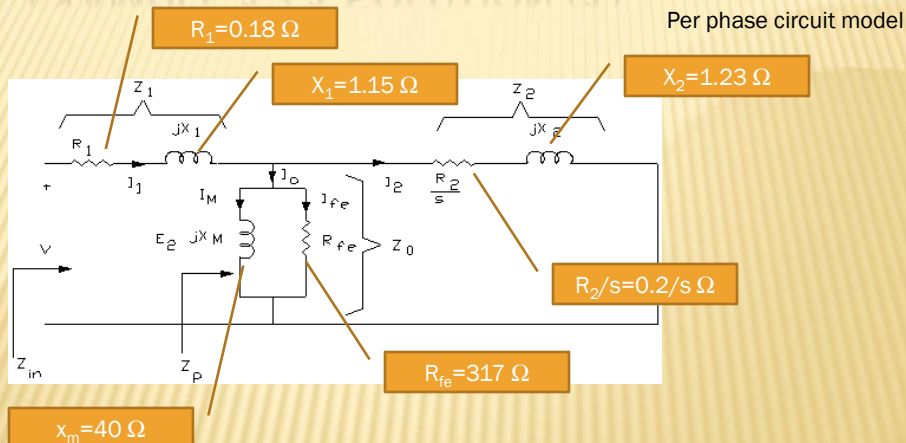

$f = 60 \text{ Hz}$ Number of poles : $P=4$ $n_r = 1778 \text{ RPM}$
 $P_{fw} + P_{stray} = 170 \text{ W}$

4

EXAMPLE 13-1 SOLUTION (2)

Find the motor slip

a.) MOTOR SLIP

$$s = \frac{n_s - n_r}{n_s} \quad n_s = \frac{120f}{p} = \frac{120(60\text{Hz})}{4}$$

$$n_s = 1800 \text{ RPM}$$

$$s = \frac{1800 - 1778}{1800} = \boxed{0.0122}$$


b.) MOTOR LINE CURRENT WYE CONNECTED $I_L = I_p = I_1$
REDUCE CIRCUIT

$$Z_2 = \frac{R_2}{s} + jX_2 = \frac{0.20}{0.0122} + j1.23 \Omega$$

$$Z_2 = 16.364 + j1.23 \Omega = 16.91 \angle 4.3^\circ$$

5

EXAMPLE 13-1 SOLUTION (3)

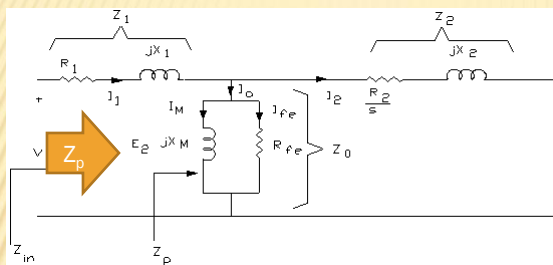

$Z_p = Z_2 \parallel R_{fe} \parallel jX_m$ Use formulas shown previously OR

$$Z_p = \frac{1}{\frac{1}{Z_2} + \frac{1}{R_{fe}} + \frac{1}{jX_m}} = \frac{1}{\frac{1}{16.91 \angle 4.3^\circ} + \frac{1}{317 \Omega} + \frac{1}{40 \angle 90^\circ}}$$


$$Z_p = \frac{1}{0.0569 \angle 4.3^\circ + 0.00315 \angle 0^\circ + 0.025 \angle -90^\circ} = 19.207 \angle 24.84^\circ$$

6

Lesson13_et332b.pptx

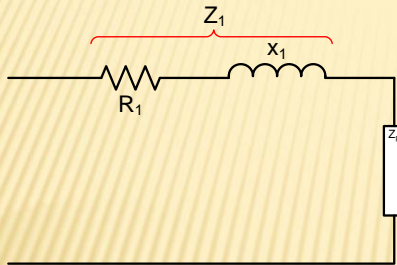EXAMPLE 13-1 SOLUTION (4)

Find Z_{in} to find the phase current in the stator



$$Z_1 = 0.18 + j1.15 \Omega = 1.164 \angle 81.1^\circ$$

$$Z_{in} = 1.164 \angle 81.1^\circ + 14.207 \angle 29.89^\circ$$

$$Z_{in} = 14.885 \angle 28.57^\circ$$

$$Z_{in} = Z_1 + Z_p$$

I_1 = STATOR CURRENT

$$I_1 = \frac{V}{Z_{in}} \quad V = \frac{V_{LL}}{\sqrt{3}} = \frac{460V}{\sqrt{3}} = 265.6V$$

$$I_1 = 17.843 \angle -28.57^\circ$$

$$I_1 = \frac{265.6 \angle 0^\circ}{14.885 \angle 28.57^\circ}$$

7

Lesson13_et332b.pptx

EXAMPLE 13-1 SOLUTION (5)

c.) Apparent Power S_{in}

$$\bar{S}_{in} = \sqrt{3} \bar{V}_{LL} \bar{I}_L^* = \sqrt{3} (460 \angle 0^\circ) (17.843 \angle +28.57^\circ) \text{ VA}$$

$$\bar{S}_{in} = 14216 \angle 28.57^\circ \text{ VA}$$

d.) Active Power motor Draws P_{in}

$$P_{in} = \sqrt{3} V_{LL} I_L \cos \theta \quad \theta = \text{angle between } V \text{ and } I$$

$$\theta = 28.57^\circ$$

$$P_{in} = \sqrt{3} (460) (17.843) \cos (28.57^\circ)$$

$$P_{in} = 12,486 \text{ W}$$

8

EXAMPLE 13-1 SOLUTION (6)

Find the power factor and the total power losses

$$e.) F_P = \frac{P_{in}}{S_{in}} = \frac{12,486W}{14,216VA} = 0.878 \text{ Lag}$$

f.) Total P_{Loss} Rotor and Stator

$$P_{rcl} = 3I_2^2 R_2 \quad P_{sc1} = 3I_1^2 R_1 \quad P_{core} = \frac{3(E_2)^2}{R_{fe}}$$

NEED I_2 AND E_2

$$E_2 = I_1 Z_p \quad Z_p = 14.207 \angle 29.89^\circ \Omega$$

$$I_1 = 17.843 \angle -28.57^\circ A$$

9

EXAMPLE 13-1 SOLUTION (7)

Compute the rotor induced voltage

$$E_2 = (17.843 \angle -28.57^\circ)(14.207 \angle 29.89^\circ)$$

$$E_2 = 253.5 \angle -3.73^\circ V$$

Value almost equal to phase voltage

Find the rotor current from the value of E_2 and the rotor impedance, Z_2

$$I_2 = \frac{E_2}{Z_2} = \frac{253.5 \angle -3.73^\circ}{16.91 \angle 4.3^\circ}$$

$$I_2 = 15.447 \angle -8.03^\circ A$$

Power loss formula

$$P_{Loss} = P_{rcl} + P_{sc1} + P_{core}$$

10

EXAMPLE 13-1 SOLUTION (8)

$$P_{\text{Loss}} = 3I_2^2 R_2 + 3I_1^2 R_1 + \frac{3(E_2)^2}{R_{fe}}$$

$$P_{\text{Loss}} = 3(15.447)^2(0.20) + 3(17.843)^2(0.18) + \frac{3(253.5)^2}{317.50}$$

$$P_{\text{Loss}} = 143.2 \text{ W} + 171.9 \text{ W} + 608 \text{ W}$$

$$P_{\text{Loss}} = 923.1 \text{ W}$$

g.) Shaft Power and Torque:

$$P_{\text{mech}} = \frac{3I_2^2(1-s)R_2}{s} = \frac{3(15.447)^2(1-0.0122)(0.20 \Omega)}{0.0122}$$

$$P_{\text{mech}} = 11,298.4 \text{ W}$$

$$P_{\text{shaft}} = P_{\text{mech}} - P_{\text{fw}} - P_{\text{stray}} = 11,298.4 - 170 = 11,128.4 \text{ W}$$

$$P_{\text{shaft}} = \frac{11,128.4 \text{ W}}{746 \text{ W/HP}} = 14.92 \text{ HP} \quad \text{NEAR RATED (15 HP)}$$

11

EXAMPLE 13-1 SOLUTION (9)

g.) SHAFT TORQUE (lb-ft)

$$P_{\text{shaft}} = 11,128.4 \text{ W}$$

$$T_{\text{shaft}} = \frac{7.04 (P_{\text{shaft}})}{n_r} = \frac{7.04 (11,128.4 \text{ W})}{1778 \text{ RPM}}$$

$$T_{\text{shaft}} = 44.06 \text{ lb-ft}$$

h.)

$$\eta = \frac{P_o}{P_{in}} \times 100\% \quad P_o = P_{\text{shaft}} = 11,128.4 \text{ W}$$

$$P_{in} = 12,486 \text{ W}$$


$$\eta = \frac{11,128.4 \text{ W}}{12,486 \text{ W}} \times 100\% = 89.13\%$$

12

Lesson13_et332b.pptx

APPROXIMATE EQUIVALENT CIRCUIT

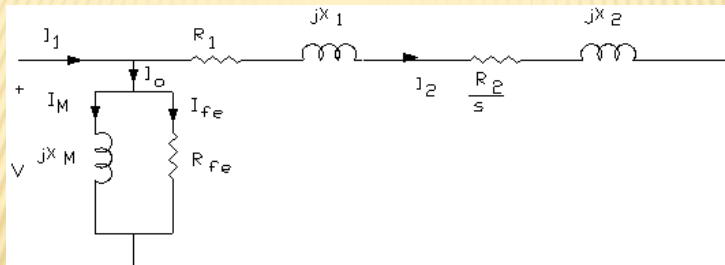Approximate Equivalent Circuit - move magnetizing branch



Stator impedance is usually small so there is little voltage drop across Z_1

13

Lesson13_et332b.pptx

APPROXIMATE EQUIVALENT CIRCUIT

Adjusting the values of R_1 and R_2 affect T_D

$$T_D = \frac{21.12}{n_s} \cdot \left[\frac{\frac{R_2}{s} \cdot V^2}{\left(R_1 + \frac{R_2}{s} \right)^2 + (X_1 + X_2)^2} \right]$$

Above equation derived from approximate equivalent circuit

T_D proportional to V^2 Reducing V reduces torques

14

Lesson13_et332b.pptx

ET 332b

Ac Motors, Generators and Power Systems

END LESSON 13 INDUCTION MOTOR MODEL EXAMPLE

15