

Lesson 4: Three Phase Sources and Loads

ET 332b
ET 332b Ac Motors, Generators and Power Systems

1

Lesson 4_et332b.pptx

Learning Objectives

After this presentation you will be able to:


- Identify circuit impedances, voltages and currents using the double subscript notation.
- Perform calculations on wye connected three-phase sources and loads.
- Perform calculations on delta connected three-phase sources and loads.
- Construct phasor diagrams of three-phase sources and loads.
- Identify the time and phasor plots of a three phase set of voltages and currents.

▶ 2

Lesson 4_et332b.pptx

Double Subscript Notation

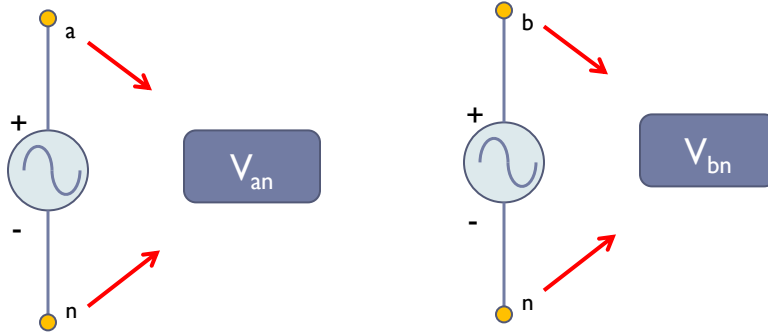Sources and voltage drops are defined by the terminal letter. Voltage drop and polarity defined by order of subscripts




Voltages considered positive if first node subscript is higher potential than second node subscript

▶ 3

Lesson 4_et332b.pptx

Double Subscript Notation

Identify current flow from point b to c

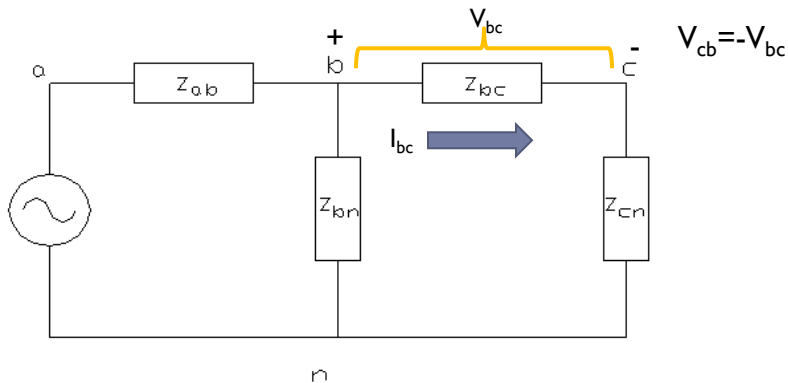

$$I_{bc} = \frac{V_{bc}}{Z_{bc}}$$

V_{bc} = difference in potential between points b and c. If voltage at point b is taken as the reference point, then the polarity is reversed.

▶ 4

Lesson 4_et332b.pptx

Three-Phase Power Systems

Balanced three-phase voltage sources

Characteristics: Three phasor voltages
 Equal voltage magnitudes
 Phase shift equally spaced 120 degrees apart

Time equations for balanced three-phase voltage sources

$$v_{an}(t) = V_p \cdot \sin(2\pi \cdot f \cdot t + 0^\circ)$$

$$v_{bn}(t) = V_p \cdot \sin(2\pi \cdot f \cdot t - 120^\circ)$$


$$v_{cn}(t) = V_p \cdot \sin(2\pi \cdot f \cdot t - 240^\circ)$$

▶ 5

Lesson 4_et332b.pptx

Three-Phase Power Systems

Time Plots of Three Phase Voltages

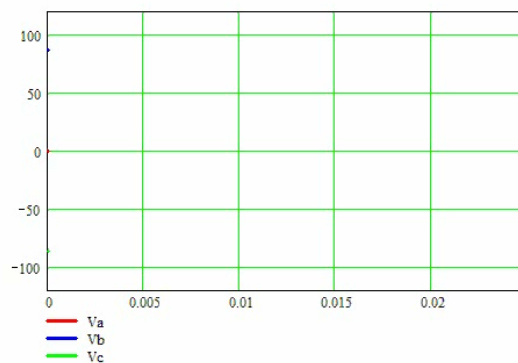


▶ 6

Lesson 4_et332b.pptx

Three-Phase Three-Phase

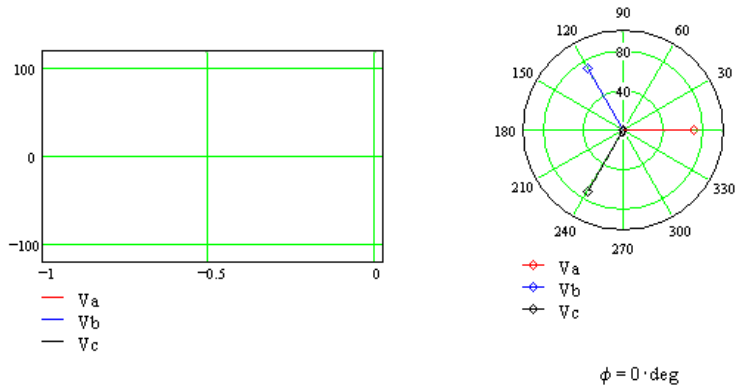Time Plots of Three Phase Voltages and Phasors




▶ 7

Lesson 4_et332b.pptx

Three-Phase Source Connections

Wye – Connected, three-phase 3ϕ sources

In wye connection:

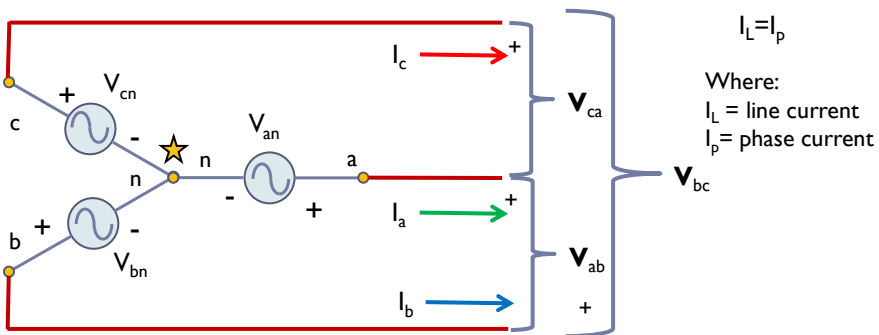


Determine the relationship between the magnitude and phase shift of each source voltage and the current and voltage at the terminals of the connection

▶ 8

Lesson 4_et332b.pptx

Wye Connected Sources

Voltage relationships

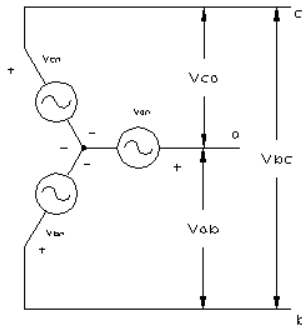

Perform phasor subtraction to find the values


Line-to-line voltage phasors

$$\bar{V}_{ab} = \bar{V}_{an} - \bar{V}_{bn}$$

$$\bar{V}_{bc} = \bar{V}_{bn} - \bar{V}_{cn}$$

$$\bar{V}_{ca} = \bar{V}_{cn} - \bar{V}_{an}$$

In balanced systems $|\bar{V}_{an}| = |\bar{V}_{bn}| = |\bar{V}_{cn}|$

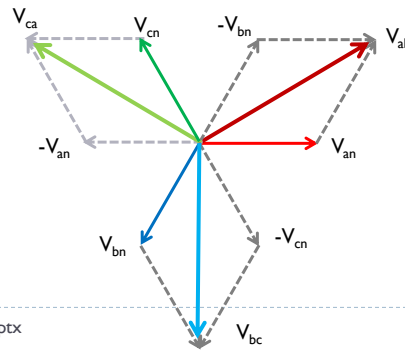


▶ 9

Lesson 4_et332b.pptx

Wye Connected Sources

Wye connected line voltage magnitudes

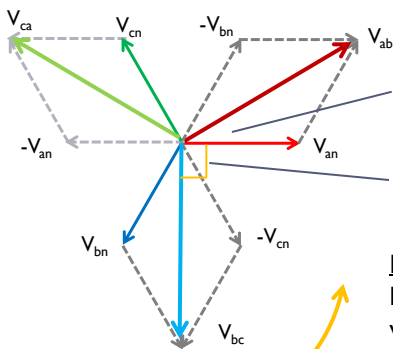

30°

90°

$$|\bar{V}_{ab}| = \sqrt{3} \cdot |\bar{V}_{an}|$$

$$|\bar{V}_{bc}| = \sqrt{3} \cdot |\bar{V}_{bn}|$$

$$|\bar{V}_{ca}| = \sqrt{3} \cdot |\bar{V}_{cn}|$$

Phase shifts

Line-to-line (line) voltages lead phase voltages by 30 degrees for CCW rotation

Rotation

$$\bar{V}_{ab} = V_{ab} \angle 30^\circ$$

$$\bar{V}_{bc} = V_{bc} \angle -90^\circ$$


$$\bar{V}_{ca} = V_{ca} \angle -210^\circ$$

▶ 10

Lesson 4_et332b.pptx

Wye Connect Systems

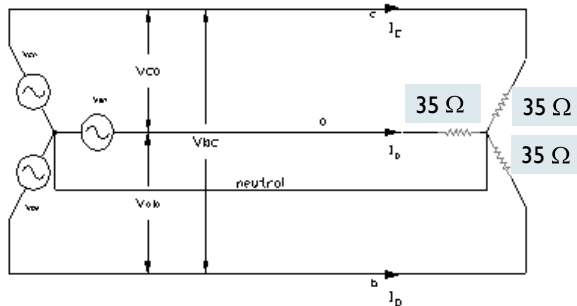Example 4-1: a) Find the line-to-line voltage phasors for the wye connected source. b) Find the line current phasors in each of the three phases of the resistive load. c) Find the current flowing in the neutral .
 $V_{an} = 100 \angle 0^\circ$ $V_{bn} = 100 \angle -120^\circ$ $V_{cn} = 100 \angle -240^\circ$



▶ 11

Lesson 4_et332b.pptx

Example 4-1 Solution (1)

Balanced 3 ϕ systems can be analyzed using a single phase to neutral and the other quantities determined by the appropriate phase shifts.

$$\begin{aligned} \text{a) } \bar{V}_{an} &= 100 \angle 0^\circ & V_{ab} &= \sqrt{3} V_{an} \\ \bar{V}_{bn} &= 100 \angle -120^\circ & V_{ad} &= \sqrt{3} (100V) = 173.2V \\ \bar{V}_{cn} &= 100 \angle -240^\circ & |\bar{V}_{ab}| &= |\bar{V}_{bc}| = |\bar{V}_{cn}| = 173.2V \end{aligned}$$

For this sequence of phasors, line-to-line voltages lead phase voltages by 30 degrees

$$\begin{aligned} \bar{V}_{ab} &= 173.2 \angle 30^\circ \\ \bar{V}_{bc} &= 173.2 \angle -90^\circ \\ \bar{V}_{ca} &= 173.2 \angle -210^\circ \end{aligned}$$


← Ans

▶ 12

Lesson 4_et332b.pptx

Example 4-1 Solution (2)

b)

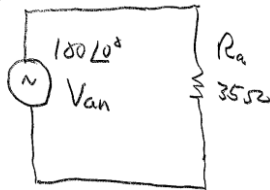

In wye connection line current equals phase current

For "a" phase

$$\bar{I}_a = \frac{\bar{V}_{an}}{R_a} = \frac{100\angle 0^\circ}{35\angle 0^\circ} = 2.857\angle 0^\circ \text{ A} \quad \leftarrow \text{Ans}$$

For other phases

$$\bar{I}_b = \frac{100\angle -120^\circ \text{ V}}{35\angle 0^\circ \Omega} = 2.857\angle -120^\circ \text{ A} \quad \leftarrow \text{Ans}$$


$$\bar{I}_c = \frac{100\angle -240^\circ}{35\angle 0^\circ \Omega} = 2.857\angle -240^\circ \text{ A} \quad \leftarrow \text{Ans}$$

▶ 13

Lesson 4_et332b.pptx

Example 4-1 Solution (3)

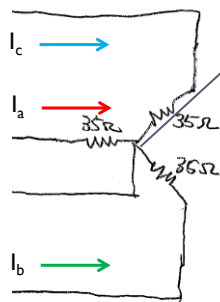c) To find the neutral current, sum the currents at the load neutral point



Neutral point

$$\bar{I}_n = \bar{I}_a + \bar{I}_b + \bar{I}_c$$

$$\bar{I}_n = 2.857\angle 0^\circ + 2.857\angle -120^\circ + 2.857\angle -240^\circ$$

Convert to rectangular form to add

$$\bar{I}_n = (2.857 + j0) + (-1.4285 - j2.474) + (-1.4285 + j2.474) \text{ A}$$

$$\bar{I}_n = 0$$


In balanced 3 ϕ system, neutral conductor carries no current. It is used for safety and to handle unbalances

▶ 14

Lesson 4_et332b.pptx


Example 4-1 Solution (4)

Phasor diagram

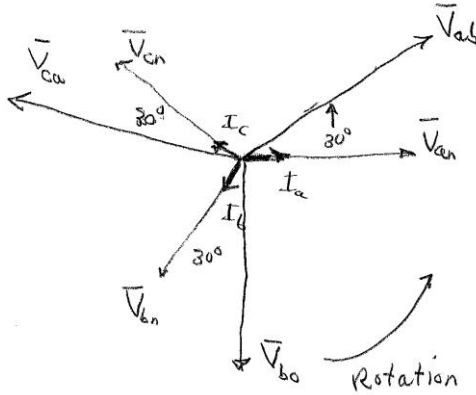

All line-to-line voltages lead the phase voltages by 30 degrees. For resistive load, the phase current is in phase with V_{pn} , the phase-to-neutral voltage.

Delta Connected Sources

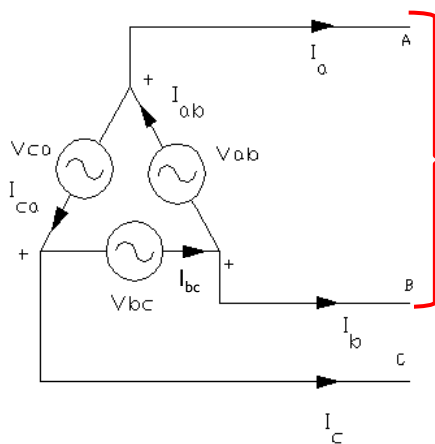

Phase voltages are equal to line-to-line voltages in delta connections

$$|\vec{V}_{LL}| = |\vec{V}_P|$$


Where: V_{LL} = line-to-line voltage
 V_p = phase voltage

$$\text{So } |\vec{V}_{ab}| = |\vec{V}_{bc}| = |\vec{V}_{ca}|$$

To find relationship between phase and line currents, perform KCL at every corner node

Delta Connected Sources

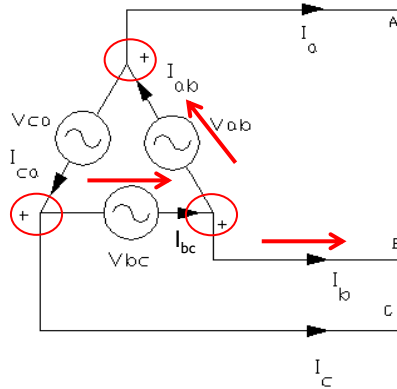Current relationships between line and phase



For node B

$$\bar{I}_{bc} - \bar{I}_{ab} - \bar{I}_b = 0$$

$$\bar{I}_{bc} - \bar{I}_{ab} = \bar{I}_b$$

For node A

$$\bar{I}_{ab} - \bar{I}_{ca} - \bar{I}_a = 0$$

$$\bar{I}_{ab} - \bar{I}_{ca} = \bar{I}_a$$

For node C

$$\bar{I}_{ca} - \bar{I}_{bc} - \bar{I}_c = 0$$

$$\bar{I}_{ca} - \bar{I}_{bc} = \bar{I}_c$$

Phasor subtraction gives the current magnitude

$$|\bar{I}_L| = \sqrt{3} \cdot |\bar{I}_p|$$

Where:

I_L = line current


I_p = phase current

▶ 17

Lesson 4_et332b.pptx

Delta Connected Sources

Phasor diagram of delta currents

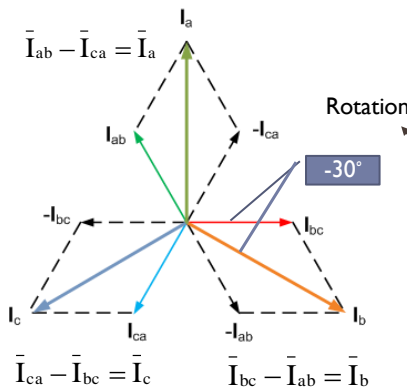

Line current phasors lag phase currents by 30 degrees in balanced delta connection

$$\bar{I}_L = \sqrt{3} \cdot \bar{I}_p \angle -30^\circ$$

Above hold for all phases with I_p as reference phasor


Phase rotation is ABC in this case

▶ 18

Lesson 4_et332b.pptx

Delta Connection Example

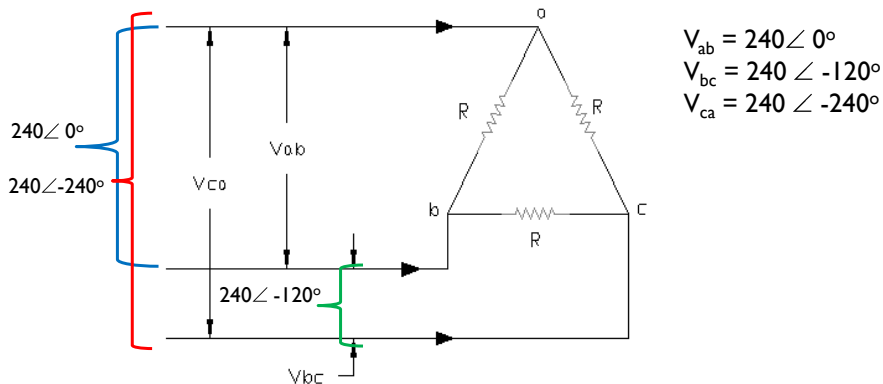Example 4-2: For the delta connected load shown, a) find the phasor values of phase and line currents for the circuit.: b) draw a phasor diagram of the computed currents and given voltages $R = 15$ ohms in each phase.



▶ 19

Lesson 4_et332b.pptx

Example 4-2 Solution (1)

For this balanced system, compute the values for single phase and then shift the angles for the other values

$$\bar{I}_{ab} = \frac{V_{ab}}{R} = \frac{240 \angle 0^\circ}{15 \angle 0^\circ} = 16 \angle 0^\circ \text{ A}$$

Now compute the line current

$$\bar{I}_a = \sqrt{3} I_{ab} \angle -30^\circ$$

$$\bar{I}_a = \sqrt{3} (16) \angle 0^\circ - 30^\circ$$

$$\bar{I}_a = 27.72 \angle -30^\circ \text{ A}$$

\bar{I}_{bc} and \bar{I}_{ca} -120° and -240° from
 \bar{I}_{ab} so

$$\bar{I}_{bc} = 16 \angle -120^\circ \quad \bar{I}_{ca} = 16 \angle -240^\circ$$

▶ 20

Lesson 4_et332b.pptx

Example 4-2 Solution (2)

Similarly for the line current


$$\vec{I}_b = 27.72 \angle -15^\circ \text{ A}$$

$$\vec{I}_c = 27.72 \angle -270^\circ \text{ A}$$

Phasor diagram for delta connected load Example 4-2

Resistive circuit, so phase currents are in phase with voltages that produce it.

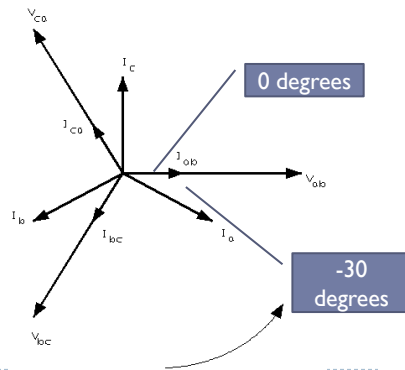Line currents lags the phase currents by the 30 degrees




▶ 21

Lesson 4_et332b.pptx

Delta Connected Load-General Impedances

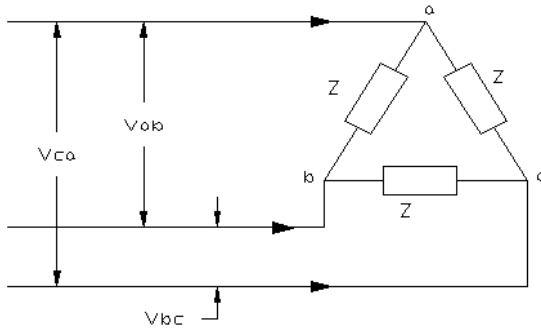Example 4-3: a) Find the phasor values of phase and line currents for the circuit shown: b) draw a phasor diagram of the computed currents and given voltages. $Z = 30 \angle -39^\circ$ ohms.



$$V_{ab} = 240 \angle 0^\circ$$

$$V_{bc} = 240 \angle -120^\circ$$

$$V_{ca} = 240 \angle -240^\circ$$

▶ 22

Lesson 4_et332b.pptx

Example 4-3 Solution (1)

Phase current of V_{ab}

$$\bar{I}_{ab} = \frac{\bar{V}_{ab}}{\bar{Z}} = \frac{240 \angle 0^\circ}{30 \angle -39^\circ}$$

$$\bar{I}_{ab} = 8 \angle 39^\circ \text{ A}$$

Line current $\bar{I}_a = \sqrt{3} I_{ab} \angle -30^\circ + \theta$ $\bar{I}_a = 13.85 \angle 49^\circ$

Other phases $\bar{I}_{bc} = 8 \angle -81^\circ \text{ A}$

$$\bar{I}_{ca} = 8 \angle -201^\circ \text{ A}$$

$$\bar{I}_b = \sqrt{3} I_{bc} \angle -30^\circ + \theta$$

$$\bar{I}_c = \sqrt{3} I_{ca} \angle -30^\circ + \theta$$

$$\bar{I}_b = 13.85 \angle -30 - 81^\circ$$

$$\bar{I}_c = 13.85 \angle -30 - 201^\circ \text{ A}$$

$$\bar{I}_b = 13.85 \angle -111^\circ$$


$$\bar{I}_c = 13.85 \angle -231^\circ \text{ A}$$

▶ 23

Lesson 4_et332b.pptx

Example 4-3 Solution (2)

Example 4-3 phasor diagram

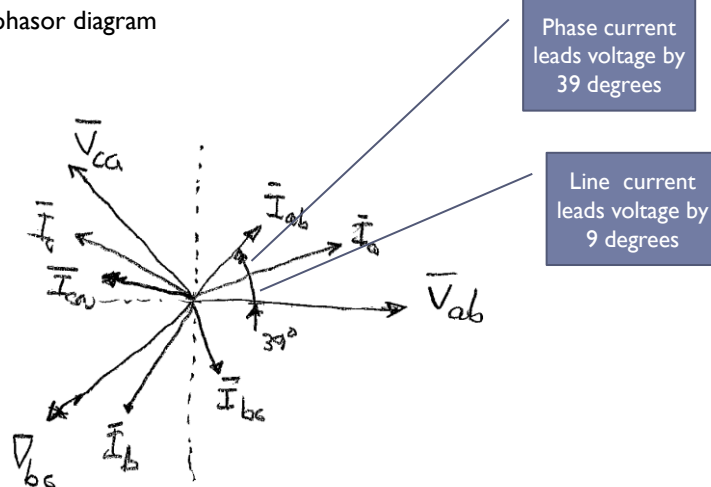

▶ 24

Lesson 4_et332b.pptx

End Lesson 4: Three Phase Sources and Loads

ET 332a Ac Motors, Generators and Power Systems