

Lesson 7: Power and Energy Measurement

ET 332b Ac Motors, Generators and Power Systems

Lesson 7_et332b.pptx

1

After this presentation you will be able to:

- Determine the phase sequence of a 3-phase voltage source
- Explain the difference between single and 3-phase ac power flow in time
- Connect power meters to read active power and reactive power
- Explain how energy meters operate
- Read and compute energy consumption

Learning Objectives

Lesson 7_et332b.pptx

2

Phase Sequence - order of voltages in a 3-phase system. Determine the direction of rotation in motors and the direction of flow in power and energy measurement

Positive sequence: Phase voltages and currents have ABC order

Negative sequence: Phase voltages and currents have BAC order

Phase Sequence in 3-Phase Systems

Lesson 7_et332b.pptx 3

Phase sequence of interconnected power systems must match. Identify phase lead of each system using voltmeter

V-meter measures no potential difference if a1 is in phase with a2

Phase Sequence Identification

Lesson 7_et332b.pptx 4

Cross-phased system

V difference between leads c1 and b2 short circuits phases C & B

V difference between leads b1 and c2 short circuits phases C & B

Phase Sequence Identification

Lesson 7_et332b.pptx 5

Procedure For Interconnecting Systems

System Must Have:

- 1) Same frequency
- 2) Same voltage
- 3) Same phase sequence ABC or BAC


Is $V \neq 0$ move T to another lead

Is $V = 0$? If so connect ?? to a1

Phase Sequence

Lesson 7_et332b.pptx 6

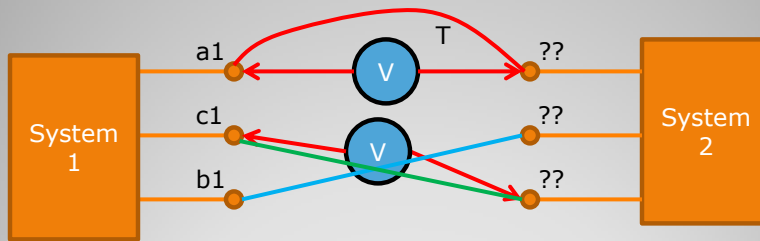Example 7-1: determine the correct connections to tie the two systems together




- 1) a1-??: V=0 connect leads
- 2) c1-?? V≠0 move T lead
- 3) c1-??: V=0 connect leads

Phase Sequence

Lesson 7_et332b.pptx

7

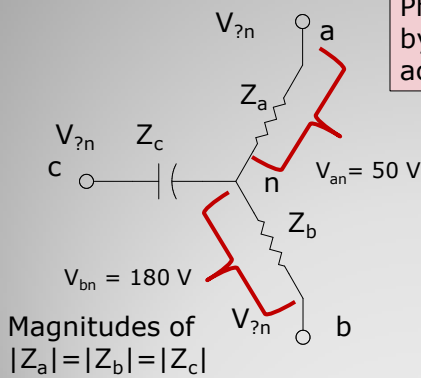Simple indicator uses unbalanced Y-connection with no ground



Phase sequence determined by voltage measurements across phase to neutral

Sequence:
V-high (A),
V-low (B),
Capacitor (C)

Example:

Phase Sequence BAC

Phase Sequence Indicator

Lesson 7_et332b.pptx

8

Balanced 3-phase V's produce balanced I's

$$V_a(t) = V_m \sin(\omega t)$$

$$I_a(t) = I_m \sin(\omega t - \theta)$$

$$V_b(t) = V_m \sin(\omega t - 120^\circ)$$

$$I_b(t) = I_m \sin(\omega t - 120^\circ - \theta)$$

$$V_c(t) = V_m \sin(\omega t + 120^\circ)$$

$$I_c(t) = I_m \sin(\omega t + 120^\circ - \theta)$$

θ = power factor angle

Single phase power

$$P_{1\phi}(t) = V_a(t) \cdot I_a(t)$$

3-phase power


$$P_{3\phi}(t) = V_a(t) \cdot I_a(t) + V_b(t) \cdot I_b(t) + V_c(t) \cdot I_c(t)$$

Time Functions of AC power

Lesson 7_et332b.pptx

9

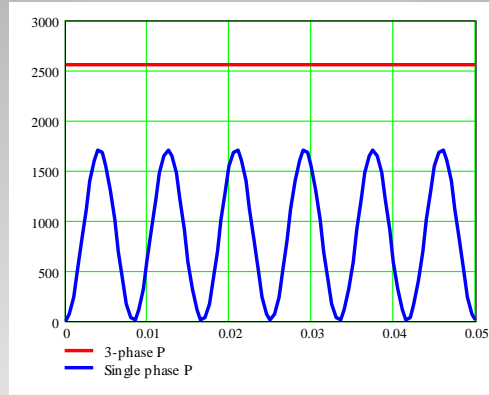Power time plots comparing single and 3-phase power



Note: Three phase power does not change in time. Single phase power instantaneously zero.

Time Functions of AC power

Lesson 7_et332b.pptx

10

Active power measurement requires measurement of both I and V

$P = V \cdot I \cdot \cos(\theta)$

Metering connections

Dotted ends of coils indicate instantaneously positive potentials and currents

Meters can be connected to measure positive for load entering or leaving the load. Convention: I entering dot gives positive P. Indicates load absorbs P. I leaving dot- negative P, load delivers P

Single Phase Power Measurements

Lesson 7_et332b.pptx 11

Blondel's Theorem - Number of meters required to measure total power in balanced three-phase system is given by

number meters = number wires - 1

Example 7-2:

| | |
|------------|-----------------------------|
| 2 elements | 3 phase 3-wire delta system |
| 3 elements | 3 phase 4-wire wye system |
| | 3 phase 3 wire wye system |

Meters can be integrated into single unit that displays total power. Each integral meter is called an **element**

Three-phase Power Metering

Lesson 7_et332b.pptx 12

Two-wattmeter method

$P_T = P_{M1} + P_{M2}$
 Meter M1 measures E_{ab} and I_a Meter M2 measures E_{cb} and I_c
 $P_{M1} = V_{ab} \cdot I_a \cdot \cos(30^\circ + \theta)$ $P_{M2} = V_{cb} \cdot I_c \cdot \cos(30^\circ - \theta)$

Three-wire Connections

Lesson 7_et332b.pptx 13

Derivation

$$P_T = P_{M1} + P_{M2} = E_{ab} I_a \cos(30^\circ + \theta) + E_{cb} I_c \cos(30^\circ - \theta)$$

Since $I_a = I_c = I_L$ and $E_{ab} = E_{cb} = E_{LL}$

$$P_T = P_{M1} + P_{M2} = E_{LL} I_L (\cos(30^\circ + \theta) + \cos(30^\circ - \theta))$$

Simplify using trigonometric identities

$$(\cos(30^\circ + \theta) + \cos(30^\circ - \theta)) = \sqrt{3} \cos(\theta)$$

$$P_T = P_{M1} + P_{M2} = \sqrt{3} E_{LL} I_L \cos(\theta)$$

Two meters read total power

2-Wattmeter Power Measurement

Lesson 7_et332b.pptx 14

Reading of meter M1 changes as load F_p changes

$\theta = 60^\circ$ then $30^\circ + \theta = 90^\circ$ so $\cos(90^\circ) = 0$ and $P_{M1} = 0$

$$F_p = \cos(60^\circ) = 0.5$$

M1 reads negative for $F_p < 0.5$

M1 reads positive for $F_p > 0.5$

M1 reads zero for $F_p = 0.5$

2-Wattmeter Power Measurement

Lesson 7_et332b.pptx

15

Example 7-3: A balanced 3-phase 3-wire load is measured using the 2-wattmeter method. The line current for the load is 125 A and the system voltage is 575 volts. The load has a power factor of 45% (0.45) lagging. Find the total load power and the readings for each meter.

$$F_p = \cos(\theta) = 0.45$$

$$P_T = \sqrt{3} E_{LL} I_L \cos(\theta) = \sqrt{3} (575)(125)(0.45) = 56,021 \text{ W}$$

Compute the reading on meter 1 and meter 2 using the equations for meter's 1 and 2

2-Wattmeter Example

Lesson 7_et332b.pptx

16

Using the formulas for M1 and M2 we get these values

$$\theta = \cos^{-1}(F_p) = \cos^{-1}(0.45) = 63.2^\circ \leftarrow$$

$$P_{M1} = E_{LL} I_L \cos(30 + \theta) = (575)(125) \cos(30 + 63.2)$$

$$P_{M1} = 71875 \cdot \cos(93.2) = -4012 \text{ W}$$

$$P_{M2} = 71875 \cos(30 - \theta) = 71875 \cos(-33.2)$$

$$P_{M2} = 60142 \text{ W}$$

$$\text{Check total value: } P_T = 60142 - 4012 = 56130 \text{ W}$$


Finding F_p from
M1 and M2 readings

$$\tan(\theta) = \sqrt{3} \cdot \frac{P_{M2} - P_{M1}}{P_{M2} + P_{M1}} \quad F_p = \cos(\theta)$$

Example 7-3 Solution (1)

Lesson 7_et332b.pptx

17

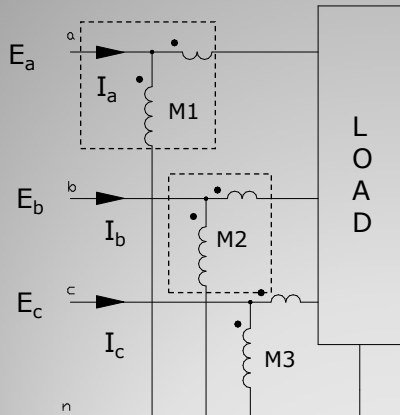

Requires a three element meter or 3 single meters

Each meter measures phase voltages and currents so

$$P_T = P_{M1} + P_{M2} + P_{M3}$$

Current entering load gives positive P readings with ABC phase sequence.

Three-Phase, 4-wire Metering Connections

Lesson 7_et332b.pptx

18

VAR and kVAR Metering

All P and Q meters measure the current components that are in phase with the load voltage.

For single phase measurements

$I_r = I_L \cos(\theta)$

$I_q = I_L \sin(\theta)$

CCW phase rotation

Active power

$P_T = EI_L \cos(\theta)$

Reactive power

$Q_T = EI_L \sin(-\theta)$

$Q_T = EI_L \cos(90 + \theta)$

$Q_T = -EI_L \sin(\theta)$

Reactive Power Metering

Lesson 7_et332b.pptx 19

Sign convention of reactive power

$I_r = I_L \cos(\theta)$

$I_q = I_L \sin(\theta)$

CCW phase rotation

Lagging current produces a negative VAR reading

$Q_T = -EI_L \sin(\theta)$

For leading current:


$Q_T = EI_L \cos(90 - \theta) = EI_L \sin(\theta)$

Leading current produces a positive VAR reading with this phase rotation

Reactive Power Metering


Lesson 7_et332b.pptx 20

VAR Measurement By Cross-Phasing Voltage

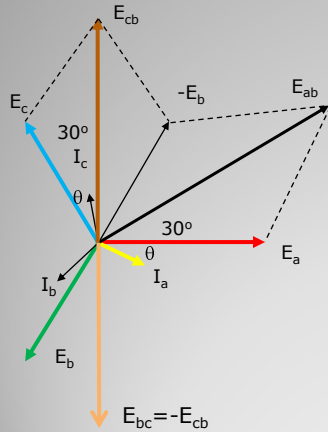

Meter measures current in phase "a" and the line- to-line voltage E_{bc} . This gives the following relationship
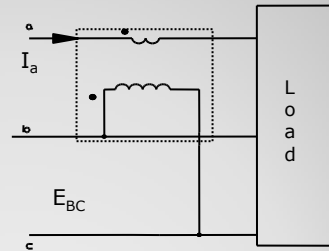
$$Q_T = \pm\sqrt{3}E_{bc}I_a \sin(\theta) = \sqrt{3}E_{LL}I_L \sin(\theta)$$



Reactive Power Measurement

Lesson 7_et332b.pptx

21

Measuring VARs from the two-watt meter method

$$P_2 - P_1 = E \cdot I \cdot \sin(\theta) = Q$$

To get total VARs, multiply both sides by square root of 3.

$$\sqrt{3} \cdot (P_2 - P_1) = \sqrt{3} \cdot E_{LL} \cdot I_L \cdot \sin(\theta) = Q_T$$

$$Q_T = \sqrt{3} \cdot (P_2 - P_1)$$

P_2 reading of meter between phases b and c

Reactive Power Measurement

Lesson 7_et332b.pptx

22

Example 7-4: The two-wattmeter connection shown below measures the power input to a load. The reading of wattmeter M1 is 5000 W and wattmeter M2 is 12,000 W. From these readings find: a.) Total active power absorbed, b.) total reactive power absorbed, c.) F_p of the load.

a) Total active power

$$P_T = P_{m1} + P_{m2}$$

$$P_{m1} = 5000 \text{ W}$$

$$P_{m2} = 12,000 \text{ W}$$

$$P_T = 5,000 + 12,000$$

$$P_T = 17,000 \text{ W}$$

← Ans

Reactive Power Measurement Two-Wattmeter Method

Lesson 7_et332b.pptx

23

b) Reactive power

$$Q_T = \sqrt{3}(P_{m2} - P_{m1})$$

$$Q_T = \sqrt{3}(12,000 - 5,000)$$

$$Q_T = \sqrt{3}(7000)$$

$$Q_T = 12,124 \text{ VAR}$$

← Ans

c) Find power factor

$$F_p = \frac{P_T}{S_T} \quad S_T = \sqrt{P_T^2 + Q_T^2}$$

$$S_T = \sqrt{17,000^2 + (12,124)^2}$$

$$S_T = 20,881 \text{ VA}$$

$$F_p = \frac{17,000 \text{ W}}{20,881 \text{ VA}}$$

$$F_p = 0.814 \text{ Lag}$$

← Ans

Example 7-4 Solution (1)

Lesson 7_et332b.pptx

24

Instrument transformers reduce voltage and current to measurable range.

Potential Transformers (PT)

Reduce voltage from high potential to
110-120 V range Typical ratios 6900/115 = 60/1 PTR

Current Transformer (CT)

Reduce high currents to 1-10A range meters rated 5 A
nominal 10 A overload. Typical ratio 600/5 = 120/1 CTR

Scaling factor for high power metering

Power ratio = (CTR)(PTR) for above case

Power ratio = (120)(60) = 7200

High Voltage and High Current Power Measurements

Lesson 7_et332b.pptx

25

ENERGY = (instantaneous power) x (time)

$W = p \times t$ where $W = \text{energy}$
 $p = \text{instantaneous power}$
 $t = \text{time}$

Electromechanical kWh meters sum power over time interval using a rotating disk.

Number of revolutions, n , proportional to energy

so $n = C_p \times P \times t$


$C_p = \text{meter energy constant}$
(units kWh/rev)

Electric Energy Measurement

Lesson 7_et332b.pptx

26

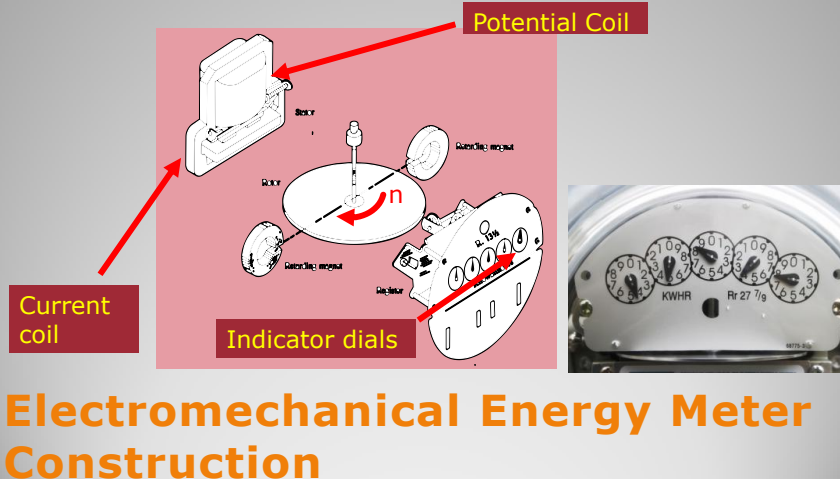kWh meter measures the electric energy we all consume in our homes and businesses



Lesson 7_et332b.pptx

27




- 1) Start from left-most Dial (10,000)
- 2) Record value just past by pointer
- 3) Record value of each dial
- 4) Subtract last reading from present meter reading
- 5) Difference is the usage in kWh for period

How to Read an Electromechanical Energy Meter

Lesson 7_et332b.pptx

28

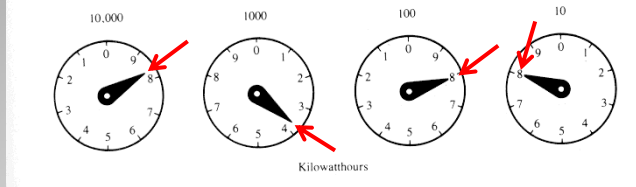Example 7-5

Compute the usage for the last 30 days if the last meter reading was 7129 and the current meter reading is shown above

Note rotation direction of the meter dials and read the last integer that the pointer has past.

Reading **8 3 8 8** Energy usage is the difference between the two readings

$$8388 - 7129 = 1259 \text{ kWh}$$

Reading an Energy Meter

Lesson 7_et332b.pptx

29



- 1) Read initial digital value at start of period
- 2) Record value
- 3) Read final digital value at end of period
- 4) Subtract last reading from present meter reading
- 5) Difference is the usage in kWh for period

Reading an Electronic Energy Meter

Lesson 7_et332b.pptx

30

Large electric customers billed on energy and average power (demand)

Units for electric energy - kWh = kilowatt-hours

$$\text{Average power} = \frac{\text{Energy consumption over period}}{\text{Time period}}$$

Average Power = Demand

$$\text{Demand} = \frac{E_e}{T} = \frac{\text{kWh}}{\text{hr}} = \text{kW}$$

Demand meters compute and record demand on intervals of 15 min 30 min and 1 hour intervals automatically

Where: E_e = electric consumption
T = time period in hours

Electric Load Characteristics

Lesson 7_et332b.pptx

31

Measuring instantaneous demand with electromechanical kWh meters

Instantaneous Demand = D_i

$$D_i = \frac{3.6 \times K_r \times K_h}{T} \text{ kW}$$

For Instrument transformer sites

$$D_i = \frac{3.6 \times K_r \times K_h \times (\text{PTR}) \times (\text{CTR})}{T} \text{ kW}$$



Where:

K_h = Watthour meter constant (Wh/rev located on meter face)

K_r = Number of revolutions / period

T = Total time (seconds)

Electric Demand

Lesson 7_et332b.pptx

32

An electromechanical watt-hour meter makes 10 revolutions in 15 seconds. ($k_h = 7.2$) Find the demand.

$$D_i = \frac{3.6 \times K_r \times K_h}{T} \text{ kW}$$

$$D_i = \frac{3.6 \times (10 \text{ rev}) \times (7.2 \text{ kWh/rev})}{15 \text{ sec}} \text{ kW}$$

$$D_i = 17.28 \text{ kW}$$

As T decrease, D_i approaches the actual instantaneous power value. Increasing T and number of revolutions produces an average value of power demand over the time interval.

Electric Demand Calculation Example 7-7

Lesson 7_et332b.pptx

33

End Lesson 7: Power and Energy Measurement

ET 332b Ac Motors, Generators and Power Systems

Lesson 7_et332b.pptx

34