 


LECTURE NOTES PART 8

ET 438B Sequential Control and Data
Acquisition


DESIGN EXAMPLE - DRAG STRIP "CHRISTMAS TREE"



A simplified starting timer is to be constructed for a drag strip. To enable the start timing for a race both cars must actuate sensor switches at the start line that indicate they are in position. When the cars are in position, the race judge receives a green light on his control panel and a green light comes on of the "Christmas Tree". He then presses a race initial button on his control panel. The Christmas tree times through the sequence shown at left.

DESIGN EXAMPLE - DRAG STRIP "CHRISTMAS TREE"

When the lower pair of green lamps come on the racers begin. A pair of photo eyes located at the finish line indicate the winner by lighting a blue light for a winner and a amber light for a loser. after the race results are indicated, the judge can press a reset button to prepare the system for the next race

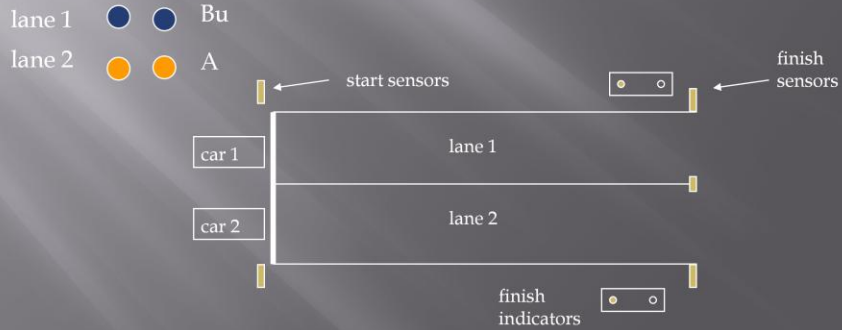

et438b-8.pptx

3

DESIGN EXAMPLE - DRAG STRIP "CHRISTMAS TREE"

Design Problem

- 1.) Identify the states, conditions and actions for this system
- 2.) Construct a flow chart of the logic for this system
- 3.) Construct a state transition diagram for this system
- 4.) Design a ladder logic system to implement these functions

Part 1: States, Conditions, Actions

States

- S0 : reset
- S1: cars at start line
- S2: 1st set red lamps on
- S3: 2nd set red lamps on
- S4: 3rd set red lamps on
- S5: Green lamps on (race start)
- S6: Lane 1 Wins
- S7: Lane 2 Wins

DESIGN EXAMPLE - DRAG STRIP "CHRISTMAS TREE"

Define conditions (Inputs)

Conditions

- I0: reset pressed
- I1: racer 1 positioned
- I2: racer 2 positioned
- I3: race timing initiated
- I4: 1st set red lamps timed out
- I5: 2nd set red lamps timed out
- I6: 3rd set red lamps timed out
- I7: lane 1 finish photo eye tripped
- I8: lane 2 finish photo eye tripped
- I9: start pressed


DESIGN EXAMPLE - DRAG STRIP "CHRISTMAS TREE"

Define actions (Outputs)

Actions


- O0: light green ready lamp
- O1: light red lamps set 1
- O2: light red lamp set 2
- O3: light red lamp set 3
- O4: light green lamp set
- O5: light blue lamp 1 if lane 1 wins
- O6: light blue lamp 2 if lane 2 wins
- O7: light amber lamp 1 if lane 1 loses
- O8: light amber lamp 2 if lane 2 loses

Part 2 Flow chart

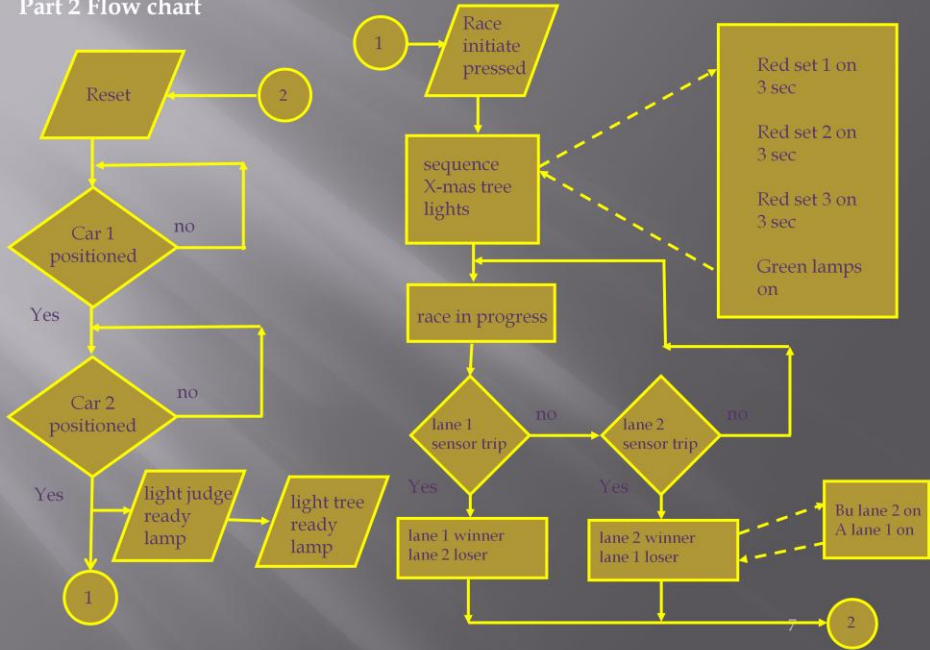

et438b-8.pptx


Example State Transition Diagram

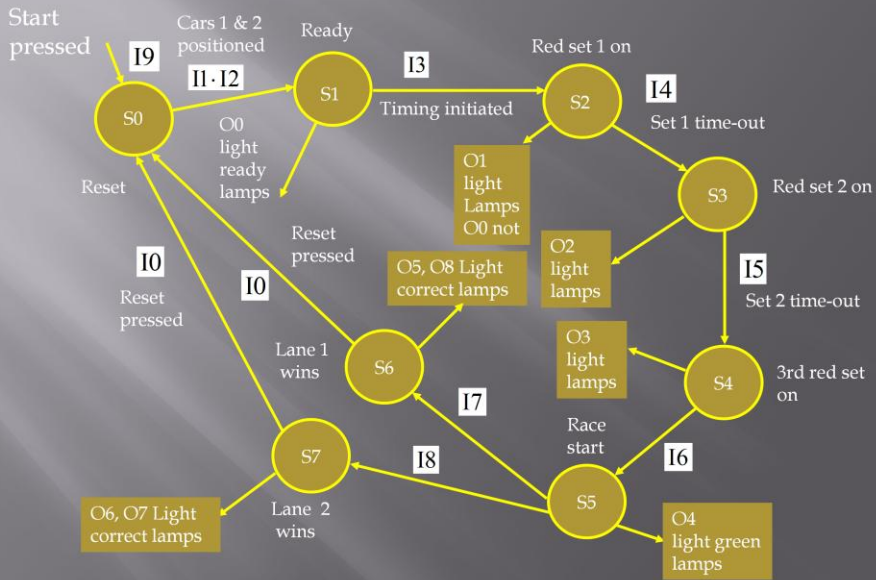

et438b-8.pptx

8

Construct State Equations

 

State 0

$$S0^{+1} = (S0 + I0 \cdot (S6 + S7) + I9) \cdot (\overline{I1} \cdot \overline{I2} \cdot S0)$$

$$S0^{+1} = (S0 + I0 \cdot (S6 + S7) + I9) \cdot (\overline{I1} + \overline{I2} + \overline{S0})$$

DeMorgans

Expand and Simplify

$$S0^{+1} = S0 \cdot \overline{I1} + S0 \cdot \overline{I2} + S0 \cdot \overline{S0} + (I0 \cdot (S6 + S7) + I9) \cdot \overline{I1} + (I0 \cdot (S6 + S7) + I9) \cdot \overline{I2} + (I0 \cdot (S6 + S7) + I9) \cdot \overline{S0}$$

Factor

$$S0^{+1} = S0 \cdot (\overline{I1} + \overline{I2}) + I9 \cdot (\overline{I1} + \overline{I2}) + I0 \cdot (S6 + S7) \cdot (\overline{I1} + \overline{I2}) + I0 \cdot (S6 + S7) \cdot \overline{S0} + I9 \cdot \overline{S0}$$

Regroup

$$S0^{+1} = S0 \cdot (\overline{I1} + \overline{I2}) + [I0 \cdot (S6 + S7) + I9] \cdot (\overline{I1} + \overline{I2}) + [I0 \cdot (S6 + S7) + I9] \cdot \overline{S0}$$

Construct State Equations

State 0 continued

Factor

$$S0^{+1} = [S0 \cdot (\bar{I1} + \bar{I2}) + (I0 \cdot (S6 + S7) + I9)](\bar{I1} + \bar{I2})[(\bar{I1} + \bar{I2}) + \bar{S0}]$$

Simplify & Regroup


$$S0^{+1} = (\bar{I1} + \bar{I2}) \cdot [S0 + (I0 \cdot (S6 + S7) + I9)] \cdot [1 + \bar{S0}]$$

$$S0^{+1} = (\bar{I1} + \bar{I2}) \cdot [S0 + (I0 \cdot (S6 + S7) + I9)]$$

$$S0^{+1} = (S0 + I0 \cdot (S6 + S7) + I9)(\bar{I1} + \bar{I2}) \quad \text{Reduced Equation}$$

Construct Ladder Logic

$$S0^{+1} = (S0 + I0 \cdot (S6 + S7) + I9) \cdot (\bar{I1} + \bar{I2})$$

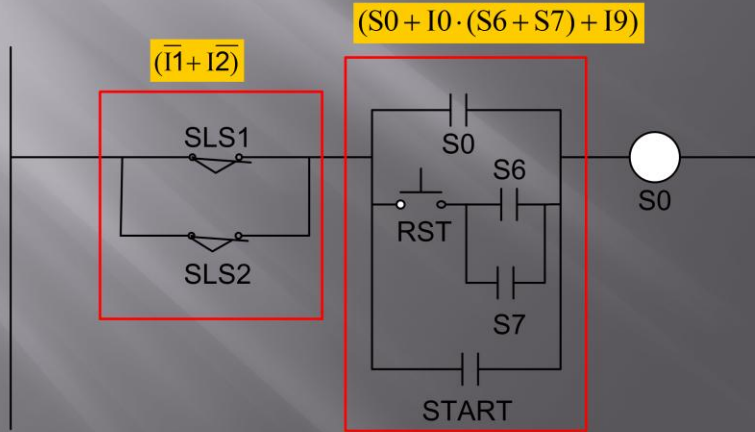

et438b-8.pptx

11

Construct State Equations



$$S1^{+1} = (S1 + I1 \cdot I2 \cdot S0) \cdot (\overline{I3} \cdot \overline{S1})$$

$$S1^{+1} = (S1 + I1 \cdot I2 \cdot S0) \cdot (\overline{I3} + \overline{S1})$$

$$S1^{+1} = S1 \cdot \overline{I3} + S1 \cdot \overline{S1} + I1 \cdot I2 \cdot S0 \cdot \overline{I3} + I1 \cdot I2 \cdot S0 \cdot \overline{S1}$$

$$S1^{+1} = S1 \cdot (\overline{I3}) + I1 \cdot I2 \cdot S0 \cdot (\overline{I3} + \overline{S1})$$

$$S1^{+1} = S1 \cdot (\overline{I3}) + I1 \cdot I2 \cdot S0 \cdot (\overline{I3}) \cdot I0 \cdot I1 \cdot I2 \cdot S0 + I1 \cdot I2 \cdot S0 \cdot \overline{S1}$$

$$S1^{+1} = S1 \cdot (\overline{I3}) + (\overline{I3})(1 + \overline{S1}) \cdot I1 \cdot I2 \cdot S0$$

$$S1^{+1} = S1 \cdot (\overline{I3}) + (\overline{I3}) \cdot I1 \cdot I2 \cdot S0$$


$$S1^{+1} = (S1 + I1 \cdot I2 \cdot S0)(\overline{I3})$$

Construct Ladder Logic


$$S1^{+1} = (S1 + I1 \cdot I2 \cdot S0)(\bar{I3})$$

State 1 Output Equation

$$O0 = S1$$

 

Construct State Equations

 

State 2

$$S2^{+1} = (S2 + I3) \cdot (\overline{I4})$$

TON#(c,t)=On-delay timer #
c = input condition
t = time delay

so

$$I4 = \text{TON1}(S2,3) = \text{timer done}$$

$$S2^{+1} = (S2 + I3) \cdot (\overline{\text{TON1}(S2,3)})$$

$$S2^{+1} = (S2 + I3) \cdot (\overline{\text{TON1}(S2,3)})$$

State 2 Output Equation **O1 = S2**

State 3

$$S3^{+1} = (S3 + I4 \cdot S2) \cdot (\overline{I5})$$

$$I5 = \text{TON2}(S3,3) = \text{timer done}$$


$$S3^{+1} = (S3 + \text{TON1}(S2,3) \cdot S2) \cdot (\overline{\text{TON2}(S3,3)})$$

State 3 Output Equation **O2 = S3**

et438b-8.pptx

14

Construct State Equations

 

State 4


$$S4^{+1} = (S4 + I6 \cdot S3) \cdot \overline{(I6)}$$

$$I6 = \text{TON3}(S4,3) = \text{timer done}$$

$$S4^{+1} = (S4 + \text{TON2}(S3,3) \cdot S3) \cdot \overline{(\text{TON3}(S4,3))}$$

State 4 Output Equation **O3 = S4**

State 5

 

$$S5^{+1} = (S5 + I6 \cdot S4) \cdot \overline{((I8 + I9))}$$

$$I6 = \text{TON3}(S4,3) = \text{timer done}$$

$$S5^{+1} = (S5 + \text{TON3}(S4,3) \cdot S4) \cdot \overline{((I7 + I8))}$$

et438b-8.pptx

15


Construct State Equations

State 5 simplification

$$S5^{+1} = (S5 + \text{TON3}(S4,3) \cdot S4) \cdot ((\overline{I7} + \overline{I8}))$$


$$S5^{+1} = (S5 + \text{TON3}(S4,3) \cdot S4) \cdot (\overline{I7} \cdot \overline{I8})$$

State 5 Output Equation $O4 = S5$

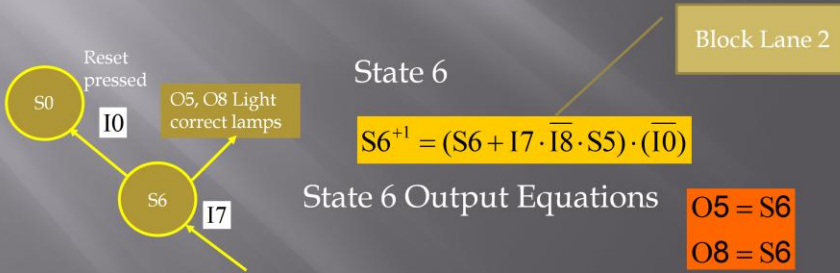

Construct State Equations

State 7

 

$$S7^{+1} = (S7 + \overline{I7} \cdot I8 \cdot S5) \cdot (\overline{I0})$$

Block Lane 1

State 7 Output Equations


$$O6 = S7$$

$$O7 = S7$$

Construct Ladder Logic

State 6

 
$$S6^{+1} = (S6 + I7 \cdot \bar{I8} \cdot S5) \cdot (\bar{I0})$$




Construct Ladder Logic

State 7
 
$$S7^{+1} = (S7 + \overline{I7} \cdot I8 \cdot S5) \cdot (\overline{I0})$$




Complete System

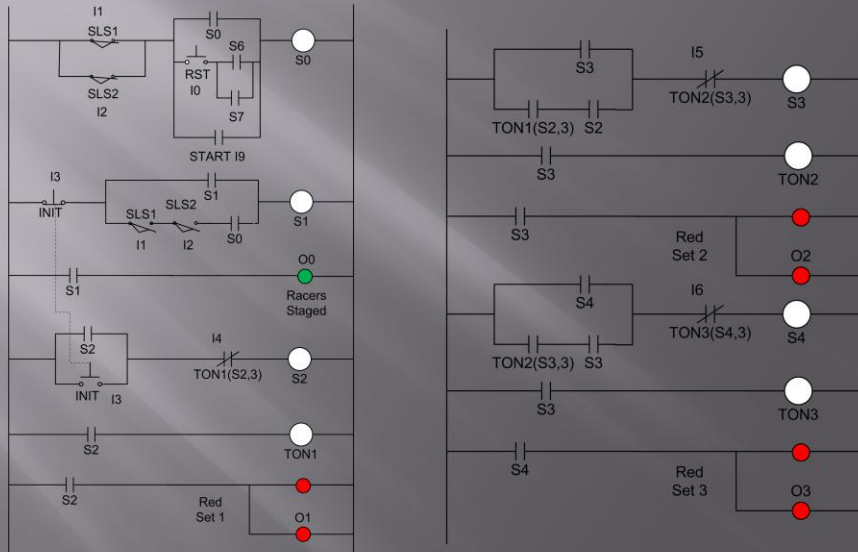

et438b-8.pptx

20

Complete System

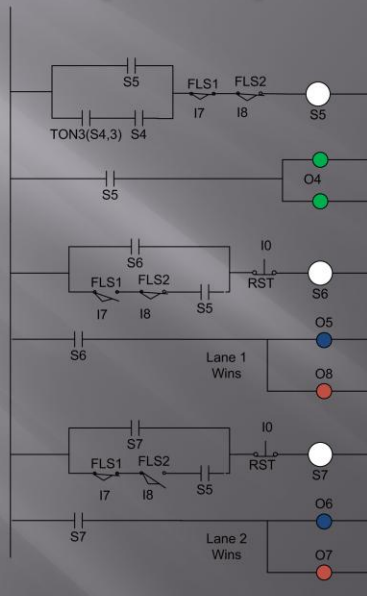

et438b-8.pptx

21

Design Considerations

Personnel and Equipment Safety

Fail-safe operation - component fail results in little or no damage or inconvenience

Common Practice

- 1.) start sequence by closing NO contacts
- 2.) stop a sequence by opening NC contact

Practice Results: if device fails to start process stops,
If started would stop **Example: Motor starter**

Troubleshooting Tips

Common causes of Failure

- 1.) Dirty or oxidized contacts
- 2.) Broken wire or loose connection
- 3.) Up stream power source interrupted causing input device to de-activate

Other Issues

Contact operation sequence

break-before-make standard


See previous example limit switches

Programmable Logic Controllers (PLC)

Microprocessor-based controller that implements ladder logic through software and hardware interface.

Definition of PLC

Digital apparatus using programmable memory and stored programs for implementing **Logic Timing Sequencing Counting**

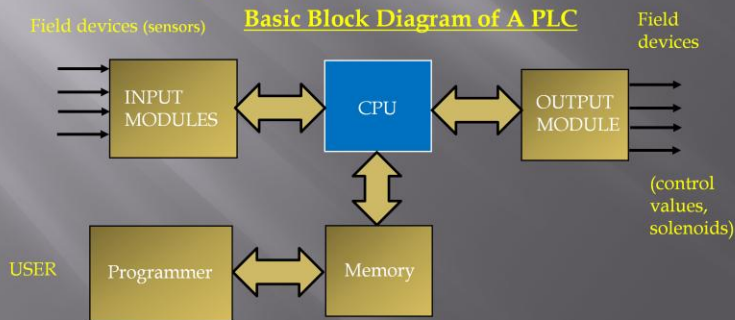

et438b-8.pptx

24

PLC Operation in Run Mode

1. Scan all Inputs

Detect change in status of field devices (Limit switches Pressure switches, etc.)



2. Execute control program based on user logic design



3. Test output status against program values.



4. Update output to fit changes dictated by input change



Time from 1 to 4 called scan time. Can be important in programs

Typical PLC Input/Output Modules

PLC I/O designed to connect to industrial devices



I/O grouped on cards with 8, 16, 24, 32 inputs



Dry contacts (standard switches)

motor contactors

Pressure, temperature, limit, flow switches

Solid state sensors (electronic)

proximity switches, photo eyes etc.

Voltage levels 24 - 240 Vac 24-240 Vdc


TTL levels, Sourcing and sinking I/O

1 set terminals
(com, n) = 1 I/O
point

PLC I/O Interfacing

PLC's use memory mapped I/O

 PLC uses microprocessors with 8-16 bit words. Each I/O point identified by location in memory. Terminals have unique addresses represented by decimal, octal or binary number. (commonly decimal)



PLC I/O Interfacing

For expandable PLCs



Level 2: Slot identifier (type of I/O card)

Level 1: Rack or chassis identifier

Non-expandable PLCs use fixed addressing: All slot 0



Level 3: I/O point. Type of point and terminal number

I/O Status Table

1	0	0	0	1	1	0	0	1	0	1	0	1	0	0	0	Word 1
																Word 2
																Word 3
																Word 4
																Word 5
																Word 6

et438b-8.pptx

28

PLC I/O Interfacing

Addressing of I/O cards (Allen-Bradley (A-B))

A-B uses decimal expandable addressing for most PLCs



Addressing Specific I/O points (Allen-Bradley)



For fixed PLC designs, all I/O addressed to slot 0

PLC I/O Interfacing

I/O Addressing Examples

<u>Function</u>	<u>Chassis Slot</u>	<u>Terminal #</u>	<u>Address</u>
input	1	4	I:1/4
output	2	13	O:2/13
input	3	2	I:3/2
input	4	4	I:4/4

Note: Decimal addressing used above

Other PLC data types:

Bit data, unsigned integer, signed integer, BCD
(binary coded decimal 0-9 binary)

Input Modules

Sequential control uses discrete (binary) inputs (on/off) from field devices (switches sensors, etc.)

Typical Type of Input Modules


Ac

24, 48, 120, 240 V
120, 240 V isolated
24 Vac/dc

Dc

24, 48, 1-60 120 Vdc
sink/source 5-50 Vdc
5 V TTL
5/12 V TTL

 Input module considered load of field device (switch)



Input Module Specifications

Pages:

Voltage	Inputs	Points per Common	Backplane Current Draw at 5 VDC	Maximum Signal Delay	Maximum Off-State Current	Input Current Nominal	Maximum Inrush Current
85 to 132 VAC	4	4	0.035 Amps	ON = 35ms OFF = 45ms	2mA	12mA at 120 VAC	0.8A
	8	8	0.050 Amps	ON = 35ms OFF = 45ms	2mA	12mA at 120 VAC	0.8A
	16	16	0.085 Amps	ON = 35ms OFF = 45ms	2mA	12mA at 120 VAC	0.8A
170 to 265 VAC	4	4	0.035 Amps	ON = 35ms OFF = 45ms	2mA	12mA at 240 VAC	1.6A
	8	8	0.050 Amps	ON = 35ms OFF = 45ms	2mA	12mA at 240 VAC	1.6A
	16	16	0.085 Amps	ON = 35ms OFF = 45ms	2mA	12mA at 240 VAC	1.6A

Figure 4-7 AC input module specifications for Allen-Bradley SLC 500 120 VAC and 240 VAC input modules. (Compiled from Allen-Bradley Discrete I/O modules data.)

Explanation of Specifications

Backplane draw current - module current drawn by electronics

Maximum signal delay - time required for PLC to sense change in field device and store it in memory


Maximum off state current - max current that can flow so that input remains in off state. (leakage I from solid state sensors)

Nominal input current - current drawn by the input point with nominal voltage applied

Input Module Specifications


Additional Specifications

 - Voltage Drop
- Leakage Current
- Load Current
- Power-up Delay




Useful when applying active (solid-state) switches and proximity sensors

Leakage Current

 

Voltage Drop

 


et438b-8.pptx

33

Inputs with Solid State Sensors

When solid-state 2-wire sensor is used with switch, sensor will be inactive until circuit is completed

Power-up Delay

 


Dealing with power up delay - add parallel resistor.

Must allow enough current to activate sensor but not turn on input module

Inputs with Solid State Sensors

 Dealing with power up delay - add parallel resistor.



Example: size $R \ V_s = 115 \text{ Vac}$
 $I_L = 1.7 \text{ mA}$


$$R = 115 \text{ V} / 1.7 \text{ mA}$$

$$R = 67.647 \text{ k}\Omega$$

Inputs with Solid State Sensors

Minimum load current-lowest I value that keeps the sensor active

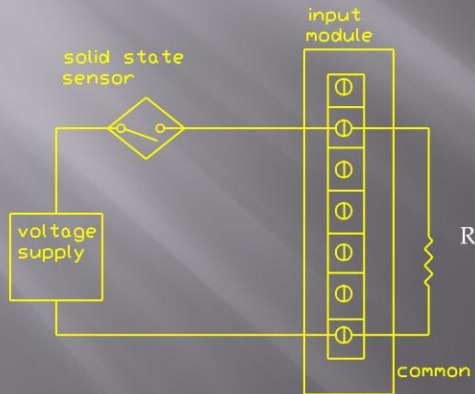May need to parallel a resistor with the input card if it has a high impedance input or sensor needs more current than card can handle without turning on the input



R called bleeder resistor.
Usually sized according to
manufacturer charts

Based on concept of
current division

et438b-8.pptx

36