

A/D Homework

Refer to the attached diagram of a counter-type A/D converter for the following questions. The latch and counter control logic tables are:

| Counter | |
|---------|--------|
| RST | Output |
| H | count |
| L | 0 |

| Latch Control | | |
|---------------|---|----------------|
| ENB | D | Q |
| H | H | H |
| H | L | L |
| L | x | Q ₀ |

The DAC is a DAC0800.

- 1.) What logic level must the enable lead take for the converter to function (H, L) _____

- 2.) The LED lights when the A/D converter is making the conversion (Yes, No) _____

- 3.) Compute the reference current for the DAC _____

- 4.) If the value of $V_{in} = 3.594$ Vdc, how many clock cycles are required to make the conversion. (Hint: compute the voltage value of the LSB of the DAC) SHOW ALL CALCULATIONS.

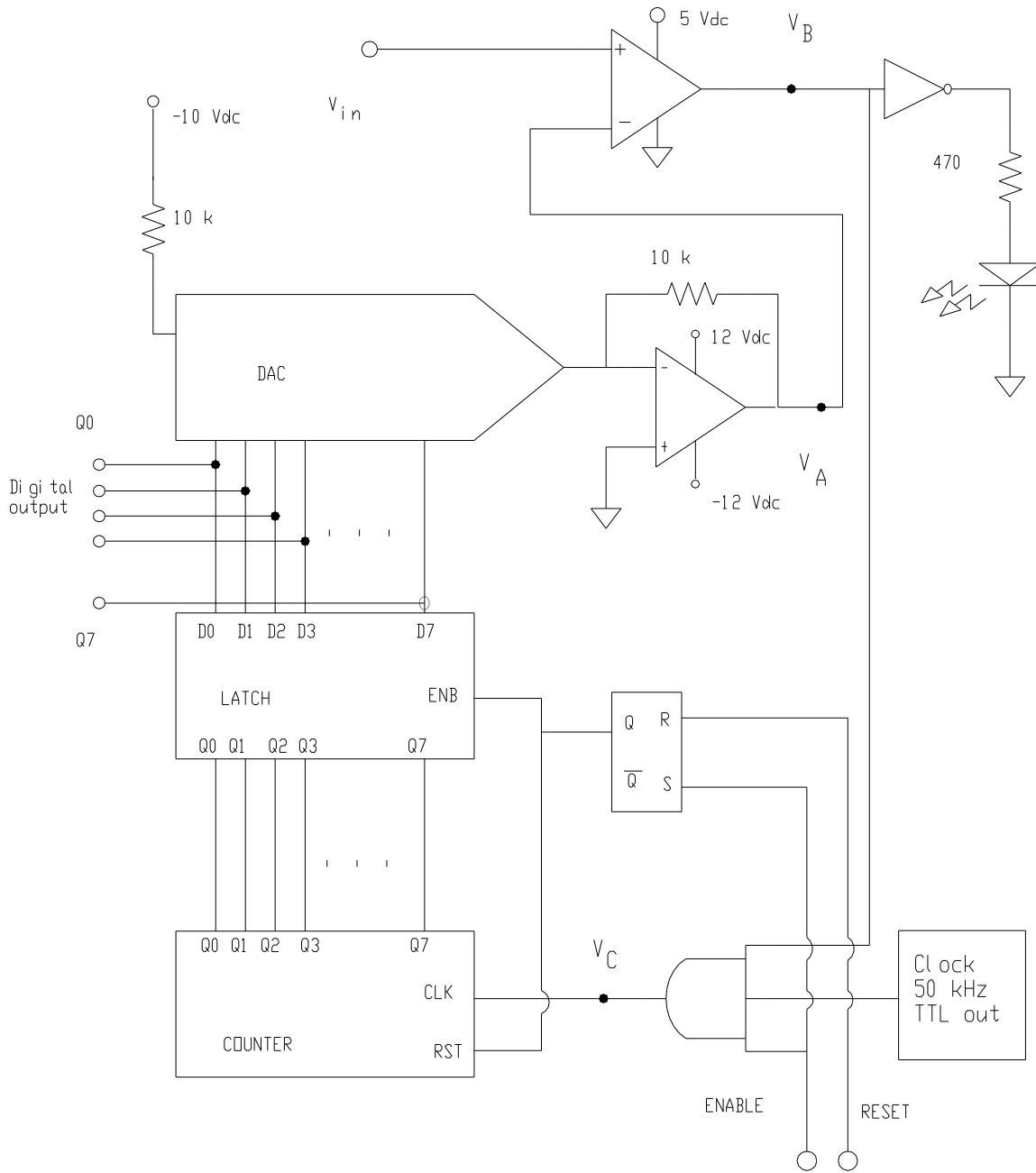


Figure 1. Analog-to-digital Converter.