

ET 438b
Binary-Weighted Resistor DAC

For the DAC shown at the left,
the values of resistors are:

$$R_1 = 20 \text{ k}\Omega$$

$$R_2 = 10 \text{ k}\Omega$$

$$R_3 = 5.0 \text{ k}\Omega$$

$$R_4 = 2.5 \text{ k}\Omega$$

The value for V_{ref} is 0.5 Vdc.


For a digital input of:

$$D_1 = 1$$

$$D_2 = 1$$

$$D_3 = 1$$

$$D_4 = 1$$

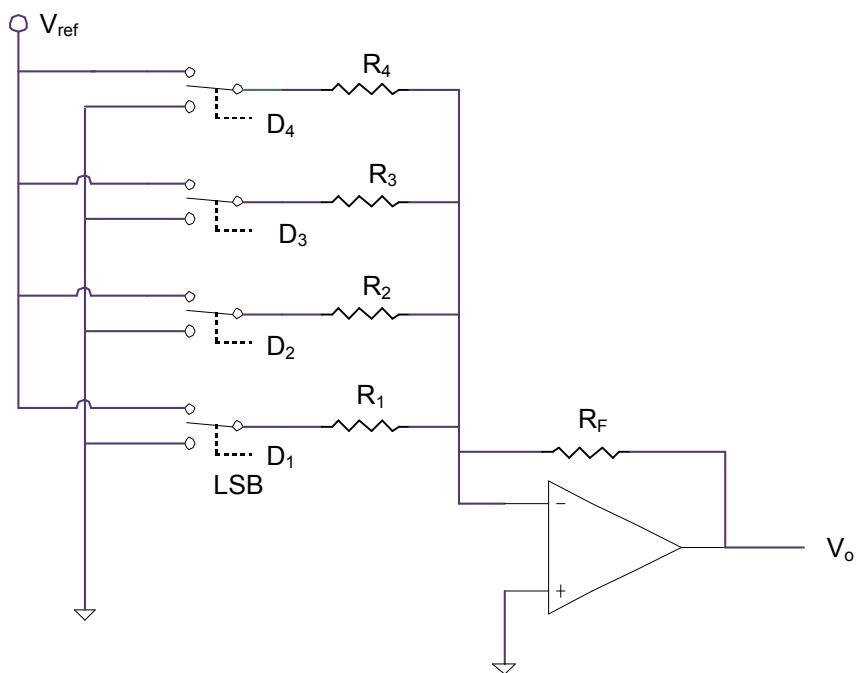

- 1.) Find the value of R_F that gives an output voltage of -10 Vdc.

- 2.) What is the voltage value of the DAC output with only the least significant bit in the logic 1 position?
- 3.) Calculate the resolution of the DAC above.