

ET438B
Window Comparator Homework

For the comparator circuit shown below,

- 1.) Determine the input/output curves for the outputs, V_{o1} and V_{o2} . Label the trip voltages on the curves.
- 2.) Determine what logic function will give a high output only when the input voltage V_{in} is between the upper and lower trip values.

