

3. The zero-based linearity line extends in both directions from the point where $i_N = 0$ mA and $R_s = 120 \Omega$. The line is positioned such that it is an equal distance from i_N at each extremity. We will use L_N for the y-coordinate of the zero-based line. The magnitude of L_N at each extremity is determined by averaging the magnitude of i_N at each extremity.

When $R_s = 140$, $L_N = (17.544 + 18.182)/2 = 17.863$ mA

When $R_s = 100$, $L_N = -17.863$ mA


The equation of the zero-based linearity line is determined by the following two points:

$$\begin{aligned} R_s = 120 \Omega & \quad L_N = 0.0 \text{ mA} \\ R_s = 140 \Omega & \quad L_N = 17.863 \text{ mA} \end{aligned}$$

Zero-based linearity line $L_N = 0.89315R_s - 107.178$

The values of L_N , $L_N - i_N$, and the percentage of difference are in the last three columns of the table below.

T (°C)	R_s (Ω)	i_N (mA)	L_N (mA)	$L_N - i_N$	% Diff.
0	100	-18.182	-17.863	0.319	0.89
25	110	-9.009	-8.931	0.078	0.22
50	120	0.000	0.000	0.000	0.00
75	130	8.850	8.931	0.081	0.23
100	140	17.544	17.863	0.319	0.89

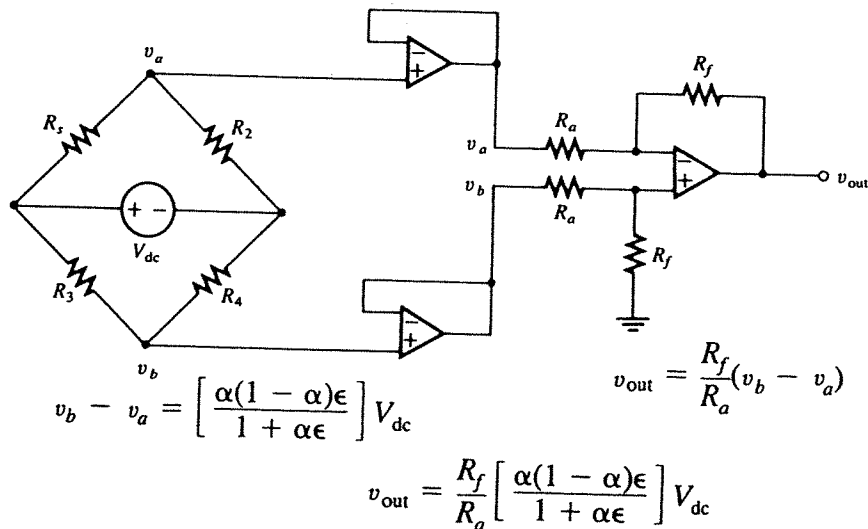

◆ **Figure 6.17** Unbalanced Wheatstone bridge and instrumentation amplifier circuit. The purpose of the circuit is to produce an output voltage that is proportional to the difference between R_3 and R_{bal} .