

ET 438 b Digital Control and Data Acquisition  
Department of Technology

## Lesson 12: Analog Signal Conditioning

Lesson 12\_et438b.pptx

1

## Learning Objectives

After this presentation you will be able to:


- Design a voltage-to-current interface for a transducer and simulate its operation using commonly available software
- List the modes of operation of a Wheatstone bridge circuit
- Explain how Wheatstone bridge resistor values effect linearity and sensitivity
- Design a signal conditioning circuit for a Wheatstone bridge.

Lesson 12\_et438b.pptx

2
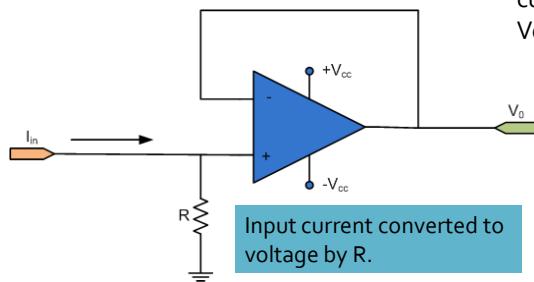
# Analog-to-Analog Conversion Signal Conditioning

Current-to-Voltage Converter  
I-to-V Converter



Since  $V^+ = V^-$

$$V_o = I_{in} \cdot R$$

**Example:** Find a value the value of R that converts a 4 mA to 20 mA current signal into a 1 – 5 V output Voltage.

$$V_o = I_{in} \cdot R \Rightarrow R = \frac{V_o}{I_{in}}$$

$$V_o = 1 \text{ V} @ I_{in} = 4 \text{ mA}$$

$$R = \frac{1 \text{ V}}{4 \text{ mA}} = 250 \Omega$$

Check output at 20 mA


$$V_o = 250 \Omega \cdot (20 \text{ mA}) = 5 \text{ V}$$

Lesson 12\_et438b.pptx

3
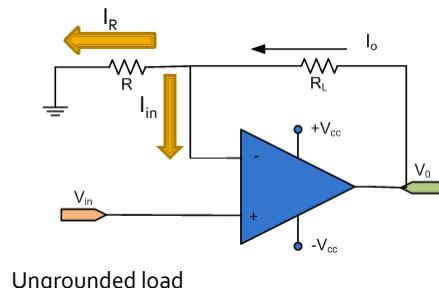
# Signal Conditioning

Voltage-to-Current Converter  
V-to-I Converter (Transconductance Amps)



$$V^+ = V^- = V_{in} \text{ and } I_{in} = 0$$

$$\text{So } I_o - I_R = 0 \text{ or } I_o = I_R$$

$$I_o = I_R = \frac{V^-}{R} \text{ but } V^- = V^+ = V_{in}$$

$$I_o = \frac{V_{in}}{R}$$


Note:  $R_L < R$  for practical circuit operation. OP AMP output voltage determines magnitude of  $R_L$  for constant current

Lesson 12\_et438b.pptx

4
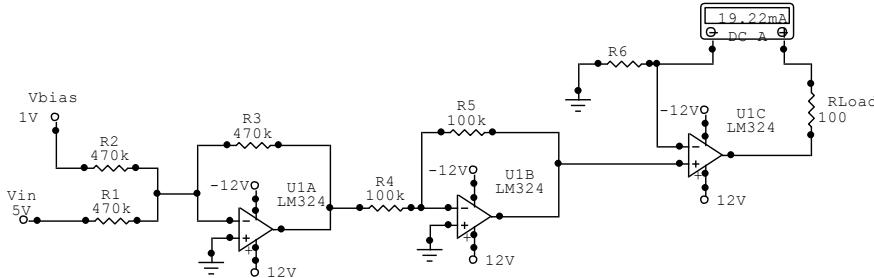
## Signal Conditioning Example

Convert a 0-5 V dc voltage signal to a 4-20 mA current signal using OP AMP circuits.



Determine the ratio of spans

$$R_6 = \frac{V_{in}}{I_0} = \frac{V_{in(max)} - V_{in(min)}}{I_{0max} - I_{0min}} = \frac{5\text{ V} - 0\text{ V}}{20\text{ mA} - 4\text{ mA}} = \frac{5\text{ V}}{16\text{ mA}} = 312.5\Omega$$

## Signal Conditioning Example

Compute the value of  $V_{bias}$  to give the value of minimum output current

Check the output with  
 $V_{in} = 5\text{ V}$

What is max value of  $R_L$ ?  
Assume  $V_{sat} = 10.5\text{ V}$

$$\begin{aligned} I_{0min} &= 4\text{ mA} \\ I_0 &= \frac{V_{in}}{R} \Rightarrow I_0 \cdot R = V_{in} \\ V_{bias} &= I_{0min} \cdot R \\ R &= 312.5\Omega \\ V_{bias} &= (4\text{ mA}) \cdot (312.5\Omega) \\ V_{bias} &= 1.25\text{ V} \end{aligned}$$


$$\begin{aligned} I_0 &= \frac{V_{in}}{R} \\ V_{max} &= V_{in(max)} + V_{bias} \\ V_{max} &= 5\text{ V} + 1.25\text{ V} \\ I_0 &= \frac{6.25\text{ V}}{312.5\Omega} \\ I_0 &= 0.02\text{ A} = 20\text{ mA} \end{aligned}$$

$$\begin{aligned} R_{L(max)} &= \frac{V_{sat} - V_{in(max)}}{I_{0max}} \\ V_{sat} &= 10.5\text{ V} \\ I_{0max} &= 0.020\text{ A} = 20\text{ mA} \\ V_{in(max)} &= 6.25\text{ V} \\ R_{L(max)} &= \frac{10.5\text{ V} - 6.25\text{ V}}{0.02\text{ A}} = 212.5\Omega \end{aligned}$$

Assumes OP AMP has sufficient current output

## Circuit Simulation of Example: Dc Sweep


Output Current Vs Input Voltage

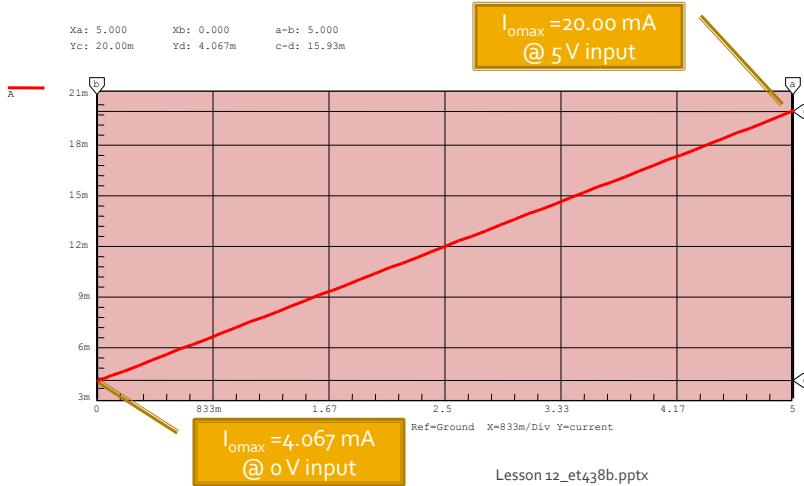

7

## Instrumentation Amps with High Impedance Input

Two-stage circuit

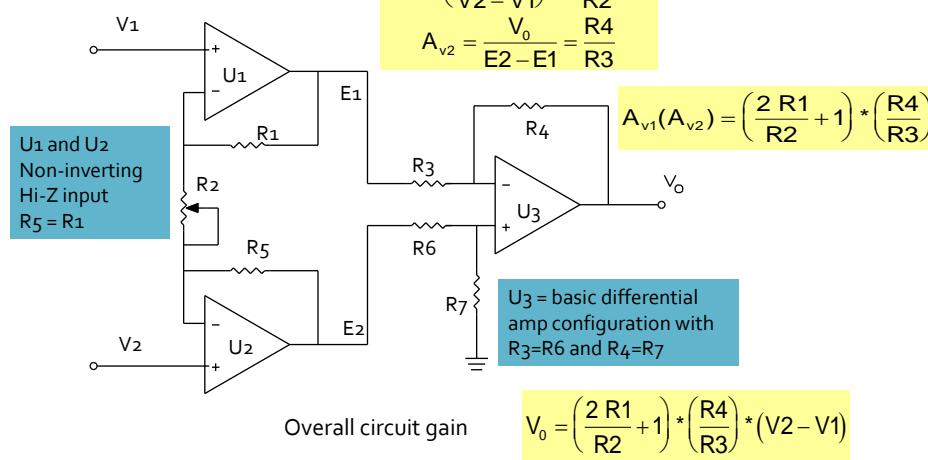


Lesson 12\_e438b.pptx

8
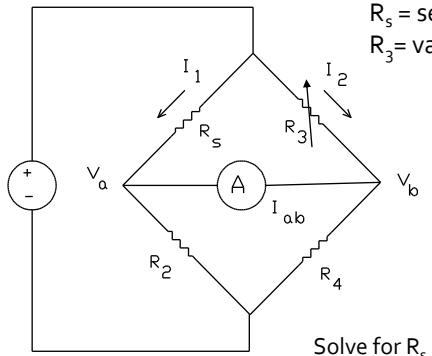
## Signal Conditioning-Bridge Circuits

**Dc bridges (Wheatstone bridges)** Used to detect small resistance changes in sensors. Typically used with sensors that measure force, temperature, and pressure.



$R_s$  = sensor R

$R_3$  = variable resistor used to balance bridge

When bridge is balanced:

$I_{ab} = 0$  since  $V_a = V_b$

so  $I_1 R_s = I_2 R_3$  and  $I_1 R_2 = I_2 R_4$

$$\frac{R_s}{R_2} = \frac{R_3}{R_4}$$

$$R_s = \frac{R_3 R_2}{R_4}$$

Adjust  $R_3$  until  $I_{ab} = 0$   
compute  $R_s$

Lesson 12\_et438b.pptx

9

## Bridge Use Methods

There are two operating modes for a dc bridge: balanced (null) and unbalanced

**Null Mode** - adjust  $R_3$  variable resistor until  $I_{ab} = 0$ . Need automatic nulling circuit for automatic operation.


**Unbalanced Mode** - insert sensor and null bridge for sensor measurement.  
When initial value of sensor changes measure difference in voltage. Bridge only balanced at one point

Lesson 12\_et438b.pptx

10
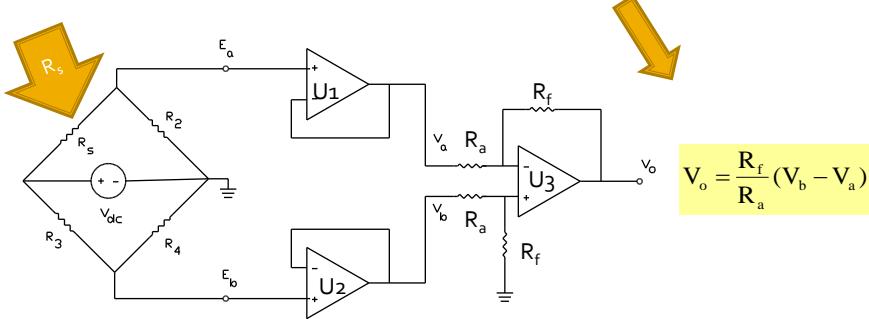
## Unbalanced Bridge Operation


Note the unbalanced bridge shown below.  $U_1$  and  $U_2$  provide high-Z input. Circuit gain provided by  $U_3$  using the following formula.



Find expression for bridge equation. in terms of the change in sensor resistance  $R_s$ .

## Unbalanced Bridge Analysis

Bridge Circuit

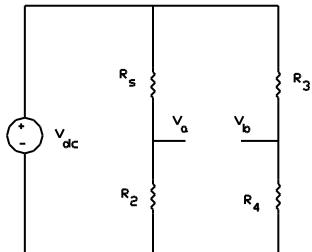

Find the voltage  $V_{ba}$  in terms of the resistors

$$V_a = \left( \frac{R_2}{R_s + R_2} \right) \cdot V_{dc}$$

$$V_b = \left( \frac{R_4}{R_3 + R_4} \right) \cdot V_{dc}$$

$$V_b - V_a = \left( \frac{R_4}{R_3 + R_4} - \frac{R_2}{R_s + R_2} \right) \cdot V_{dc}$$

Normalize  $V_{ba}$  by dividing by supply  $V$ .  
Find common denominator

$$R_{bal} = \frac{R_2 R_3}{R_4}$$

$$\frac{V_b - V_a}{V_{dc}} = \left( \frac{R_4}{R_3 + R_4} - \frac{R_2}{R_s + R_2} \right) = \frac{R_4(R_s + R_2) - R_2(R_3 + R_4)}{(R_3 + R_4)(R_s + R_2)}$$

# Unbalanced Bridge Analysis

Bridge Analysis (Continued)

Expand terms and simplify

$$\frac{V_b - V_a}{V_{dc}} = \frac{R_4 R_s + \cancel{R_4 R_2} - R_2 R_3 - \cancel{R_2 R_4}}{(R_3 + R_4)(R_s + R_2)} = \frac{R_4 R_s - R_2 R_3}{(R_3 + R_4)(R_s + R_2)}$$

From the previous balance equation

$$\frac{R_{bal} R_4}{R_3} = R_2$$

Substitute these equations into the above relationship

$$\frac{V_b - V_a}{V_{dc}} = \frac{R_4 R_s - R_{bal} R_4}{(R_3 + R_4)(R_s + R_{bal} R_4 / R_3)} \quad \leftarrow$$

$$(R_3 + R_4)(R_s + R_{bal} R_4 / R_3) = R_3 R_s + R_4 R_s + R_{bal} R_4 + R_{bal} R_4^2 / R_3$$

Lesson 12\_et438b.pptx

13

# Unbalanced Bridge Analysis

Bridge Analysis (Continued)

Combine the past two equations and clear  $R_3$  from the denominator.

$$\frac{V_b - V_a}{V_{dc}} = \frac{R_3 R_4 (R_s - R_{bal})}{R_3^2 R_s + R_3 R_4 R_s + R_3 R_4 R_{bal} + R_{bal} R_4^2}$$

Now let  $R_4 = R_3$  and simplify further

$$\frac{V_b - V_a}{V_{dc}} = \frac{R_3^2 (R_s - R_{bal})}{R_3^2 (2(R_s + R_{bal}))} = \frac{R_3^2 (R_s - R_{bal})}{R_3^2 R_s + R_3^2 R_s + R_3^2 R_{bal} + R_{bal} R_3^2}$$

$$\frac{V_b - V_a}{V_{dc}} = \frac{R_3^2 (R_s - R_{bal})}{2R_3^2 R_s + 2R_3^2 R_{bal}} = \frac{R_3^2 (R_s - R_{bal})}{R_3^2 (2(R_s + R_{bal}))}$$

$$\frac{V_b - V_a}{V_{dc}} = \frac{(R_s - R_{bal})}{2(R_s + R_{bal})} \quad \leftarrow \text{Desired Relationship}$$

Lesson 12\_et438b.pptx


14

## Unbalanced Bridge Analysis

Equation below relates the output voltage change (per volt of supply V) to the change in sensor resistance.

$$\frac{V_b - V_a}{V_{dc}} = \frac{(R_s - R_{bal})}{2(R_s + R_{bal})} \quad \text{When } R_3 = R_4$$

Original Bridge

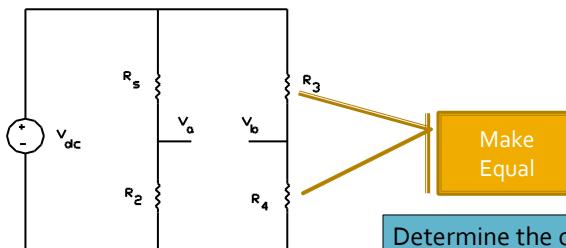

Determine the output voltage linearity compared to the sensor resistance change.

Lesson 12\_et438b.pptx

15

## Bridge Output Linearity Analysis

**Example:** An unbalanced bridge circuit converts temperature sensor resistance into a differential voltage that is amplified by a instrumentation amplifier. The temperature sensor has a resistance of 120 ohms at 35 C and a resistance range of 90 to 150 ohms.


- 1.) Design a dc bridge circuit with a 10 V supply that will give zero output at 35 C.
  - a.) Using  $R_3 = R_4 = 1000$  ohms
  - b.) Using  $R_3 = 120$ ,  $R_4 = 1000$  ohms
- 2.) Plot the output voltage over the range of operation at 5 ohm increments for both designs a.)  $R_3 = R_4 = 1000$  ohms b.)  $R_3 = 120$  and  $R_4 = 1000$  ohms
- 3.) Find the zero based linear approximation of the bridge output responses.
- 4.) Determine the maximum non-linearity for each case
- 5.) Determine the gain required for the instrumentation amplifier gain if a span of 15 V dc is required.

Lesson 12\_et438b.pptx

16

## Bridge Output Linearity Analysis

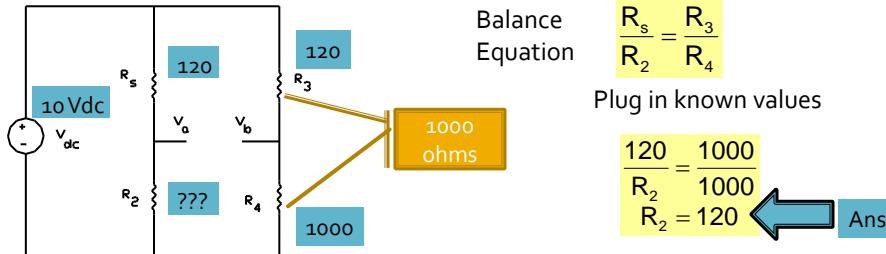**Example Solution (Part 1a)** Balance bridge with  $R_3 = R_4 = 1000$  ohms



**Example Solution (Part 1b)** Balance bridge with  $R_3 = 120$  ohms  $R_4 = 1000$  ohms

$$\frac{R_s}{R_2} = \frac{R_3}{R_4}$$

$$\frac{120}{R_2} = \frac{120}{1000}$$

$$R_2 = 1000$$

Ans

Lesson 12\_et438b.pptx

17

## Bridge Output Linearity Analysis

**Example Solution (Part 2a)** plot output V with  $R_3 = R_4 = 1000$  ohms

$$V_b - V_a = \frac{(R_s - R_{bal})}{2(R_s + R_{bal})} V_{dc}$$

$$R_{bal} = \frac{R_2 R_4}{R_3} = \frac{120(1000)}{1000} = 120$$

$$R_{bal} = 120$$

Plot values of  $R_s$  from 90 to 150 with Excel or MathCAD using the equation below

$$V_d = V_b - V_a = \frac{(R_s - 120)}{2(R_s + 120)} 10$$

Sample calculation  
 $R_s = 90$  ohms

$$V_d = \left[ \frac{(90\Omega - 120\Omega)}{2(90\Omega + 120\Omega)} \right] \cdot 10V$$


$$V_d = -0.714V$$

Lesson 12\_et438b.pptx

18

## Output Plot $R_3=R_4=1000$ Ohms

$r_s =$	$V_d(r_s) =$
90	-0.714
95	-0.581
100	-0.455
105	-0.333
110	-0.217
115	-0.106
120	0
125	0.102
130	0.2
135	0.294
140	0.385
145	0.472
150	0.556

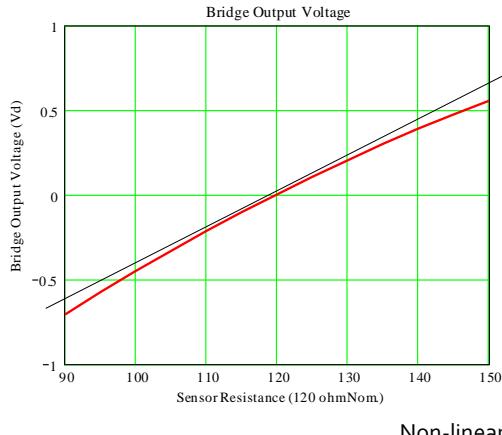

Non-linear output

Lesson 12\_et438b.pptx

19

## Linearity With $R_3 \neq R_4$

Example Solution (Part 2b) plot output V with  $R_3=120$   $R_4=1000$  ohms

Use the alternative formula written as function of  $r_s$ , sensor resistance

$$V_{d1}(r_s) = \left[ \frac{R_4(r_s - R_{bal})}{(R_3 + R_4) \left( r_s + \frac{R_{bal} \cdot R_4}{R_3} \right)} \right] \cdot V_{dc}$$

$$\text{Where } R_{bal} = \frac{R_2 \cdot R_3}{R_4} = \frac{(1000\Omega)(120\Omega)}{1000\Omega} = 120\Omega$$

$$\begin{aligned} \text{Substitute Values } V_d(r_s) &:= \frac{(1000\Omega) \cdot (r_s - 120\Omega) \cdot 10V}{(1120\Omega) \cdot (r_s + 1000\Omega)} \\ &\quad V_{d1} = \frac{(1000\Omega) \cdot (90\Omega - 120\Omega) \cdot 10V}{(1120\Omega) \cdot (90\Omega + 1000\Omega)} \end{aligned}$$

Sample Calculation


$$V_{d1} = -0.246V$$

Lesson 12\_et438b.pptx

20

## Output Plot $R_3 = 120$ and $R_4 = 1000$ Ohms

$V_{d1}(r_s) =$	$r_s =$
-0.246 V	90 Ω
-0.204	95
-0.162	100
-0.121	105
-0.08	110
-0.04	115
0	120
0.04	125
0.079	130
0.118	135
0.157	140
0.195	145
0.233	150

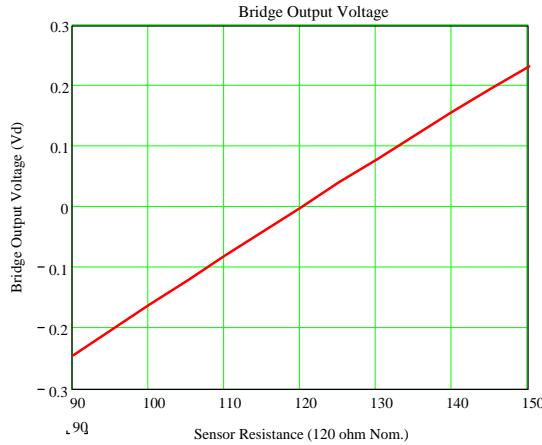

Less output voltage than first case

## Linear Approximations

**Example Solution (Part 3)** Find zero based linear approximation. Assume line passes through zero and the average of the end points

For bridge with  $R_3=R_4=1000$  ohms

$$\begin{aligned} \text{at } R_s = 90 \quad V_d = -0.714 \\ \text{at } R_s = 150 \quad V_d = 0.556 \end{aligned}$$

$$\text{Average max value } (|-0.714| + |0.556|)/2 = 0.635$$

$$\begin{aligned} \text{Use two data points: } & R_{s1}=120 \quad V_{d1}=0 \\ & R_{s2}=150 \quad V_{d2}=V_{\text{ave}}=0.635 \end{aligned}$$

Use two-point form of line to find equation


$$\begin{aligned} (V_d - V_{d1}) &= \frac{(V_{d2} - V_{d1})}{(R_{s2} - R_{s1})} (r_s - R_{s1}) \\ (V_d - 0) &= \frac{(0.635 - 0)}{(150 - 120)} (r_s - 120) \\ V_d &= 0.021167 r_s - 2.54 \end{aligned}$$

Equation
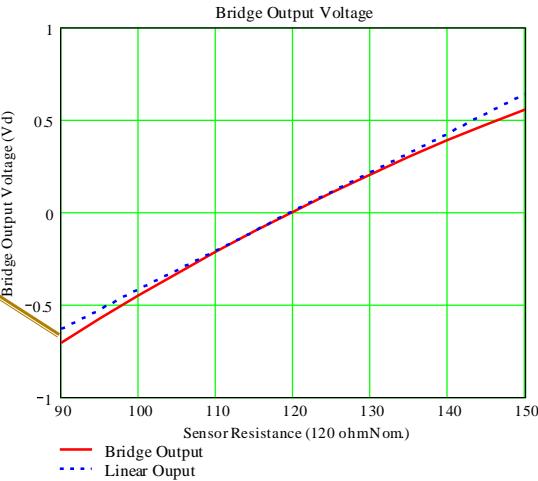
# Linear Approximations

For bridge with  
 $R_3=R_4=1000$  ohms

Non-linearity  
Increase as  
 $R_s$  moves from  
balance point



Lesson 12\_et438b.pptx


23

# Linear Approximations

For bridge with  $R_3=120$ ,  $R_4=1000$  ohms

$$\begin{aligned} \text{at } R_{s1} = 90 & \quad V_{d1} = -0.246 \\ \text{at } R_{s2} = 150 & \quad V_{d2} = 0.233 \end{aligned}$$

$$\text{Average max value } (|-0.246| + |0.233|)/2 = 0.2395$$

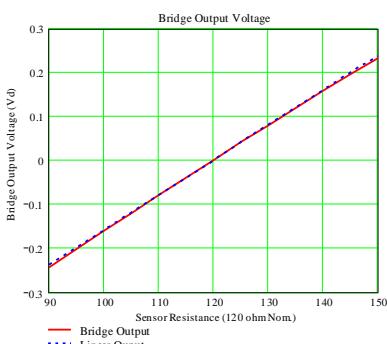

$$\begin{aligned} (V_d - V_{d1}) &= \frac{(V_{d2} - V_{d1})}{(R_2 - R_1)} (r_s - R_1) \\ (V_d - 0) &= \frac{(0.2395 - 0)}{(150 - 120)} (r_s - 120) \\ V_d &= 0.007983 r_s - 0.958 \end{aligned}$$

Equation

Less output voltage but greater linearity  
Dc bridge approximately linear for small  
deviations around balance point

Lesson 12\_et438b.pptx

24

## Maximum Non-Linearity

**Example Solution (Part 4)** Determine the maximum non-linearity for each bridge.

Take difference between actual bridge output and the zero based lines.  
Maximum occurs at either end of the graph.

$$V_d(r_s) =$$

-0.714 V
-0.581
-0.455
-0.333
-0.217
-0.106
0
0.102
0.2
0.294
0.385
0.472
0.556

$$V_{dl}(r_s) =$$

-0.635 V
-0.529
-0.423
-0.317
-0.212
-0.106
0
0.106
0.212
0.318
0.423
0.529
0.635

$$|V_{dl}(r_s) - V_d(r_s)|$$

0.0793 V
0.0523
0.0312
0.0159
0.0058
0.0006
0
0.0038
0.0117
0.0234
0.0388
0.0575
0.0795

$$V_{dl}(r_s) =$$

-0.246 V
-0.204
-0.162
-0.121
-0.08
-0.04
0
0.04
0.079
0.118
0.157
0.195
0.233

$$V_{dl1}(r_s) =$$

0.0062 V
0.0042
0.0026
0.0014
0.0006
0.0001
0
0.0002
0.0008
0.0017
0.003
0.0046
0.0065

R<sub>3</sub>=1000 Ω  
R<sub>4</sub>=1000 Ω

R<sub>3</sub>=120 Ω  
R<sub>4</sub>=1000 Ω

Bridge

Linearized

Bridge

Linearized

Lesson 12\_et438b.pptx


25

## Percent Non-Linearity

Determine the percent non-linearity using the following formula

$$\% \text{error} = \frac{|V_{dl} - V_d|}{|2 \cdot V_{dl(\max)}|} 100\%$$

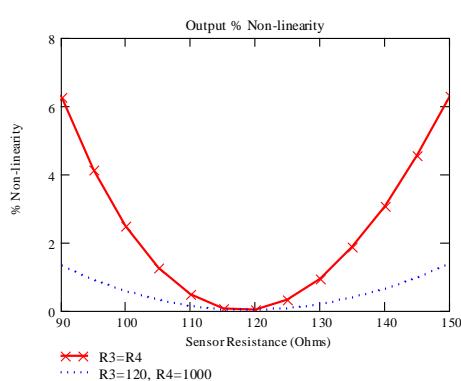Where  $V_{dl(\max)}$  = max linear output



Non-linearity greatly improved by making R<sub>3</sub> equal to nominal resistive sensor value

Lesson 12\_et438b.pptx

26

## Instrumentation Amplifier Gains

**Example Solution (Part 5)** Determine the gain necessary for a span of 15 Vdc

Use average value of  $V_d$  to compute gain

For  $R_3 = R_4 = 1000$  ohms


Average max value

$$(|-0.714| + |0.556|)/2 = 0.635 \text{ V}$$

For  $R_3 = 120$  and  $R_4 = 1000$  ohms

Average max value

$$(|-0.246| + |0.233|)/2 = 0.2395 \text{ V}$$

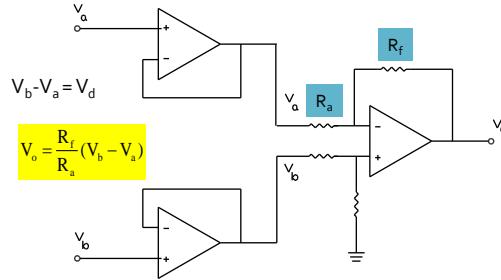

## Instrumentation Amplifier Gains

Compute the Amp gains using the gain formula

For  $R_3 = R_4 = 1000$  ohms

$$\begin{aligned} V_o &= 15 \text{ V dc } V_d = 0.635 \text{ V} \\ \frac{V_o}{V_d} &= \frac{R_f}{R_a} = A_v \\ \frac{15 \text{ V}}{0.635 \text{ V}} &= \frac{R_f}{R_a} = A_v \\ 23.62 &= A_v \end{aligned}$$

For  $R_3 = 120$  and  $R_4 = 1000$  ohms

$$\begin{aligned} V_o &= 15 \text{ V dc } V_d = 0.2395 \text{ V} \\ \frac{V_o}{V_d} &= \frac{R_f}{R_a} = A_v \\ \frac{15 \text{ V}}{0.2395 \text{ V}} &= \frac{R_f}{R_a} = A_v \\ 62.63 &= A_v \end{aligned}$$

Note that increasing linearity reduces  $V_d$  and requires higher gains

# End Lesson 12: Analog Signal Conditioning

ET 438 b Digital Control and Data Acquisition  
Department of Technology

Lesson 12\_et438b.pptx

29