

Lesson 17: State-Based Design Example

ET 438B Sequential Control and Data Acquisition
Department of Technology

1

Lesson 17_et438b.pptx

Learning Objectives


After this presentation you will be able to:

- Determine the inputs, outputs and states of a sequential process from the problem statement
- Write state equations based on defined inputs, outputs and previous states
- Convert state equations into ladder rungs.

2

Lesson 17_et438b.pptx

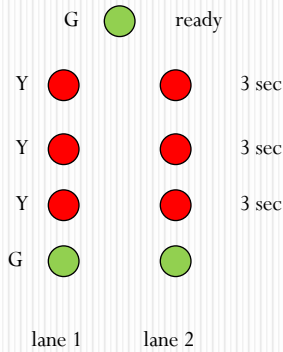DESIGN EXAMPLE - DRAG STRIP "CHRISTMAS TREE"




A simplified starting timer is to be constructed for a drag strip. To enable the start timing for a race both cars must actuate sensor switches at the start line that indicate they are in position. When the cars are in position, the race judge receives a green light on his control panel and a green light comes on of the "Christmas Tree". He then presses a race initial button on his control panel. The Christmas tree times through the sequence shown at left.

3

Lesson 17_et438b.pptx

DESIGN EXAMPLE - DRAG STRIP "CHRISTMAS TREE"

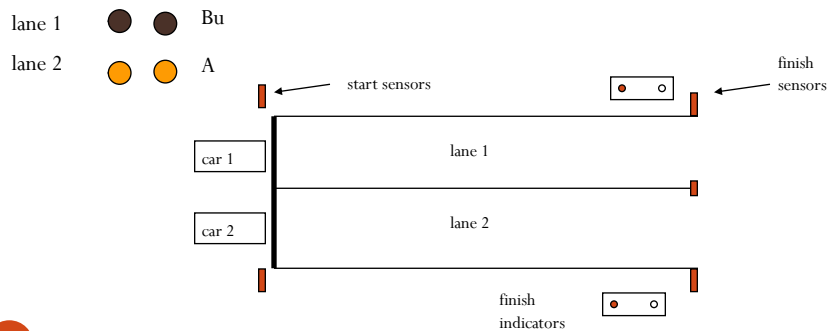When the lower pair of green lamps come on the racers begin. A pair of photo eyes located at the finish line indicate the winner by lighting a blue light for a winner and a amber light for a loser. after the race results are indicated, the judge can press a reset button to prepare the system for the next race



4

Lesson 17_et438b.pptx

DESIGN EXAMPLE - DRAG STRIP "CHRISTMAS TREE"

Design Problem

- 1.) Identify the states, conditions and actions for this system
- 2.) Construct a flow chart of the logic for this system
- 3.) Construct a state transition diagram for this system
- 4.) Design a ladder logic system to implement these functions

Part 1: States, Conditions, Actions

States

- S0 : reset
- S1: cars at start line
- S2: 1st set red lamps on
- S3: 2nd set red lamps on
- S4: 3rd set red lamps on
- S5: Green lamps on (race start)
- S6: Lane 1 Wins
- S7: Lane 2 Wins

5

Lesson 17_et438b.pptx

DESIGN EXAMPLE - DRAG STRIP "CHRISTMAS TREE"

Define conditions (Inputs)

Conditions

- I0: reset pressed
- I1: racer 1 positioned
- I2: racer 2 positioned
- I3: race timing initiated
- I4: 1st set red lamps timed out
- I5: 2nd set red lamps timed out
- I6: 3rd set red lamps timed out
- I7: lane 1 finish photo eye tripped
- I8: lane 2 finish photo eye tripped
- I9: start pressed

6

Lesson 17_et438b.pptx

DESIGN EXAMPLE - DRAG STRIP "CHRISTMAS TREE"

Define actions (Outputs)


Actions

- O0: light green ready lamp
- O1: light red lamps set 1
- O2: light red lamp set 2
- O3: light red lamp set 3
- O4: light green lamp set
- O5: light blue lamp 1 if lane 1 wins
- O6: light blue lamp 2 if lane 2 wins
- O7: light amber lamp 1 if lane 1 loses
- O8: light amber lamp 2 if lane 2 loses


7

Lesson 17_et438b.pptx

Part 2 Flow chart

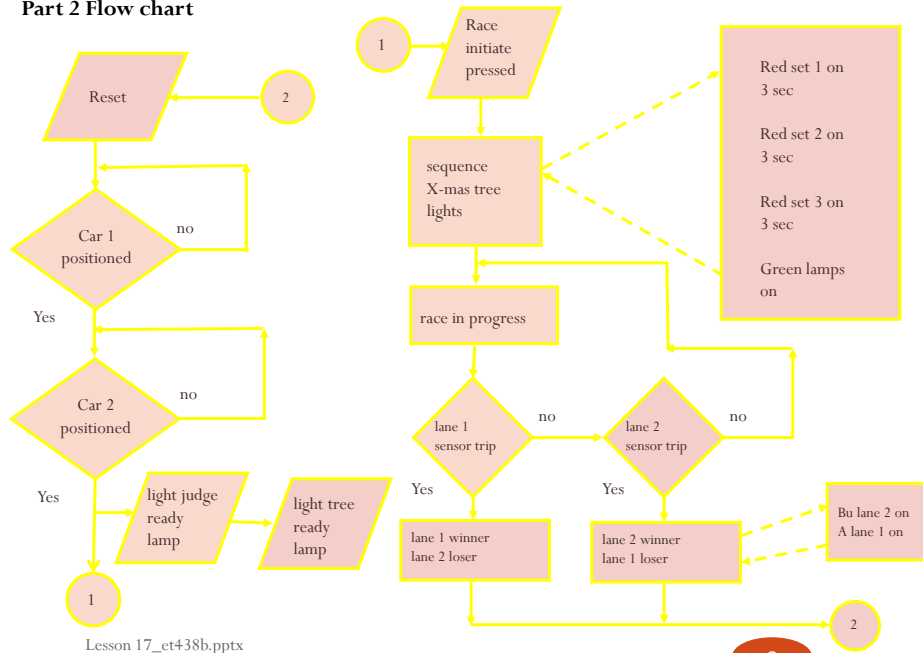

8

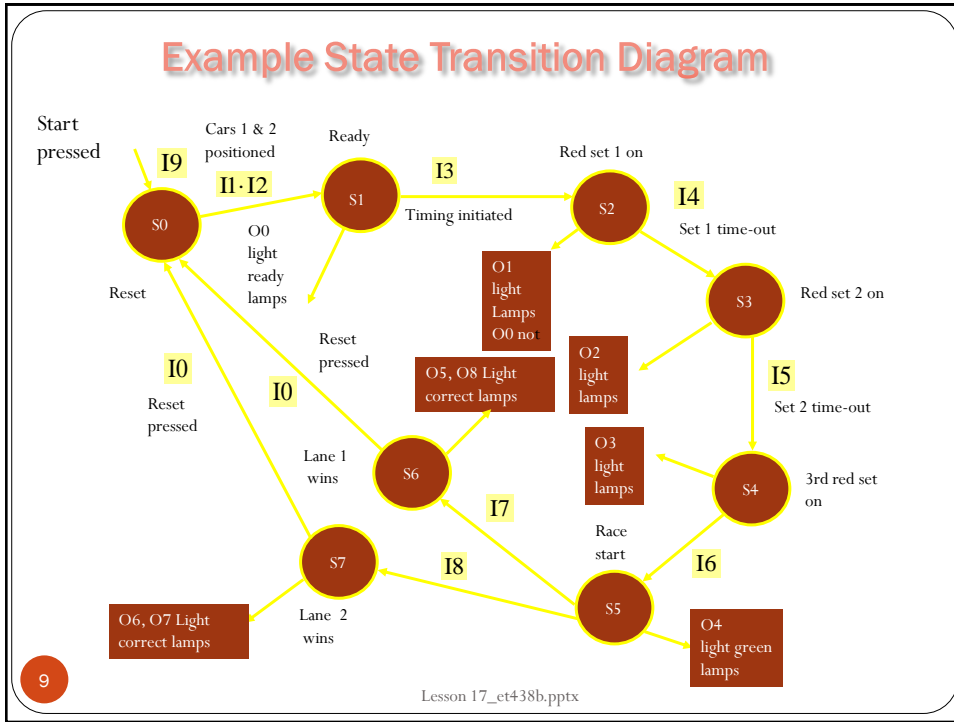

Construct State Equations

State 0

$$S0^{+1} = (S0 + I0 \cdot (S6 + S7) + I9) \cdot (\bar{I1} \cdot \bar{I2} \cdot S0)$$

$$S0^{+1} = (S0 + I0 \cdot (S6 + S7) + I9) \cdot (\bar{I1} + \bar{I2} + \bar{S0})$$

DeMorgans

Expand and Simplify

$$S0^{+1} = S0 \cdot \bar{I1} + S0 \cdot \bar{I2} + S0 \cdot \bar{S0} + (I0 \cdot (S6 + S7) + I9) \cdot \bar{I1} + (I0 \cdot (S6 + S7) + I9) \cdot \bar{I2} + (I0 \cdot (S6 + S7) + I9) \cdot \bar{S0}$$

Factor

$$S0^{+1} = S0 \cdot (\bar{I1} + \bar{I2}) + I9 \cdot (\bar{I1} + \bar{I2}) + I0 \cdot (S6 + S7) \cdot (\bar{I1} + \bar{I2}) + I0 \cdot (S6 + S7) \cdot \bar{S0} + I9 \cdot \bar{S0}$$

Regroup

$$S0^{+1} = S0 \cdot (\bar{I1} + \bar{I2}) + [I0 \cdot (S6 + S7) + I9] \cdot (\bar{I1} + \bar{I2}) + [I0 \cdot (S6 + S7) + I9] \cdot \bar{S0}$$

0

Construct State Equations

State 0 continued

Factor

$$S0^{+1} = [S0 \cdot (\bar{I1} + \bar{I2}) + (I0 \cdot (S6 + S7) + I9)](\bar{I1} + \bar{I2})[(\bar{I1} + \bar{I2}) + \bar{S0}]$$

Simplify &
Regroup

$$S0^{+1} = (\bar{I1} + \bar{I2}) \cdot [S0 + (I0 \cdot (S6 + S7) + I9)] \cdot [1 + \bar{S0}]$$

$$S0^{+1} = (\bar{I1} + \bar{I2}) \cdot [S0 + (I0 \cdot (S6 + S7) + I9)]$$


$$S0^{+1} = (S0 + I0 \cdot (S6 + S7) + I9)(\bar{I1} + \bar{I2}) \quad \text{Reduced Equation}$$

11

Lesson 17_et438b.pptx

Construct Ladder Logic

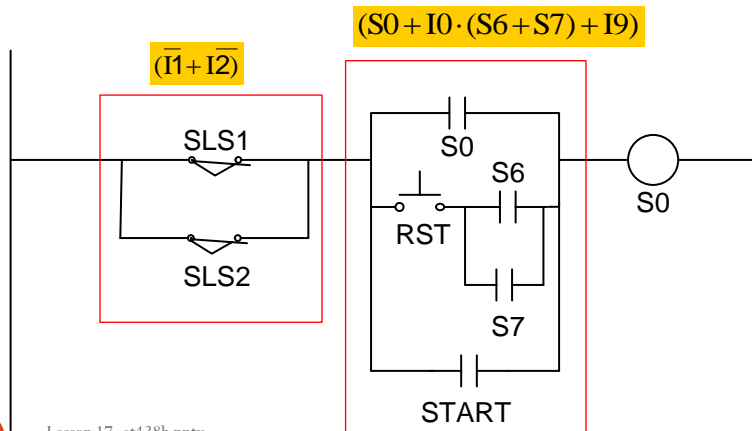
$$S0^{+1} = (S0 + I0 \cdot (S6 + S7) + I9) \cdot (\bar{I1} + \bar{I2})$$



12

Lesson 17_et438b.pptx

Construct State Equations

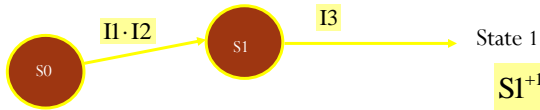

$$S1^{+1} = (S1 + I1 \cdot I2 \cdot S0) \cdot (\overline{I3} \cdot \overline{S1})$$

$$S1^{+1} = (S1 + I1 \cdot I2 \cdot S0) \cdot (\overline{I3} + \overline{S1})$$

$$S1^{+1} = S1 \cdot \overline{I3} + S1 \cdot \overline{S1} + I1 \cdot I2 \cdot S0 \cdot \overline{I3} + I1 \cdot I2 \cdot S0 \cdot \overline{S1}$$

$$S1^{+1} = S1 \cdot (\overline{I3}) + I1 \cdot I2 \cdot S0 \cdot (\overline{I3} + \overline{S1})$$

$$S1^{+1} = S1 \cdot (\overline{I3}) + I1 \cdot I2 \cdot S0 \cdot (\overline{I3}) \cdot I0 \cdot I1 \cdot I2 \cdot S0 + I1 \cdot I2 \cdot S0 \cdot \overline{S1}$$

$$S1^{+1} = S1 \cdot (\overline{I3}) + (\overline{I3})(1 + \overline{S1}) \cdot I1 \cdot I2 \cdot S0$$

$$S1^{+1} = S1 \cdot (\overline{I3}) + (\overline{I3}) \cdot I1 \cdot I2 \cdot S0$$

$$S1^{+1} = (S1 + I1 \cdot I2 \cdot S0)(\overline{I3})$$

13


Lesson 17_et438b.pptx

Construct Ladder Logic

$$S1^{+1} = (S1 + I1 \cdot I2 \cdot S0)(\overline{I3})$$

State 1 Output Equation

$$OO = S1$$

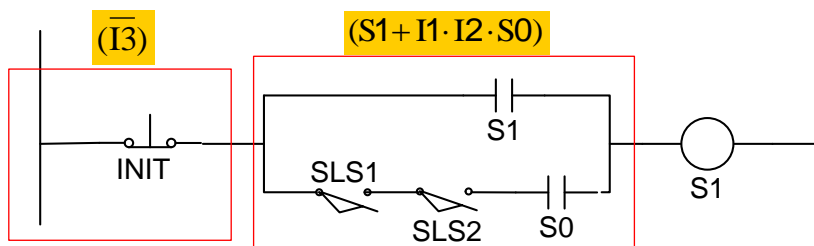

14

Lesson 17_et438b.pptx

Construct State Equations

State 2

$S2^{+1} = (S2 + I3) \cdot (\overline{I4})$

TON#(c,t)=On-delay timer #
c = input condition
t = time delay

so

$I4 = \text{TON1}(S2,3) = \text{timer done}$

$S2^{+1} = (S2 + I3) \cdot (\overline{\text{TON1}(S2,3)})$

$S2^{+1} = (S2 + I3) \cdot (\overline{\text{TONI}(S2,3)})$

State 2 Output Equation **O1 = S2**

State 3

$S3^{+1} = (S3 + I4 \cdot S2) \cdot (\overline{I5})$

$I5 = \text{TON2}(S3,3) = \text{timer done}$

$S3^{+1} = (S3 + \text{TONI}(S2,3) \cdot S2) \cdot (\overline{\text{TON2}(S3,3)})$

State 3 Output Equation **O2 = S3**

15

Lesson 17_et438b.pptx

Construct State Equations

State 4

$S4^{+1} = (S4 + I5 \cdot S3) \cdot (\overline{I6})$

$I5 = \text{TON3}(S4,3) = \text{timer done}$

$S4^{+1} = (S4 + \text{TON2}(S3,3) \cdot S3) \cdot (\overline{\text{TON3}(S4,3)})$

State 4 Output Equation **O3 = S4**

State 5

$S5^{+1} = (S5 + I6 \cdot S4) \cdot ((\overline{I7 + I8}))$

$I6 = \text{TON3}(S4,3) = \text{timer done}$

$S5^{+1} = (S5 + \text{TON3}(S4,3) \cdot S4) \cdot (\overline{(I7 + I8)})$

16

Lesson 17_et438b.pptx

Construct State Equations


State 5 simplification

$$S5^{+1} = (S5 + \text{TON3}(S4,3) \cdot S4) \cdot (\overline{I7} + \overline{I8})$$

$$S5^{+1} = (S5 + \text{TON3}(S4,3) \cdot S4) \cdot (\overline{I7} \cdot \overline{I8})$$

State 5 Output Equation

$$O4 = S5$$

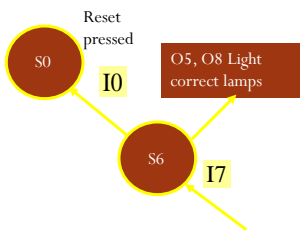

State 6

$$S6^{+1} = (S6 + I7 \cdot \overline{I8} \cdot S5) \cdot (\overline{I0})$$

State 6 Output Equations

$$O5 = S6$$

$$O8 = S6$$


Block Lane 2

17

Lesson 17_et438b.pptx

Construct State Equations

State 7

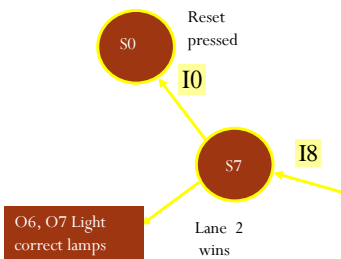

$$S7^{+1} = (S7 + \overline{I7} \cdot I8 \cdot S5) \cdot (\overline{I0})$$

State 7 Output Equations

$$O6 = S7$$

$$O7 = S7$$

Block Lane 1


18

Lesson 17_et438b.pptx

Construct Ladder Logic

State 6
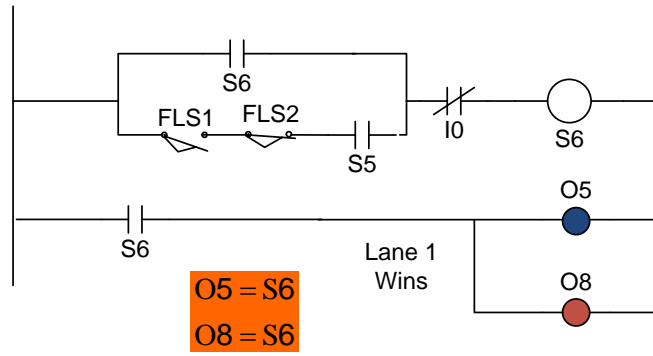
$$S6^{+1} = (S6 + I7 \cdot \bar{I8} \cdot S5) \cdot (\bar{I0})$$




19

Lesson 17_et438b.pptx

Construct Ladder Logic

State 7

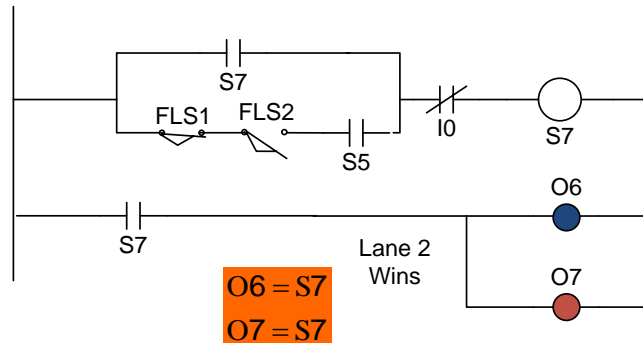
$$S7^{+1} = (S7 + \bar{I7} \cdot I8 \cdot S5) \cdot (\bar{I0})$$



20

Lesson 17_et438b.pptx


Complete System

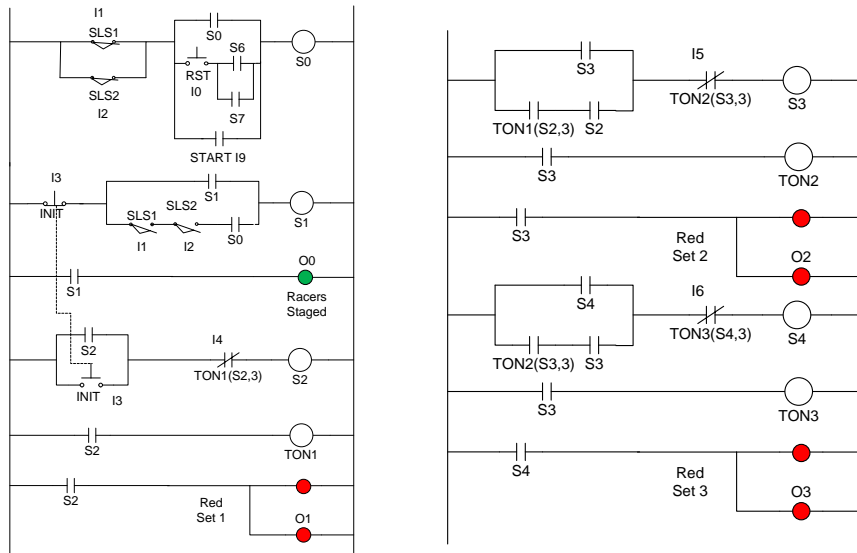

21

Lesson 17_et438b.pptx

Complete System

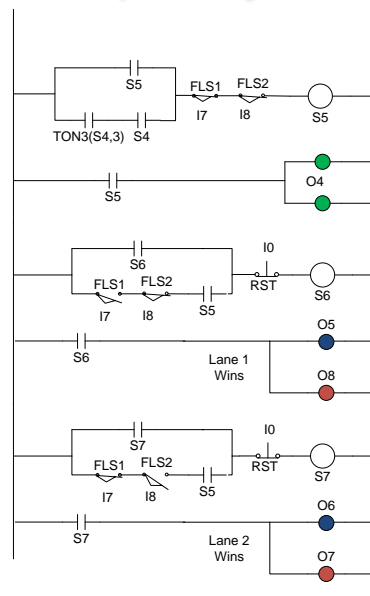

22

Lesson 17_et438b.pptx

Design Considerations

Personnel and Equipment Safety

Fail-safe operation - component fail results in little or no damage or inconvenience

Common Practice

- 1.) start sequence by closing NO contacts
- 2.) stop a sequence by opening NC contact

Practice Results: if device fails to start process stops,
If started would stop **Example:** Motor starter

23

Lesson 17_et438b.pptx

Troubleshooting Tips

Common causes of Failure

- 1.) Dirty or oxidized contacts
- 2.) Broken wire or loose connection
- 3.) Up stream power source interrupted causing input device to de-activate

Other Issues

Contact operation sequence

break-before-make standard

See previous example limit switches

24

Lesson 17_et438b.pptx

End Lesson 17: State-Based Design Example

ET 438B Sequential Control and Data Acquisition
Department of Technology

25

Lesson 17_et438b.pptx