

ET 438 b Digital Control and Data Acquisition
Department of Technology

LESSON 19: PLC PROGRAMMING TECHNIQUES

1

LEARNING OBJECTIVES

After this presentation you will be able to:

- Identify the similarities and differences between ladder logic and ladder programming of a PLC
- Convert ladder diagrams into PLC programs
- Use bit manipulating instructions to implement sequential logic control
- Use timer and counter instructions to implement more complex control functions.

2

Lesson 19_et438b

PLC LADDER LOGIC PROGRAMMING

Basic Concepts of PLC Ladder Logic Programming

Instructions look like schematic symbols

Symbols attached to bit addresses in data maps

PLC ladder logic program based on logical "continuity"


All input symbols must test true for the output symbol to be true

3

Lesson 19_et438b

PLC LADDER LOGIC PROGRAMMING

Example system

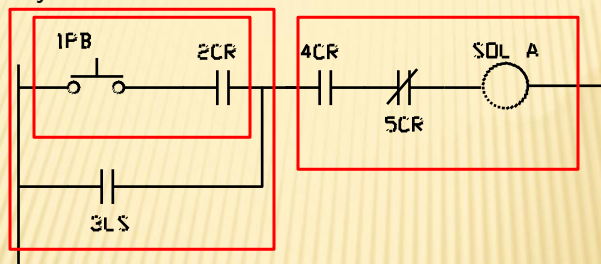

Boolean Equation

$$(1PB \cdot 2CR)$$

$$((1PB \cdot 2CR) + 3LS) \cdot 4CR \cdot \overline{5CR} = SOLA$$

Could program PLC in verbose language or use ladder logic symbols.
Ladder logic used to reduce training of maintenance personnel

4

BASIC PLC PROGRAMMING INSTRUCTIONS

Bit or relay Instructions - test memory location bits

Examine if closed: XIC

examines an input bit for closed condition



Bit address

Logic of XIC

Input bit	Evaluation	Rung Effect
1	TRUE	Pass logical continuity
0	FALSE	Block logical continuity

Examine if open: XIO

examines an input bit for an open condition



Bit address


Logic of XIO

Input bit	Evaluation	Rung Effect
1	FALSE	Block logical continuity
0	TRUE	Pass logical continuity

BASIC PLC PROGRAMMING INSTRUCTIONS

Output Instructions - Toggle output map bits when rung evaluates true


Output Energize (OTE)

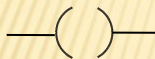

Bit address


Instruction becomes true when all instructions to rung become true

Output latch and Output unlatch

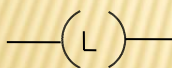

Bit address

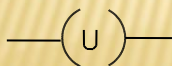Output latch become TRUE when input rung instructions become TRUE. Remains TRUE after rung becomes FALSE



Bit address


Output unlatch is used to reset the output latch instruction

Lesson 19_et438b

BASIC PLC PROGRAMMING INSTRUCTIONS

More Output Instructions

One Shot Instruction

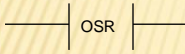

Input that allows an event to occur only once during a program scan.

Instruction only responds to rising hardware input signal


Responds to only FALSE to TRUE transitions

7

Lesson 19_et438b

PROGRAMMING EXAMPLES

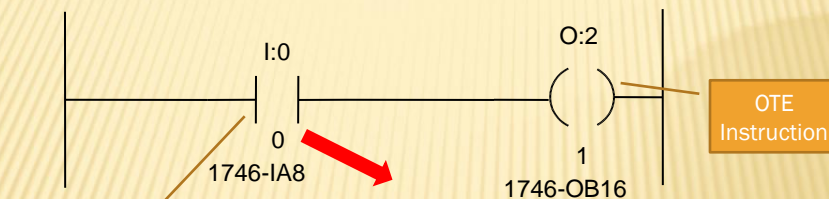Rung Examples: What is the condition of the output instruction (T/F)?



XIC
Instruction

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0	addr.
															0	I:0
																I:3
																I:4


Input image table shows a 0 bit, so XIC evaluates to a FALSE

8

Lesson 19_et438b

PROGRAMMING EXAMPLES

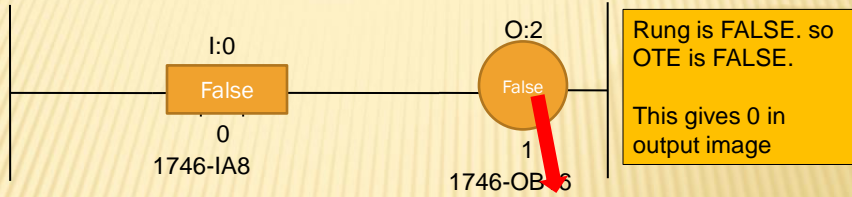Rung example continued: What is the condition of the output instruction (T/F)?



Rung is FALSE. so OTE is FALSE.

This gives 0 in output image


15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0	addr.
																O:0
															0	O:2
																O:4

9

Lesson 19_et438b

PROGRAMMING EXAMPLES

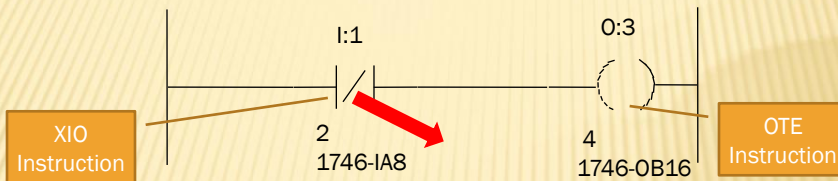Rung Examples: What is the condition of the output instruction? (T/F)?



15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0	addr
																I:0
															0	I:1
																I:4

Input image table shows 0 bit in I:1/2 XIO evaluates TRUE.


Input image table

10

Lesson 19_et438b

PROGRAMMING EXAMPLES

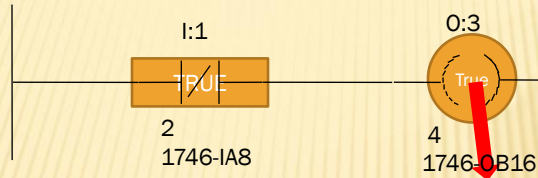Rung Examples: What is the condition of the output instruction? (T/F)?



Rung is TRUE, so OTE is TRUE.


Output image table

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0	addr
											1					0:2
																0:3
																0:5

Lesson 19_et438b

PROGRAMMING EXAMPLES

Rung Examples: What is the condition of the output instruction? (T/F)?

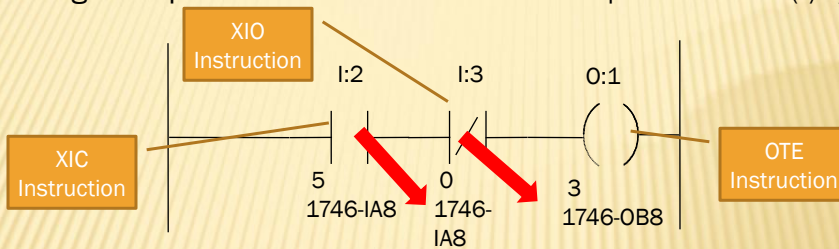

Location I:2/5 = 1. XIC evaluates as TRUE..

Location I:3/0 = 0. XIO instruction evaluates as TRUE.


Input image table

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0	addr
										1						I:2
															0	I:3
																I:4

Lesson 19_et438b

PROGRAMMING EXAMPLES

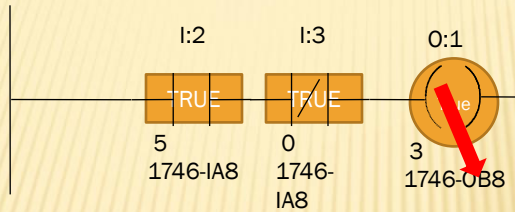Rung Examples: What is the condition of the output instruction? (T/F)?



TRUE AND TRUE = TRUE
Output image will have 1
at address O:1/3

Output image table


15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0	addr
												1				O:0
																O:1
																O:5

13

Lesson 19_et438b

PROGRAMMING EXAMPLES

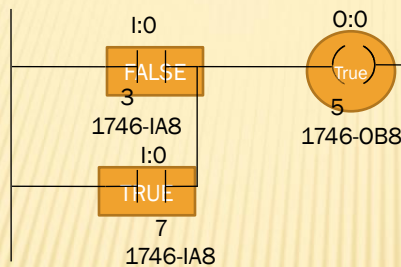Rung Examples: What is the condition of the output instruction? (T/F)?



TRUE OR FALSE = TRUE
so rung is TRUE, OTE is
TRUE

Output Image Table location
O:0/5 = 1. This output will
be energized

Input image table

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0	addr
								1				0				I:0
																I:1
																I:4

The first XIC
instruction at input
I:0/3 evaluates as a
FALSE


XIC at input I:0/7
evaluates
as TRUE (bit =1)

Input image table
shows I:0/0 = 1
and I:0/3 = 0

14

PROGRAMMING EXAMPLES

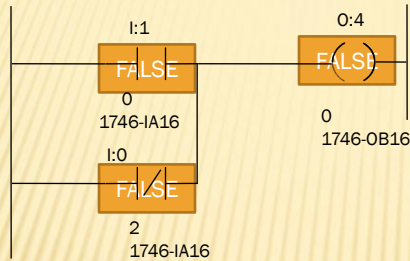Rung Examples: What is the condition of the output instruction? (T/F)?



FALSE OR FALSE = FALSE
The rung evaluates FALSE

The instruction OTE evaluates FALSE

In the output image file, O:4/0 = 0 and output will not be energized

Input image table

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0	addr
													1			I:0
														0		I:1


At input I:1/0 = 0, XIC evaluates FALSE

At input I:0/2 = 1, XIO evaluates FALSE

TOGGLING BITS IN THE BIT FILE

The instructions XIC, XIO and OTE operate on bits in the B4 bit file also. Use these bits like control relays in electromechanical schemes. Not related to I/O points

Rung Examples

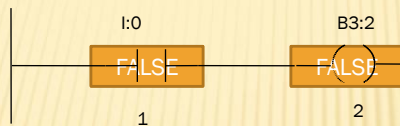

I:0/1=0


B3:2/2=0

I:0/1=1

B3:2/2=1

B3:2/2 = bit number 2 in word 2 of the B3 file

This will be toggled by the input I:0/1

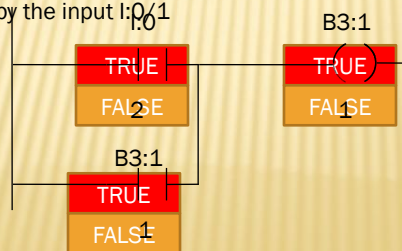


Input at location I:0/2 toggles the bit B3:1/1

The XIC instruction acts like a seal-in contact in electromechanical systems


TIMER INSTRUCTIONS

Timer on-delay (TON)

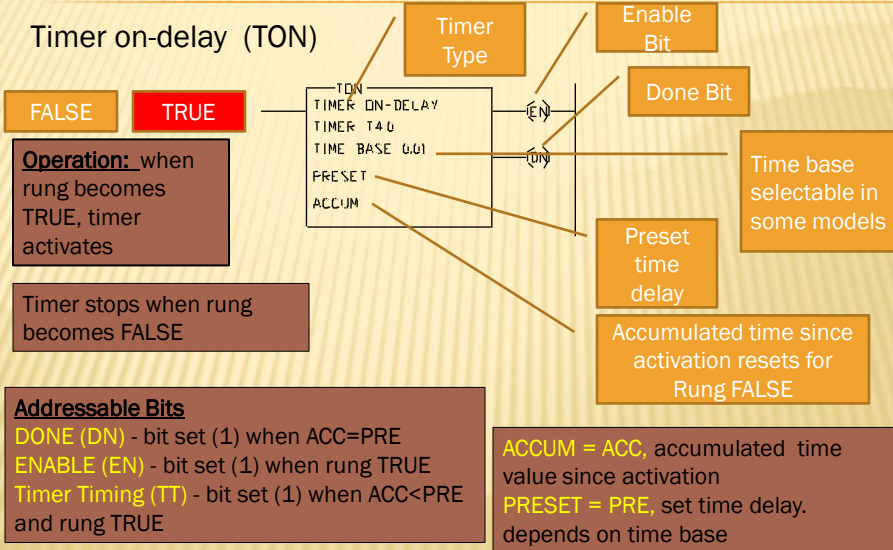

Timer Instructions

Timer: off-delay (TOF)

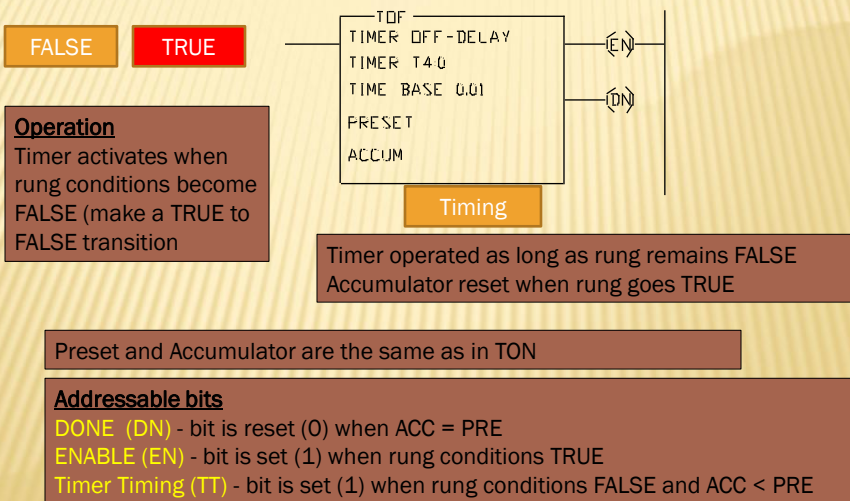

TIMER INSTRUCTION EXAMPLES

TRUE

Timer T4:0 first timer in program

Time base 0.01 sec, preset to 100 (1 sec) delay

Initial conditions I:0/2 = 0 Rung evaluates FALSE

I:0/2 = 1 rung evaluates TRUE t= 0 sec

Bit status EN = 0 TT = 0 DN = 0

Bit status EN = 1 TT = 1 DN = 0

15	14	13							0
EN	TT	DN	INTERNAL USE ONLY						
1	1		Preset Value (PRE)						
0	0	0	Accumulated Value (ACC)						

When PRE = ACC = 100

Bit status

EN = 1 TT = 0 DN = 1

EN = 1 until I:0/2 = 0

19

OFF-DELAY TIMER EXAMPLE

TRUE

Initial conditions: input bit instruction XIC B3:0/1 = 1 rung is TRUE . Timer is not activated

B3:0/1 = 0 TRUE to FALSE transition timer starts

Bit status EN = 0 TT = 1 ACC < PRE
DN = 1 ACC < PRE
Note: DN remains set until ACC = PRE

When PRE = ACC = 100 (1 sec)

Bit status EN = 0 TT = 0
ACC = PRE DN = 0

If rung goes TRUE ACC = 0
EN = 1 DN = 1 TT = 0

15	14	13							0
EN	TT	DN	INTERNAL USE ONLY						
0	1	1	Preset Value (PRE)						
0	0		Accumulated Value (ACC)						

20

TIMER EXAMPLE

Lesson 19_et438b

Example: Using a timer to turn on an output after a 3 second delay

When input changes state

I:1/3 = 1 Rung is TRUE t
 Timer bit status
 EN = 1 TT=1 DN = 0

Initial conditions: Input address I:1/3 = 0
 Rung 1 evaluates FALSE
 Timer Bit status EN = 0 TT = 0 DN = 0 PRE = 300

Rung 2 T4:0/DN = 0 XIC instruction evaluates FALSE so 0:0/0 = 0

21

Timer Example-Continued

Lesson 19_et438b

Rung 2 T4:0/DN = 0 rung FALSE 0:0/0 = 0
 Output is de-energized

At t = 3 seconds
 Rung 1 I:1/3 = 1
 PRE = ACC = 300
 Timer bits EN = 1 TT = 0 DN = 1

Rung 2: T4:0/DN = 1 XIC evaluates TRUE
 Rung is TRUE 0:0/0 = 1 Output energized


22

COUNTER INSTRUCTIONS

Counters used to accumulate a count of events that cause FALSE to TRUE transitions on the input to the counter rung

Count Up (CTU) and Count Down (CTD)

Count up instruction

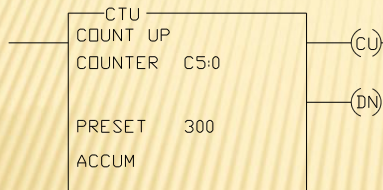

Addressable Bits

Counter up enable (CU) = bit is set (1) when the rung goes TRUE


Counter Done (DN) = bit is set (1) when the preset and accumulated values are equal

Counter accumulator values are retentive. The value is not cleared until a RES instruction is issued that addresses the counter

23

Counter Instructions

Count Down (CTD)

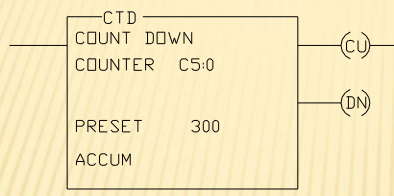

Counter decrements the preset value by 1 each time the rung makes FALSE-TRUE transition

When $ACCUM < PRESET$ the $DN = 1$

Underflow and Overflow conditions
 Bit OV set (1) when $ACC = 32,767 + 1$
 Bit UV set (1) when $ACC = -32768 - 1$


Counter Done bit (CD) = set (1) when rung is TRUE Reset when the rung is FALSE

24

THE RESET INSTRUCTION


Reset (RES) - instruction used to reset timing and counting functions

Reset - output instruction resets counters and retentive timers having the same address as the RES instruction. Reset occurs when rung becomes TRUE

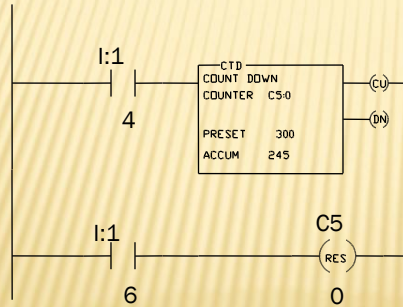

Input I:1/6 actuates RES instruction that clears counter C5:0
 ACCUM = 0 CU = 0

COUNTER ADDRESSING EXAMPLE

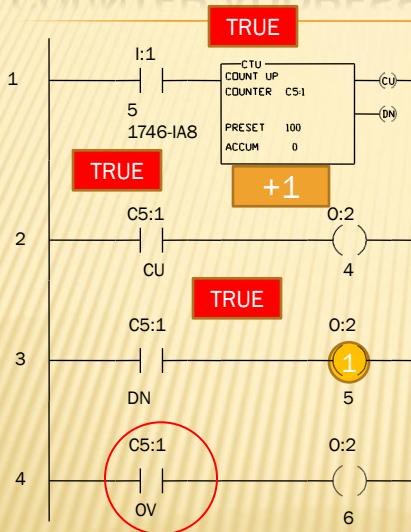

When I:1/5 = 1, rung 1 evaluates TRUE CTU increments

C5:1/CU = 1 when rung 1 TRUE
 Turning on O:2/4

C5:1/DN bit will be set when ACC = PRE = 100 setting O:2/5=1

The overflow bit C5:1\OV = 1 when ACC = 32,767+1
 Counter "wraps around" 32,767+1 = -32,768

Lesson 19_et438b

PROGRAMMING LADDER LOGIC IN A PLC

Ladder Logic is similar to PLC rungs **but not identical**

Logical continuity **not equivalent** to electrical continuity

Programming Process

Must divide system into field inputs, field outputs and internal (bit) devices


Evaluate the function of the field contacts when assigning XIO and XIC instructions to field inputs

27

Lesson 19_et438b

Programming Ladder Logic in a PLC

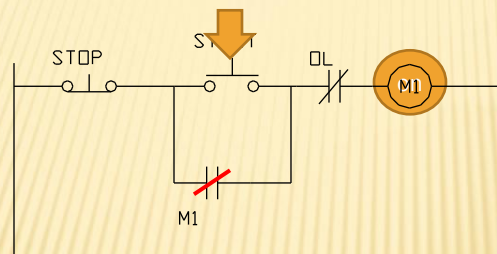Example: Three wire motor starter control with overload protection relay



M1 is motor contactor coil, contact M1 is auxiliary contact mechanically linked to M1


Demonstrate operation

28

Lesson 19_et438b

Programming Ladder Logic in a PLC

Defining Field Devices

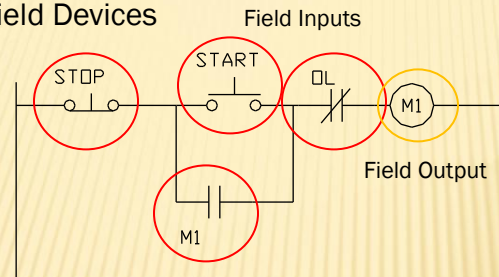

Start/Stop, M1 contact and OL contacts are **all field inputs** for PLC operation. Contacts located on external equipment.

M1 coil is a **field output**. PLC must energize the motor contactor coil based on the state of the inputs

29

Lesson 19_et438b

Programming Ladder Logic in a PLC

Step 1 – Defining I/O and Developing External Wiring Diagrams

Define Address of I/O points and wire field devices to I/O points.

Assume only slot 0 is populated with I/O points and all I/O 120 V ac

Inputs **Output(s)**

STOP = I:0/0 M1 =

START = I:0/1 O:0/0

OL = I:0/2

M1 = I:0/3


Contacts need a source of 120 V ac to actuate the electronics of the I/O cards (120 V ac I/O)

30

Lesson 19_et438b

Programming Ladder Logic in a PLC

Module External Wiring

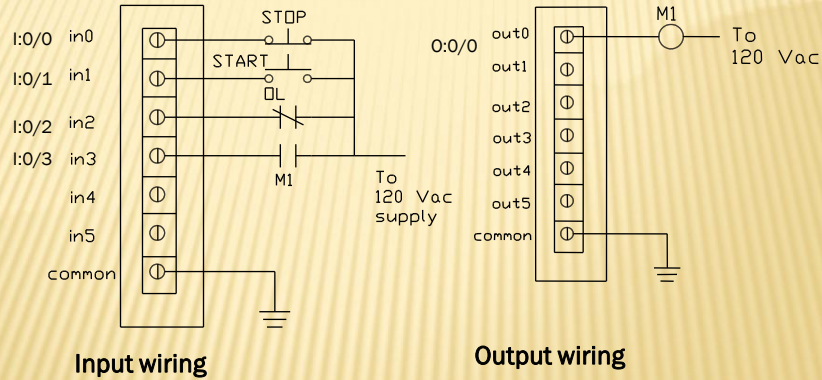

31

Lesson 19_et438b

Programming Ladder Logic in a PLC

Step 2 – Converting Ladder Diagram into PLC Program

Having Field devices in the NC state does not automatically translate to XIC instruction (NC symbol)

Rung instructions must evaluate to TRUE for OTE instruction to evaluate TRUE and energizing the external hardware

Review logic of bit instructions



Logic of XIC

Bit	Result
1	TRUE
0	FALSE



Logic of XIO

Bit	Result
1	FALSE
0	TRUE


32

Lesson 19_et438b

Programming Ladder Logic in a PLC

Rung Logic After the Pressing Stop

XIC at input I:0/0 evaluates as FALSE

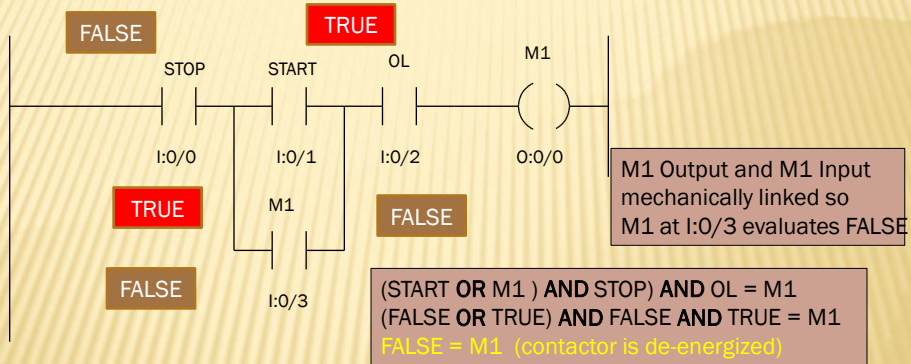

37

Lesson 19_et438b

ET-438b Sequential Control and Data Acquisition
Department of Technology

END LESSON 19: PLC PROGRAMMING TECHNIQUES

38