

ET 438b Sequential Control and Data Acquisition  
Department of Technology

## LESSON 3: OP AMP FUNDAMENTALS AND OPEN LOOP APPLICATIONS

1

## LEARNING OBJECTIVES

After completing this lesson you will be

- ✘ List the characteristics of an ideal OP AMP
- ✘ Determine the frequency limit of an OP AMP due to slew rate limits
- ✘ Explain the effects of gain-bandwidth limits
- ✘ Explain the operation of voltage comparators using ideal and non-ideal OP AMPS

2

## IDEAL OP AMPS

### Ideal OP AMP Model

#### Parameters

#### Idea

Voltage Gain:

Input Resistance:

Output Resistance:

Input I:

Cutoff Frequency,  $f_c$ :


$A_v = \text{infinite}$

$R_{in} = \text{infinite}$

$R_o = 0$

$I_1 = I_2 = 0$

infinite

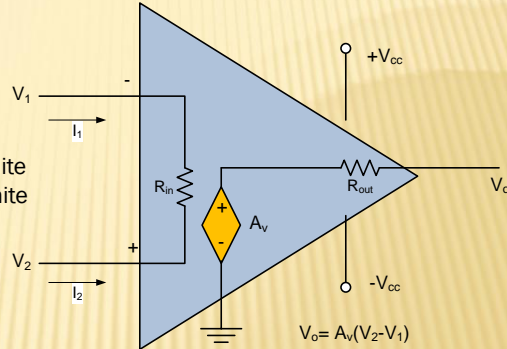

#### Typical (LM741)

$A_v = 200,000$

$R_i = 1\text{-}2 \text{ M}\Omega$

$R_o = 75 \Omega$

$I_1 = I_2 = 80 \text{ nA}$

$f_c = 1.5 \text{ MHz}$

3

## NON-IDEAL OP AMP MODEL

### Non-idea OP AMP parameters and characteristics

Output offset voltage - voltage on the output when both of the inputs are grounded. Typical value - 2 mV (LM741)

Slew rate - maximum rate of change of output voltage for large changes in the input voltage. Typical value -  $0.5 \text{ V}/\mu\text{s} = 500,000 \text{ V/s}$

Gain-Bandwidth Product-rate of frequency roll-off for OP AMP without feedback. Frequency at which the open loop gain of the OP AMP is 1 (0 dB). Typical 1 MHz (LM741) Applies to small signal level changes.

4

## NON-IDEA OP AMP PARAMETERS

Determine the frequency limit due to slew rate limiting.

Assume sine input and determine the rate of voltage change,  $dv/dt$

$$v(t) = V_p \sin(2\pi ft)$$

$$\frac{dv}{dt} = (V_p 2\pi f) \cos(2\pi ft)$$

Maximum rate of change in sine occurs at  $t=0$ , so set  $t=0$  in derivative to find  $f_{\max}$

$$\frac{dv}{dt} = V_p 2\pi f_{\max}$$

$$\frac{dv}{dt} = 2\pi V_p f_{\max}$$

Example  $dv/dt = 500,000 \text{ V/s}$ ,  $V_p = 10 \text{ V}$


Found in OP  
AMP Data  
Sheets

$$\frac{dv}{dt} = 2\pi V_p f_{\max} \quad \frac{500,000}{2\pi(10)} = 7958 \text{ Hz}$$

5

## NON-IDEA OP AMP PARAMETERS

Gain-Bandwidth Product=GBP

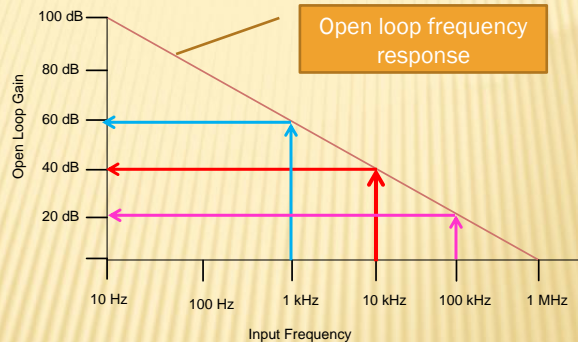

$$\text{GBP} = (\text{Gain})(\text{Input Frequency}) = 1 \text{ MHz}$$

$$\text{Find max frequency for 20 dB gain: } 1 \text{ MHz} / 10^{(20/20)} = 1,000,000 / 10 = 100 \text{ kHz}$$

$$\text{Find max frequency for 40 dB gain: } 1 \text{ MHz} / 10^{(40/20)} = 1,000,000 / 100 = 10 \text{ kHz}$$

$$\text{Find max frequency for 60 dB gain: } 1 \text{ MHz} / 10^{(60/20)} = 1,000,000 / 1000 = 1 \text{ kHz}$$

6

## PRACTICAL OP AMP OUTPUT LIMITS

OP AMP outputs typically saturate at 80% of supply voltages  $\pm V_{cc}$

$$\text{Output Voltage } V_o = A_v(V_2 - V_1)$$

$$\text{Output Range } 0.8(-V_{cc}) \leq V_o \leq 0.8(+V_{cc})$$

For a practical OP AMP with  $A_v = 100,000$  find the difference voltage that will cause output saturation. ( $\pm V_{cc} = 15 \text{ Vdc}$ )

$$V_d = (V_2 - V_1) \text{ so } V_o/V_d = A_v$$


$$\frac{0.8(+V_{cc})}{A_v} = V_d = (V_2 - V_1)$$

$$\frac{0.8(15)}{100,000} = 0.12 \text{ mV} = V_d$$

7

## IDEAL VOLTAGE COMPARATORS

Open loop OP AMP operation

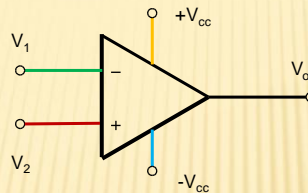

Ideal Voltage Comparator Operation

Transition take place exactly when voltages are equal

Operation Logic

When  $V_1 \geq V_2$ ,  $V_o = -V_{sat}$   
 When  $V_2 \geq V_1$ ,  $V_o = +V_{sat}$

8


## NON-IDEAL VOLTAGE COMPARATORS

Determine the voltage where output transition takes place with  $V_2$  as input

$$V_2 - 0.12 \text{ mV} = V_1$$

$$V_2 - 0.12 \text{ mV} \geq V_1 \text{ then } V_0 = + V_{\text{sat}}$$

Input/Output Diagram

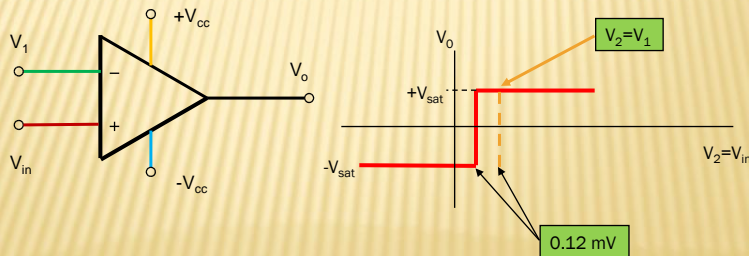

$A_v < \text{infinity}$  produces small voltage error in comparator circuits

9

## NON-IDEAL OP AMP COMPARATORS

Assume  $\pm 15 \text{ Vdc} = \pm V_{\text{cc}}$   $A_v = 100,000$ . so  
 $V_{\text{sat}} = 0.8(\pm V_{\text{cc}}) = 0.8(\pm 15) = \pm 12 \text{ Vdc}$

From previous calculation  $V_d = 0.12 \text{ mV}$

so  $V_d = V_2 - V_1$  which gives  $0.12 \text{ mV} = V_2 - V_1$

Take  $V_1$  as the input voltage

$$.12 \text{ mV} = (V_2 - V_1)$$

$$0.12 \text{ mV} + V_1 \geq V_2 \text{ then } V_0 = -V_{\text{sat}}$$

Take  $V_2$  as the input voltage


$$0.12 \text{ mV} = (V_2 - V_1)$$

$$0.12 \text{ mV} - V_2 = -V_1$$

10

## NON-INVERTING COMPARATORS

Circuit realization with OP AMPS

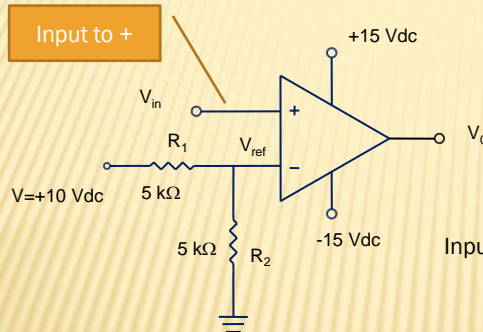


Find  $V_{ref}$  using voltage divider

$$V_{ref} = V \left( \frac{R_2}{R_1 + R_2} \right)$$

$$V_{ref} = 10 \left( \frac{5000}{5000 + 5000} \right) = 10(0.5) = 5.0 \text{ Vdc}$$

If  $V_{in} > 5$  then  $V_O = +12 \text{ Vdc}$

Input/output plot

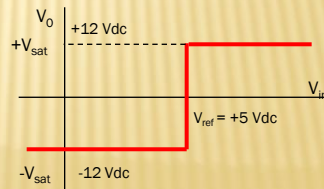


Logic: When  $V_{in} > V_{ref}$   $V_O = +V_{sat}$

11
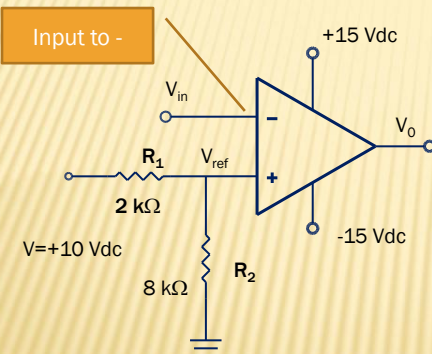
## INVERTING COMPARATORS

Use standard OP AMPS when slow transitions are expected in the input signal. (e.g. thermostat application). When higher speeds are needed use dedicated comparator IC. (LM311)




Find  $V_{ref}$  using voltage divider

$$V_{ref} = V \left( \frac{R_2}{R_1 + R_2} \right)$$

$$V_{ref} = 10 \left( \frac{8000}{8000 + 2000} \right) = 10(0.8) = 8.0 \text{ Vdc}$$

If  $V_{in} > 8$  then  $V_O = -12 \text{ Vdc}$

Input/output plot

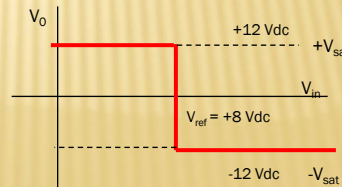

Logic: When  $V_{in} > V_{ref}$   $V_O = -V_{sat}$

12

Lesson 3\_et438b.pptx

ET 438b Sequential Control and Data Acquisition  
Department of Technology

# END LESSON 3: OP AMP FUNDAMENTALS AND OPEN LOOP APPLICATIONS

13