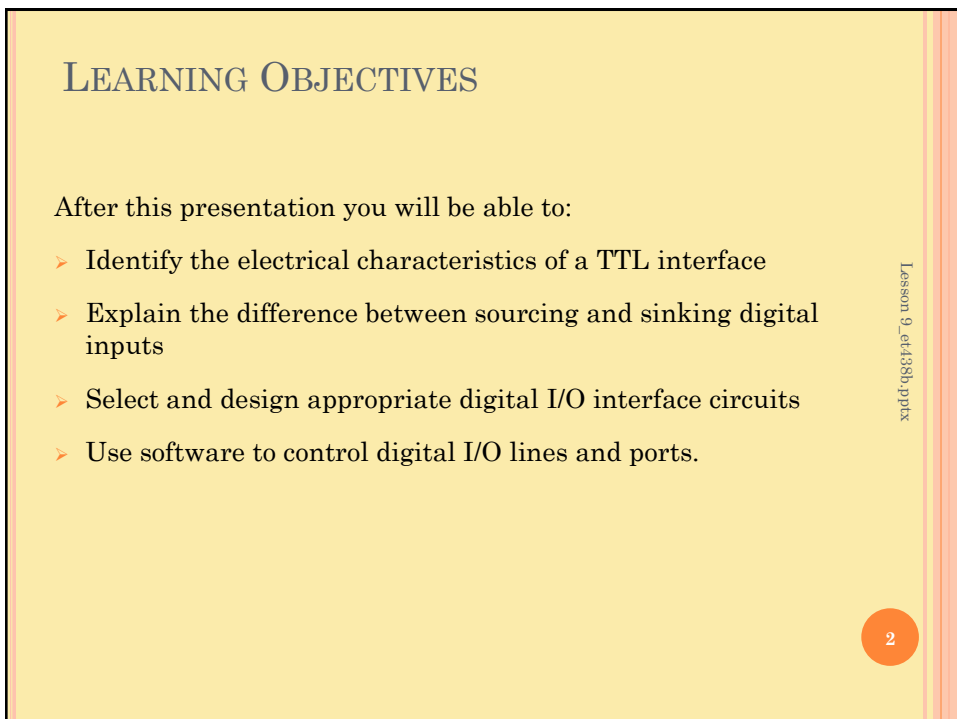


Lesson 9_et1438b.pptx

LESSON 9: DIGITAL INPUT- OUTPUT SIGNAL INTERFACING

1 ET 438b Sequential Control and Data Acquisition
Department of Technology

This slide features a light yellow background with vertical orange stripes on the left and right sides. A large orange circle is positioned on the left, with several smaller orange circles of varying sizes scattered around it. The text is centered and includes the lesson title, a slide number '1', and course information.



LEARNING OBJECTIVES

After this presentation you will be able to:

- Identify the electrical characteristics of a TTL interface
- Explain the difference between sourcing and sinking digital inputs
- Select and design appropriate digital I/O interface circuits
- Use software to control digital I/O lines and ports.

Lesson 9_et1438b.pptx

2

This slide has a light yellow background with vertical orange stripes on the right side. The text is left-aligned and includes the heading 'LEARNING OBJECTIVES', a paragraph 'After this presentation you will be able to:', and a bulleted list of four objectives. A slide number '2' is in a small orange circle at the bottom right.

DIGITAL INPUT & OUTPUT SIGNALS

Digital input and output control and monitor external devices that have only on/off levels

Boolean Logic form basis of numbering system and computer structure.

Boolean Logic	
Boolean Logic Symbol	State
1	logic high
0	logic low

Lesson 9_et438b.pptx

Logical Groupings

Individual bits: 1 and 0's
 Groups of bits: 8-bits = byte
 16-bits = 2 bytes = 1 word
 All collections of bits are powers of 2

3

DIGITAL INPUT & OUTPUT SIGNALS

Addressing bits in a byte

7	6	5	4	3	2	1	0	Address location
1	1	0	0	0	1	1	0	Bit

Bit 7 = 1 Bit 5 = 0 Bit 3 = 0 Bit 1 = 1
 Bit 6 = 1 Bit 4 = 0 Bit 2 = 1 Bit 0 = 0

Weighted number system - conversion from binary to decimal

$$n = 1 \cdot 2^7 + 1 \cdot 2^6 + 0 \cdot 2^5 + 0 \cdot 2^4 + 0 \cdot 2^3 + 1 \cdot 2^2 + 1 \cdot 2^1 + 0 \cdot 2^0$$

$$n = 1 \cdot 128 + 1 \cdot 64 + 1 \cdot 4 + 1 \cdot 2 = 198$$

198 decimal equivalent of binary number

4

Lesson 9_et438b.pptx

DIGITAL HARDWARE STANDARDS

Digital standards specify voltage levels of logic highs and logic lows, current output and input levels. Makes chips from same family compatible with each other

Logic Standards

Transistor-Transistor Logic (TTL) 7400 74LS00 series devices

Nominal 5 V dc logic high and 0 V dc logic low

TTL chip I/O pin electrical characteristics

Source current: 400 μ A

Sink current: 1.6 mA (1 unit load)

Logic 1 threshold voltage : $V \geq 2.4$ V dc

Logic 0 threshold voltage $V \leq 0.8$ V dc


5

Lesson 9_et438b.pptx

DIGITAL HARDWARE STANDARDS- SOURCE AND SINK CURRENTS

What is sourcing and sinking of device currents?

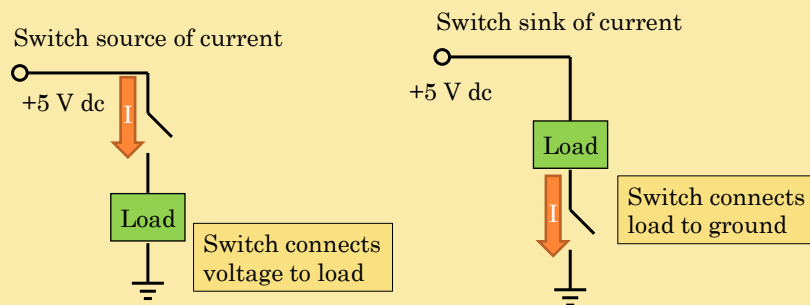Determined by position of voltage source, the switching device, and the load.




6

Lesson 9_et438b.pptx


DIGITAL HARDWARE STANDARDS- SOURCE AND SINK CURRENTS

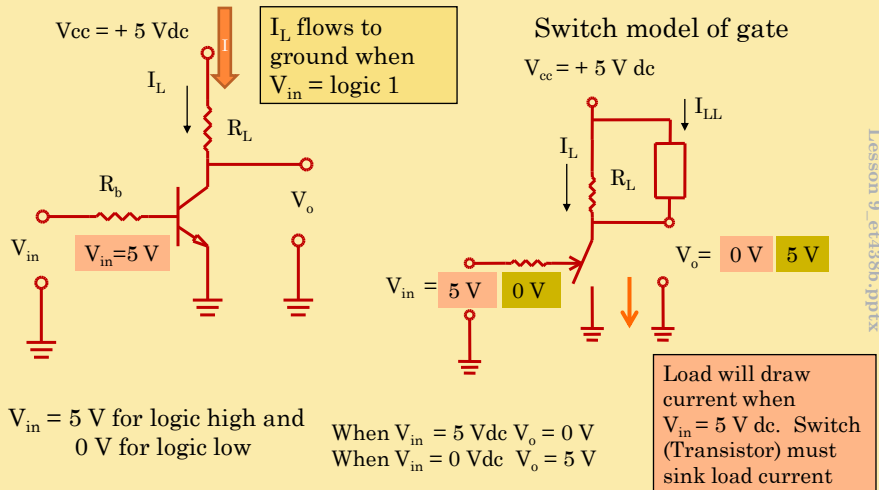Simple transistor sink and source representations



SOURCE AND SINK CURRENTS


Switch model of gate - current sourcing

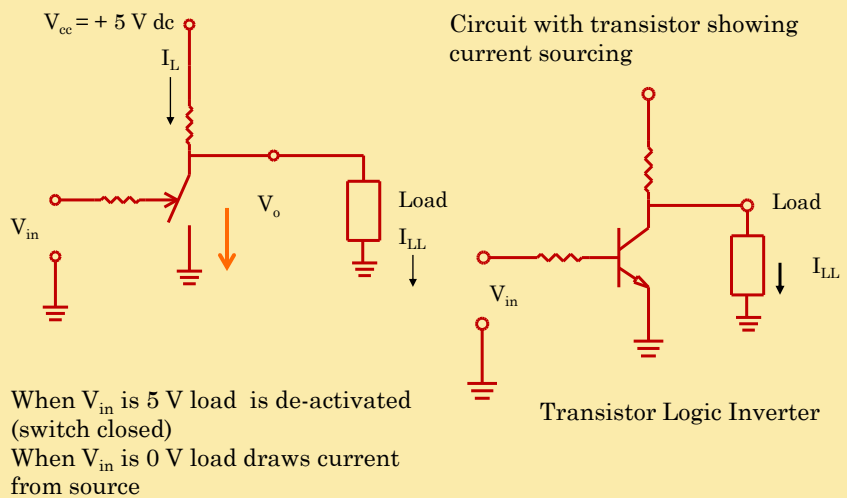

SOURCE AND SINK CURRENTS

TTL Inverter symbol

TTL Inverters Sinking Current

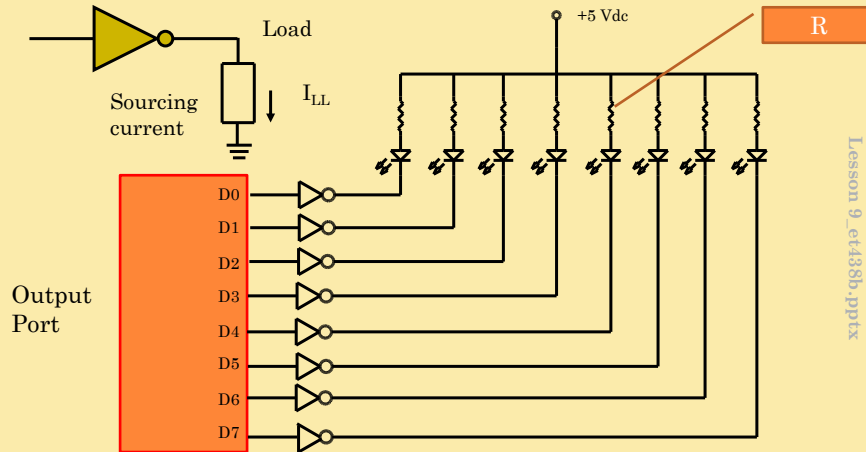


Resistors used to limit current through gate.
TTL buffer limit: 16 mA (10 unit loads)

DIGITAL INTERFACES

For high current output use discrete transistor or relay (electromechanical or solid state)

Solid State Relay

 


Devices integrated on the same chip. LED light output triggers TRIAC that passes ac current.

Does not electrically disconnect load from source – beware of leakage currents

DIGITAL INTERFACES

Typical Application – Ac Motor starting


Lesson 9_et438b.pptx

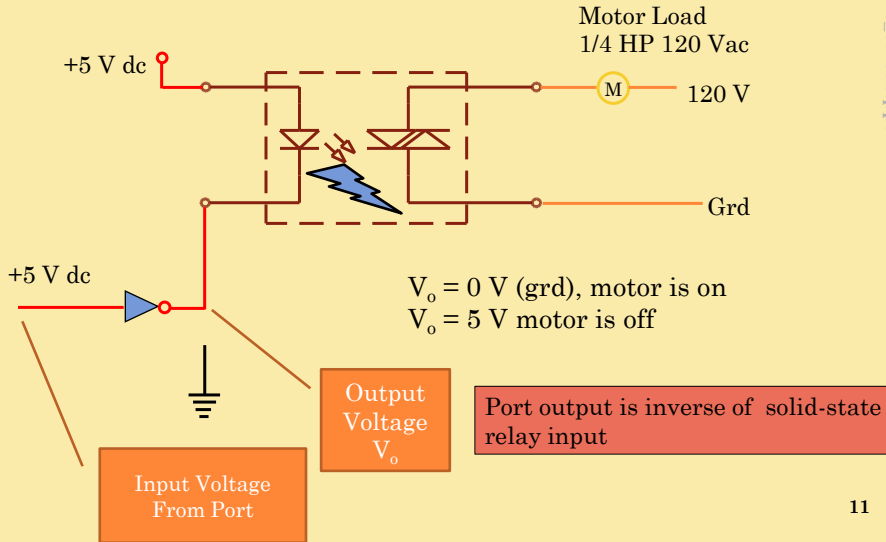

DIGITAL INTERFACES

Electromechanical Relays

Lesson 9_et438b.pptx

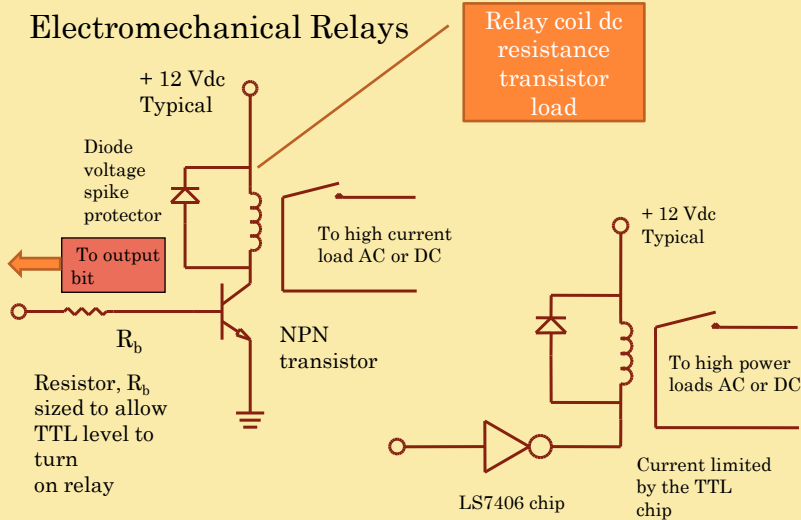


Relay interface using open collector TTL inverter

DIGITAL INPUT INTERFACES

Interface should limit currents and voltage levels to TTL limits


Mechanical switch interfacing

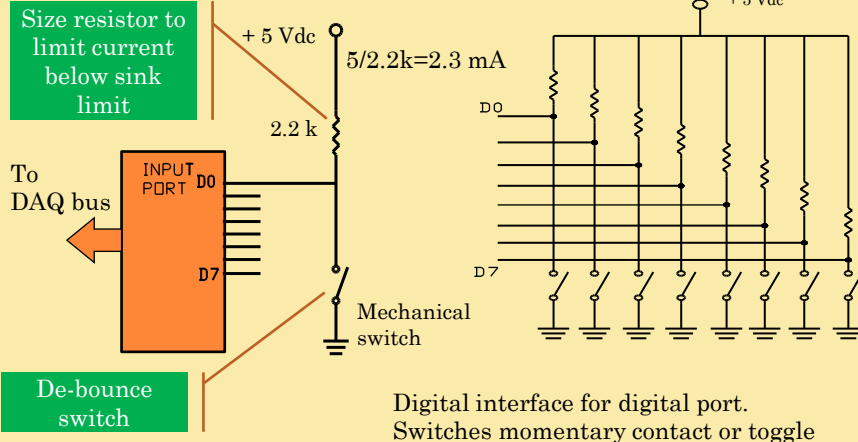

Lesson 9_cet438b.pptx

DIGITAL INTERFACE: NON-TTL LEVELS

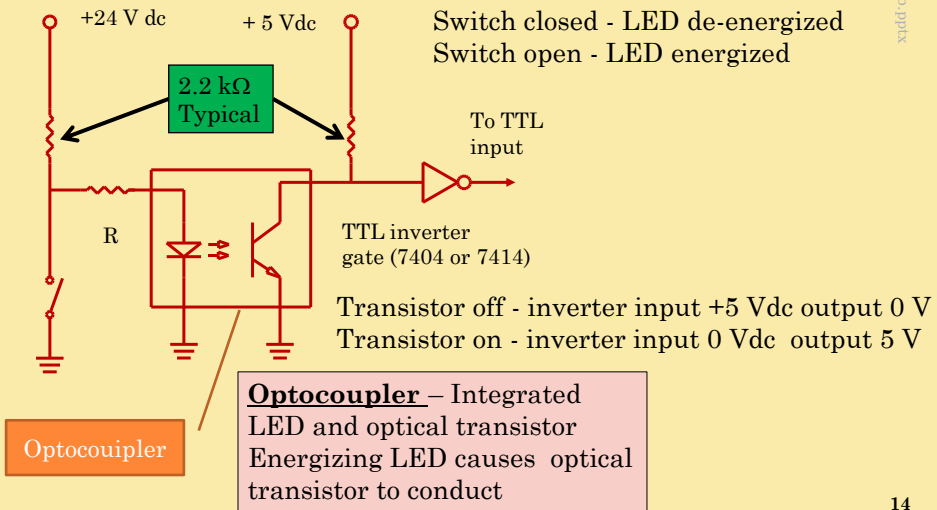
Use Optocoupler to isolate high voltages from TTL levels



Lesson 9_cet438b.pptx

INTERFACE EXAMPLE

 Determine the logic levels and currents in the digital interface circuit shown below. Assume that the optocoupler diode has an on-state voltage drop of 1.4 V and the optical transistor has an on-state collector-to-emitter drop of 0.4 V.



Lesson 9_et438b.pptx

15


INTERFACE EXAMPLE SOLUTION

Device Specification 4N35

I_f = continuous forward current: 60 mA

I_c = continuous collector current: 150 mA

Source voltage isolation: 7500 V peak

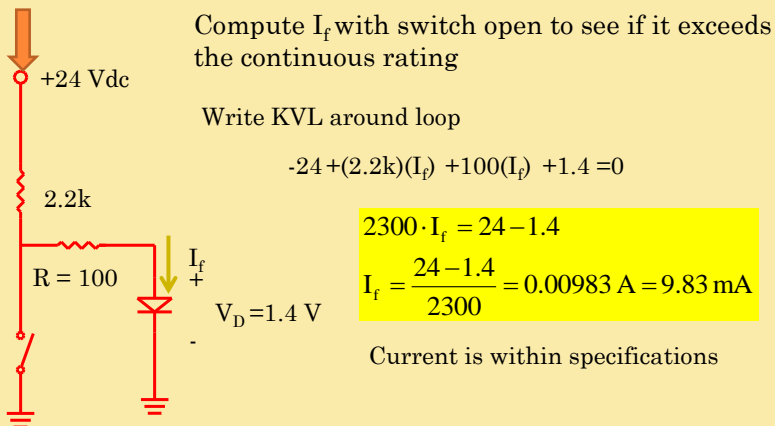


Lesson 9_et438b.pptx

16

INTERFACE EXAMPLE SOLUTION (CONTINUED)

 With switch closed, LED is shorted out so $I_f=0$. Switch must be open for optical transistor to conduct



7404 Specifications

I_{OH} = maximum source current from output: **400 μ A**

I_{OL} = maximum sink current into output: **16 mA**

I_{IL} = current flowing out of input when logic low V level (0.4 V) is applied: **1.6 mA** (1 unit load)

Assume optical transistor is in saturation

Find I_C and determine if it is below 150 mA

$$I_C = I_L + I_{IL}$$

Find I_L from KVL around collector-emitter loop

$$-5 + (2.2k)(I_L) + 0.4 = 0$$

$$I_L = \frac{5 - 0.4}{2.2k} = 2.1 \text{ mA}$$

$$I_C = 2.1 \text{ mA} + 1.6 \text{ mA} = 3.7 \text{ mA} \leftarrow \text{Below maximum}$$


Lesson 9_etf438b.pptx

17

INTERFACE EXAMPLE SOLUTION (CONTINUED)

Determine the interface logic.

 When optocoupler transistor conducts, the 7404 input is logic low, therefore the inverter output is high. See table below




Switch Position	LED	Transistor	7404 Input	7404 Output
open	on	on	Low (0.4 V)	High (4.6)
closed	off	off	High (5 V)	Low (0.4 V)

Lesson 9_etf438b.pptx

18

ELECTROMECHANICAL RELAY EXAMPLE

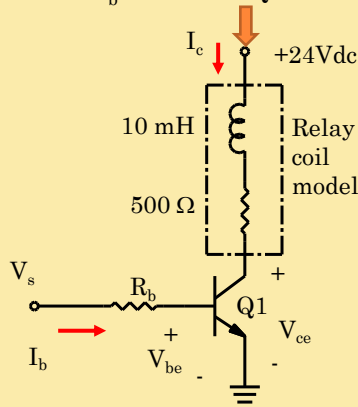Size R_b such that Q1 will activate with a TTL input



Transistor Parameters, Q1
(2N3904)

$$h_{FE} = 200 \text{ (nominal)}$$

$$V_{ce(sat)} = 0.2 \text{ V}$$

$$V_{be(sat)} = 0.8 \text{ V}$$

Assume transistor is in saturation and compute the value of I_c

Write a KVL equation around the collector-emitter circuit

$$-24 + 500(I_c) + V_{CE(sat)} = 0$$

$$-24 + 500(I_c) + 0.2 = 0$$

$$500I_c = 24 - 0.2$$


$$I_c = \frac{24 - 0.2}{500} = 47.6 \text{ mA}$$

Lesson 9_et438b.pptx

19

ELECTROMECHANICAL RELAY EXAMPLE (CONTINUED)

 Relate the collector current, I_c , to the base current I_b using the dc gain, h_{FE} .



The parameter, h_{FE} also known as β is:

$$h_{FE} = \frac{I_c}{I_b} = 200$$

Dc gain drops in saturation. Use $h_{FE}/10$ to account for this phenomena

$$\frac{h_{FE}}{10} = \frac{200}{10} = \frac{I_c}{I_b}$$

$$20 = \frac{I_c}{I_b} \Rightarrow I_b = \frac{I_c}{20} = \frac{47.6 \text{ mA}}{20} = 2.38 \text{ mA}$$


$$I_b = 2.38 \text{ mA}$$

Lesson 9_et438b.pptx

20

ELECTROMECHANICAL RELAY EXAMPLE (CONTINUED)

 Find value of R_b from a KVL equation around the base-emitter circuit



Assume a TTL high level of 4.8 V
Remember $V_{be(sat)} = 0.8 \text{ V}$

$$-V_s + I_b(R_b) + V_{be(sat)} = 0$$

$$R_b = \frac{4.8 \text{ V} - 0.8 \text{ V}}{2.38 \text{ mA}} = 1.68 \text{ k}\Omega$$

Ans


Note: this value is above the maximum TTL source current of 400 μA .

Drive Q1 from open-collector inverter

Lesson 9_et438b.pptx

ELECTROMECHANICAL RELAY EXAMPLE (CONTINUED)

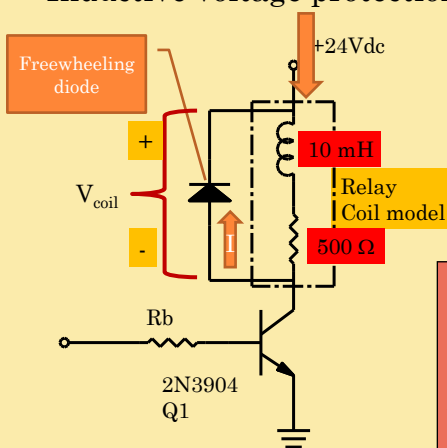Inductive voltage protection using freewheeling diodes



Cutting-off Q1 reduces I_c to zero

Coil voltage changes polarity due to induction

Collapsing magnetic field produces I

Diode D1 provides a path for the current induced when the transistor is switched off. It also clamps the induced voltage to the forward drop of the diode. (0.7 V)



Lesson 9_et438b.pptx

SIMULATION RESULTS-LTSPICE

23

Simulation without diode



Circuit simulated

  

Lesson 9_et438b.pptx

SIMULATION RESULTS-LTSPICE

Simulation with diode

  

Lesson 9_et438b.pptx

24

SOFTWARE CONTROL OF DIGITAL I/O

Individual bit of an output byte can be toggled by the application of a binary mask number and the appropriate bit-wise logic function.

These functions include: OR, AND, XOR

Procedure:


1.) Identify present port binary pattern
2.) Determine desired port binary pattern
3.) Select appropriate bitwise operator
4.) Determine correct mask value
5.) Apply bitwise operator to present pattern and mask to create desired pattern.

Lesson 9_et438b.pptx

25

SOFTWARE CONTROL EXAMPLE

 Example: An 8 bit digital output port drives a group of 8 LEDs through TTL inverters.




Determine the binary byte value that will cause LEDs 0, 3, 5, 6 to light. Convert this byte to a decimal value.

Lesson 9_et438b.pptx

26

SOFTWARE CONTROL EXAMPLE SOLUTION

 

Answer

To light the LEDs, port outputs must be Logic 1 (5 Vdc) input to the inverting buffer. This causes the inverter output to go to a logic 0 (0 V dc) sinking current through the inverter.

Lesson 9_et438b.pptx

Bit	7							0
	0	1	1	0	1	0	0	1

Convert to decimal

$$1 \cdot 2^6 + 1 \cdot 2^5 + 1 \cdot 2^3 + 1 \cdot 2^0 = 64 + 32 + 8 + 1 = 105$$

27

SOFTWARE CONTROL EXAMPLE SOLUTION

Determine the binary mask value and logic function that will toggle off LED 5 yet leave the other LEDs in their original state.

New byte value

0	1	0	0	1	0	0	1
---	---	---	---	---	---	---	---

Note: Bit 5 (the third bit from the left) is highlighted in red.

Answer

Use AND function and a mask value that has a logic low bit in bit location 5.

	0	1	1	0	1	0	0	1	original
AND	0	1	0	0	1	0	0	1	mask
	0	1	0	0	1	0	0	1	desired

Note: Bit 5 (the third bit from the left) is highlighted in red in the original and desired rows.

Lesson 9_et438b.pptx

28


SOFTWARE CONTROL EXAMPLE SOLUTION

Determine the decimal value of the mask value from above.

$$\text{Mask } 01001001 = 1 \cdot 2^6 + 1 \cdot 2^3 + 1 = 73$$

Now use a mask value and a logic function to turn on LEDs 1 and 2 while leaving the others unchanged.

Answer

 


Use the OR function and set the bits in positions 1 and 2 in the mask to the high position. Make all the other bit values 0 to complete the mask.

29

SOFTWARE CONTROL EXAMPLE SOLUTION

Toggle bits 1 and 2

 

XOR function could also be used to toggle bits if a different mask value is used. Use the XOR function to turn all LEDs off.

30

SOFTWARE CONTROL EXAMPLE SOLUTION

Review of XOR logic $Y = A \oplus B$


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

Like bits produce logic 0
Unlike bits produce logic 1

Lesson 9_et438b.pptx

Answer

 Copy the original byte value and use it as the mask value.
Using the XOR bit-wise logic function will set all bits low.



31

SOFTWARE CONTROL EXAMPLE SOLUTION

XOR Mask Result


	7							0	
	0	1	0	0	1	1	1	1	original
XOR	0	1	0	0	1	1	1	1	mask
	0	0	0	0	0	0	0	0	desired

Lesson 9_et438b.pptx

Example Summary

- 1.) AND Function with 0 bit in mask resets output bit
- 2.) OR Function with 1 bit in mask sets output bit
- 3.) XOR Function with opposite bit value from original set output bit
XOR with same value as original value resets output bit

32

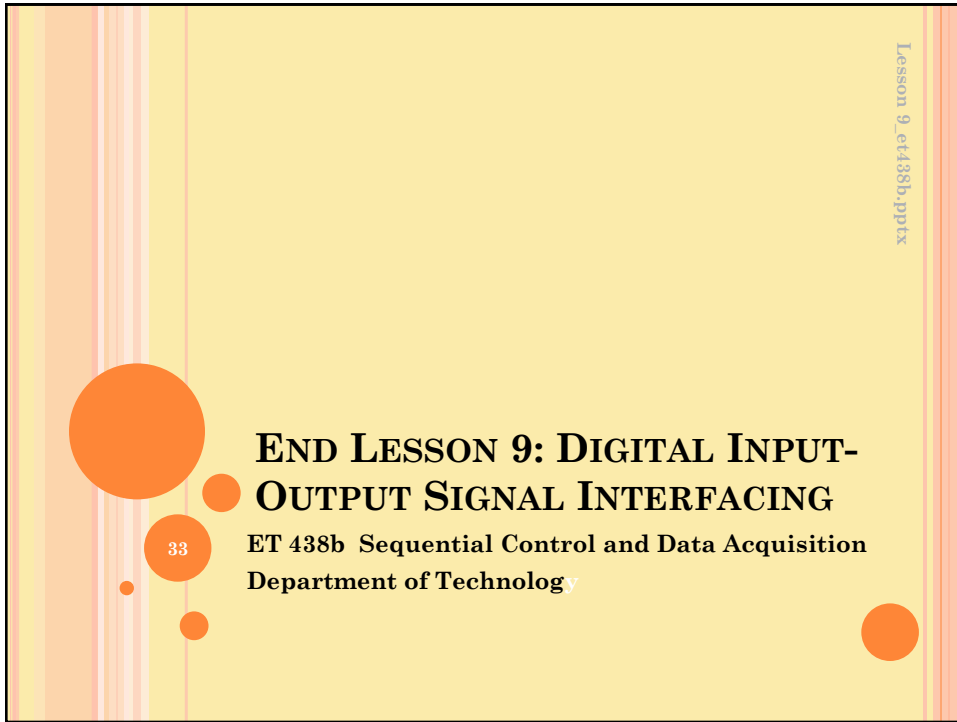

Lesson 9_et438b.pptx

END LESSON 9: DIGITAL INPUT- OUTPUT SIGNAL INTERFACING

33 ET 438b Sequential Control and Data Acquisition
Department of Technology