

Nodal Analysis (General Approach)

This method employs KCL's at network nodes and works best when network has mostly current sources.


- 1.) Determine the number of nodes in the network.
- 2.) Pick a reference node and assign voltages ($V_1, V_2, \dots$) to all other nodes.
- 3.) Apply KCL at each node except the reference node.
- 4.) Solve resulting equations for node voltages.

Warning:

Do not write a KCL at a node connected to a voltage source. (Its current can't be found with ohms Law)

Do not write a KVL through a current source. (Its voltage can't be found with ohms Law)

ex /

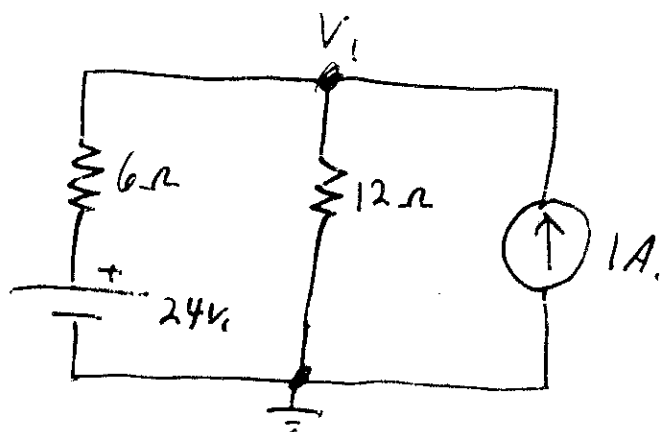


Apply nodal analysis:

- 1.) Circuit has 2 nodes
- 2.) Label nodes: V_1

(Continued)

ex/ continued

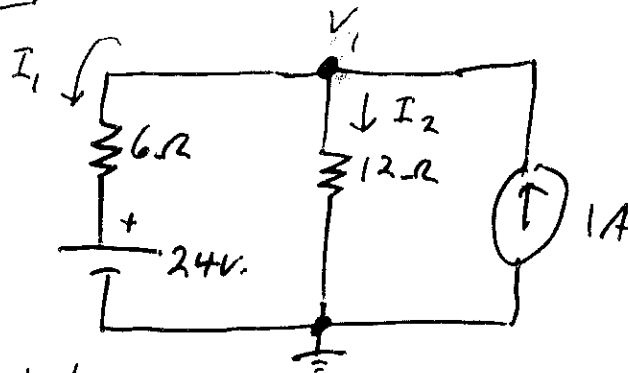

subst:

$$1 = \frac{V_1 - 24}{6} + \frac{V_1}{12}$$

solve for V_1 :

$$12 = 2(V_1 - 24) + V_1$$

$$12 = 3V_1 - 48$$


$$V_1 = \frac{60}{3} = \boxed{20V_1}$$

Substituting into I_1 and I_2 eqns. gives:

$$I_1 = \frac{V_1 - 24}{6} = \frac{20 - 24}{6} = \frac{-4}{6} = \boxed{-0.667A.}$$

$$I_2 = \frac{V_1}{12} = \frac{20}{12} = \boxed{1.667A.}$$

ex/

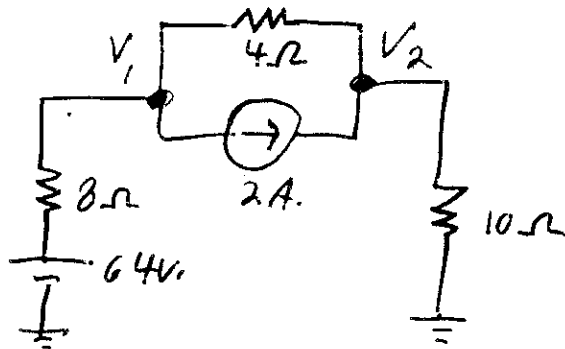


Find all I and V for ckt.

Solution:

1.) Determine the number of nodes requiring KCL's.
(2 nodes)

2.) Label nodes: V_1 & V_2

3.) Apply KCL: at V_1 & V_2

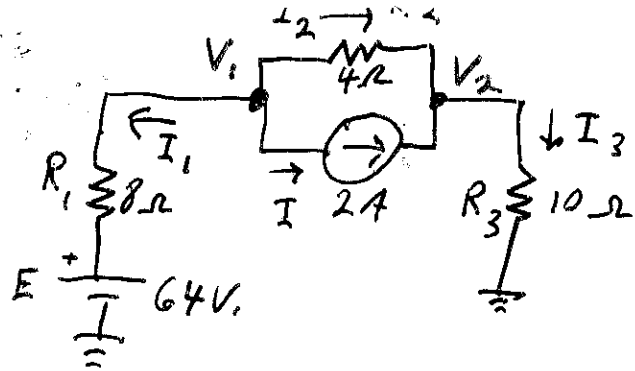

KCL at node V_1 :

$$I + I_1 + I_2 = 0$$

Apply Ohm's Law:

$$I_1 = \frac{V_1 - E}{R_1}$$

$$I_2 = \frac{V_1 - V_2}{R_2}$$

note: voltage on side of R that I enters

← minus voltage on side of R that I leaves

Now substitute into KCL eqn:

$$I + \frac{V_1 - E}{R_1} + \frac{V_1 - V_2}{R_2} = 0$$

$$2 + \frac{V_1 - 64}{8} + \frac{V_1 - V_2}{4} = 0 \quad \leftarrow \text{multiply both sides by 8}$$

$$16 + V_1 - 64 + 2V_1 - 2V_2 = 0$$

$$3V_1 - 2V_2 = 48 \quad \leftarrow \text{eqn. ①}$$

KCL at node V_2 :

$$I_2 + I = I_3$$

Apply Ohm's Law:

$$I_2 = \frac{V_1 - V_2}{R_2}, \quad I_3 = \frac{V_2 - 0}{R_3}$$

Substitute into KCL:

$$\frac{V_1 - V_2}{R_2} + I = \frac{V_2}{R_3}$$

$$\frac{V_1 - V_2}{4} + 2 = \frac{V_2}{10}$$

← multiply both sides by 20

$$5V_1 - 5V_2 + 40 = 2V_2$$

$$5V_1 - 7V_2 = -40 \quad \text{eqn. (2)}$$

Now solve eqns (1) and (2) simultaneously for V_1 and V_2 :

$$3V_1 - 2V_2 = 48 \quad \text{eqn (1)}$$

$$5V_1 - 7V_2 = -40 \quad \text{eqn (2)}$$

$$V_1 = \frac{\begin{vmatrix} 48 & -2 \\ -40 & -7 \end{vmatrix}}{\begin{vmatrix} 3 & -2 \\ 5 & -7 \end{vmatrix}} = \frac{-336 - (80)}{-21 - (-10)} = \frac{-416}{-11} = \boxed{37.82 \text{ V.}}$$

$$V_2 = \frac{\begin{vmatrix} 3 & 48 \\ 5 & -40 \end{vmatrix}}{-11} = \frac{-120 - 240}{-11} = \frac{-360}{-11} = \boxed{32.73 \text{ V.}}$$


Can now use ohm's law to find currents if desired:

$$I_1 = \frac{V_1 - E}{R_1} = \frac{37.82 - 64}{8} = \boxed{-3.273 \text{ A.}}$$

$$I_2 = \frac{V_1 - V_2}{R_2} = \frac{37.82 - 32.73}{4} = \boxed{1.273 \text{ A.}}$$

$$I_3 = \frac{V_2 - 0}{R_3} = \frac{V_2}{R_3} = \frac{32.73}{10} = \boxed{3.273 \text{ A.}}$$

EX

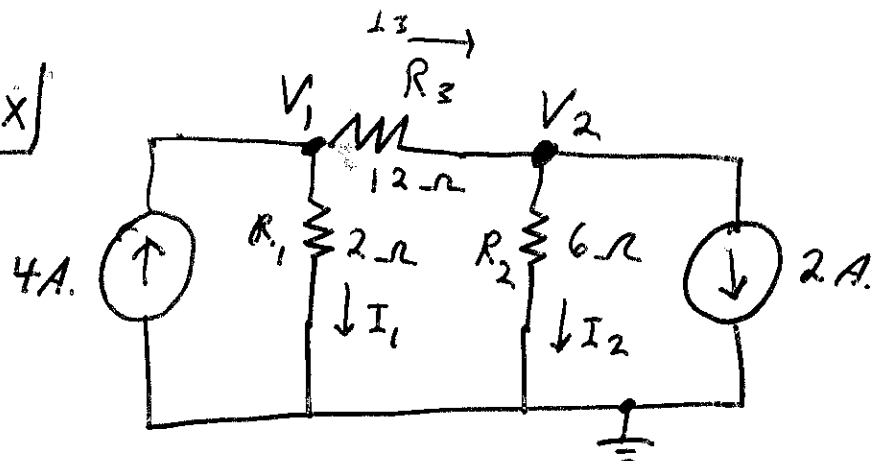

Find node voltages:

1.) Determine the number nodes requiring KCLs.
There are 2 non-reference nodes

2.) Label nodes: V_1 and V_2

3.) Apply KCL's at V_1 & V_2 nodes:

KCL at node V_1 :

$$4 = I_1 + I_3$$

Apply ohm's law: $I_1 = \frac{V_1 - 0}{2}$, $I_3 = \frac{V_1 - V_2}{12}$

Now substitute into KCL eqn:

$$4 = \frac{V_1}{2} + \frac{V_1 - V_2}{12}$$

$$48 = 6V_1 + V_1 - V_2$$

$$-7V_1 + V_2 = -48$$

$$7V_1 - V_2 = 48 \quad \leftarrow \text{eqn ①}$$

KCL at node V_2 :

$$I_3 = I_2 + 2$$

Apply Ohm's Law: $I_3 = \frac{V_1 - V_2}{12}$, $I_2 = \frac{V_2 - 0}{6}$

Substitute into KCL eqn:

$$\frac{V_1 - V_2}{12} = \frac{V_2}{6} + 2$$

$$V_1 - V_2 = 2V_2 + 24$$

$$V_1 - 3V_2 = 24 \quad \leftarrow \text{eqn (2)}$$

4.) Now solve eqn. (1) and (2) simultaneously:

$$7V_1 - V_2 = 48 \quad \leftarrow \text{eqn (1)}$$

$$V_1 - 3V_2 = 24 \quad \leftarrow \text{eqn (2)}$$

$$V_1 = \frac{\begin{vmatrix} 48 & -1 \\ 24 & -3 \end{vmatrix}}{\begin{vmatrix} 7 & -1 \\ 1 & -3 \end{vmatrix}} = \frac{-144 - (-24)}{-21 - (-1)} = \frac{-120}{-20} = \boxed{6 \text{ V.}}$$

$$V_2 = \frac{\begin{vmatrix} 7 & 48 \\ 1 & 24 \end{vmatrix}}{-20} = \frac{168 - 48}{-20} = \frac{120}{-20} = \boxed{-6 \text{ V.}}$$


If desired, I_1 , I_2 & I_3 can be found:

$$I_1 = \frac{V_1}{2} = \frac{6}{2} = \boxed{3 \text{ A}} \quad I_2 = \frac{V_2}{6} = \frac{-6}{6} = \boxed{-1 \text{ A}}$$

$$I_3 = \frac{V_1 - V_2}{12} = \frac{6 - (-6)}{12} = \frac{12}{12} = \boxed{1 \text{ A}}$$

Supernode

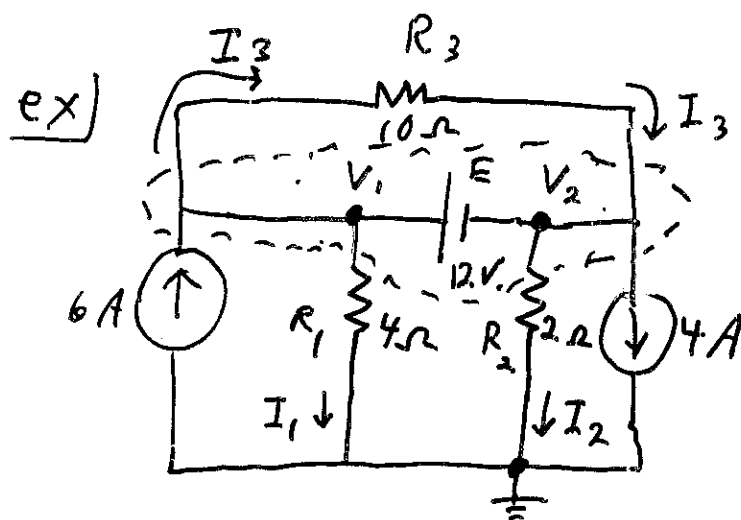If there are voltage sources in the network, do not write a KCL equation at any node adjacent to a voltage source. If necessary combine more than one node into a supernode or region and then write a KCL for the currents entering and leaving the supernode or region. The current passing thru the voltage source should not be included in the KCL.



Find V_1 and V_2 by nodal analysis.

Since a voltage source is present, it is necessary to form a Supernode.

(Note: all of the currents crossing the boundary of the supernode can be found with Ω law or are given)

KCL: for supernode

$$\sum I_{\text{entering}} = \sum I_{\text{leaving}}$$

$$6A. + I_3 = I_3 + I_1 + I_2 + 4A.$$

$$I_1 + I_2 = 6 - 4 = 2$$

Apply ohm's law to get a node voltage eqn:

$$I_1 = \frac{V_1 - 0}{4}, \quad I_2 = \frac{V_2 - 0}{2}$$

Substituting:

$$\frac{V_1}{4} + \frac{V_2}{2} = 2$$

$$V_1 + 2V_2 = 8 \quad \text{eqn (1)}$$

Get another equation by relating V_1 and V_2 to the value of the voltage source.

$$V_1 - V_2 = E$$

$$V_1 - V_2 = 12 \quad \text{eqn (2)}$$

Now solve eqns (1) and (2) simultaneously:

$$V_1 + 2V_2 = 8 \quad \leftarrow \text{eqn. (1)}$$

$$V_1 - V_2 = 12 \quad \leftarrow \text{eqn. (2)}$$

$$V_1 = \frac{\begin{vmatrix} 8 & 2 \\ 12 & -1 \end{vmatrix}}{\begin{vmatrix} 1 & 2 \\ 1 & -1 \end{vmatrix}} = \frac{-8 - 24}{-1 - 2} = \frac{-32}{-3} = \boxed{10.67 \text{ V}}$$


$$V_2 = \frac{\begin{vmatrix} 1 & 8 \\ 1 & 12 \end{vmatrix}}{-3} = \frac{12 - 8}{-3} = \frac{4}{-3} = \boxed{-1.333 \text{ V}}$$

$$I_1 = \frac{V_1}{4} = \frac{10.67}{4} = \boxed{2.667 \text{ A}} \quad I_2 = \frac{V_2}{2} = \frac{-1.333 \text{ V}}{2} = \boxed{-0.667 \text{ A}}$$

$$I_3 = \frac{V_1 - V_2}{10} = \frac{10.67 - (-1.333)}{10} = \boxed{1.2 \text{ A}}$$

Nodal Analysis with voltage sources

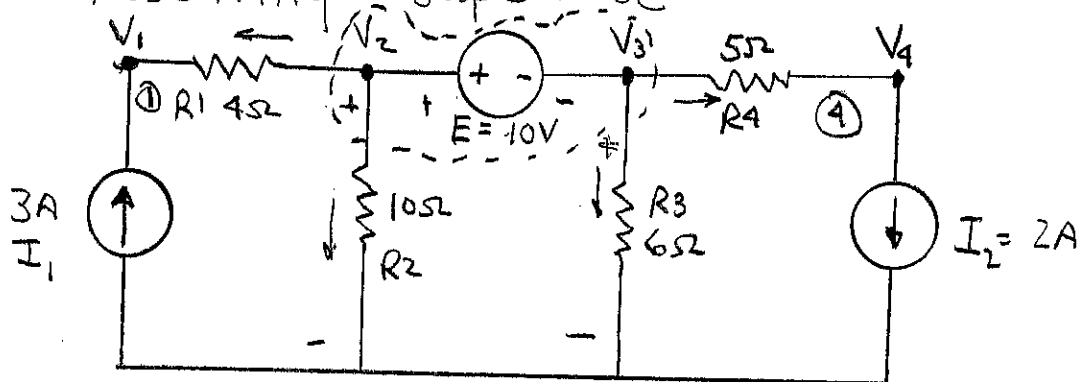Short voltage source and write KCL around resulting super-node



KCL at node 1

$$I_1 = \frac{V_1 - V_2}{R_1} \quad (1)$$

KCL at super node (assume all currents leave)

$$-I_{R1} - I_{R2} - I_{R3} - I_{R4} = 0 \rightarrow I_{R1} + I_{R2} + I_{R3} + I_{R4} = 0$$

write in terms of node voltages

$$\frac{V_2 - V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \frac{V_3 - V_4}{R_4} = 0 \quad (2)$$

Relate E to node voltages, KVL $V_2 - E - V_3 = 0 \Rightarrow E = 10V$

Assume all R current leave

$$V_2 - V_3 = E \Rightarrow V_2 - V_3 = 10 \quad (3)$$

KCL AT NODE 4

$$-I_{R4} - I_2 = 0, \quad I_{R4} = -I_2, \quad \frac{V_4 - V_3}{R_4} = -I_2 \quad (4)$$

$$3A = \frac{V_1 - V_2}{4} \quad (1)$$

$$\frac{V_2 - V_1}{4} + \frac{V_2}{10} + \frac{V_3}{6} + \frac{V_3 - V_4}{5} = 0 \quad (2)$$

$$3A = 0.25V_1 - 0.25V_2 \quad (1) \quad -0.25V_1 + 0.35V_2 + 0.3667V_3 - 0.2V_4 = 0 \quad (2)$$

$$(4) \quad \frac{V_4 - V_3}{5} = -2A$$

$$-0.2V_3 + 0.2V_4 = -2A$$

$$3A = 0.25V_1 - 0.25V_2$$

use Relationship $V_2 = 10 + V_3$ to eliminate V_2 from (1) & (2)

$$3 = 0.25V_1 - 0.25(10 + V_3)$$

$$3 = 0.25V_1 - 2.5 - 0.25V_3$$

$$0.25V_1 - 0.25V_3 = 5.5$$

-2-

Remove V_2 from equ. ②

$$-0.25V_1 + 0.35(10 + V_3) + 0.3667V_3 - 0.2V_4 = 0$$

$$-0.25V_1 + 3.5 + 0.35V_3 + 0.3667V_3 - 0.2V_4 = 0$$

$$-0.25V_1 + 0.7167V_3 - 0.2V_4 = -3.5$$

$$-0.2V_3 + 0.2V_4 = -2$$

Collect equations

$$0.25V_1 - 0.25V_3 + 0V_4 = 5.5$$

$$-0.25V_1 + 0.7167V_3 - 0.2V_4 = -3.5$$

$$0V_1 - 0.2V_3 + 0.2V_4 = -2$$

Note symmetry of coefficients, diagonals are

sum of conductances at nodes

off-diagonals neg of conductances between nodes

Solve using Cramer's rule or TI-85


TI-85 solution

$$V_1 = \underline{\underline{22V}} \quad V_3 = \underline{\underline{0}} \quad V_4 = \underline{\underline{-10}}$$

To find V_2 use $V_2 = 10 + V_3 \Rightarrow V_2 = 10 + 0 = \underline{\underline{10V}}$

Ex

Ladder network by nodal analysis

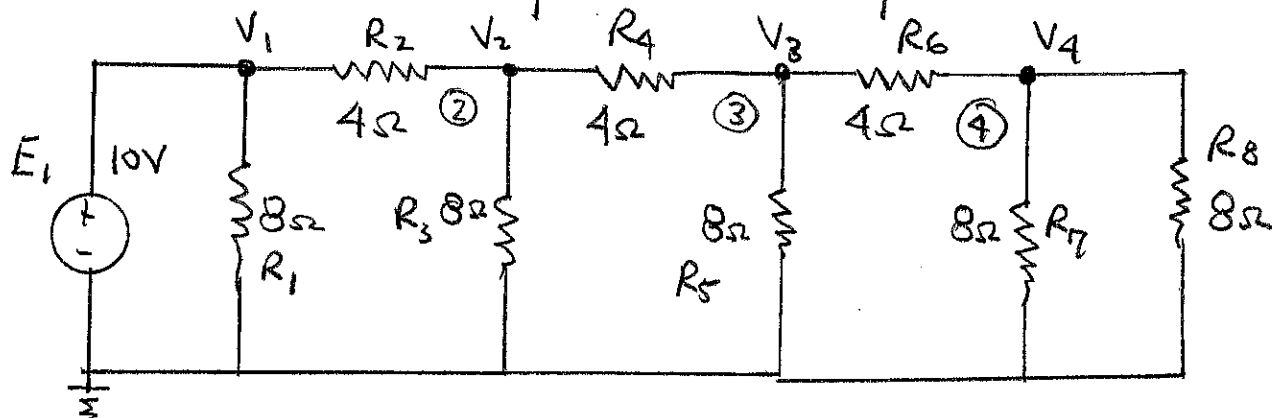

Voltage known at V_1 $V_1 = E_1$

WRITE KCL AT OTHER NODES

3- node 2 Assume all currents leave nodes

$$\frac{V_2 - V_1}{R_2} + \frac{V_2}{R_3} + \frac{V_2 - V_3}{R_4} = 0 \quad \frac{V_2 - V_1}{4} + \frac{V_2}{8} + \frac{V_2 - V_3}{4} = 0 \quad (1)$$

node 3

$$\frac{V_3 - V_2}{R_4} + \frac{V_3}{R_5} + \frac{V_3 - V_4}{R_6} = 0 \quad \frac{V_3 - V_2}{4} + \frac{V_3}{8} + \frac{V_3 - V_4}{4} = 0 \quad (2)$$

node 4

$$\frac{V_4 - V_3}{R_6} + \frac{V_4}{R_7} + \frac{V_4}{R_8} = 0 \quad \frac{V_4 - V_3}{4\Omega} + \frac{2V_4}{8} \quad (3)$$

Simplify (1) (2) (3) and substitute $V_1 = E_1 = 10$

$$(1) \quad 0.25V_2 - 0.25V_1 + 0.125V_2 + 0.25V_2 - 0.25V_3 = 0$$

$$-0.25(10) + 0.625V_2 - 0.25V_3 = 0$$

$$0.625V_2 - 0.25V_3 = 2.5$$

$$(2) \quad 0.25V_3 - 0.25V_2 + 0.125V_3 + 0.25V_3 - 0.25V_4 = 0$$

$$-0.25V_2 + 0.625V_3 - 0.25V_4 = 0$$

(3)

$$0.25V_4 - 0.25V_3 + 0.25V_4 = 0$$

$$-0.25V_3 + 0.5V_4 = 0$$

Collected equations (1) (2) (3)
Place in standard form

$$0.625V_2 - 0.25V_3 + 0V_4 = 2.5$$

$$-0.25V_1 + 0.625V_3 - 0.25V_4 = 0$$

$$0V_1 + 0.25V_3 + 0.5V_4 = 0$$

Note symmetry of equations check signs of diagonal and off-diagonal

Solve using Cramer's rule or other numerical method.

4- USING "SOLVE" Function of TI-85

$$V_2 = \underline{5V} \quad \underline{V_1 = 10} \text{ from inspection}$$

$$V_3 = \underline{2.5}$$

$$V_4 = \underline{1.25}$$

Calculate Currents in R_1, R_3, R_5, R_7 & R_8

$$I_{R8} = \frac{V_4}{R_8} = \frac{1.25V}{8} = 0.1563A$$

$$I_{R3} = \frac{V_2}{R_3} = \frac{5}{8} = 0.625A$$

$$I_{R7} = I_{R8} = 0.1563A$$

$$I_{R1} = \frac{V_1}{R_1} = \frac{10}{8} = 1.25A$$


$$I_{R5} = \frac{V_3}{R_5} = \frac{2.5}{8} = 0.3125A$$

CURRENTS DIVIDE BY 2 with each step through network

BASIC CIRCUIT USED IN DIGITAL-TO-ANALOG CONVERTERS
CALLED R-2R Ladder

Resistive Bridges

Consider a basic dc voltage divider.

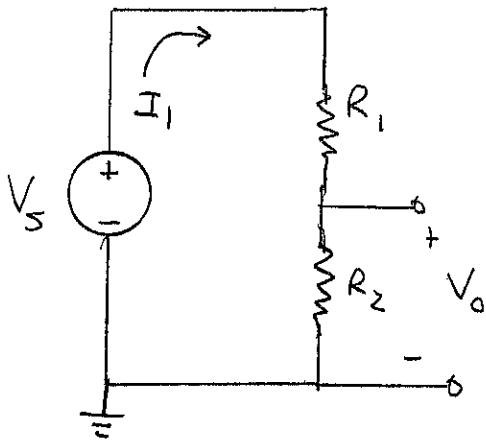


$$V_o = \frac{R_2}{R_1 + R_2} V_s$$

Increasing R_2 increases V_o

Decreasing R_2 decreases V_o
for Fixed V_s & R_1

-5-

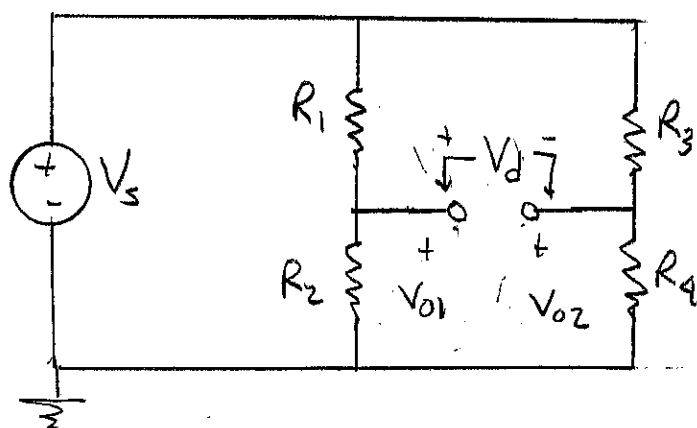Consider 2 voltage dividers supplied from same source.



find V_{01} and V_{02}

$$V_{01} = \frac{R_2}{R_1 + R_2} V_s$$

$$V_{02} = \frac{R_4}{R_3 + R_4} V_s$$

Difference in voltage $V_d = V_{01} - V_{02}$

When $V_{01} = V_{02}$ Then

$$\frac{R_2}{R_1 + R_2} V_s = \frac{R_4}{R_3 + R_4} V_s \quad \frac{R_2}{R_1 + R_2} = \frac{R_4}{R_3 + R_4}$$

Bridge is considered


Balanced when $V_{01} = V_{02}$

$$\frac{R_2}{R_1} + 1 = \frac{R_4}{R_3} + 1 \Rightarrow \frac{R_2}{R_1} = \frac{R_4}{R_3}$$

When Ratio of divider resistors is equal

$V_d = 0$ $V_d = 0$ means no current will flow

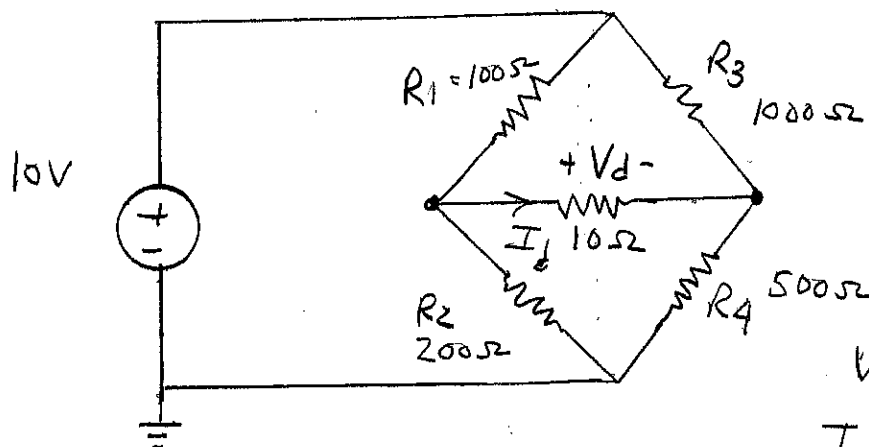When $\frac{R_2}{R_1} \neq \frac{R_4}{R_3}$ must solve circuit using mesh or node equations



$$\frac{R_1}{R_2} = \frac{100\Omega}{200\Omega} = \frac{1}{2}$$

$$\frac{R_3}{R_4} = \frac{1000\Omega}{500\Omega} = 2$$


$$\frac{1}{2} \neq 2$$

$V_d \neq 0$ correct


$I_d \neq 0$

Bridge Networks

General Form of a Bridge Circuit:

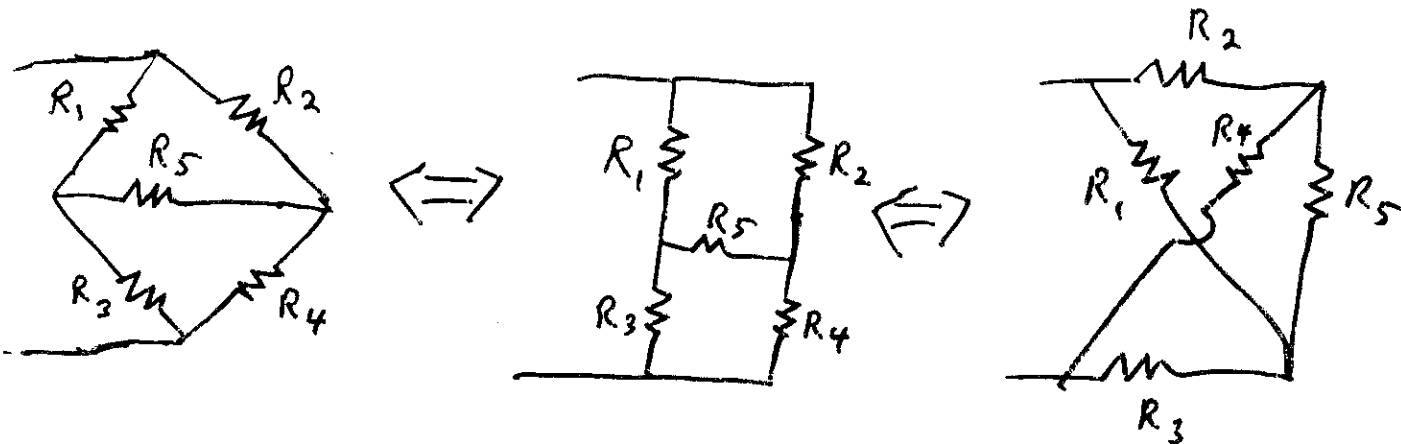

ex/

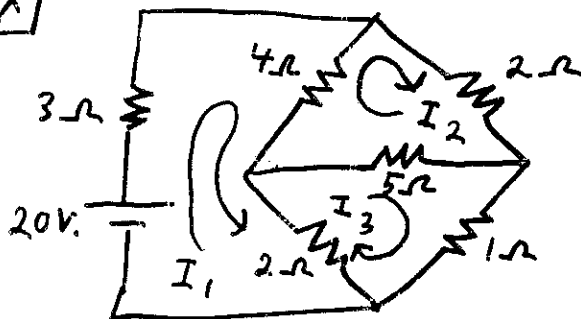

find current through each resistor.

Apply mesh analysis for 3 meshes.

KVL mesh 1:

$$-20 + 3I_1 + 4(I_1 - I_2) + 2(I_1 - I_3) = 0$$

$$9I_1 - 4I_2 - 2I_3 = 20 \leftarrow \text{eqn. (1)}$$

KVL mesh 2:

$$4(I_2 - I_1) + 2I_2 + 5(I_2 - I_3) = 0$$

$$-4I_1 + 11I_2 - 5I_3 = 0 \leftarrow \text{eqn. (2)}$$

KVL mesh 3:

$$2(I_3 - I_1) + 5(I_3 - I_2) + 1(I_3) = 0$$

$$-2I_1 - 5I_2 + 8I_3 = 0 \leftarrow \text{eqn. (3)}$$

Now solve eqns. (1), (2) and (3) simultaneously

$$9I_1 - 4I_2 - 2I_3 = 20 \quad \leftarrow \text{eqn (1)}$$

$$4I_1 - 11I_2 + 5I_3 = 0 \quad \leftarrow \text{eqn (2) (multiplied by -1)}$$

$$2I_1 + 5I_2 - 8I_3 = 0 \quad \leftarrow \text{eqn (3) (multiplied by -1)}$$

$$I_1 = \frac{\begin{vmatrix} 20 & -4 & -2 \\ 0 & -11 & 5 \\ 0 & 5 & -8 \end{vmatrix}}{\begin{vmatrix} 9 & -4 & -2 \\ 4 & -11 & 5 \\ 2 & 5 & -8 \end{vmatrix}} = \boxed{4A}$$

$$I_2 = \frac{\begin{vmatrix} 9 & 20 & -2 \\ 4 & 0 & 5 \\ 2 & 0 & -8 \end{vmatrix}}{\begin{vmatrix} 9 & -4 & -2 \\ 4 & -11 & 5 \\ 2 & 5 & -8 \end{vmatrix}} = \boxed{2.667A}$$


$$I_3 = \frac{\begin{vmatrix} 9 & -4 & 20 \\ 4 & -11 & 0 \\ 2 & 5 & 0 \end{vmatrix}}{\begin{vmatrix} 9 & -4 & -2 \\ 4 & -11 & 5 \\ 2 & 5 & -8 \end{vmatrix}} = \boxed{2.667A}$$

The net current thru the 5Ω resistor is:

$$I_{5\Omega} = I_2 - I_3 = 2.667 - 2.667 = 0A$$

$$\text{The voltage } V_{5\Omega} = I_{5\Omega}(5\Omega) = 0(5\Omega) = 0$$

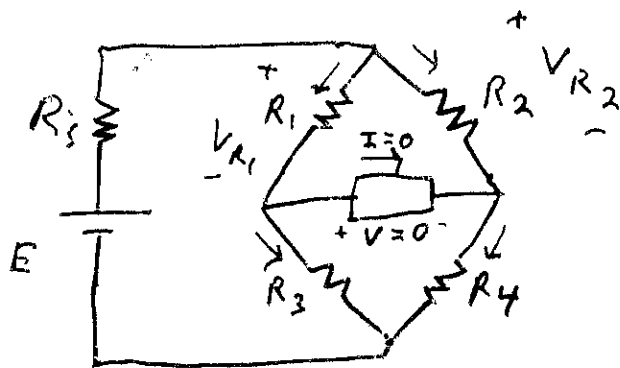A bridge network is said to be balanced when $I=0$ and $V=0$ for the center element.



For the balanced condition:

$$I=0, V=0$$

$$\text{Then } V = V_{R_2} - V_{R_1} \quad \text{or}$$

$$V_{R_1} = V_{R_2}$$

$$\text{Then } I_{R_1} R_1 = I_{R_2} R_2$$

$$\text{so } I_{R_1} = I_{R_2} \frac{R_2}{R_1} \quad \leftarrow \text{eqn (1)}$$

$$\text{Similarly, } V_{R_3} = V_{R_4}$$

$$I_{R_3} R_3 = I_{R_4} R_4 \quad \leftarrow \text{eqn. (2)}$$

Since $I=0$ at balance, then $I_{R_1} = I_{R_3}$ and $I_{R_2} = I_{R_4}$

Substituting eqn (1) into eqn (2) gives:

$$\left(I_{R_2} \frac{R_2}{R_1} \right) R_3 = I_{R_2} R_4$$

or re-arranging gives:


The condition for the bridge circuit to be balanced is :

$$\boxed{\frac{R_1}{R_3} = \frac{R_2}{R_4}}$$


This concept is used in measurement equipment. i.e. If the bridge is adjusted to a balanced condition, an unknown bridge arm R_x can be computed from the 3 known bridge arms.

Y- Δ (T- π) AND Δ -Y (π -T) Conversions

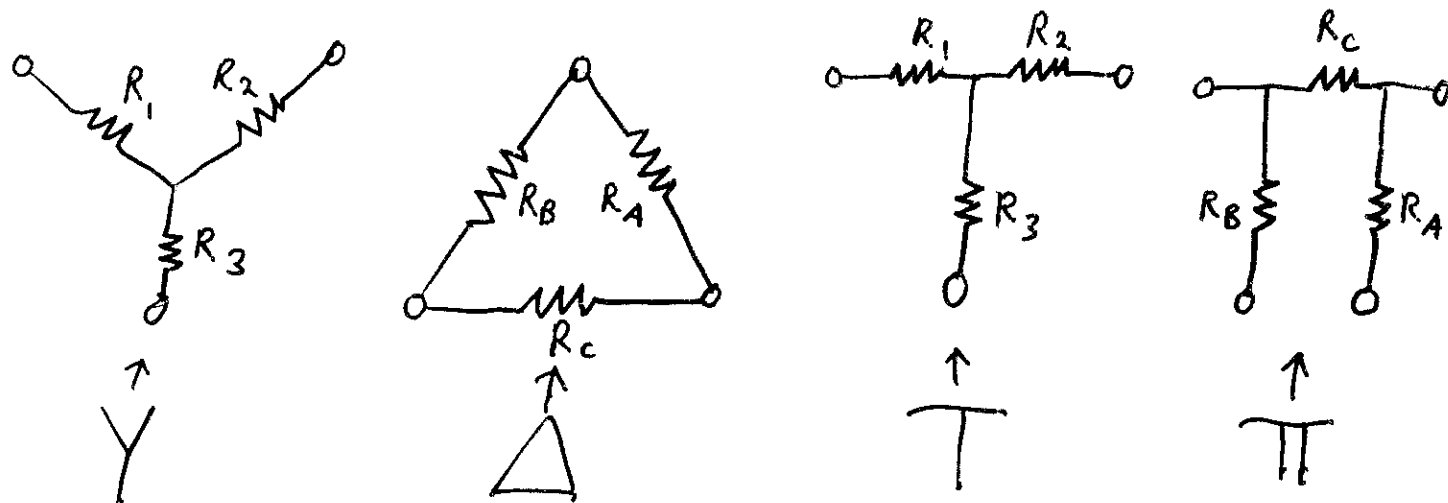Circuit analysis can sometimes be simplified by converting a circuit in one form to another equivalent form.



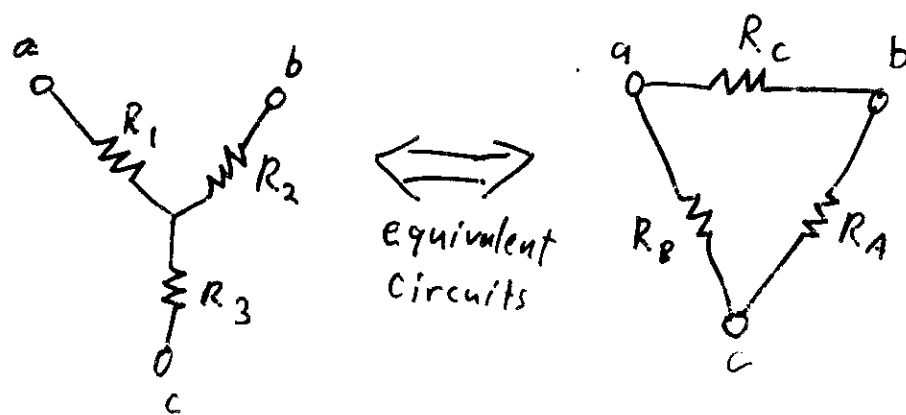The Y and the T are identical circuits that are drawn differently!
The Δ and the π are identical circuits that are drawn differently!



$\Delta \rightarrow Y$ Conversion:

$$R_1 = \frac{R_B R_C}{R_A + R_B + R_C} \quad R_2 = \frac{R_A R_C}{R_A + R_B + R_C} \quad R_3 = \frac{R_A R_B}{R_A + R_B + R_C}$$

$Y \rightarrow \Delta$ Conversion:

$$R_A = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1} \quad R_B = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2}$$
$$R_C = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_3}$$


For a Δ of three equal resistors, the value of each resistor of the equivalent Y is equal to three times the value of any resistor of the Y .

$$R_{\Delta} = 3 R_Y$$

$$R_Y = \frac{R_{\Delta}}{3}$$



When $R_1 = R_2 = R_3 = R_Y$
 $R_A = R_B = R_C = R_{\Delta}$

ex Find the total resistance R_T :

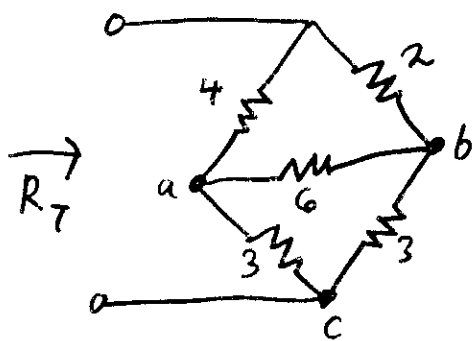

Note: None of the resistors are in parallel or series.

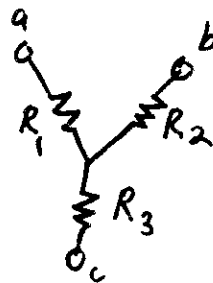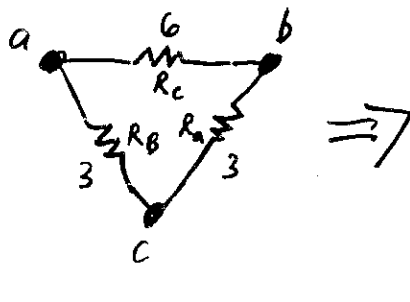In order to simplify the network we can replace the Δ section with a Y section




Using the conversion formulas to find R_1, R_2, R_3 gives:

$$R_1 = \frac{R_B R_C}{R_A + R_B + R_C} = \frac{(3)(6)}{3+3+6} = \frac{18}{12} = 1.5 \Omega$$

$$R_2 = \frac{R_A R_C}{R_A + R_B + R_C} = \frac{(3)(6)}{12} = \frac{18}{12} = 1.5 \Omega$$

$$R_3 = \frac{R_A R_B}{R_A + R_B + R_C} = \frac{(3)(3)}{12} = \frac{9}{12} = 0.75 \Omega$$

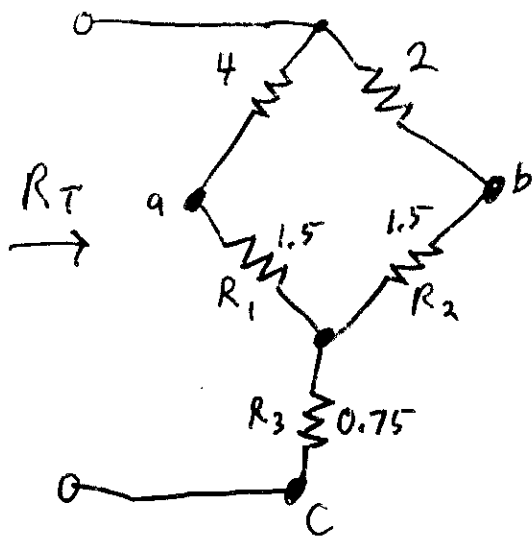Now re-draw the original ckt. with the Y network inserted in place of the Δ network.



In this new equivalent ckt. it is possible to use series and parallel resistor combining rules to simplify the network.

$$R_T = 0.75 + (R_1 + 4) \parallel (R_2 + 2)$$

$$R_T = 0.75 + \frac{(1.5 + 4)(1.5 + 2)}{(1.5 + 4) + (1.5 + 2)} = 0.75 + \frac{(5.5)(3.5)}{5.5 + 3.5}$$

$$R_T = 0.75 + 2.139$$

$$R_T = \boxed{2.889 \Omega}$$

Superposition Theorem


The Superposition Theorem states that the current through, or voltage across, an element in a linear bilateral network is equal to the algebraic sum of the currents or voltages produce independently by each source.

Super position Method:

To find a particular I or V in a multisource network (n sources): $S_1, S_2, \dots, S_n$


1. Kill all of the sources except S_1
(to kill a voltage source, replace it with a short ckt.)
(to kill a current source, replace it with an open ckt.)
2. Solve the resulting network for V and I ,
let these values equal: $V = V_1, I = I_1$
3. Kill all of the sources except S_2
4. solve the resulting network for V and I ,
let these values equal: $V = V_2, I = I_2$
5. Repeat steps 3 and 4 for sources $S_3, S_4, \dots, S_n$
6. The total values are the found:
$$V = V_1 + V_2 + V_3 + \dots + V_n$$
$$I = I_1 + I_2 + I_3 + \dots + I_n$$

ex/

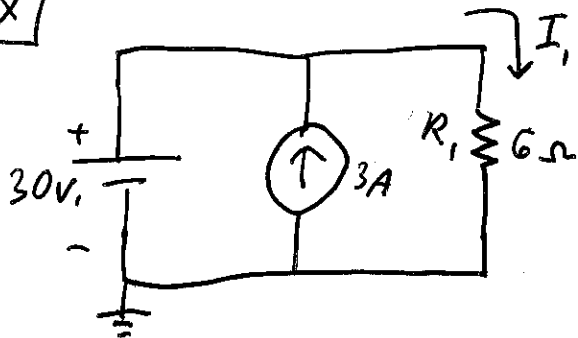

Find I_1 using
Superposition Theorem:

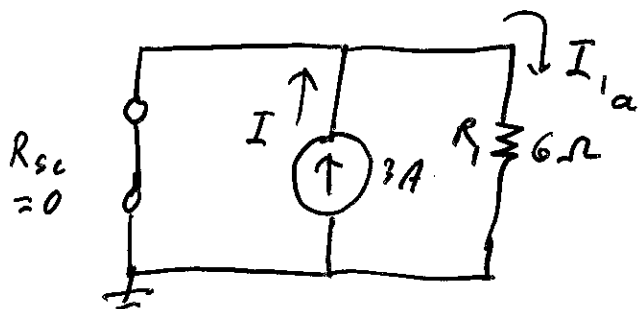1. kill 30V. source (replace it with a short ckt. $v=0$)




(note: I_{1a} is the part of
 I_1 due to the 3A.
Source)

2. Solve resulting network:

By Current Divider Rule: $I_{1a} = I \frac{R_{sc}}{R_1 + R_{sc}} = 3 \frac{0\Omega}{6 + 0} = 0 \text{ A.}$

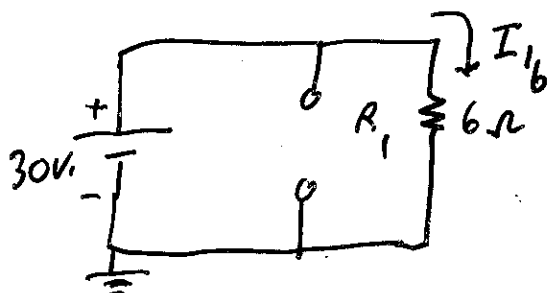3. Start with original ckt. and now kill 3A. source;
(replace 3A. source with open ckt. $I=0$)



(Note: I_{1b} is the part of
 I_1 due to 30V. source)

4. Solve resulting network:


$$I_{1b} = \frac{30V}{6\Omega} = 5A.$$

Now combine results:


$$I = I_{1a} + I_{1b} = 0 + 5 = \boxed{5A}$$

Note: Superposition principle does not work for Power computations.


ex)

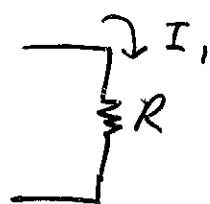

$$P_1 = I_1^2 R$$

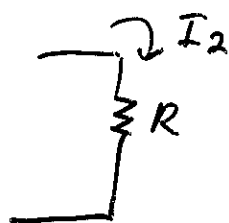

$$P_2 = I_2^2 R$$

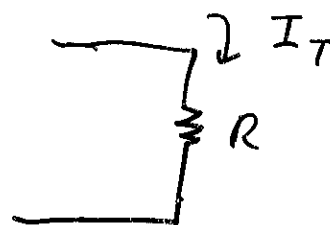

$$P_T = I_T^2 R$$

If superposition applied:

$$P_T = P_1 + P_2$$

Since $I_T = I_1 + I_2$

$$\text{Then } P_T = (I_1 + I_2)^2 R = (I_1^2 + I_2^2 + 2I_1 I_2) R$$

$$P_T = I_1^2 R + I_2^2 R + 2I_1 I_2 R$$


$$P_T = P_1 + P_2 + 2I_1 I_2 R \neq P_1 + P_2$$

Superposition only applies for linear functions. Power is a square law and therefore not linear.

So:


The total power delivered to a resistive element must be determined using the total current through or voltage across the element and cannot be determined by a simple sum of the power levels established by each source.

ex/

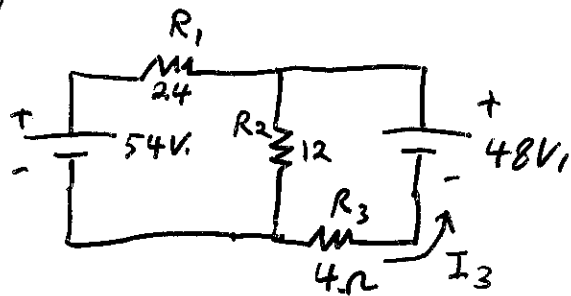

Find I_3 using superposition.

1.) Kill 48V, source;

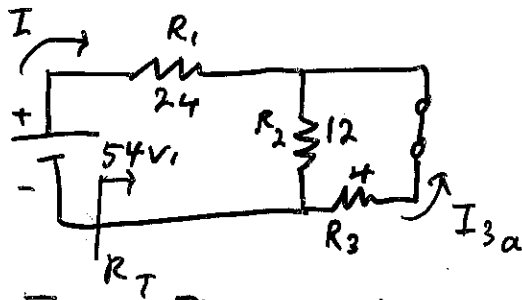


$$R_T = R_1 + R_2 \parallel R_3$$

$$R_T = 24 + \frac{(4)(12)}{4+12} = 24 + 3 = 27 \Omega$$

$$I = \frac{54}{R_T} = \frac{54}{27} = 2A.$$

By CDR: $I_{3a} = -I \frac{R_2}{R_2 + R_3} = -2 \frac{(12)}{12+4} = -\frac{24}{16} = -1.5A$

2.) Kill 54V, source;

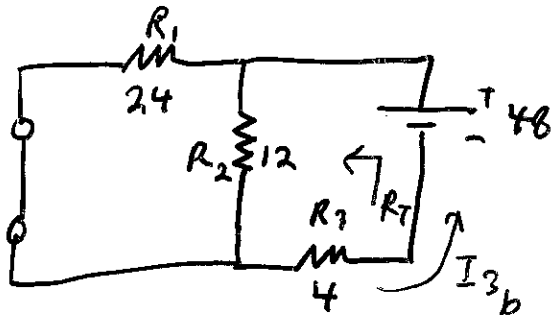

$$R_T = R_3 + R_1 \parallel R_2$$


$$R_T = 4 + \frac{(24)(12)}{24+12} = 4 + 8 = 12 \Omega$$

$$I_{3b} = \frac{48}{R_T} = \frac{48}{12} = 4A.$$

4.) Combine results:


$$I_3 = I_{3a} + I_{3b} = -1.5A + 4A = \boxed{2.5A}$$

ex

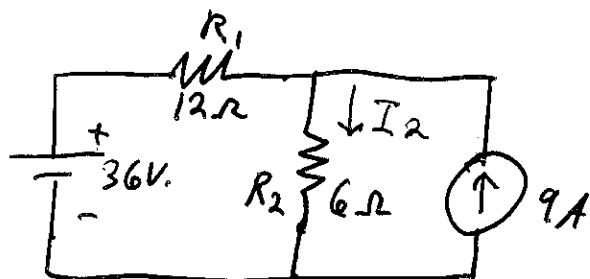


Find I_2 using Superposition.

1.) Kill 9A. source:

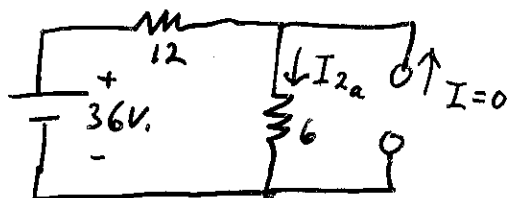

$$I_{2a} = \frac{36V}{12\Omega + 6\Omega} = 2A.$$

2.) kill 36V. source:

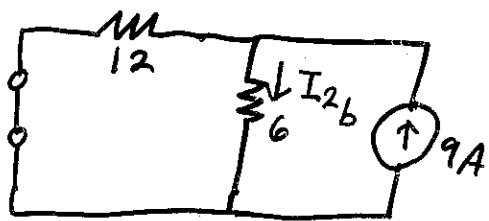

By CDR:

$$I_{2b} = (9A) \frac{12}{12+6} = 6A.$$

3.) combine results:

$$I_2 = I_{2a} + I_{2b} = 2A + 6A = \boxed{8A.}$$

$$P_{6\Omega} = I^2 R = (8)^2 6 = 384W.$$

If we misuse the superposition principle for combining power we get:


$$P_a = (I_{2a})^2 R = (2)^2 6 = 24W.$$

$$P_b = (I_{2b})^2 R = (6)^2 6 = 216W.$$

$$P_a + P_b = 240W. \neq 384W.$$


↑ erroneous value

ex

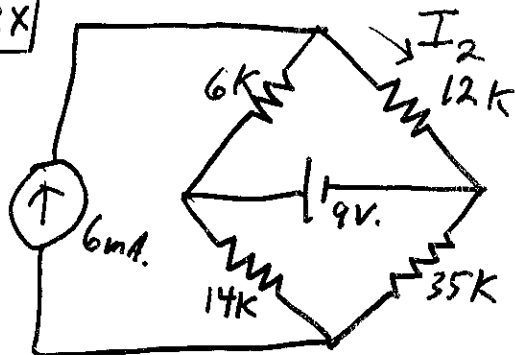

Find I_2 using
Superposition:


1.) Kill 9V. source;

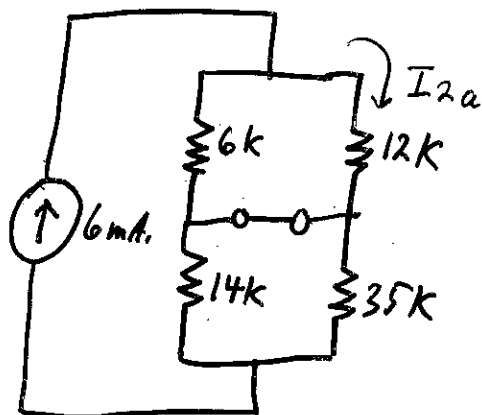

By CDR:

$$I_{2a} = (6\text{mA}) \frac{6\text{k}}{6\text{k} + 12\text{k}} = 2\text{mA}$$

2.) Kill 6mA. source:

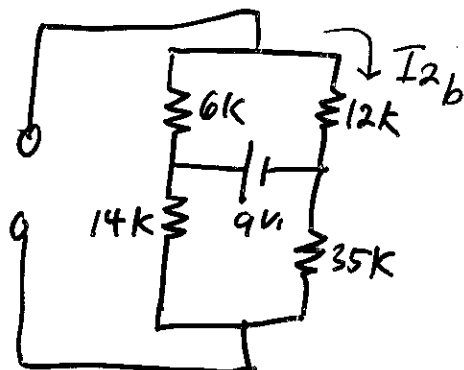


$$I_{2b} = \frac{9\text{V}}{6\text{k} + 12\text{k}} = 0.5\text{mA}$$

3.) Combine Results:


$$I_2 = I_{2a} + I_{2b} = 2\text{mA} + 0.5\text{mA} = \boxed{2.5\text{mA}}$$

ex/

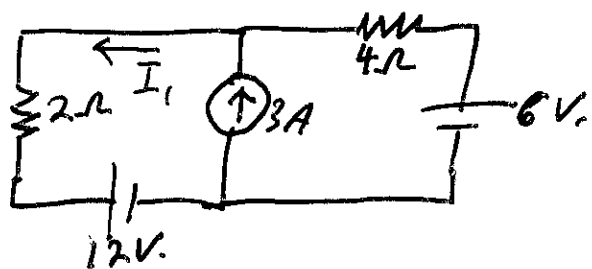


Find I_1 using Superposition:

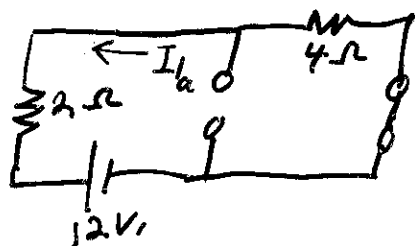- 1.) Kill 3A and 6V. sources: (leave only 12V. source active)




$$I_{1a} = -\frac{12V.}{2\Omega + 4\Omega} = -2A.$$

- 2.) Kill 3A. and 12V. sources:

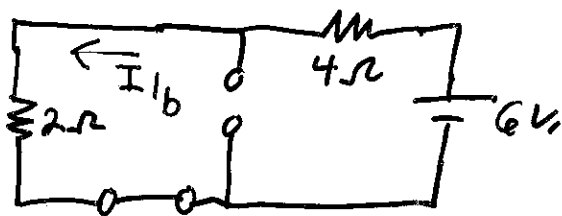

$$I_{1b} = \frac{6V.}{2+4} = 1A.$$

- 3.) kill 12V. and 6V. sources:

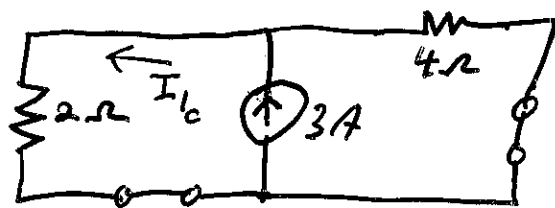

By CDR:

$$I_{1c} = (3A) \frac{4}{2+4} = 2A.$$

- 4.) Combine Results:

$$I_1 = I_{1a} + I_{1b} + I_{1c} = -2 + 1 + 2 = \boxed{1A.}$$