
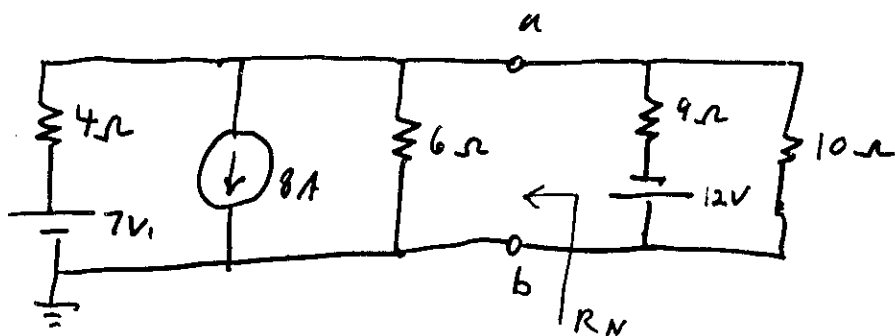


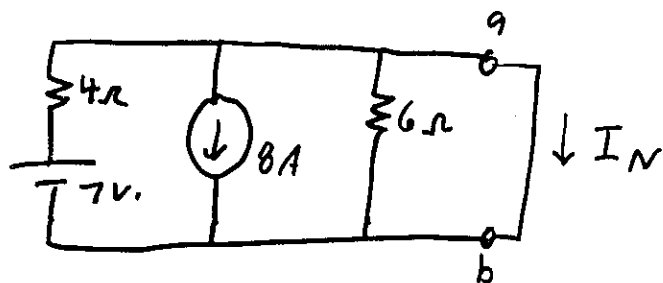Prob 24 ex/ Find the Norton equiv. ckt. to the left of terminals a and b.




Solution:

1.) Remove the external circuitry and apply a short ckt.



2.) Solve for I_N which is the current through the short ckt. Since 2 sources are present use superposition theorem:

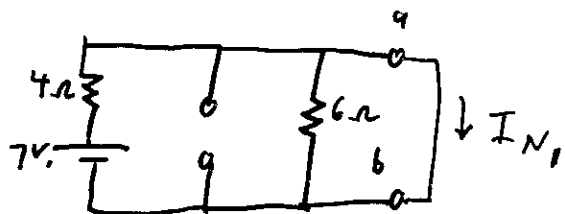
1. Kill Current source (replace with open ckt.)



Note: 6Ω resistor is "shorted out"

So, $I_{N1} = \frac{7V}{4\Omega} = 1.75A$

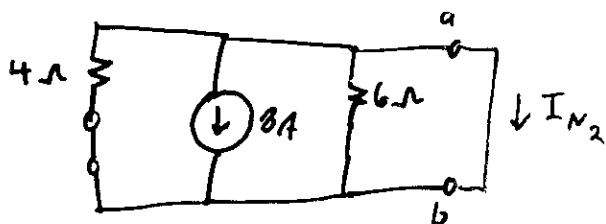2. Kill voltage source (replace with short ckt.)



By CDR:


$$I_{N2} = (8A) \frac{4}{4+0} = -8A$$

3. Combine to get $I_N = I_{N1} + I_{N2} = 1.75 + (-8) = \boxed{-6.25A}$

continued....


ex/ continued...

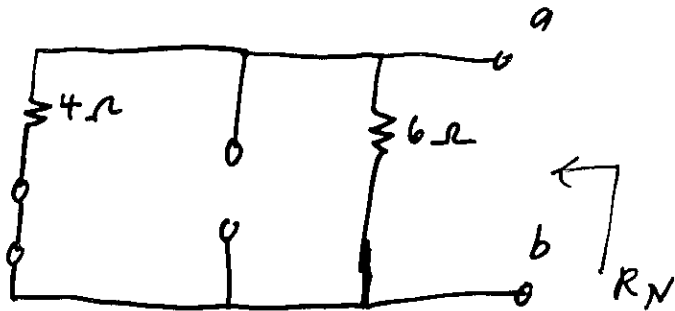- 3.) kill sources and solve for R_N
(replace current source with open ckt.)
(replace voltage source with short ckt.)



$$R_N = 4\Omega \parallel 6\Omega = \frac{(4)(6)}{4+6} = \frac{24}{10} = \boxed{2.4\Omega}$$

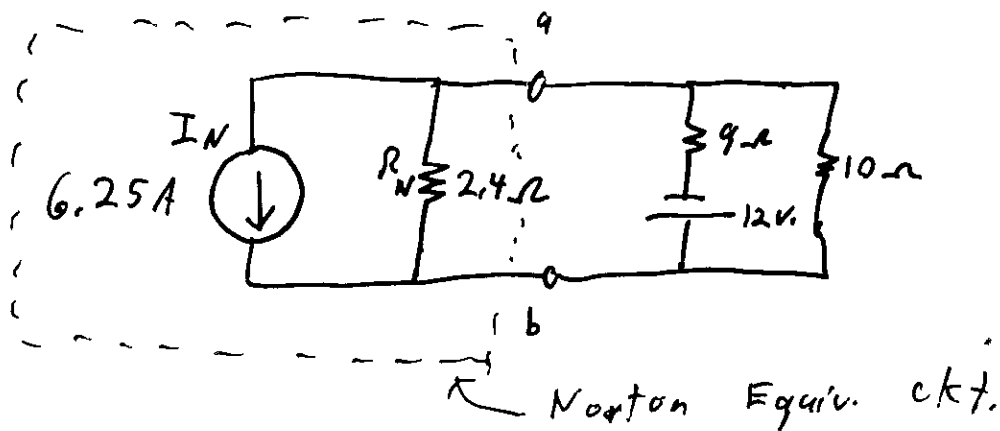- 4.) Redraw original ckt. with Norton Equiv. ckt. in place



Note: In schematic I_N was shown as being forced out of terminal "a". Since the computed I_N value was negative, the direction of the current source is drawn to force current out of terminal "b".


Maximum Power Transfer Theorem

A load will receive maximum power from a linear bilateral dc network when its total resistive value is exactly equal to the Thevenin resistance of the network as "seen" by the load.

For maximum power transfer;


$$R_L = R_{TH}$$

ex/

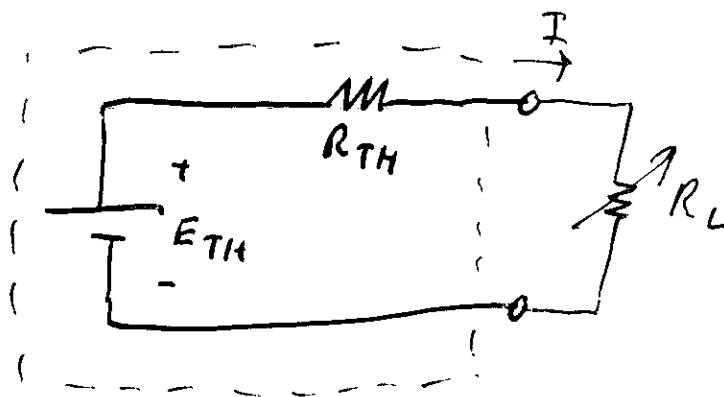

$$I = \frac{E_{TH}}{R_{TH} + R_L}, \quad P_L = I^2 R_L = \left(\frac{E_{TH}}{R_{TH} + R_L} \right)^2 R_L$$
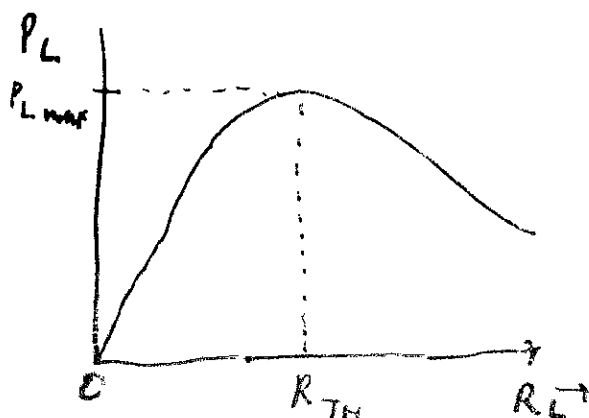
$$P_L = \frac{E_{TH}^2 R_L}{(R_{TH} + R_L)^2}$$



Operating Efficiency:

$$\eta = \frac{P_L}{P_S} \times 100\%$$

Complex Numbers :



$$\bar{C} = A + jB \leftarrow \text{rectangular form}$$

OR

$$\bar{C} = C \angle \theta \leftarrow \text{Polar form}$$

$$-\bar{C} = -C \angle \theta = C \angle \theta \pm \pi$$

Conversion Between Forms.

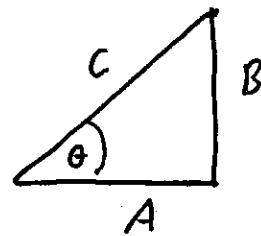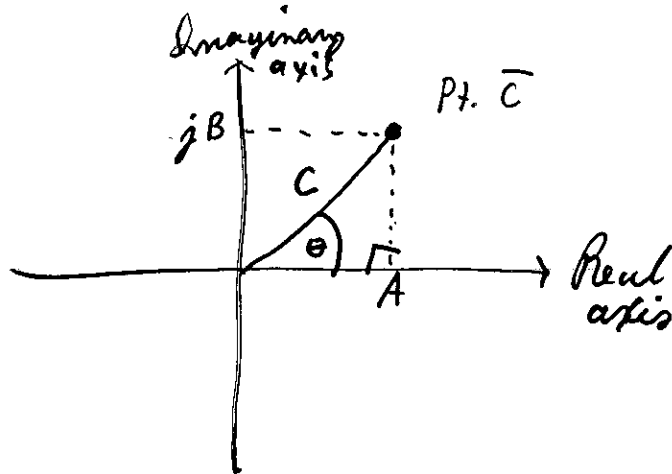

$$\begin{aligned} A &= C \cos \theta \\ B &= C \sin \theta \end{aligned}$$

$$\begin{aligned} C &= \sqrt{A^2 + B^2} \\ \theta &= \tan^{-1} \frac{B}{A} \end{aligned}$$

$$j = \sqrt{-1}$$

$$j^2 = -1$$

$$\frac{1}{j} = -j$$

Complex Conjugate :

$$\bar{C}^* = A - jB$$

OR

$$\bar{C}^* = C \angle -\theta$$

Math Operations with Complex Numbers

Given: $\bar{C}_1 = A_1 + jB_1$ and $\bar{C}_2 = A_2 + jB_2$

Addition: $\bar{C}_1 + \bar{C}_2 = (A_1 + A_2) + j(B_1 + B_2)$

Subtraction: $\bar{C}_1 - \bar{C}_2 = (A_1 - A_2) + j(B_1 - B_2)$

Addition and Subtraction are easiest in rectangular form.

Multiplication: $\bar{C}_1 \cdot \bar{C}_2 = C_1 C_2 \angle (\theta_1 + \theta_2)$

Division: $\frac{\bar{C}_1}{\bar{C}_2} = \frac{C_1}{C_2} \angle (\theta_1 - \theta_2)$


Multiplication and Division are easiest in polar form.

$$\frac{1}{\bar{C}_1 \angle \theta_1} = \frac{1}{C_1} \angle -\theta_1$$

⚡ note: 1 is really $1 \angle 0^\circ$

Phasors

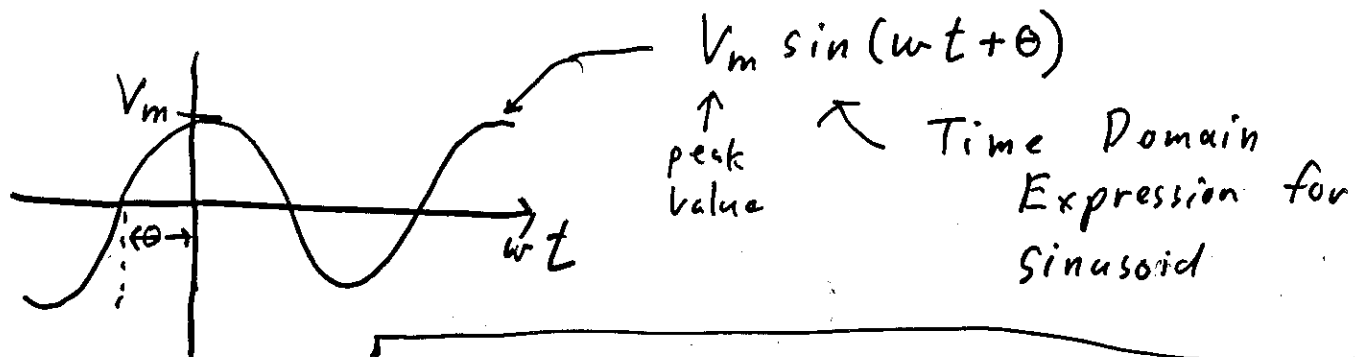
A Phasor is a complex number which can be used to represent a sinusoidal AC waveform.



$$\boxed{V_m \sin(\omega t + \theta) \Leftrightarrow V_m \angle \theta}$$

Time Domain Phasor Domain

ex

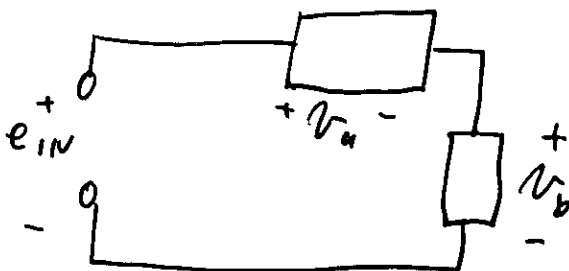

Given: $f = 60 \text{ Hz}$

$$v_a = 50 \sin(377t + 30^\circ)$$

$$v_b = 30 \sin(377t + 60^\circ)$$

Find e_{IN}

Solution:

By KVL $-e_{IN} + v_a + v_b = 0$

$$e_{IN} = v_a + v_b$$

Convert to Phasor Domain:

$$v_a = 50 (0.707) \angle 30^\circ = 35.35 \angle 30^\circ = 30.61 + j17.68 = \bar{V}_a$$

↑ converts peak to RMS

$$v_b = 30 (0.707) \angle 60^\circ = 21.21 \angle 60^\circ = 10.61 + j18.37 = \bar{V}_b$$

$$\bar{E}_{IN} = \bar{V}_a + \bar{V}_b = (30.61 + 10.61) + j(17.58 + 18.37)$$

$$\bar{E}_{IN} = 41.22 + j36.05 = 54.76 \angle 41.17^\circ$$

Now convert back to time domain

$$e_{IN} = \sqrt{2} (54.76) \sin(377t + 41.17^\circ) = 77.43 \sin(377t + 41.17^\circ)$$

Impedance and the Phasor Diagram

Resistive Elements

For a purely resistive element the current and voltage are in phase.

$$\bar{Z}_R = R \angle 0^\circ$$


where $\bar{Z}_R$ is the Impedance of a resistor.

$$\bar{I} = \frac{\bar{V}}{\bar{Z}_R}$$

← Ohm's Law for Phasors

$$\bar{V} = \bar{I} \bar{Z}_R$$

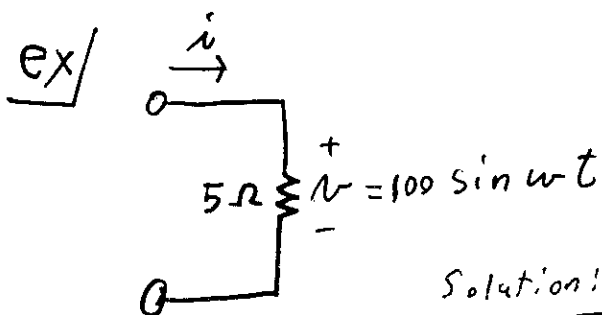A phasor is a rotating vector with a magnitude and phase angle associated with it.



Find the current i .
Sketch i and v


Solution:

Solution: 1.) First convert v to Phasor form:
 $v = 100 \sin \omega t \Rightarrow \bar{V} = 100 \angle 0^\circ$


2.) Apply ohm's Law:

$$\bar{I} = \frac{\bar{V}}{\bar{Z}_R} = \frac{100 \angle 0^\circ}{5 \angle 0^\circ} = 20 \angle 0^\circ$$

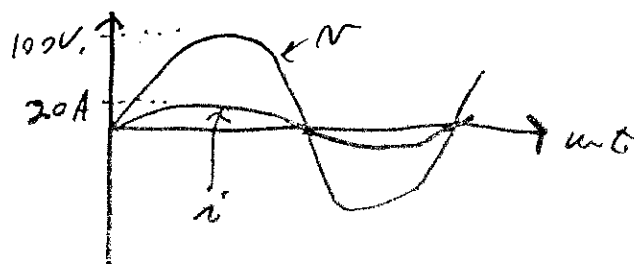3.) Convert back to time domain:
 $i = 20 \sin \omega t$ Amps.



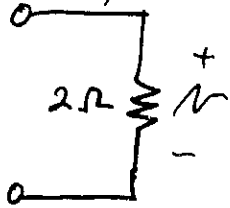ex/ $i = 4 \sin(\omega t + 30^\circ)$ Find v , sketch i and v



solution:

1.) Convert i to Phasor form:


$$i = 4 \sin(\omega t + 30^\circ) \Rightarrow \bar{I} = 4 \angle 30^\circ \text{ Amps.}$$

2.) Apply Ohm's Law:

$$\bar{V} = \bar{I} \bar{Z}_R = (4 \angle 30^\circ)(2 \angle 0^\circ) = 8 \angle 30^\circ \text{ volts.}$$

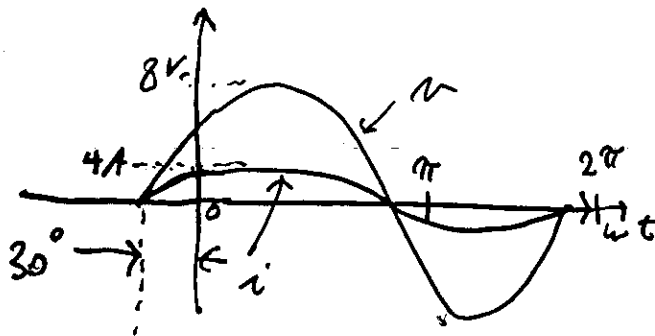
3.) Convert back to time domain:

$$v = 8 \sin(\omega t + 30^\circ) \text{ volts}$$



A Phasor Diagram is plot in the complex plane showing the magnitude and phase relationships of circuit quantities.

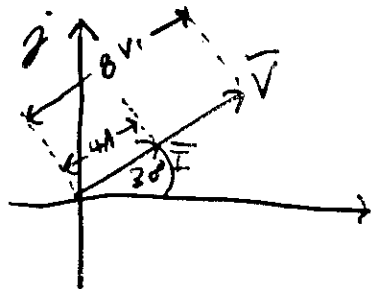For the above example the Phasor Diagram would be:



Note: $\bar{I}$ and $\bar{V}$ are in phase since it's a resistive circuit

Inductive Reactance

For a purely inductive element the current lags the voltage by 90° .

$$\bar{Z}_L = X_L \angle 90^\circ$$


where $\bar{Z}_L$ is the Impedance of an inductor

$$X_L = 2\pi fL = \omega L$$

In rectangular form; $\bar{Z}_L = j\omega L = jX_L$

Ohm's Law for Inductors; $\bar{I} = \frac{\bar{V}}{\bar{Z}_L}$, $\bar{V} = \bar{I} \bar{Z}_L$

ex/ $i = 5 \sin(\omega t + 30^\circ)$

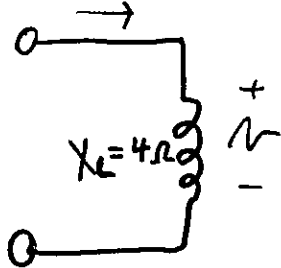

Find voltage v .
Sketch v and i .

Solution:



1.) Convert i and Z_L to phasor form:

$$i = 5 \sin(\omega t + 30^\circ) \Rightarrow \bar{I} = 5 \angle 30^\circ$$

$$\bar{Z}_L = X_L \angle 90^\circ = 4 \angle 90^\circ$$

2.) Apply Ohm's Law: $\bar{V} = \bar{I} \bar{Z}_L = (5 \angle 30^\circ)(4 \angle 90^\circ) = 20 \angle 120^\circ$

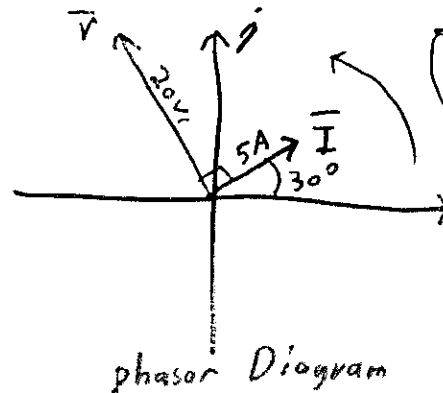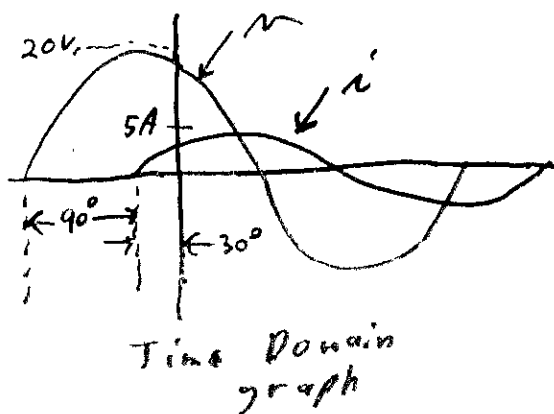3.) Convert back to time domain: $v = 20 \sin(\omega t + 120^\circ)$



Can think of Phasors as rotating ccw

I lags V by 90°

Capacitive Reactance

For a purely capacitive element the current leads the voltage by 90° .

$$\bar{Z}_c = X_c \angle -90^\circ$$

where $\bar{Z}_c$ is the impedance of a capacitor


$$X_c = \frac{1}{2\pi fC} = \frac{1}{\omega C}$$

In rectangular form: $\bar{Z}_c = \frac{1}{j\omega C} = -\frac{j}{\omega C}$

Ohm's Law for Capacitors: $\bar{I} = \frac{\bar{V}}{\bar{Z}_c}$, $\bar{V} = \bar{I} \bar{Z}_c$

ex/ $i = 6 \sin(\omega t - 60^\circ)$

Find voltage v
Sketch v and i

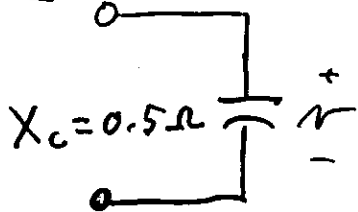

Solution:


1.) Convert i and Z_c to phasor form

$$\bar{I} = 6 \angle -60^\circ, \quad \bar{Z}_c = X_c \angle -90^\circ = 0.5 \angle -90^\circ$$


2.) Apply Ohm's Law: $\bar{V} = \bar{I} \bar{Z}_c = (6 \angle -60^\circ)(0.5 \angle -90^\circ)$

$$\bar{V} = 3 \angle (-60 + (-90)) = 3 \angle -150^\circ$$

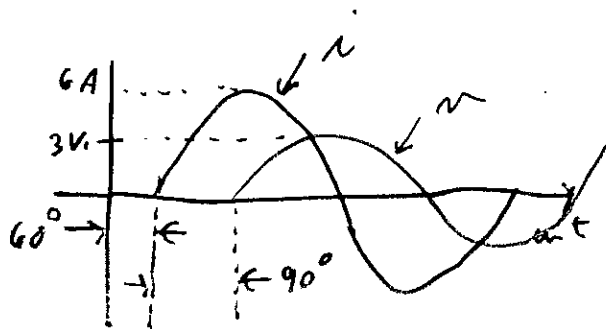3.) Convert back to time domain: $v = 3 \sin(\omega t - 150^\circ)$




Time Domain Graph

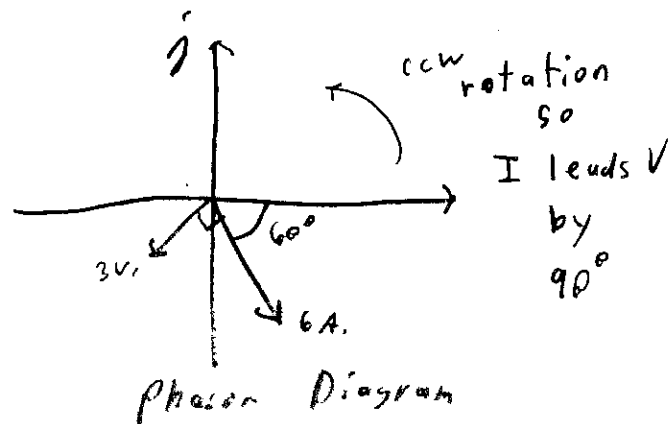

Phasor Diagram

Impedance Diagram

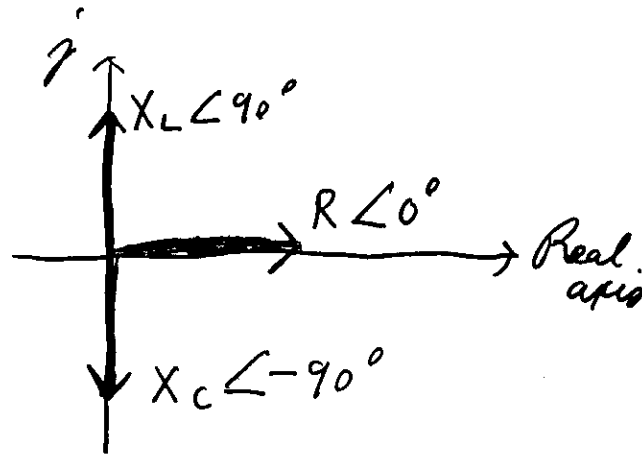The complex quantities corresponding to the impedance of R , L , and C elements can be graphed in the complex plane.




For any configuration (series, parallel, series-parallel, etc.) the angle associated with the total impedance is the angle by which the source current lags the applied voltage.

For inductive networks θ_T will be positive.


For capacitive networks θ_T will be negative.

Series Configuration

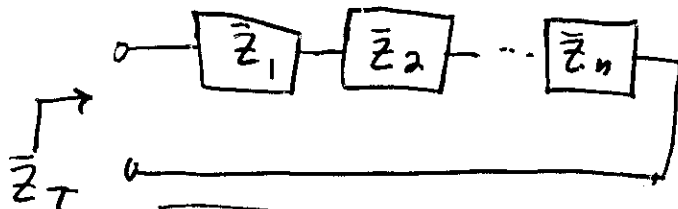

For Impedances in series the total impedance is: $\bar{Z}_T = \bar{Z}_1 + \bar{Z}_2 + \dots + \bar{Z}_n$

ex/

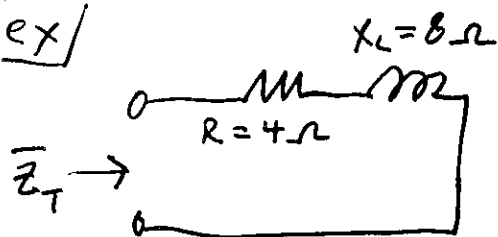

Draw the Impedance diagram. Find total impedance Z_T .

Solution: 1.) Convert impedances to phasor form:

$$\bar{Z}_R = 4 \angle 0^\circ, \quad \bar{Z}_L = 8 \angle 90^\circ$$

2.) Apply series Z rule:



$$\bar{Z}_T = \bar{Z}_R + \bar{Z}_L = 4 \angle 0^\circ + 8 \angle 90^\circ$$

convert to rectangular form to add:

$$\bar{Z}_T = 4 + 8j$$

convert back to polar form:

$$\bar{Z}_T = 8.944 \angle 63.43^\circ$$

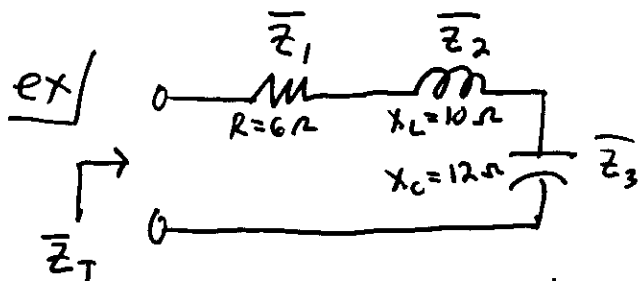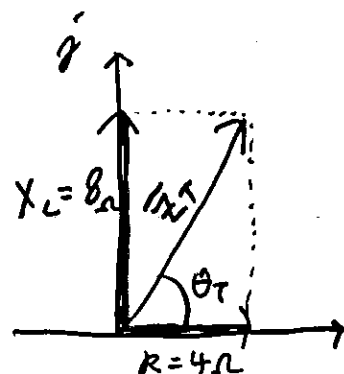

Determine total $\bar{Z}$.
Draw $\bar{Z}$ diagram.

Solution: 1.) Convert to phasor form:

$$\bar{Z}_1 = 6 \angle 0^\circ, \quad \bar{Z}_2 = 10 \angle 90^\circ, \quad \bar{Z}_3 = 12 \angle -90^\circ$$

2.) Apply series Z rule:

$$\bar{Z}_T = 6 \angle 0^\circ + 10 \angle 90^\circ + 12 \angle -90^\circ$$


convert to rect. form to add:

$$\bar{Z}_T = 6 + 10j - 12j = 6 - 2j$$


Convert back to polar form:

$$\bar{Z}_T = 6.325 \angle -18.43^\circ$$

θ_T neg. $\rightarrow Z_T$ is capacitive

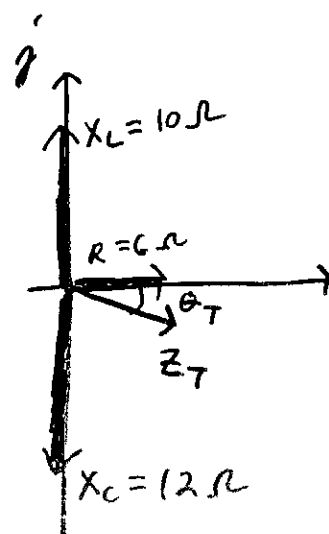

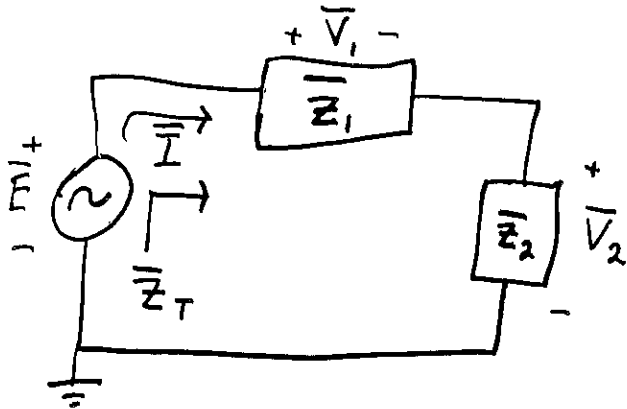For the Series AC circuit the current is the same through each element.



Phasor Equations:

$$\bar{I} = \frac{\bar{E}}{\bar{Z}_T}$$

$$\bar{Z}_T = \bar{Z}_1 + \bar{Z}_2$$

$$\bar{V}_1 = \bar{I} \bar{Z}_1, \quad \bar{V}_2 = \bar{I} \bar{Z}_2$$

By KVL: $-\bar{E} + \bar{V}_1 + \bar{V}_2 = 0$

$$\bar{E} = \bar{V}_1 + \bar{V}_2$$

By Voltage Divider Rule: $\bar{V}_2 = \bar{E} \left(\frac{\bar{Z}_2}{\bar{Z}_1 + \bar{Z}_2} \right)$

The Power supplied to the circuit is:

$$P = EI \cos \theta_T$$

Where: E is voltage in RMS

I is current in RMS

θ_T is the phase angle between $\bar{E}$ and $\bar{I}$

θ_T is also the angle of $\bar{Z}_T$.


The Power Factor F_p is:

$$F_p = \cos \theta_T$$

so $P = EI F_p$

R-L Circuit

ex/

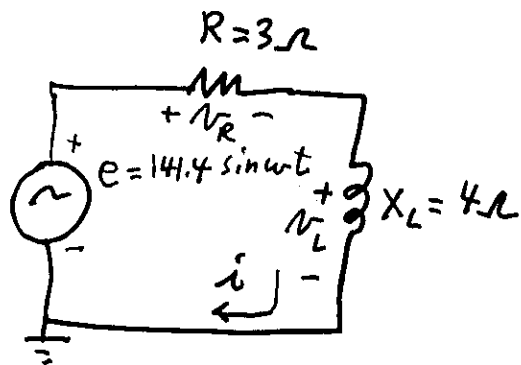

Convert to Phasors:

$$e = 141.4 \sin \omega t \rightarrow \bar{E} = 141.4 \angle 0^\circ$$

Convert to RMS

$$\bar{E} = 141.4 (.707) \angle 0^\circ = 100 \angle 0^\circ \text{ volts RMS}$$

Find total impedance:

$$\bar{Z}_T = \bar{Z}_R + \bar{Z}_L = 3 \angle 0^\circ + 4 \angle 90^\circ$$

converting to rect. form:


$$\bar{Z}_T = 3 + j4 \Omega$$

converting to polar form:

$$\bar{Z}_T = 5 \Omega \angle 53.13^\circ$$

By Ohm's Law:
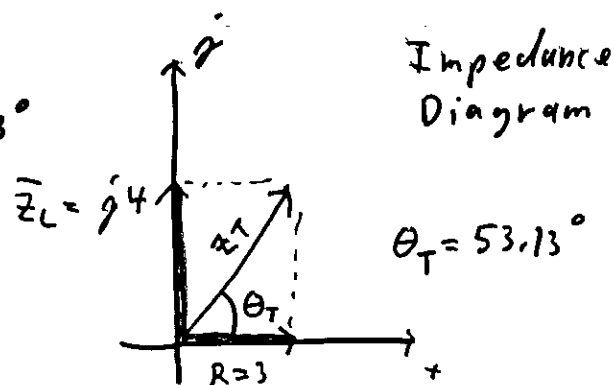
$$\bar{I} = \frac{\bar{E}}{\bar{Z}_T} = \frac{100 \angle 0^\circ}{5 \angle 53.13^\circ} = 20 \text{ A.} \angle -53.13^\circ \text{ RMS}$$



$$\bar{V}_R = \bar{I} \bar{Z}_R = (20 \angle -53.13^\circ)(3 \angle 0^\circ)$$

$$\bar{V}_R = 60 \text{ V.} \angle -53.13^\circ$$


$$\bar{V}_L = \bar{I} \bar{Z}_L = (20 \angle -53.13^\circ)(4 \angle 90^\circ) = 80 \angle 36.87^\circ \text{ V. RMS}$$

Check by KVL:

$$-\bar{E} + \bar{V}_R + \bar{V}_L = 0 \rightarrow \bar{E} = \bar{V}_R + \bar{V}_L = 60 \angle -53.13^\circ + 80 \angle 36.87^\circ$$

Converting to rect. form: $\bar{E} = 36 - j48 + 64 + j48$
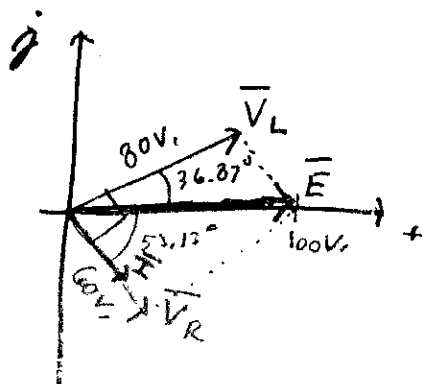
$$\bar{E} = 100 + j0 = 100 \angle 0^\circ \text{ V.} \checkmark \text{ checks}$$



← Phasor Diagram

ex/ ... continued

Total Power delivered to R-L ckt:

$$P_T = E I \cos \theta_T \quad \leftarrow E \text{ \& I are effective (RMS) values}$$

$$P_T = (100 \text{ V.})(20 \text{ A.}) \cos 53.13^\circ = 2000 \text{ W.} (.6) = 1200 \text{ W.}$$

Power dissipated by Resistor:

$$P_R = I^2 R = (20 \text{ A.})^2 (3 \Omega) = 400(3) = 1200 \text{ W.}$$

Total Power dissipated by R-L ckt:

$$P_T = P_R + P_L = V_R I \cos \theta_R + V_L I \cos \theta_L$$

$$= (60)(20) \cos 0^\circ + (80)(20) \cos 90^\circ$$
$$= 1200 \text{ W.} \quad + \quad 0 \quad = 1200 \text{ W.}$$

Note: Inductor dissipates zero power

Power Factor:

$$F_p = \cos \theta_T = \cos 53.13^\circ = 0.6 \text{ Lagging}$$

F_p is Lagging because I lags E in an inductive ckt.

Also:


$$F_p = \frac{P}{EI} \quad \leftarrow \begin{array}{l} \text{since } P = EI F_p \\ P \text{ called "Real Power" in watts} \end{array}$$

$\sqrt{EI}$ called "VA" or Apparent Power

$$\text{Also } F_p = \frac{R}{Z_T}$$

$$\cos \theta = \frac{P}{EI} = \frac{I^2 R}{EI} = \frac{IR}{E} = \frac{R}{E/I} = \frac{R}{Z_T}$$

R - C Circuit

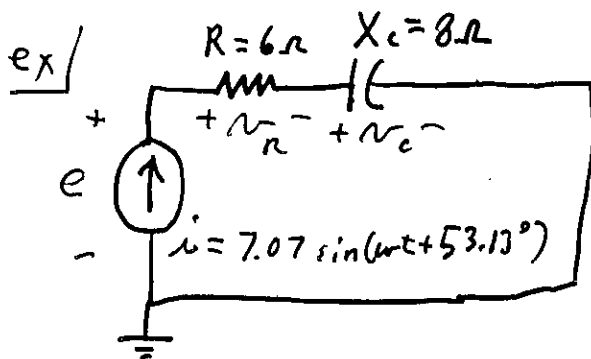

Convert to Phasors:

$$i = 7.07 \sin(\omega t + 53.13^\circ) \rightarrow \bar{I} = 7.07 \angle 53.13^\circ \text{ Peak}$$

Convert to RMS:

$$\bar{I} = 7.07(0.707) \angle 53.13^\circ = 5 \text{ A} \angle 53.13^\circ \text{ RMS}$$

Find total impedances

$$\bar{Z}_T = \bar{Z}_R + \bar{Z}_C = 6 \angle 0^\circ + 8 \angle -90^\circ$$

converting to rect. form: $\bar{Z}_T = 6 - j8 \Omega$

converting to polar form: $\bar{Z}_T = 10 \Omega \angle -53.13^\circ$


By Ohm's Law:

$$\bar{E} = \bar{I} \bar{Z}_T = (5 \text{ A} \angle 53.13^\circ)(10 \Omega \angle -53.13^\circ)$$

$$\bar{E} = 50 \text{ V} \angle 0^\circ$$

$$\bar{V}_R = \bar{I} \bar{Z}_R = (5 \text{ A} \angle 53.13^\circ)(6 \Omega \angle 0^\circ)$$
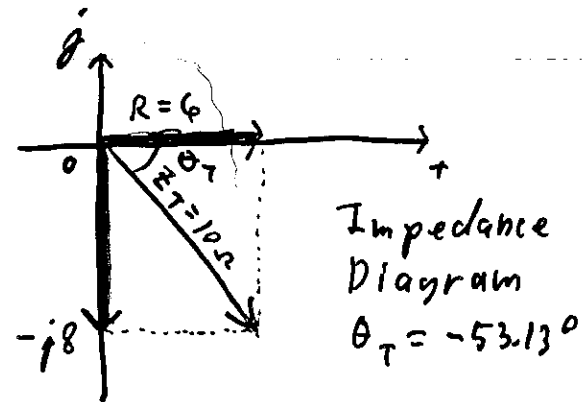
$$\bar{V}_R = 30 \text{ V} \angle 53.13^\circ$$



$$\bar{V}_C = \bar{I} \bar{Z}_C = (5 \text{ A} \angle 53.13^\circ)(8 \Omega \angle -90^\circ) = 40 \text{ V} \angle -36.87^\circ$$

Check by KVL:

$$-\bar{E} + \bar{V}_R + \bar{V}_C = 0 \rightarrow \bar{E} = \bar{V}_R + \bar{V}_C = 30 \angle 53.13^\circ + 40 \angle -36.87^\circ$$

$$\text{Convert to rect. form: } \bar{E} = 18 + j24 + 32 - j24 = 50 + j0$$

$$\bar{E} = 50 \angle 0^\circ \checkmark \text{ checks}$$



Convert to time domain:

$$\bar{E} = 50 \angle 0^\circ \text{ RMS} \rightarrow e = \sqrt{2} 50 \sin \omega t = 70.7 \sin \omega t$$

$$\bar{V}_R = 30 \angle 53.13^\circ \rightarrow v_R = \sqrt{2} 30 \sin(\omega t + 53.13^\circ) = 42.42 \sin(\omega t + 53.13^\circ)$$

$$\bar{V}_C = 40 \angle -36.87^\circ \rightarrow v_C = \sqrt{2} 40 \sin(\omega t - 36.87^\circ) = 56.56 \sin(\omega t - 36.87^\circ)$$

ex/ ... continued

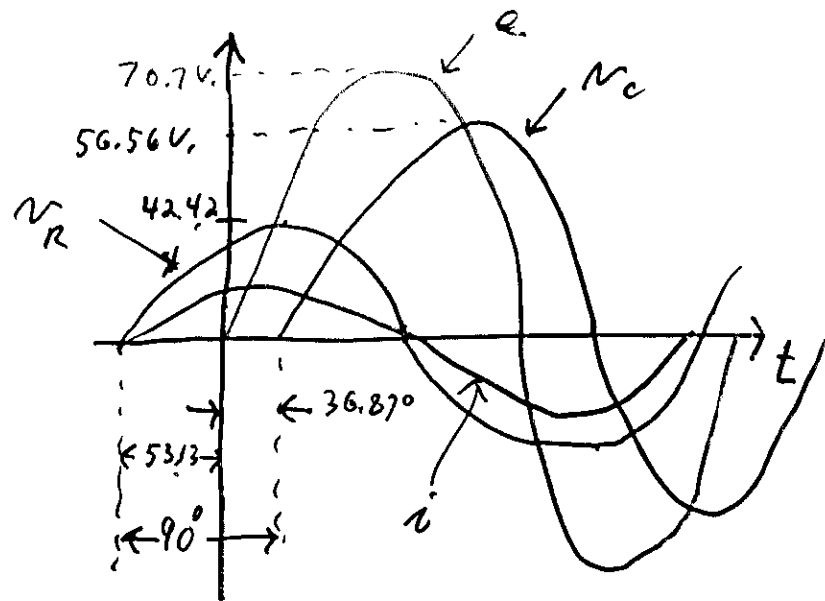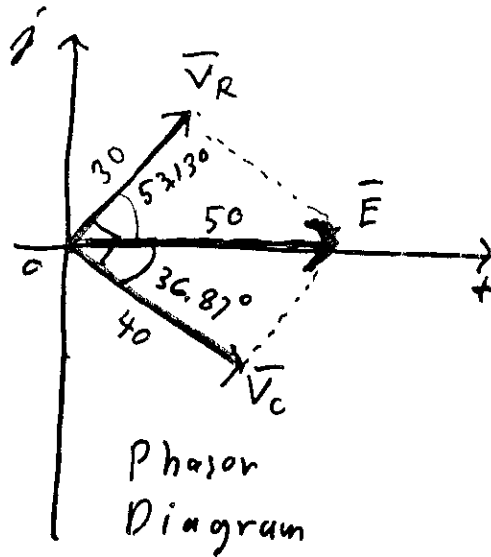

Note: V_R and i are in phase
 i leads V_C by 90°

Total Power :

$$P_T = \overset{\substack{\text{RMS} \\ \text{Values}}}{E I} \cos \overset{\substack{\text{angle of} \\ \vec{Z}_T}}{\theta_T} = (50V)(5A) \cos 53.13^\circ = 250(.6) = 150 \text{ watts}$$

Or alternately ; $P_T = I^2 R = (5A)^2 6\Omega = 25(6) = 150 \text{ watts}$

Or alternately ;

$$P_T = P_R + P_C = V_R I \cos \theta_R + V_C I \cos \theta_C \\ = (30)(5) \cos 0^\circ + (40)(5) \cos 90^\circ = 150 + 0 = 150 \text{ watts}$$


Power Factor : $F_p = \cos \theta_T = \cos 53.13^\circ = 0.6 \text{ leading}$

Or alternately : $F_p = \cos \theta = \frac{R}{Z_T} = \frac{6}{10} = 0.6 \text{ leading}$

R-L-C Circuit

ex/

$$e = 70.7 \sin \omega t$$

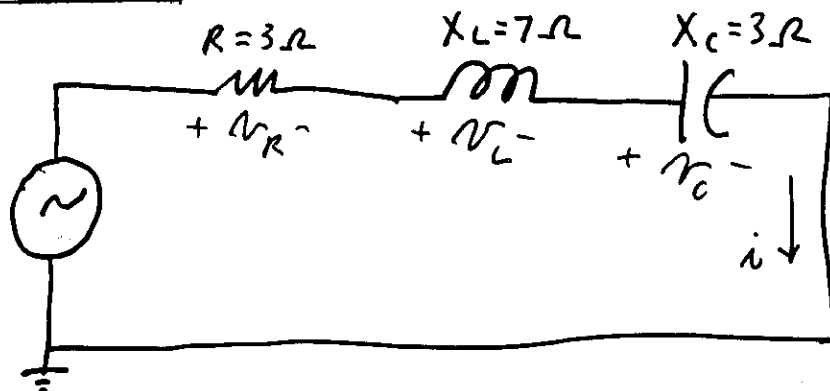

Convert to Phasors:

$$e = 70.7 \sin \omega t \rightarrow \bar{E} = 70.7 \angle 0^\circ$$

Convert to RMS:

$$\bar{E} = 70.7(0.707) \angle 0^\circ = 50 \angle 0^\circ$$

Find total impedance:

$$\bar{Z}_T = \bar{Z}_R + \bar{Z}_L + \bar{Z}_C = 3 \angle 0^\circ + 7 \angle 90^\circ + 3 \angle -90^\circ$$

Convert to rect. form to add:

$$\bar{Z}_T = 3 + j0 + j7 + (-j3) = 3 + j4$$

Convert to polar form to multiply or divide:

$$\bar{Z}_T = 5 \angle 53.13^\circ$$

By Ohm's Law:

$$\bar{I} = \frac{\bar{E}}{\bar{Z}_T} = \frac{50 \angle 0^\circ}{5 \angle 53.13^\circ} = 10 \text{ A.} \angle -53.13^\circ$$

$$\bar{V}_R = \bar{I} \bar{Z}_R = (10 \angle -53.13^\circ)(3 \angle 0^\circ) = 30 \text{ V.} \angle -53.13^\circ$$

$$\bar{V}_L = \bar{I} \bar{Z}_L = (10 \angle -53.13^\circ)(7 \angle 90^\circ) = 70 \text{ V.} \angle 36.87^\circ$$

$$\bar{V}_C = \bar{I} \bar{Z}_C = (10 \angle -53.13^\circ)(3 \angle -90^\circ) = 30 \text{ V.} \angle -143.13^\circ$$

(Note that V_L is larger than the source voltage.)

By KVL: $\bar{E} = \bar{V}_R + \bar{V}_L + \bar{V}_C$


in time domain:

$$i = \sqrt{2}(10) \sin(\omega t - 53.13^\circ) = 14.14 \sin(\omega t - 53.13^\circ)$$

$$v_R = \sqrt{2}(30) \sin(\omega t - 53.13^\circ) = 42.42 \sin(\omega t - 53.13^\circ)$$


$$v_L = \sqrt{2}(70) \sin(\omega t + 36.87^\circ) = 98.98 \sin(\omega t + 36.87^\circ)$$
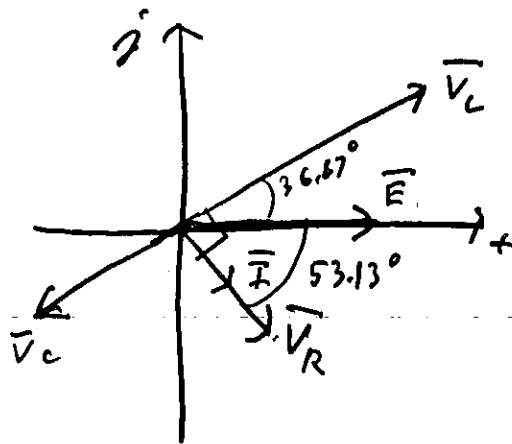
$$v_C = \sqrt{2}(30) \sin(\omega t - 143.13^\circ) = 42.42 \sin(\omega t - 143.13^\circ)$$



Phasor Diagram

Note: $\bar{I}$ lags $\bar{E}$ by 53.13°

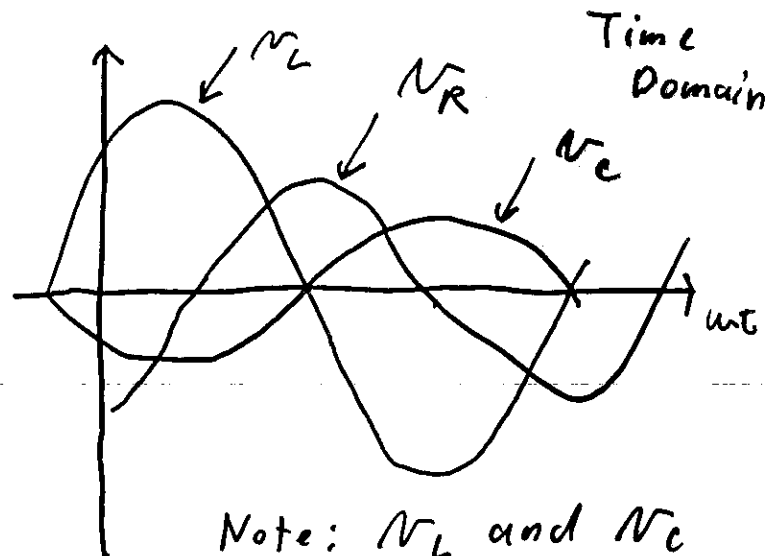

Note: v_L and v_C are 180° out of phase

Total Power: $P_T = EI \cos \theta_T = (50)(10) \cos 53.13^\circ = 300 \text{ Watts}$

Also: $P_T = I^2 R = (10)^2 (3) = 300 \text{ Watts}$

All of the power is dissipated by the resistor; Capacitors and Inductors do not dissipate any power

Power Factor: $F_p = \cos \theta_T = \cos 53.13^\circ = 0.6 \text{ lagging}$

Also: $F_p = \frac{R}{Z_T} = \frac{3}{5} = 0.6 \text{ lagging}$

Note: In this example the inductive reactance dominates over the capacitive reactance making the total impedance "inductive" with a lagging power factor.

Voltage Divider Rule

This rule applies for AC ckt. as it did for D.C. ckt.


$$\boxed{\bar{V}_x = \frac{\bar{E} \bar{Z}_x}{\bar{Z}_T}}$$

where: $\bar{V}_x$ is the voltage across one or more series elements that have impedance $\bar{Z}_x$

$\bar{E}$ is the total voltage across the series ckt.

$\bar{Z}_T$ is the total impedance of the series ckt.

ex/

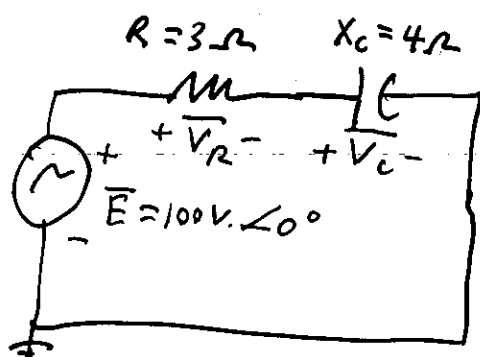

Find $\bar{V}_C$ and $\bar{V}_R$

solution:


By Voltage Divider Rule:

$$\bar{V}_R = \frac{\bar{Z}_R \bar{E}}{\bar{Z}_C + \bar{Z}_R} = \frac{(3 \angle 0^\circ)(100 \angle 0^\circ)}{3 \angle 0^\circ + 4 \angle -90^\circ}$$

$$\bar{V}_R = \frac{300 \angle 0^\circ}{3 - j4} = \frac{300 \angle 0^\circ}{5 \angle -53.13^\circ} = \boxed{60V \angle +53.13^\circ}$$

$$\bar{V}_C = \frac{\bar{Z}_C \bar{E}}{\bar{Z}_C + \bar{Z}_R} = \frac{(4 \angle -90^\circ)(100 \angle 0^\circ)}{5 \angle -53.13^\circ} = \boxed{80V \angle -36.87^\circ}$$

ex/

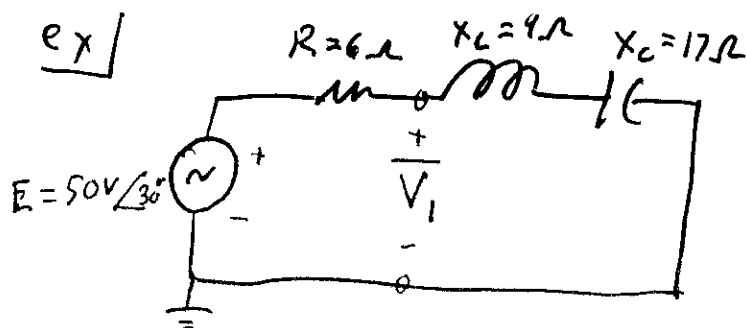

Find $\bar{V}_1$

solution:

By VDR


$$\bar{V}_1 = \frac{(\bar{Z}_L + \bar{Z}_C) \bar{E}}{\bar{Z}_T}$$

ex/ ... continued

$$\bar{V}_1 = \frac{((9\Omega \angle 90^\circ) + (17\Omega \angle -90^\circ))(50 \angle 30^\circ)}{6\Omega \angle 0^\circ + 9\Omega \angle 90^\circ + 17\Omega \angle -90^\circ}$$

$$\bar{V}_1 = \frac{(j9 - j17)(50 \angle 30^\circ)}{6 + j9 - j17}$$
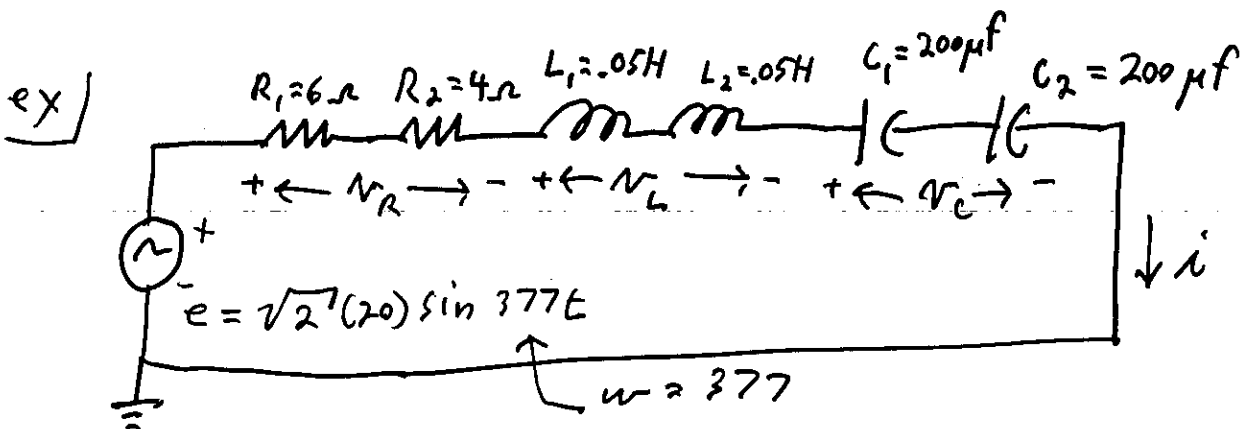
$$\bar{V}_1 = \frac{(-j8)(50 \angle 30^\circ)}{6 - j8} = \frac{(8 \angle -90^\circ)(50 \angle 30^\circ)}{(10 \angle -53.13^\circ)} = \boxed{40V \angle -6.87^\circ}$$



a.) Calculate $\bar{I}$, $\bar{V}_R$, $\bar{V}_L$, $\bar{V}_C$ in phasor form

Combining series elements: $R_T = R_1 + R_2 = 6 + 4 = 10\Omega$

$$L_T = 0.05H + 0.05H = 0.1H$$

$$C_T = \frac{200\mu f}{2} = 100\mu f$$

Note:
Capacitors
in series
combine
like Resistors
in parallel

Find X_L and X_C using ω :

$$X_L = \omega L = (377 \text{ rad/sec})(0.1H) = 37.7\Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{(377 \text{ rad/sec})(100 \times 10^{-6} \text{ f.})} = 26.53\Omega$$

Find Total series impedance:

$$\bar{Z}_T = R \angle 0^\circ + X_L \angle 90^\circ + X_C \angle -90^\circ = 10\Omega + j37.7 - j26.53$$

$$\bar{Z}_T = 10 + j11.17 = 15\Omega \angle 48.16^\circ$$

Ex. ... continued

$$\bar{I} = \frac{\bar{E}}{\bar{Z}_T} = \frac{20 \angle 0^\circ}{15 \angle 48.16^\circ} = \boxed{1.33 \text{ A} \angle -48.16^\circ}$$

Then: $\bar{V}_R = \bar{I} \bar{Z}_R = (1.33 \angle -48.16^\circ)(10 \angle 0^\circ) = \boxed{13.3 \text{ V} \angle -48.16^\circ}$

$$\bar{V}_L = \bar{I} \bar{Z}_L = (1.33 \angle -48.16^\circ)(37.7 \angle 90^\circ) = \boxed{50.14 \text{ V} \angle 41.84^\circ}$$

$$\bar{V}_C = \bar{I} \bar{Z}_C = (1.33 \angle -48.16^\circ)(26.53 \angle -90^\circ) = \boxed{35.28 \angle -138.16^\circ}$$

b.) Calculate total power factor

The angle between $\bar{E}$ and $\bar{I}$ is also the angle of $\bar{Z}_T$


$$F_p = \cos \theta_{Z_T} = \cos 48.16^\circ = \boxed{0.667 \text{ lagging}}$$

Note: "lagging" because Z_T is inductive with a positive angle, i lags v


c.) Calculate the total power in watts delivered to the ckt.

$$P = EI \cos \theta = (20 \text{ V})(1.33 \text{ A})(0.667) = \boxed{17.74 \text{ watts}}$$

d.) Draw Phasor Diagram

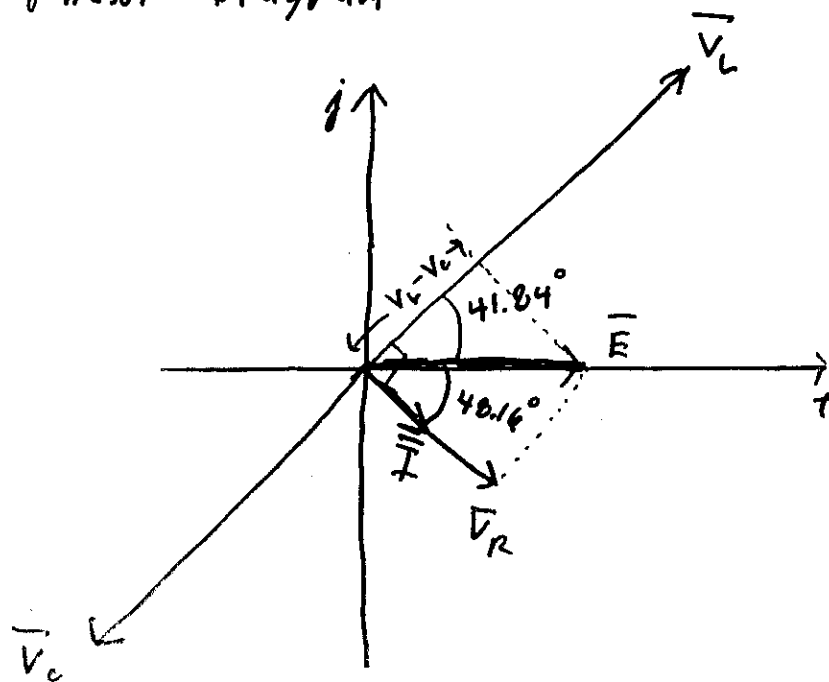


Frequency response of the RC circuit

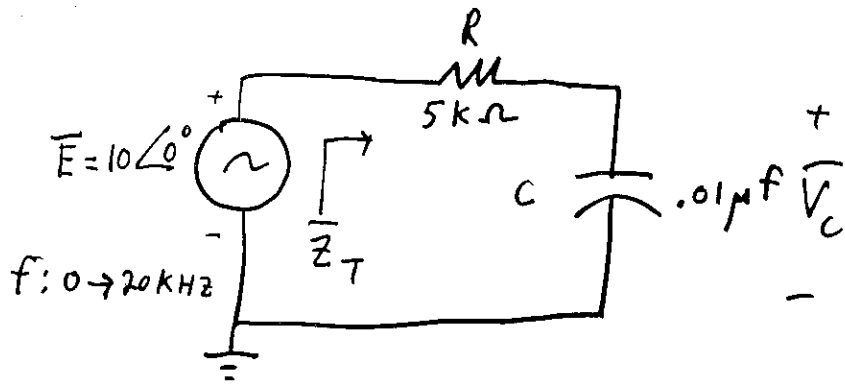

+ The impedance $\bar{Z}_T$ will vary with frequency. This is due to X_C decreasing as frequency is increased.

$$X_C = \frac{1}{2\pi fC}$$

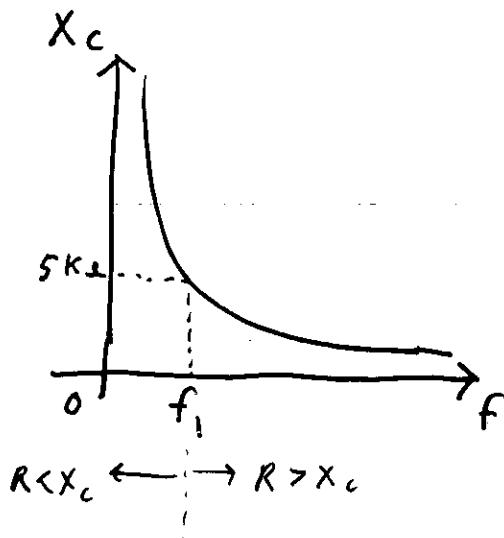

At some frequency f_1 , X_C will equal R :

$$X_C = \frac{1}{2\pi f_1 C} = R$$

$$f_1 = \frac{1}{2\pi RC}$$

f_1 called cut-off frequency or 3-DB freq.

ex/ $f_1 = \frac{1}{2\pi(5\text{k})(0.01\mu\text{F})} = 3183.1 \text{ Hz}$

$$\bar{Z}_T = R - jX_C = Z_T \angle \theta_T = \sqrt{R^2 + X^2} \angle -\tan^{-1} \frac{X_C}{R}$$

For $f = 100 \text{ Hz}$: $X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(100\text{Hz})(0.01\mu\text{F})} = 159.16 \text{ k}\Omega$

$$Z_T = \sqrt{R^2 + X_C^2} = \sqrt{(5\text{k})^2 + (159.16\text{k})^2} = 159.24 \text{ k}\Omega$$

$$\theta_T = -\tan^{-1} \frac{X_C}{R} = -\tan^{-1} \frac{159.16\text{k}}{5\text{k}} = -88.2^\circ$$

$$\bar{Z}_T = 159.24\text{k} \angle -88.2^\circ$$

ex) continued



$\bar{Z}_T$ computed for other freq. values:

$$f = 1 \text{ kHz} \rightarrow \bar{Z}_T = 5.93 \text{ k} \angle -32.48^\circ$$

$$f = 10 \text{ kHz} \rightarrow \bar{Z}_T = 5.25 \text{ k} \angle -17.66^\circ$$

$$f = 20 \text{ kHz} \rightarrow \bar{Z}_T = 5.06 \text{ k} \angle -9.04^\circ$$


Plotting Gives:

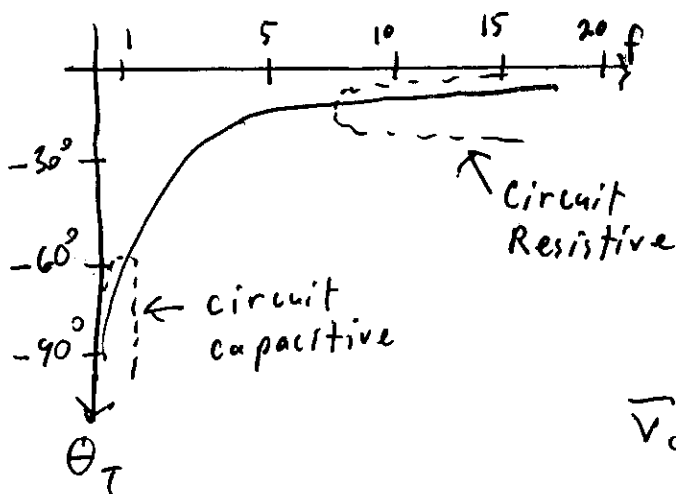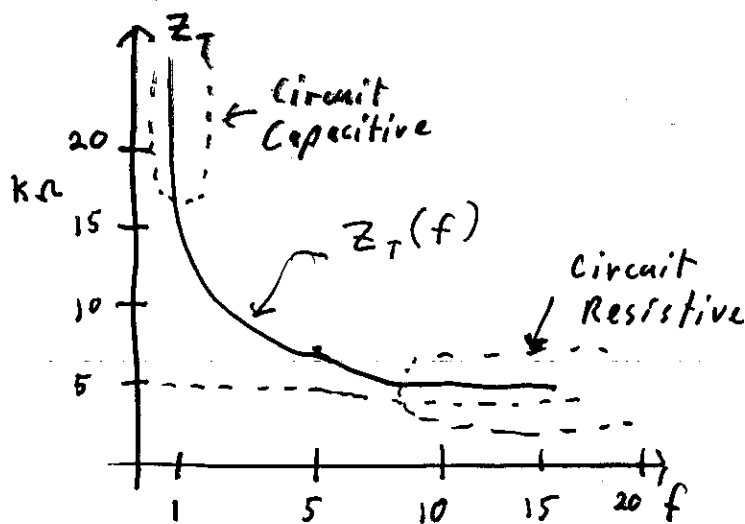

$$\bar{V}_C = \frac{X_C E}{\sqrt{R^2 + X_C^2}} \angle -90^\circ + \tan^{-1} \frac{X_C}{R}$$

For $f = 0 \text{ Hz}$ (D.C.) $\rightarrow X_C = \frac{1}{2\pi f C} = \frac{1}{0} \leftarrow$ very large (acts like open ckt.)

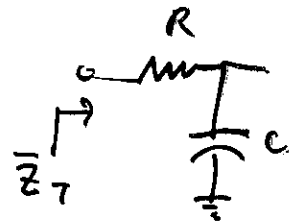So $\bar{V}_C = \bar{E} = 10 \text{ V} \angle 0^\circ$



$$\text{Since } \bar{Z}_T = R - jX_C,$$

at low freq. X_C is large
so the Capacitance dominates

At high freq. X_C is small
so the Resistance dominates

By the voltage divider rule:

$$\bar{V}_C = \frac{\bar{Z}_C \bar{E}}{\bar{Z}_C + \bar{Z}_R}$$

$$\bar{V}_C = \frac{(X_C \angle -90^\circ)(E \angle 0^\circ)}{R - jX_C}$$

$$\bar{V}_C = \frac{X_C E \angle -90^\circ}{\sqrt{R^2 + X_C^2}} \angle -\tan^{-1} \frac{X_C}{R}$$

ex / ... continued

From the equation:

$$V_c = \frac{X_c E}{\sqrt{R^2 + X_c^2}}$$

For $f = 0 \text{ Hz} \rightarrow X_c^2 \gg R^2$ so $\sqrt{R^2 + X_c^2} \approx \sqrt{X_c^2} = X_c$

then $V_c = \frac{X_c E}{X_c} = E$

also $\theta_c = -\tan^{-1} \frac{R}{X_c} = -\tan^{-1} 0 = 0^\circ$

for $f = 1 \text{ kHz}$: $X_c = \frac{1}{2\pi f c} = \frac{1}{2\pi (10^3)(0.01 \times 10^{-6})} = 15.92 \text{ k}\Omega$

$$\sqrt{R^2 + X_c^2} = \sqrt{(5 \text{ k})^2 + (15.92 \text{ k})^2} = 16.69 \text{ k}\Omega$$

$$V_c = \frac{X_c E}{\sqrt{R^2 + X_c^2}} = \frac{15.92 \text{ k} (10)}{16.69 \text{ k}} = 9.54 \text{ V}$$




$$\theta_c = -\tan^{-1} \frac{R}{X_c} = -\tan^{-1} \frac{5 \text{ k}}{15.9 \text{ k}} = -17.46^\circ$$

$$\bar{V}_c = 9.53 \text{ V} \angle -17.46^\circ$$

Similarly: for $f = 5 \text{ kHz} \rightarrow \bar{V}_c = 5.37 \text{ V} \angle -57.38^\circ$

$f = 10 \text{ kHz} \rightarrow \bar{V}_c = 3.03 \text{ V} \angle -72.34^\circ$

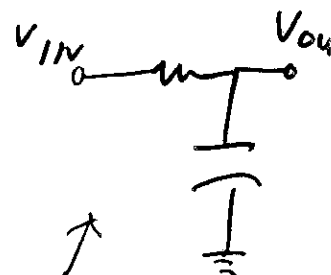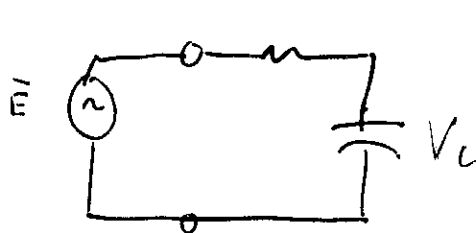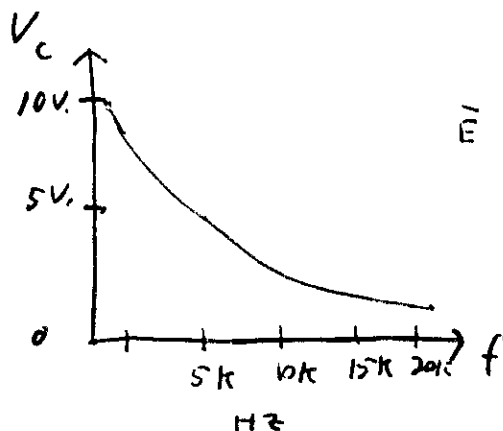$f = 20 \text{ kHz} \rightarrow \bar{V}_c = 1.57 \text{ V} \angle -80.79^\circ$



This RC circuit acts as a Low PASS filter

It passes low freq. and attenuates high freq.

Parallel A.C. Circuits

Admittance and Susceptance

For D.C. ckts we defined Conductance G as:


$$G = \frac{1}{R}$$

Similarly for A.C. ckts we define:

Admittance $\rightarrow \boxed{\bar{Y} = \frac{1}{\bar{Z}}}$ $\leftarrow \bar{Z} = \text{impedance}$

Susceptance $\rightarrow \boxed{B = \frac{1}{X}}$ $\leftarrow X = \text{reactance}$

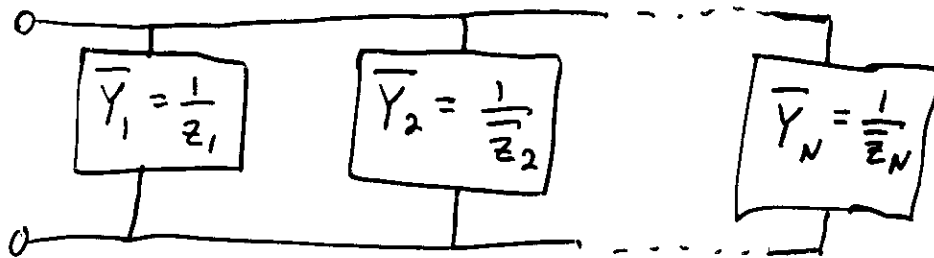The reciprocal quantities simplify analysis of parallel ckts.



$$\boxed{\bar{Y}_T = \bar{Y}_1 + \bar{Y}_2 + \dots + \bar{Y}_N}$$

Admittances in parallel add together

Also:

$$\boxed{\frac{1}{\bar{Z}_T} = \frac{1}{\bar{Z}_1} + \frac{1}{\bar{Z}_2} + \dots + \frac{1}{\bar{Z}_N}}$$

$\leftarrow$ parallel impedance combining rule

For 2 elements in parallel:

$$\boxed{\bar{Z}_T = \frac{\bar{Z}_1 \bar{Z}_2}{\bar{Z}_1 + \bar{Z}_2}}$$

For a Resistor:


$$\bar{Y}_R = \frac{1}{\bar{Z}_R} = \frac{1}{R \angle 0^\circ} = G \angle 0^\circ$$

For an Inductor:

$$\bar{Y}_L = \frac{1}{\bar{Z}_L} = \frac{1}{X_L \angle 90^\circ} = \frac{1}{X_L} \angle -90^\circ = B_L \angle -90^\circ$$


For a Capacitor:
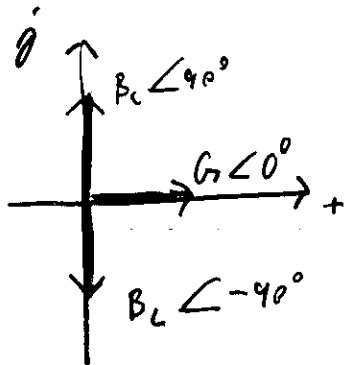
$$\bar{Y}_C = \frac{1}{\bar{Z}_C} = \frac{1}{X_C \angle -90^\circ} = \frac{1}{X_C} \angle 90^\circ = B_C \angle 90^\circ$$



← Admittance Diagram.

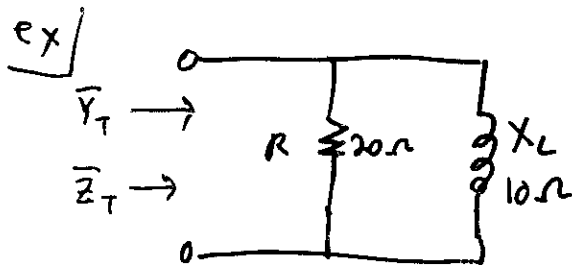Note: L and C interchange roles between parallel and series ckt's.



a) Find $\bar{Y}$ of each branch.

Sol: $\bar{Y}_R = G \angle 0^\circ = \frac{1}{R} \angle 0^\circ = \frac{1}{20} \angle 0^\circ$

$\bar{Y}_R = .05 \text{ S}$
 units of Siemens or $\frac{1}{\Omega}$

$\bar{Y}_L = B_L \angle -90^\circ = \frac{1}{X_L} \angle -90^\circ = \frac{1}{10} \angle -90^\circ = 0.1 \angle -90^\circ = -j(0.1)$

b) Find $\bar{Y}_T$

Sol: $\bar{Y}_T = \bar{Y}_R + \bar{Y}_L = (.05) - j0.1 \text{ S}$


c) Find $\bar{Z}_T$

Sol: $\bar{Z}_T = \frac{1}{\bar{Y}_T} = \frac{1}{(.05) - j0.1} = .112 \angle 63.43^\circ$


$\bar{Z}_T = 8.93 \angle 63.43^\circ$

also $\bar{Z}_T = \frac{\bar{Z}_R \bar{Z}_L}{\bar{Z}_R + \bar{Z}_L}$

d.) Draw Admittance Diagram

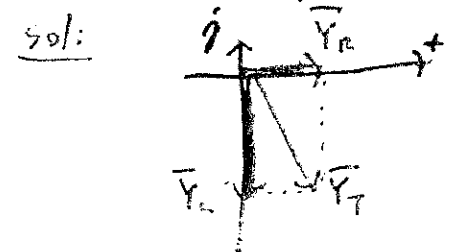

ex/

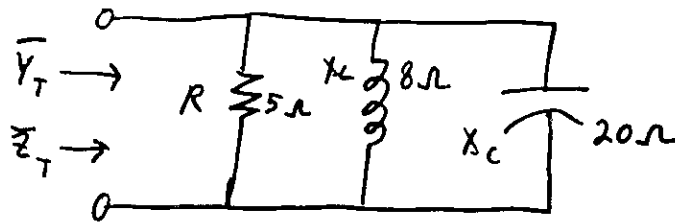

a.) Find $\bar{Y}$ of each branch

Sol: $\bar{Y}_R = \frac{1}{R} \angle 0^\circ = \frac{1}{5\Omega} \angle 0^\circ$

$$\bar{Y}_R = 0.2 S \angle 0^\circ = 0.2 S + j0$$

$$\bar{Y}_L = \frac{1}{X_L} \angle -90^\circ = \frac{1}{8\Omega} \angle -90^\circ = 0.125 S \angle -90^\circ = 0 - j0.125 S.$$

$$\bar{Y}_C = \frac{1}{X_C} \angle 90^\circ = \frac{1}{20\Omega} \angle 90^\circ = 0.05 S \angle 90^\circ = 0 + j0.05 S.$$

b.) Find $\bar{Y}_T$


Sol: $\bar{Y}_T = \bar{Y}_R + \bar{Y}_L + \bar{Y}_C = 0.2 - j0.125 + j0.05 = 0.2 - j0.075$
 $= 0.2136 \angle -20.56$

c.) Find $\bar{Z}_T$

Sol: $\bar{Z}_T = \frac{1}{\bar{Y}_T} = \frac{1}{0.2136} \angle -20.56 = 4.68\Omega \angle 20.56$

d.) Draw the admittance diagram

Sol:

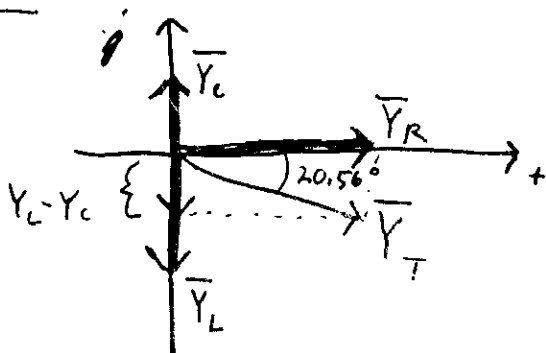


The total $\bar{Y}_T$ is inductive because the smaller X_L value will draw more of the current than the larger X_C value.

It is easier to use Admittances for parallel circuits instead of Impedances.

Parallel A.C. Networks

By Ohm's Law:

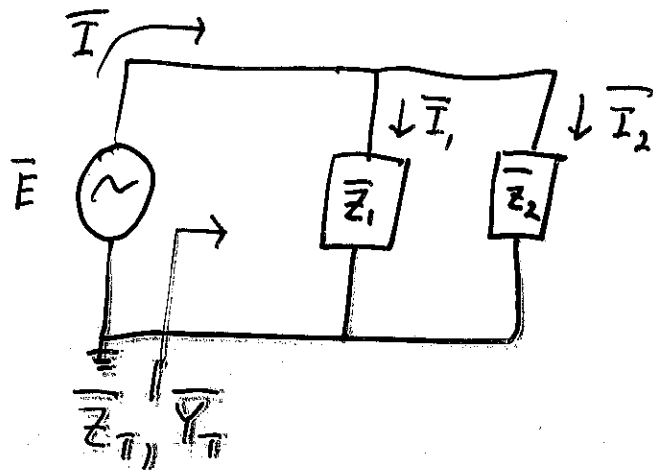


$$\bar{I} = \frac{\bar{E}}{\bar{Z}_T} = \bar{E} \bar{Y}_T$$

$$\bar{I}_1 = \frac{\bar{E}}{\bar{Z}_1} = \bar{E} \bar{Y}_1$$

$$\bar{I}_2 = \frac{\bar{E}}{\bar{Z}_2} = \bar{E} \bar{Y}_2$$

By KCL: $\bar{I} = \bar{I}_1 + \bar{I}_2$

Also $P = EI \cos \theta_T$

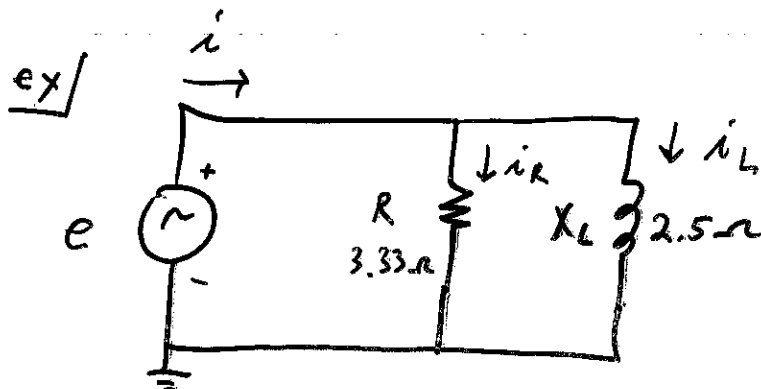

Find i , i_R , i_L

Given: $e = \sqrt{2}(20) \sin(\omega t + 53.13^\circ)$

Solution: $\bar{Y}_T = \bar{Y}_R + \bar{Y}_L = \frac{1}{3.33} \angle 0^\circ + \frac{1}{2.5} \angle -90^\circ = 0.3 \angle 0^\circ + 0.4 \angle -90^\circ$

$$\bar{Y}_T = 0.3 - j0.4 = 0.5 \angle -53.13^\circ$$

$$\bar{I} = \bar{E} \bar{Y}_T = (20 \angle 53.13^\circ)(0.5 \angle -53.13^\circ) = 10 \text{ A} \angle 0^\circ$$

$$i = (\sqrt{2}) 10 \sin \omega t$$

$$\bar{I}_R = \bar{E} \bar{Y}_R = (20 \angle 53.13^\circ)(0.3 \angle 0^\circ) = 6 \text{ A} \angle 53.13^\circ$$

$$i_R = (\sqrt{2}) 6 \sin(\omega t + 53.13^\circ)$$


$$\bar{I}_L = \bar{E} \bar{Y}_L = (20 \angle 53.13^\circ)(0.4 \angle -90^\circ) = 8 \text{ A} \angle -36.87^\circ$$

$$i_L = (\sqrt{2}) 8 \sin(\omega t - 36.87^\circ)$$


$$P = (20)(10) \cos 53.13^\circ$$

$$P = 120 \text{ W}$$

Current Divider Rule

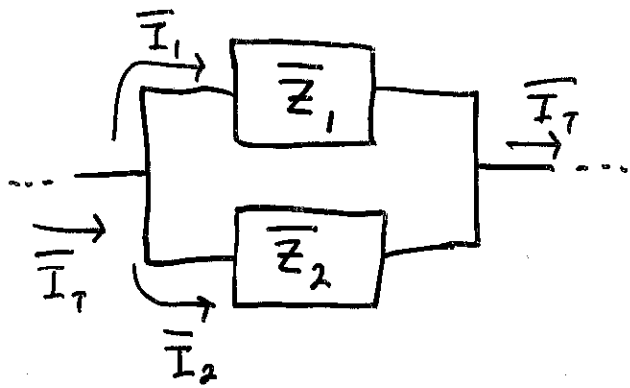
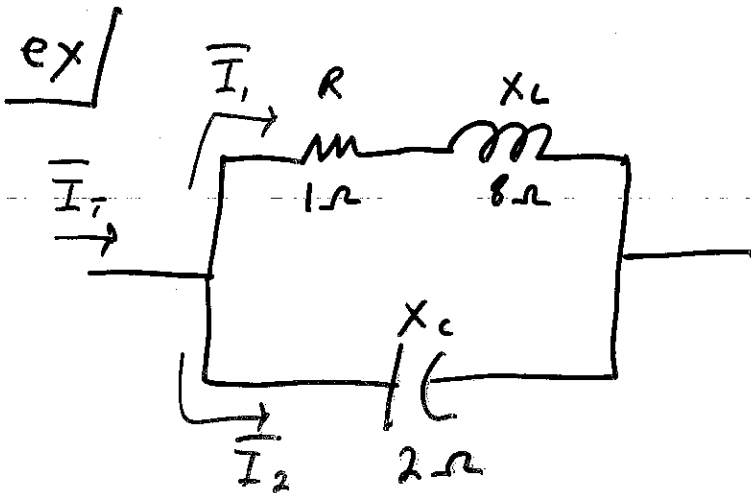
$$\boxed{\begin{aligned}\bar{I}_1 &= \bar{I}_T \frac{\bar{Z}_2}{\bar{Z}_1 + \bar{Z}_2} \\ \bar{I}_2 &= \bar{I}_T \frac{\bar{Z}_1}{\bar{Z}_1 + \bar{Z}_2}\end{aligned}}$$



Find $\bar{I}_1$ and $\bar{I}_2$

Given $\bar{I}_T = 5A \angle 30^\circ$

Solution:

By Current Divider Rule:

$$\bar{I}_1 = \bar{I}_T \frac{\bar{Z}_C}{\bar{Z}_C + \bar{Z}_{RL}} = \frac{(5 \angle 30^\circ) (2 \angle -90^\circ)}{2 \angle -90^\circ + (1 \angle 0^\circ + 8 \angle 90^\circ)}$$

$$\bar{I}_1 = \frac{10 \angle -60^\circ}{-j2 + 1 + j8} = \frac{10 \angle -60^\circ}{1 + j6} = \frac{10 \angle 60^\circ}{6.08 \angle 80.54^\circ} = 1.64A \angle -140.54^\circ$$

$$\bar{I}_2 = \bar{I}_T \frac{\bar{Z}_{RL}}{\bar{Z}_C + \bar{Z}_{RL}} = \frac{(5 \angle 30^\circ) (1 + j8)}{6.08 \angle 80.54^\circ} = \frac{(5 \angle 30^\circ) (8.06 \angle 82.87^\circ)}{6.08 \angle 80.54^\circ}$$

$$\bar{I}_2 = 6.625A \angle 32.33^\circ$$

Can check by KCL: $\bar{I}_T = \bar{I}_1 + \bar{I}_2$