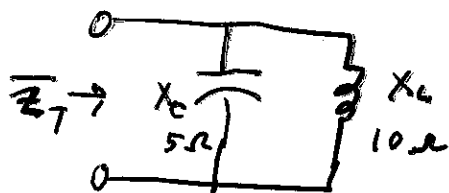


Equivalent Circuits

Equivalent circuits will have the same impedance and the same input current will result for the same applied voltage.


ex/




$$\bar{Z}_T = \frac{\bar{Z}_C \bar{Z}_L}{\bar{Z}_C + \bar{Z}_L}$$

$$\bar{Z}_T = \frac{(5 \angle -90^\circ)(10 \angle 90^\circ)}{5 \angle -90^\circ + 10 \angle 90^\circ} = \frac{50 \angle 0^\circ}{5 \angle 90^\circ} = 10 \Omega \angle -90^\circ$$

The equivalent circuit is;

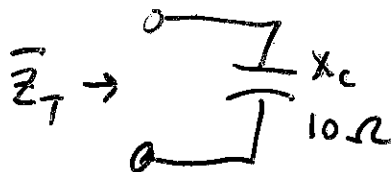

ex/

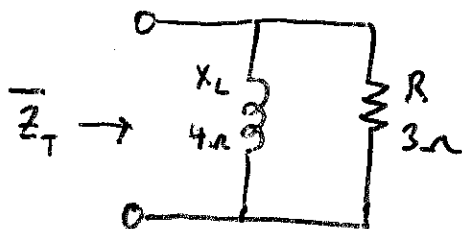


$$\bar{Z}_T = \frac{\bar{Z}_L \bar{Z}_R}{\bar{Z}_L + \bar{Z}_R} = \frac{(4 \angle 90^\circ)(3 \angle 0^\circ)}{4 \angle 90^\circ + 3 \angle 0^\circ}$$

$$\bar{Z}_T = \frac{12 \angle 90^\circ}{5 \angle 53.13^\circ} = 2.4 \angle 36.87^\circ$$

$$\bar{Z}_T = 1.92 + j 1.44 \Omega$$

Equivalent
ckt. is:

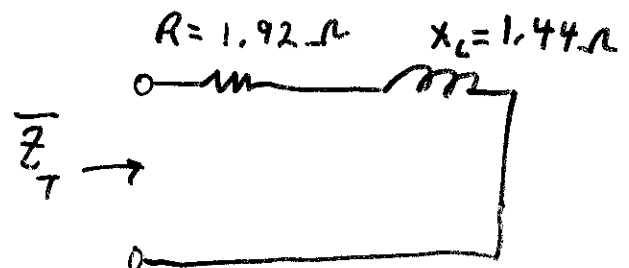

To find a parallel equivalent circuit it is easier to work with admittance instead of impedance.

1.) First total impedance: $\bar{Z}_T$


2.) Convert to total admittance: $\bar{Y}_T = \frac{1}{\bar{Z}_T}$

3.) Identify the Real part of $\bar{Y}_T$. G
Then $R = \frac{1}{G}$

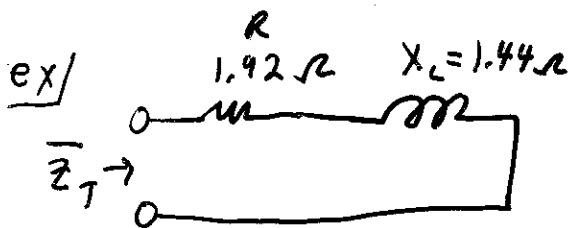4.) Identify the Imaginary part of $\bar{Y}_T$. B
Then $X = \frac{1}{B}$

If B is negative then $X = X_L$ (inductive).

If B is positive then $X = X_C$ (Capacitive)



Find equivalent parallel ckt.


Sol: $\bar{Z}_T = 1.92 + j1.44 = 2.4 \angle 36.87^\circ$

$$\bar{Y}_T = \frac{1}{2.4 \angle 36.87^\circ} = 0.4167 \angle -36.87^\circ = 0.333 - j0.25$$

$$R = \frac{1}{0.333} = 3 \Omega$$


$$X = \frac{1}{0.25} = 4 \Omega = X_L$$

since its negative its inductive

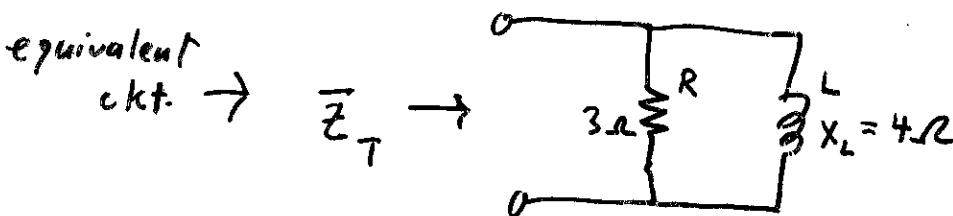


Series - Parallel AC Networks

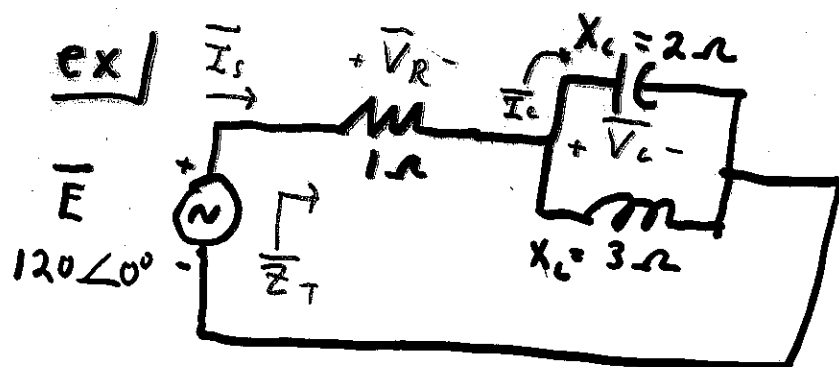It is often useful to combine elements together into impedance blocks to simplify the circuit analysis.



Find: $\bar{Z}_T$, $\bar{I}_s$, $\bar{V}_R$,
 $\bar{V}_c$, $\bar{I}_c$, P ,
 F_P

Solution: Redraw Ckt.

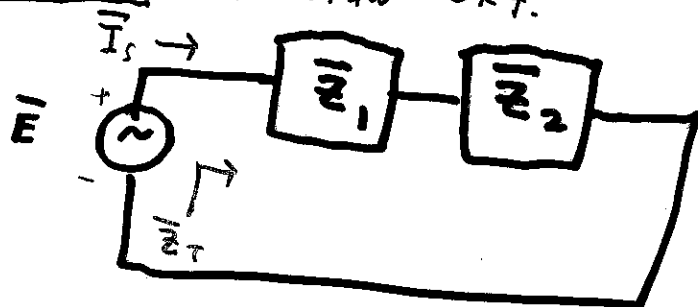

$$\bar{Z}_T = \bar{Z}_1 + \bar{Z}_2$$

$$\bar{Z}_1 = 1\Omega \angle 0^\circ$$

$$\bar{Z}_2 = \bar{Z}_c || \bar{Z}_l = \frac{(2\angle -90^\circ)(3\angle 90^\circ)}{-j2 + j3} = \frac{6\angle 0^\circ}{j1} = \frac{6\angle 0^\circ}{1\angle 90^\circ} = 6\angle -90^\circ$$

$$\bar{Z}_T = 1\Omega - j6\Omega = \boxed{6.08\Omega \angle -80.54^\circ}$$

By Ohms Law:

$$\bar{I}_s = \frac{\bar{E}}{\bar{Z}_T} = \frac{120\angle 0^\circ}{6.08\angle -80.54^\circ} = \boxed{19.74A \angle 80.54^\circ}$$

$$\bar{V}_R = \bar{I}_s \bar{Z}_1 = (19.74\angle 80.54^\circ)(1\Omega \angle 0^\circ) = \boxed{19.74V \angle 80.54^\circ}$$

$$\bar{V}_c = \bar{I}_s \bar{Z}_2 = (19.74\angle 80.54^\circ)(6\Omega \angle -90^\circ) = \boxed{118.44V \angle -9.46^\circ}$$

ex) continued

$$\bar{I}_c = \frac{\bar{V}_c}{\bar{Z}_c} = \frac{118.44 \text{ V. } \angle -9.46^\circ}{2 \Omega \angle -90^\circ} = \boxed{59.22 \text{ A. } \angle 80.54^\circ}$$

The total power delivered to the ckt. from the source is dissipated by the resistor.

$$P = I_s^2 R = (19.74 \text{ A.})^2 (1 \Omega) = \boxed{389.67 \text{ W.}}$$

Power could also have been found from:


$$P = E I_s \cos \theta$$

↑ θ is the angle of $\bar{Z}_T$

The power factor F_p is:


$$F_p = \cos \theta = \cos(-80.54^\circ) = \boxed{0.164 \text{ leading}}$$

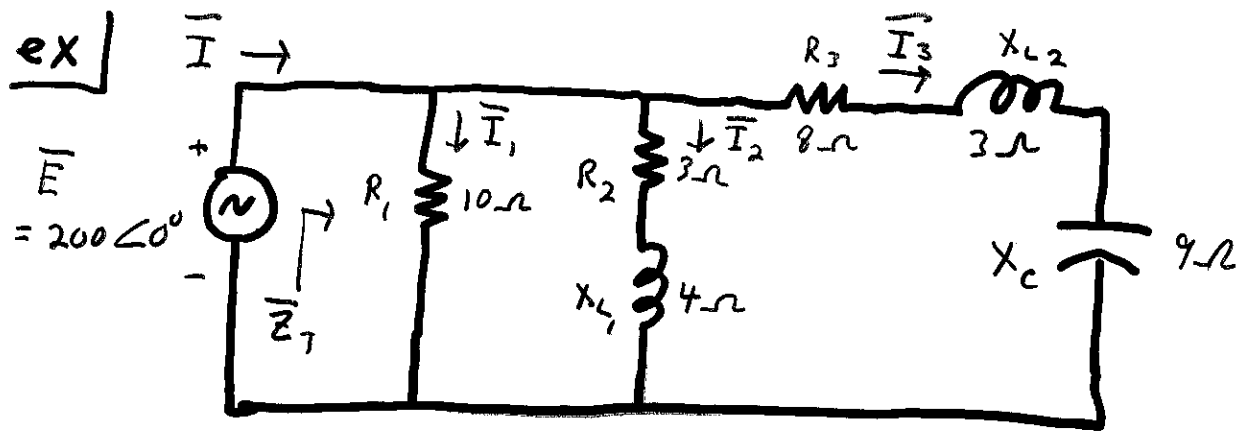It's leading since the angle of $\bar{Z}_T$ is negative which means the net impedance is capacitive.



Find: $\bar{I}$, $\bar{I}_1$, $\bar{I}_2$, $\bar{I}_3$, $\bar{Z}_T$

Solution: Redraw ckt.

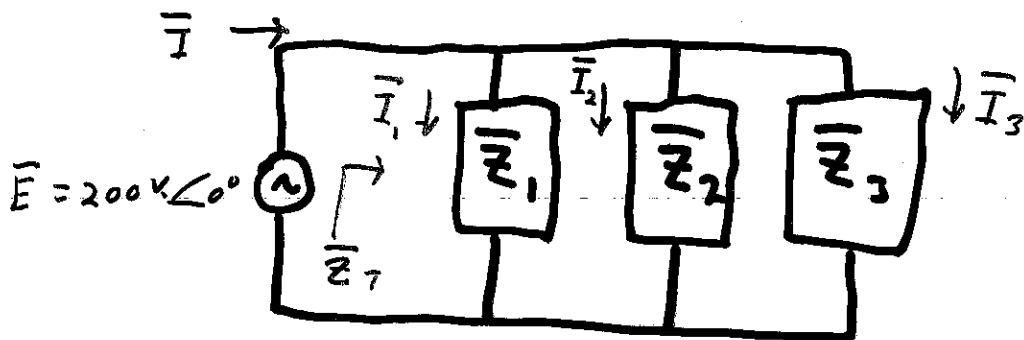

$$\bar{Z}_1 = R_1 = 10 \angle 0^\circ \Omega$$

$$\bar{Z}_2 = R_2 + jX_{L1} = 3\Omega + j4\Omega$$

$$\bar{Z}_3 = R_3 + jX_{L2} - jX_C = 8 + j3 - j9 = 8 - j6 \Omega$$

For a parallel ckt. it's easier to work with admittance.

$$\bar{Y}_T = \bar{Y}_1 + \bar{Y}_2 + \bar{Y}_3 = \frac{1}{\bar{Z}_1} + \frac{1}{\bar{Z}_2} + \frac{1}{\bar{Z}_3} = \frac{1}{10} + \frac{1}{3+j4} + \frac{1}{8-j6}$$

$$\bar{Y}_T = 0.1 + \frac{1}{5 \angle 53.13^\circ} + \frac{1}{10 \angle -36.87^\circ} = 0.1 + 0.2 \angle -53.13^\circ + 0.1 \angle 36.87^\circ$$

$$\bar{Y}_T = 0.1 + 0.12 - j0.16 + 0.08 + j0.06 = 0.3 - j0.1 = 0.316 \angle -18.435^\circ$$

By Ohm's Law:

$$\bar{I} = \bar{E} \bar{Y}_T = (200 \text{ V} \angle 0^\circ)(0.316 \angle -18.435^\circ) =$$

$$\bar{I} = \boxed{63.2 \text{ A} \angle -18.435^\circ}$$

ex/ continued

$$\bar{I}_1 = \frac{\bar{E}}{\bar{Z}_1} = \frac{200V \angle 0^\circ}{10\Omega \angle 0^\circ} = \boxed{20A \angle 0^\circ}$$

$$\bar{I}_2 = \frac{\bar{E}}{\bar{Z}_2} = \frac{200V \angle 0^\circ}{5\Omega \angle 53.13^\circ} = \boxed{40A \angle -53.13^\circ}$$

$$\bar{I}_3 = \frac{\bar{E}}{\bar{Z}_3} = \frac{200V \angle 0^\circ}{10\Omega \angle -36.87^\circ} = \boxed{20A \angle 36.87^\circ}$$

We can check results using KCL:

$$\bar{I} = \bar{I}_1 + \bar{I}_2 + \bar{I}_3$$

$$63.2A \angle -18.435^\circ \stackrel{?}{=} 20 \angle 0^\circ + 40 \angle -53.13^\circ + 20 \angle 36.87^\circ$$

$$60 - j20 = (20 + j0) + (24 - j32) + (16 + j12)$$

$$60 - j20 = 60 - j20$$

checks ✓

Also,

$$\bar{Z}_T = \frac{1}{\bar{Y}_T} = \frac{1}{0.316 S \angle -18.435^\circ}$$


$$\bar{Z}_T = \boxed{3.165\Omega \angle 18.435^\circ}$$

$$P = I_1^2 R_1 + I_2^2 R_2 + I_3^2 R_3$$

$$F_p = \cos \theta = \cos 18.435^\circ$$

Ladder Networks

ex/

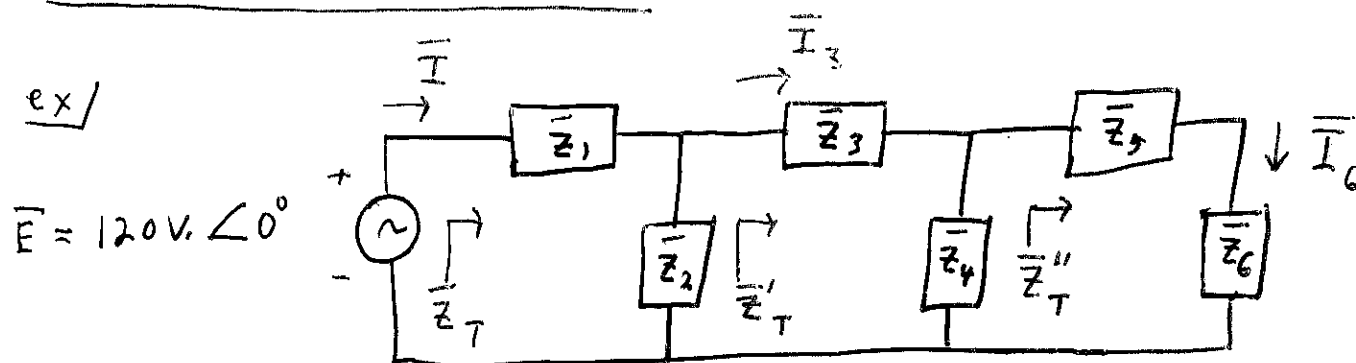

Find $\bar{I}_6$

Solution Method:

Begin at far end and find $\bar{Z}_T$

$$\bar{Z}_T'' = \bar{Z}_5 + \bar{Z}_6$$

$$\bar{Z}_T' = \bar{Z}_3 + \bar{Z}_4 \parallel \bar{Z}_T''$$

$$\bar{Z}_T = \bar{Z}_1 + \bar{Z}_2 \parallel \bar{Z}_T'$$

Then find total current $\bar{I}$: $\bar{I} = \frac{\bar{E}}{\bar{Z}_T}$


Use repeated application of CDR to find other currents:

$$\bar{I}_3 = \frac{\bar{Z}_2 \bar{I}}{\bar{Z}_2 + \bar{Z}_T'}$$

$$\bar{I}_6 = \frac{\bar{Z}_4 \bar{I}_3}{\bar{Z}_4 + \bar{Z}_T''}$$

Resonance

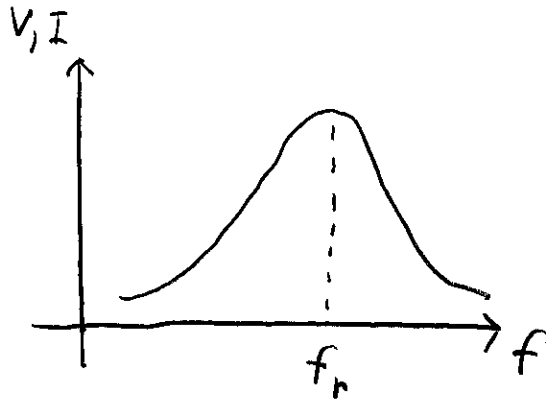
At a particular frequency f_r , an L-C circuit will exhibit resonance.



At the resonant frequency: $X_L = X_C$

The LC circuit is also called a tuned circuit.


Series Resonant Circuit

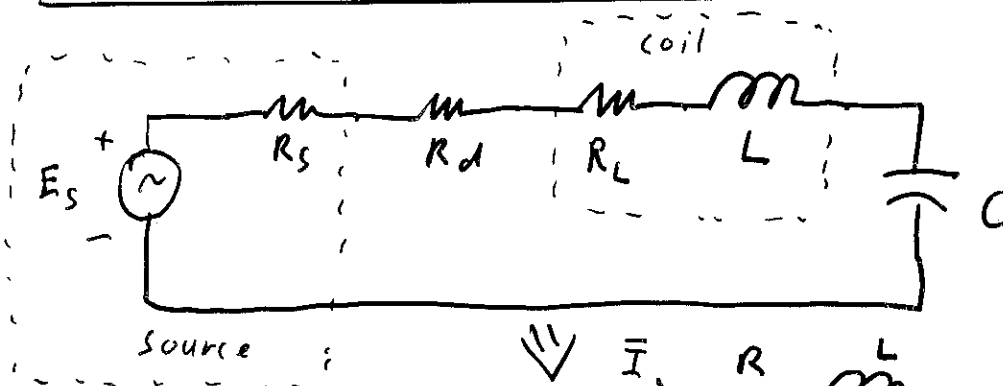

Source:

Equiv. ckt:

$$R = R_s + R_d + R_L$$

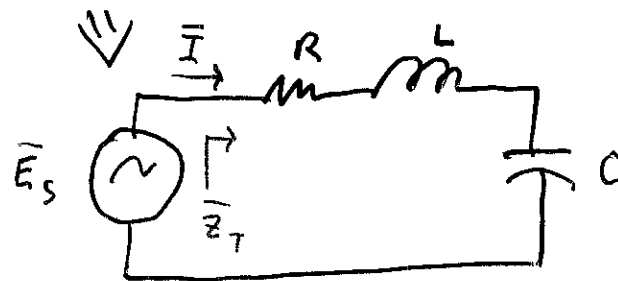

$$\bar{Z}_T = R + jX_L - jX_C = R + j(X_L - X_C)$$

At the resonant frequency the inductive reactance and the capacitive reactance cancel each other out.

At Resonance:

$$X_L = X_C$$

$$\bar{Z}_{T_s} = R$$

When $X_L = X_C$,

$$\omega L = \frac{1}{\omega C}$$

$$\omega^2 = \frac{1}{LC}$$

$f = \text{Hz.}$

$L = \text{Henries}$


$C = \text{Farads}$

$$\omega_s = \frac{1}{\sqrt{LC}} \quad f_s = \frac{1}{2\pi\sqrt{LC}}$$

Resonant Frequency


$$\begin{aligned} \bar{V}_L &= (I \angle 0^\circ)(X_L \angle 90^\circ) = IX_L \angle 90^\circ \\ \bar{V}_C &= (I \angle 0^\circ)(X_C \angle -90^\circ) = IX_C \angle -90^\circ \end{aligned} \quad \left. \vphantom{\begin{aligned} \bar{V}_L &= (I \angle 0^\circ)(X_L \angle 90^\circ) = IX_L \angle 90^\circ \\ \bar{V}_C &= (I \angle 0^\circ)(X_C \angle -90^\circ) = IX_C \angle -90^\circ \end{aligned}} \right\} 180^\circ \text{ out of phase}$$

$$V_{L_s} = V_{C_s}$$

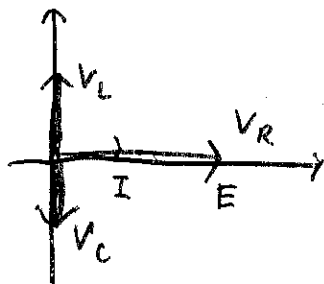

At resonance $\bar{Z}_T$ is
Purely Real (the imaginary
parts cancel out).

$$\text{So } F_{p_s} = \cos \theta = 1$$

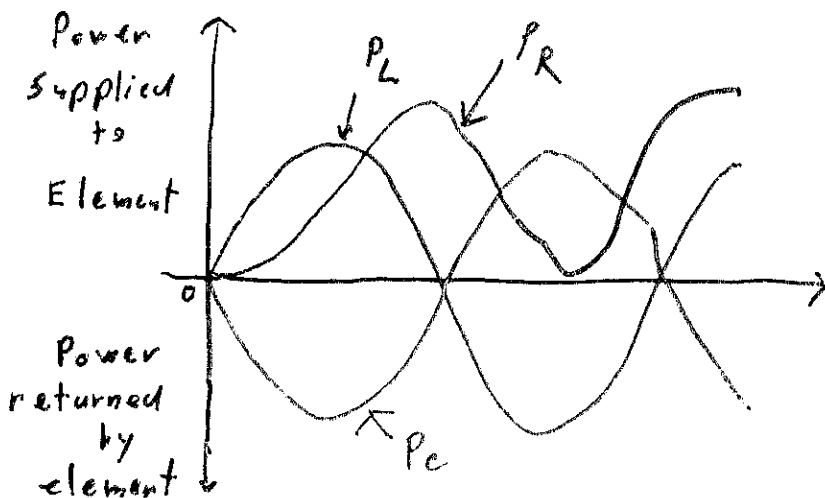

Energy is exchanged
between L and C
during each half
Cycle.

The Quality Factor "Q"

The Q of a resonant circuit is measure of how much the reactive elements dominate over the resistive elements. i.e. how close it resembles a "loss less" tuned circuit.

$$Q_s = \frac{\text{reactive Power} \leftarrow \text{VARs}}{\text{average Power} \leftarrow \text{Watts}}$$


For the series RL circuit:

$$Q_s = \frac{I^2 X_L}{I^2 R}$$

$$Q_s = \frac{X_L}{R} = \frac{\omega_s L}{R}$$

For a coil where R_L is the wire's resistance:

$$Q_{\text{coil}} = \frac{X_L}{R_L}$$

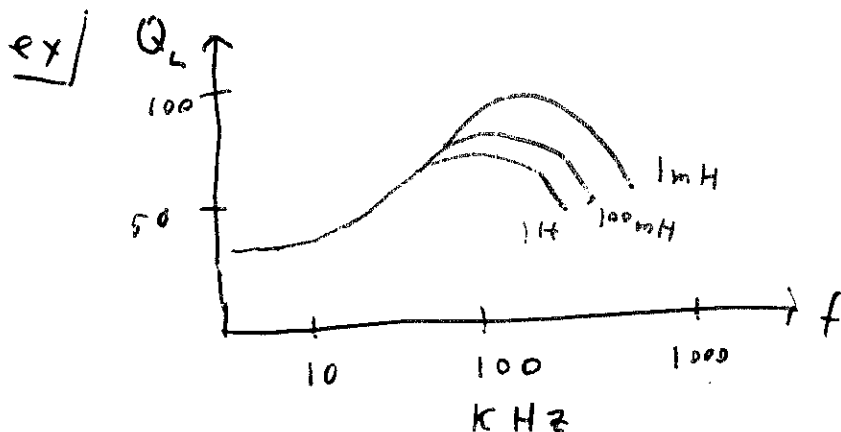

For an RLC series circuit:

$$Q_s = \frac{\omega_s L}{R} = \frac{2\pi f_s L}{R}$$

$$\text{Also } f_s = \frac{1}{2\pi\sqrt{LC}}$$

Substituting gives:


$$Q_s = \frac{2\pi \left(\frac{1}{2\pi\sqrt{LC}} \right) L}{R}$$

$$\boxed{Q_s = \frac{1}{R} \sqrt{\frac{L}{C}}} \quad \leftarrow \text{for series RLC}$$

At resonance $V_L = \frac{X_L E}{Z_T} = \frac{X_L}{R} E$

$$\boxed{V_{L_s} = Q_s E} \quad \text{similarly} \quad \boxed{V_{C_s} = Q_s E}$$

ex/

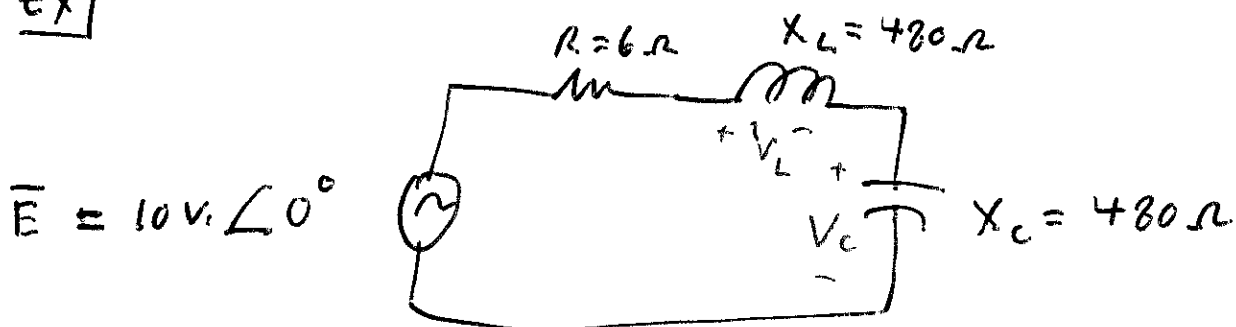

$$Q_s = \frac{X_L}{R} = \frac{480\Omega}{6\Omega} = 80$$

$$V_L = V_C = Q_s E = (80)(10) = 800\text{V} \quad \leftarrow$$

Note: V_L and V_C
much larger
than applied voltage


Z_T Versus Frequency

For the series RLC circuit

$$\bar{Z}_T = R + jX_L - jX_C = R + j(X_L - X_C)$$


Magnitude of $\bar{Z}_T$:

$$|Z_T| = \sqrt{R^2 + (X_L - X_C)^2}$$

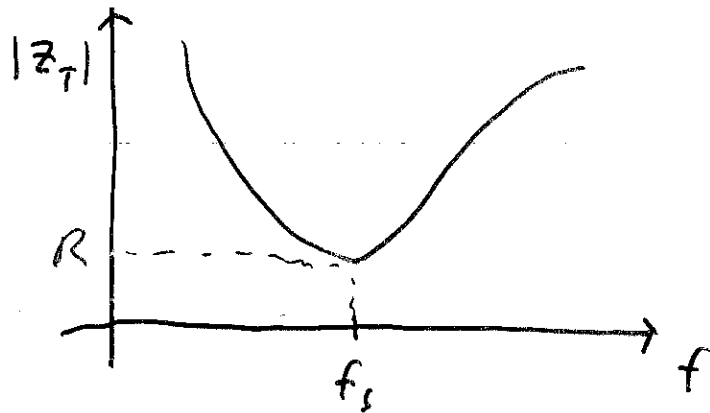


$|Z_T|$ is a minimum at resonance for the series RLC circuit
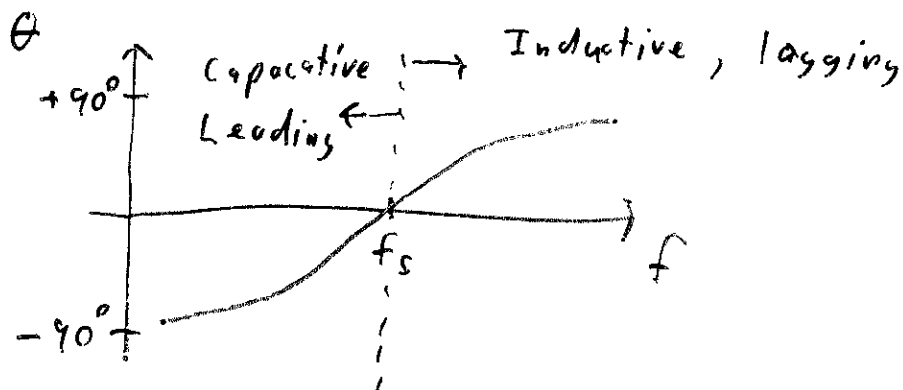
$$\theta = \tan^{-1} \frac{(X_L - X_C)}{R}$$



Selectivity

For the series RLC circuit:

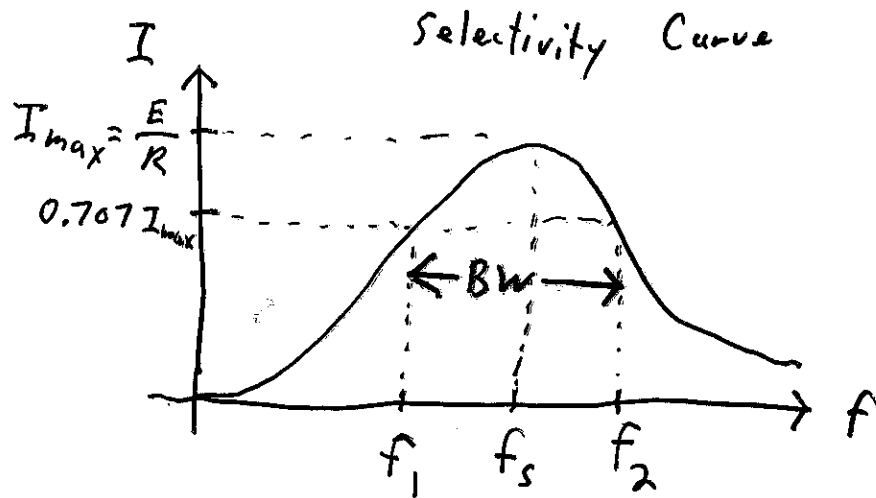

$$P = I^2 R$$

$$\frac{1}{2} P = \left(\frac{I}{\sqrt{2}} \right)^2 R$$

Power:

$$P_{HPF} = \frac{1}{2} P_{max}$$

$$BW = f_2 - f_1$$

f_s is the resonant or center frequency.

f_1 is the lower cutoff or half-power frequency.

f_2 is the upper cutoff or half-power frequency.


The range of frequencies between f_1 and f_2 is called the Bandwidth (BW).

The BW depends upon the Q of the c/c/t.

$$BW = \frac{f_s}{Q_s}$$

$$\frac{f_2 - f_1}{f_s} = \frac{1}{Q_s}$$

↑
fractional
BW

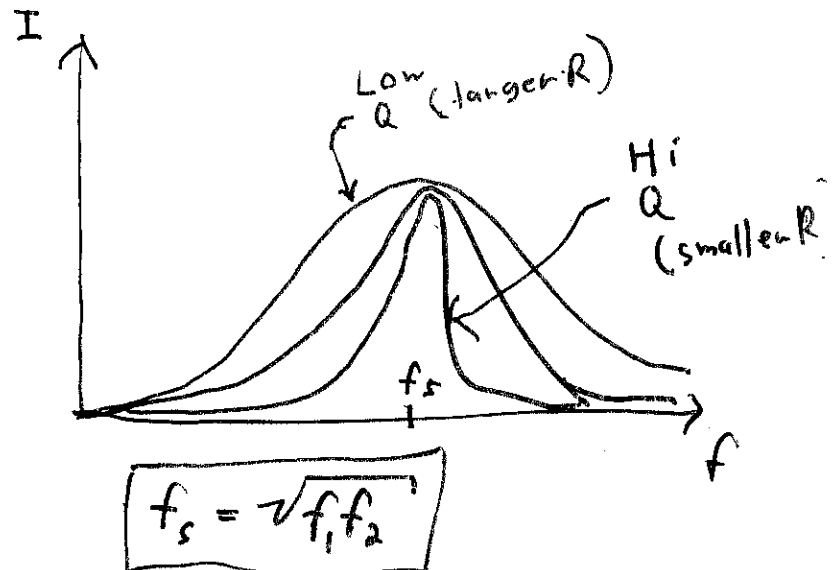

For the series RLC circuit:

$$f_s = \frac{1}{2\pi\sqrt{LC}}$$

$$Q_s = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$f_1 = \frac{1}{2\pi} \left[-\frac{R}{2L} + \frac{1}{2} \sqrt{\left(\frac{R}{L}\right)^2 + \frac{4}{LC}} \right]$$


$$f_2 = \frac{1}{2\pi} \left[\frac{R}{2L} + \frac{1}{2} \sqrt{\left(\frac{R}{L}\right)^2 + \frac{4}{LC}} \right]$$

$$BW = f_2 - f_1 = \frac{R}{2\pi L}$$

For $Q \geq 10$ it can be assumed that f_s is in the center of the BW. This simplifies finding f_1 and f_2 to:

$$f_1 = f_s - \frac{BW}{2}$$

$$f_2 = f_s + \frac{BW}{2}$$

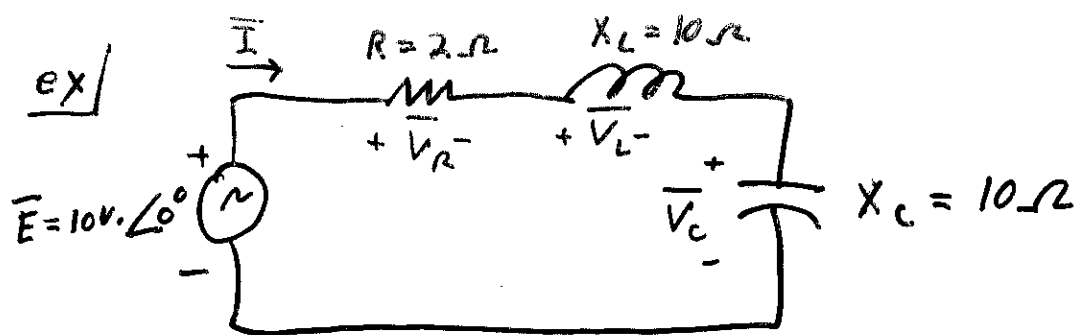

a) Find $\bar{I}$, $\bar{V}_R$, $\bar{V}_L$ and $\bar{V}_C$ for series resonant ckt.

Solution:

$$\bar{Z}_{T_s} = R = 2\Omega$$

$$\bar{I} = \frac{\bar{E}}{\bar{Z}_{T_s}} = \frac{10V \angle 0^\circ}{2\Omega \angle 0^\circ} = \boxed{5A \angle 0^\circ}$$

$$\bar{V}_R = \bar{E} = \boxed{10V \angle 0^\circ}$$

$$\bar{V}_L = \bar{I} \bar{Z}_L = (5 \angle 0^\circ)(10 \angle 90^\circ) = \boxed{50V \angle 90^\circ}$$

$$\bar{V}_C = \bar{I} \bar{Z}_C = (5 \angle 0^\circ)(10 \angle -90^\circ) = \boxed{50V \angle -90^\circ}$$

b) Find Q_s

Solution:

$$Q_s = \frac{X_L}{R} = \frac{10\Omega}{2\Omega} = \boxed{5}$$

c) If the resonant frequency is 5 kHz, find BW.

Solution:

$$BW = f_2 - f_1 = \frac{f_s}{Q_s} = \frac{5000\text{ Hz}}{5} = \boxed{1\text{ kHz}}$$

d) What is the power dissipated in the circuit at the half-power frequencies?

Solution:

$$P_{HPF} = \frac{1}{2} P_{max} = \frac{1}{2} I_{max}^2 R = \left(\frac{1}{2}\right)(5A)^2(2\Omega) = \boxed{25W}$$

ex The bandwidth of a series resonant circuit is 400 Hz.

a.) If the resonant frequency is 4000 Hz, what is the Q?

solution:

$$BW = \frac{f_s}{Q_s} \quad \text{so} \quad Q = \frac{f_s}{BW} = \frac{4000 \text{ Hz}}{400 \text{ Hz}} = \boxed{10}$$

b.) If $R = 10 \Omega$, what is the value of X_L at resonance?

solution:

$$Q_s = \frac{X_L}{R} \quad \text{so} \quad X_L = Q_s R = (10)(10 \Omega) = \boxed{100 \Omega}$$

c.) Find the inductance L and Capacitance C of the circuit.

solution:

$$X_L = 2\pi f_s L \quad \text{so} \quad L = \frac{X_L}{2\pi f_s} = \frac{100 \Omega}{2\pi(4000 \text{ Hz})} = \boxed{3.98 \text{ mH}}$$

$$X_C = \frac{1}{2\pi f_s C} \quad \text{so} \quad C = \frac{1}{2\pi f_s X_C} = \frac{1}{2\pi(4000)(100)} = \boxed{0.398 \mu\text{F}}$$

ex A series RLC circuit has a resonant frequency of 12,000 Hz.

a.) If $R = 5 \Omega$ and X_L at resonance is 300Ω , find BW.

solution:

$$Q_s = \frac{X_L}{R} = \frac{300 \Omega}{5 \Omega} = 60 \quad \text{Then} \quad BW = \frac{f_s}{Q_s} = \frac{12,000 \text{ Hz}}{60} = \boxed{200 \text{ Hz}}$$

b.) Find the cutoff frequencies.

solution: Since $Q_s \geq 10$:

$$f_1 = f_s + \frac{BW}{2} = 12,000 \text{ Hz} + 100 \text{ Hz} = \boxed{12,100 \text{ Hz}}$$

$$f_2 = f_s - \frac{BW}{2} = 12,000 - 100 = \boxed{11,900 \text{ Hz}}$$

ex/ A series RLC circuit is designed to resonate at $\omega_s = 10^5 \text{ rad/s}$, have a $BW = 0.15 \omega_s$ and draw 16 W. from a 120 V. source at resonance.

a.) Determine the value of R

solution: $P = \frac{E^2}{R}$ so, $R = \frac{E^2}{P} = \frac{(120 \text{ V})^2}{16 \text{ W}} = \boxed{900 \Omega}$

b.) Find BW in Hertz.

solution: $f_s = \frac{\omega_s}{2\pi} = \frac{10^5 \text{ rad/s}}{2\pi} = 15,915 \text{ Hz}$

$$BW = 0.15 f_s = 0.15 (15,915) = \boxed{2387 \text{ Hz.}}$$

c.) Find the values of L and C.

solution: $BW = \frac{R}{2\pi L}$ so, $L = \frac{R}{2\pi BW} = \frac{900 \Omega}{2\pi (2387 \text{ Hz})} = \boxed{60 \text{ mH.}}$

Then $f_s = \frac{1}{2\pi \sqrt{LC}}$ so, $C = \frac{1}{4\pi^2 f_s^2 L} = \frac{1}{4\pi^2 (15,915)^2 (60 \times 10^{-3})} = \boxed{1.67 \text{ nF}}$

d.) What is the Q_s of the circuit?

solution: $Q_s = \frac{X_L}{R} = \frac{2\pi f_s L}{R} = \frac{2\pi (15,915) (60 \text{ mH})}{900 \Omega} = \boxed{6.67}$


e.) Determine the fractional BW.

solution: $\frac{f_2 - f_1}{f_s} = \frac{BW}{f_s} = \frac{1}{Q_s} = \frac{1}{6.67} = \boxed{0.15}$

L-C Filters



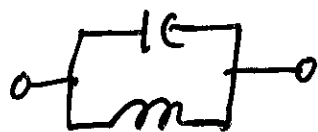
The series LC ckt. looks like a short circuit (Minimum Z) at resonance.




← Also called a "Tank Circuit"

The parallel LC ckt. looks like an open circuit (Maximum Z) at resonance.


ex/

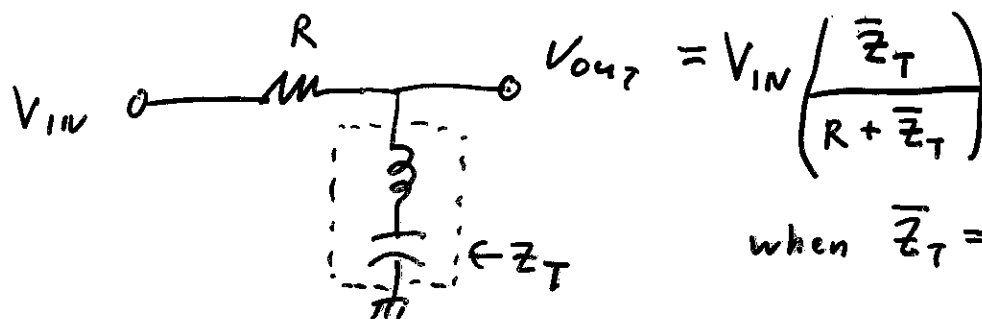


when $Z_T = 0$, $V_{OUT} = 0$

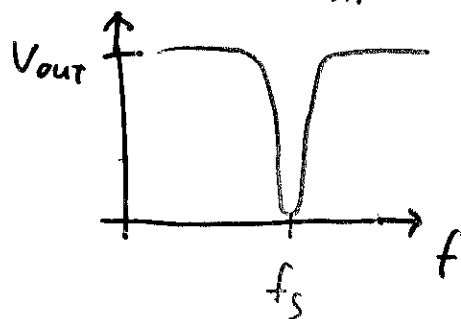

called a "Band Stop" or Notch Filter

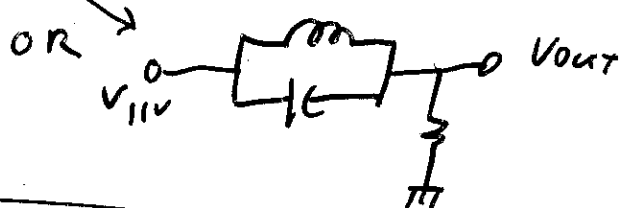


ex/

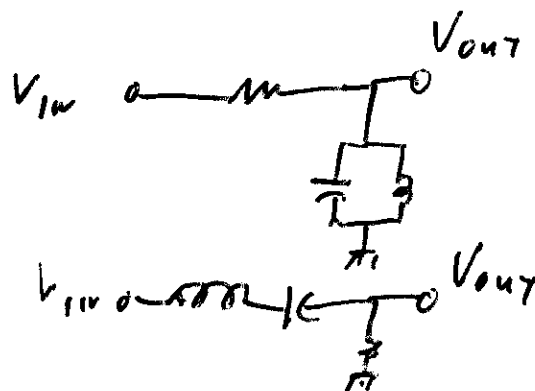

↗ "Band Pass" Filters



Quality Factor Series Resonant Circuits

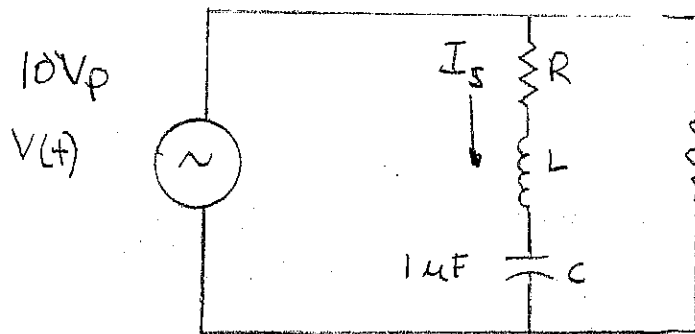

$$V(t) = 10 \sin(2\pi ft)$$

$$Q_s = 5 \quad f_s = \frac{1}{2\pi\sqrt{LC}}$$

Set $f_s = 100 \text{ Hz}$ find L and R

$$\frac{1}{2\pi f_s} = \sqrt{LC} \quad \left(\frac{1}{2\pi f_s}\right)^2 = LC \quad \left(\frac{1}{2\pi f_s}\right)^2 \frac{1}{C} = L \quad \begin{matrix} L \text{ (Henry)} \\ C \text{ (Farads)} \end{matrix}$$

$$\left(\frac{1}{2\pi(100 \text{ Hz})}\right)^2 \frac{1}{1 \times 10^{-6}} = L \Rightarrow L = 2.54 \text{ H}$$

$$\text{For } Q_s = 5 \quad Q_s = \frac{1}{R} \sqrt{\frac{L}{C}} \Rightarrow R = \frac{1}{Q_s} \sqrt{\frac{L}{C}} \quad \begin{matrix} C = 1 \times 10^{-6} \text{ F} \\ L = 2.54 \text{ H} \end{matrix}$$

$$R = \frac{1}{5} \sqrt{\frac{2.54}{1 \times 10^{-6}}} = 318.5 \Omega \quad \text{INCREASE } Q_s \text{ to } 10, 20, 40, 80$$

Keep f_s at 100 Hz Re compute R for new values of Q

$$R_{10} = \frac{1}{10} \sqrt{\frac{2.54}{1 \times 10^{-6}}} = 159.4 \Omega \quad R_{20} = \frac{1}{20} \sqrt{\frac{2.54 \text{ H}}{1 \times 10^{-6} \text{ F}}} = 79.7 \Omega$$

$$R_{40} = \frac{1}{40} \sqrt{\frac{2.54 \text{ H}}{1 \times 10^{-6} \text{ F}}} = 39.9 \Omega \quad R_{80} = \frac{1}{80} \sqrt{\frac{2.54 \text{ H}}{1 \times 10^{-6} \text{ F}}} = 20 \Omega$$

Compute I_s when $V(t) = 10 \sin(2\pi 60t)$ for each
Series Resonant circuit

$$Q = 5 \quad \frac{1}{R_L} = \frac{1}{300} = 0.0033 \text{ v}$$

$$Z_s = 318.5 + j 2\pi 60 (2.54 \text{ H}) + \frac{1}{2\pi 60 1 \times 10^{-6} \text{ F}}$$

$$Z_s = 318.5 + j 958 \Omega - j 2653 \Omega$$

Ex: $Z_5 = 318.5 - 1695j = 1725 \angle -79.1^\circ$

$Y_5 = 5.797 \times 10^{-4} \angle 79.1^\circ$

$Z_{10} = 159.4 - 1695j$ REACTIVE components do not CHANGE

$Z_{10} = 1702.5 \angle -84.6^\circ$

$Y_{10} = 5.5 \times 10^{-4} \angle 84.6^\circ$

$Z_{20} = 79.7 - 1695j = 1697 \angle -87.3^\circ$

$Y_{20} = 5.893 \times 10^{-4} \angle 87.3^\circ$

$Z_{40} = 39.9 - 1695j$

$Z_{40} = 1696 \angle -88.6^\circ$

$Y_{40} = 5.9 \times 10^{-4} \angle 88.6^\circ$

$Z_{80} = 20 - 1695j = 1695.1 \angle -89.3^\circ$ $Y_{80} = 5.99 \times 10^{-4} \angle 89.3^\circ$

Find Total Source Current

$I_s = V_s Y_T$ $Y_{T5} = 0.0033 \angle 0^\circ + 5.797 \times 10^{-4} \angle 79.1^\circ$

$V_{sRMS} = 7.07 \angle 0^\circ$ $Y_{T5} = 0.00346 \angle 9.5^\circ$

$I_T = 7.07 \angle 0^\circ (0.00346 \angle 9.5^\circ) = 0.0244 A \angle 9.5^\circ$

$Q_s = 5$ $\bar{I}_s = \frac{\bar{V}_s}{\bar{Y}_{T5}} \bar{I}_T$ $I_s = \frac{5.797 \times 10^{-4} \angle 79.1^\circ}{0.00346 \angle 9.5^\circ} 0.0244 \angle 9.5^\circ$

$I_s = 0.0041 A \angle 79.1^\circ$

$Q_s = 10$ $Y_{T10} = 0.0033 \angle 0^\circ + 5.5 \times 10^{-4} \angle -84.6^\circ$

$Y_{T10} = 0.00334 \angle 9.3^\circ$

$I_T = 7.07 \angle 0^\circ (0.00334 \angle 9.3^\circ) = 0.024 \angle 9.3^\circ A$

Ex

$$I_s = \frac{Y_{10}}{Y_{T10}} I_T \quad I_s = \frac{5.5 \times 10^{-9} \angle 84.6^\circ}{0.00334 \angle 19.3^\circ} = 0.024 \angle 7.3^\circ$$

$$I_s = 0.00395 \angle 84.6^\circ$$

$$Q_s = 20 \quad Y_{T20} = 0.0033 \angle 0^\circ + 5.89 \times 10^{-4} \angle 87.3^\circ = 0.00338 \angle 10.03^\circ$$

$$Q_s = 40 \quad Y_{T40} = 0.0033 \angle 0^\circ + 5.9 \times 10^{-4} \angle 88.6^\circ = 0.00337 \angle 10.1^\circ$$

$$Q_s = 80 \quad Y_{T80} = 0.0033 \angle 0^\circ + 5.99 \times 10^{-4} \angle 89.3^\circ = 0.00336 \angle 10.3^\circ$$

$$Q_s = 20 \quad I_{T20} = 7.07 \angle 0^\circ (0.00338 \angle 10.03^\circ) = 0.0238 \angle 10.03^\circ A$$

$$Q_s = 40 \quad I_{T40} = 7.07 \angle 0^\circ (0.00337 \angle 10.1^\circ) = 0.0238 \angle 10.1^\circ$$

$$Q_s = 80 \quad I_{T80} = 7.07 \angle 0^\circ (0.00336 \angle 10.3^\circ) = 0.02375 \angle 10.3^\circ$$

$$Q_s = 20 \quad I_s = \frac{Y_{20}}{Y_{T20}} I_{T20} = \frac{5.893 \times 10^{-4} \angle 87.3^\circ}{0.00338 \angle 10.03^\circ} (0.0238 \angle 10.03^\circ)$$

$$I_s = 0.0041 \angle 87.3^\circ A$$

$$Q_s = 40 \quad I_s = \frac{Y_{40}}{Y_{T40}} I_{T40} = \frac{5.9 \times 10^{-4} \angle 88.6^\circ}{0.00337 \angle 10.1^\circ} (0.0238 \angle 10.1^\circ)$$

$$I_s = 0.0042 \angle 88.6^\circ A$$

$$Q_s = 80 \quad I_s = 0.004 \angle 89.3^\circ A$$

RESONANT CIRCUIT APPLICATIONS

SHUNT FILTERS FOR HARMONIC CANCELLATION

HARMONIC - INTEGER MULTIPLE OF BASE Frequency

Ex. base frequency $100 \text{ Hz} = f_b$

1st harmonic 100 Hz $1 \times f_b$ odd harmonic

2nd harmonic 200 Hz $2 \times f_b$ even harmonic


3rd harmonic 300 Hz $3 \times f_b$

nth harmonic $100n \text{ Hz}$ $n \times f_b$

Harmonics occur in power systems & Communications Circuits

Active Circuits - Transistors produce harmonics

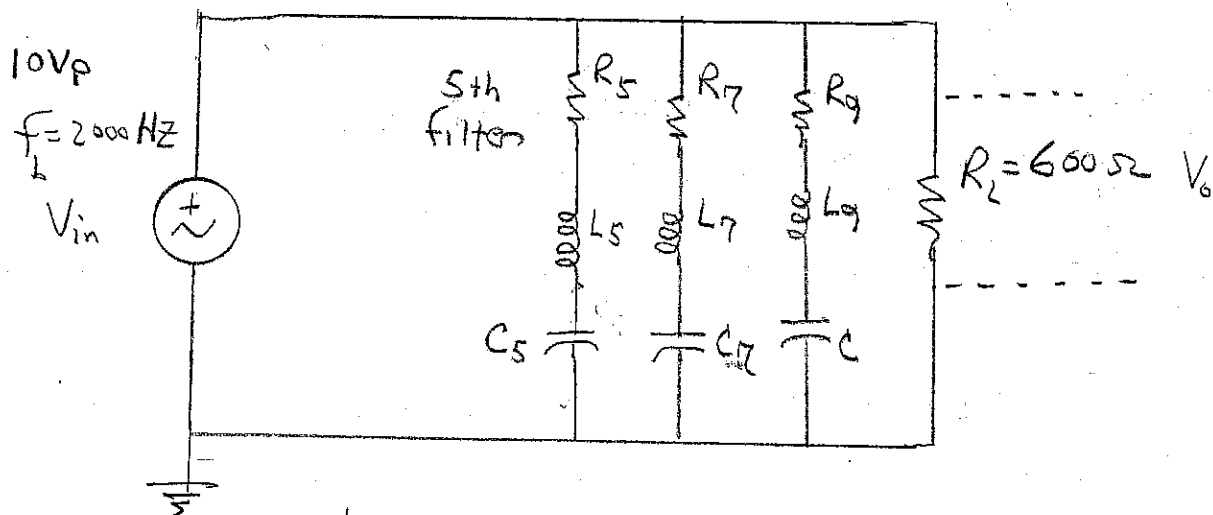Ex. Design a set of series resonant circuits to cancel the 5th, 7th and 9th harmonic of a sinusoidal tone of 2000 Hz . for the circuit below.



Filter $Q = 20$

Ex cont. Inductors available have a value of 100 mH
 with a negligible winding Resistance
 Size the other components and find V_o when V_{in}
 is 10V_p at 2000 Hz

Size Components for 5th harmonic

$$f_5 = 5 \times f_b = 5(2000 \text{ Hz}) = 10,000 \text{ Hz}$$

At Resonance filter should act as a short to
 10 kHz currents.

$$f_5 = \frac{1}{2\pi\sqrt{L_5 C_5}} \quad (1) \quad Q_5 = \frac{1}{R_5} \sqrt{\frac{L_5}{C_5}} \quad (2)$$

100 mH = L_5 only L available

Solve (1) for C

$$f_5 2\pi\sqrt{L_5 C_5} = 1$$

$$\sqrt{L_5 C_5} = \frac{1}{2\pi f_5}$$

$$L_5 C_5 = \left(\frac{1}{2\pi f_5}\right)^2$$

$$C_5 = \left(\frac{1}{2\pi f_5}\right)^2 \frac{1}{L_5}$$

$$C_5 = \left[\frac{1}{2\pi(10000)}\right]^2 \frac{1}{100 \times 10^{-3} \text{ H}}$$

$$C_5 = 2.54 \times 10^{-9} \text{ F}$$

Solve (2) for R

$$Q_5 = \frac{1}{R_5} \sqrt{\frac{L_5}{C_5}}$$

$$R_5 Q_5 = \sqrt{\frac{L_5}{C_5}}$$

$$R_5 = \frac{1}{Q_5} \sqrt{\frac{L_5}{C_5}}$$

$Q_5 = 20$
 for All filters

$$R_5 = \frac{1}{20} \sqrt{\frac{100 \times 10^{-3}}{2.54 \times 10^{-9}}}$$

$$R_5 = 313.7 \Omega$$

for 5th harmonic

$$L_5 = 100 \text{ mH} \quad C_5 = 0.0025 \mu\text{F} \quad R_5 = 313.7 \Omega$$

Ex Cont.

Size Components For 7th Harmonic

$$f_s = 7f_b = 7(2000 \text{ Hz}) = 14,000 \text{ Hz}$$

At Resonance filter will be short to 14 KHz currents

$L_7 = 100 \text{ mH}$ only L available

$$f_s = \frac{1}{2\pi\sqrt{LC}}$$

Solve for C

$$C_7 = \left[\frac{1}{2\pi f_s} \right]^2 \frac{1}{L_7} = \left[\frac{1}{2\pi(14000)} \right]^2 \frac{1}{100 \times 10^{-3} \text{ H}}$$

$$C_7 = \frac{1.294 \times 10^{-10}}{100 \times 10^{-3}} = 1.294 \times 10^{-9} \text{ F}$$

$$R_7 = \frac{1}{Q_s} \sqrt{\frac{L_7}{C_7}} = \frac{1}{20} \sqrt{\frac{100 \times 10^{-3} \text{ H}}{1.294 \times 10^{-9} \text{ F}}} = 440.5 \Omega$$

for 7th Harmonic filter

$$L_7 = 100 \text{ mH} \quad C_7 = 0.0013 \mu\text{F} \quad R_7 = 440.5 \Omega$$

Size Components for 9th Harmonic

$$f_s = 9f_b = 9(2000 \text{ Hz}) = 18,000 \text{ Hz}$$

At Resonance filter will short 18 KHz current


$$C_9 = \left[\frac{1}{2\pi f_s} \right]^2 \frac{1}{L_9} = \left[\frac{1}{2\pi(18 \times 10^3)} \right]^2 \frac{1}{100 \times 10^{-3}} = 7.83 \times 10^{-10} \text{ F}$$

$$R_9 = \frac{1}{20} \sqrt{\frac{100 \times 10^{-3} \text{ H}}{7.83 \times 10^{-10} \text{ F}}} = 565.2 \Omega$$

Ex cont | Components for 9th Harmonic

$$L_9 = 100 \text{ mH} \quad C_9 = 783 \text{ pF} \quad R = 565.2 \Omega$$

CIRCUIT WITH VALUES

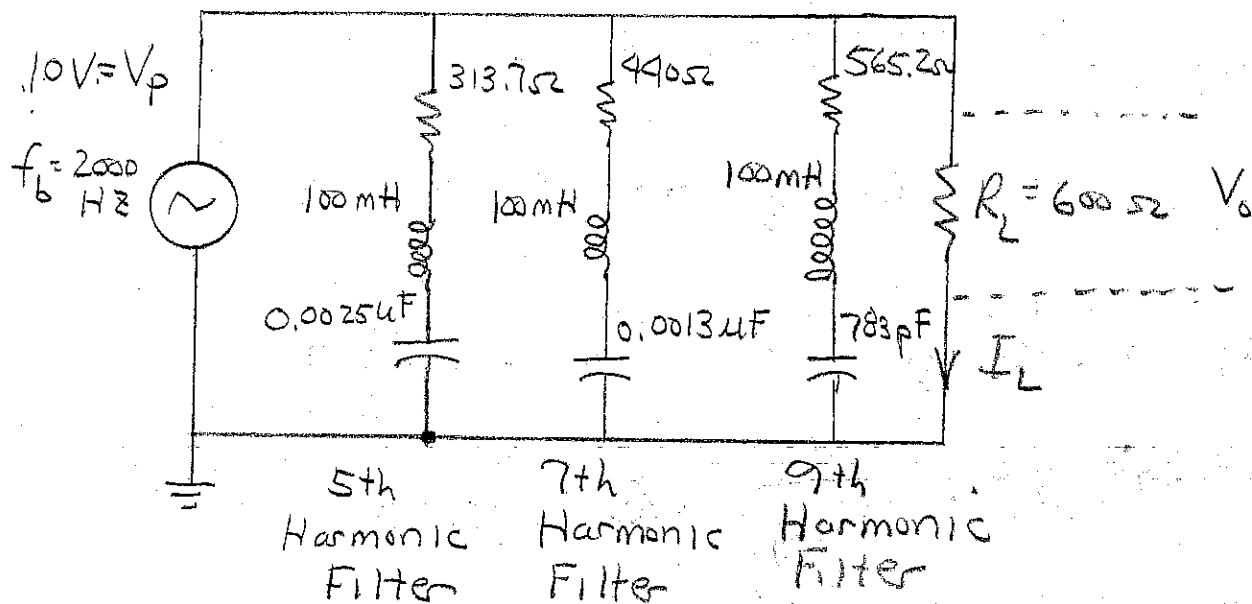

Find CURRENT I_L (Rms) when $f = f_b$

$$V(t) = 10 \sin(2\pi 2000t) \text{ to Phasor } V_{\text{rms}} = \frac{10}{\sqrt{2}} = 7.07$$

$$V_{\text{in}} = 7.07 \angle 0^\circ \quad f_b = 2000 \text{ Hz}$$

$$Z_5 = R_5 + 2\pi f L_5 j + \frac{1}{2\pi f C_5 j} \quad R_5 = 313.7 \Omega$$

$$X_{L5} = 2\pi(2000)(100 \times 10^{-3}) j = 1256 j \Omega$$

$$X_{C5} = \frac{1}{2\pi 2000(0.0025 \times 10^{-6}) j} = -31847 j \Omega$$

$$Z_5 = 313.7 + 1256 j - 31847 j = 313.7 - 30591 j \Omega$$

$$Y_5 = \frac{1}{Z_5} = \frac{1}{313.7 - 30591 j} = 3.351 \times 10^{-7} + 3.269 \times 10^{-5} j \text{ S}$$

Ex cont.

$$Z_7 = R_7 + 2\pi f_b L_7 j + \frac{1}{2\pi f_b C_7} \quad R_7 = 440 \Omega$$

$$X_{L7} = 2\pi(2000)100 \times 10^{-3} = 1256 j \Omega$$

$$X_{C7} = \frac{1}{2\pi(2000)(0.0013 \times 10^{-6})} j = -61244 j \Omega$$

$$Z_7 = 440 \Omega + 1256 j - 61244 j = 440 - 59988 j \Omega$$

$$Y_7 = \frac{1}{Z_7} = \frac{1}{440 - 59988 j} = 1.223 \times 10^{-7} + 1.667 \times 10^{-5} j \text{ S}$$

$$Z_9 = R_9 + 2\pi f_b L_9 j + \frac{1}{2\pi f_b C_9} \quad R_9 = 565.2 \Omega$$

$$X_{L9} = 2\pi(2000)100 \times 10^{-3} = 1256 j$$

$$X_{C9} = \frac{1}{2\pi(2000)(783 \times 10^{-12})} j = -101683 j$$

$$Z_9 = 565.2 + 1256 j - 101683 j = 565.2 - 100427 j$$

$$Y_9 = 5.604 \times 10^{-8} + j9.957 \times 10^{-6} \text{ S}$$

$$Y_L = \frac{1}{R_L} = \frac{1}{600 \Omega} = 0.001667 \text{ S}$$

$$I_s = \frac{V_s}{Z_T} = V_s \frac{1}{Z_T} = V_s Y_T$$

$$Y_T = Y_5 + Y_7 + Y_9 + Y_L$$

Ex cont.

$$Y_T = (3.351 \times 10^{-7} + 3.269 \times 10^{-5} j) + (1.223 \times 10^{-7} + 1.667 \times 10^{-5} j) + \dots + (5.604 \times 10^{-8} + 9.957 \times 10^{-6} j) + (0.001667 + j0)$$

$$Y_T = 0.0016675 + 5.9317 \times 10^{-5} j = 0.001669 \angle 2.04^\circ$$

$$I_S = V_S Y_T = (7.07 \angle 0^\circ)(0.001669 \angle 0.035^\circ) = 0.0118 A \angle 2.04^\circ$$

Find I_L by current division using admittances

Y_f = sum of all filter branches

Y_L = admittance of load

$$I_L = \frac{Y_L}{Y_L + Y_f} I_S \Rightarrow I_L = \frac{0.001667 \angle 0^\circ}{0.001669 \angle 2.04^\circ} 0.0118 A \angle 2.04^\circ$$

$$Y_L + Y_f = Y_T \quad I_L = 0.9988 \angle -2.04^\circ (0.0118 A \angle 2.04^\circ)$$

$$I_L = 0.01178 A \angle 0^\circ \text{ Through Load}$$

All Filter Branches Are High Impedance At Frequency of interest. Almost all current Flows through load R.

CREATE IMPEDANCE PLOT WITH MATHCAD

Plot the total impedance of the circuit as a function of frequency

$N := 5$ Plot the values to 100 kHz

$i := 60$ This is the number of points that are generated in each decade

$k := 140 \dots i \cdot N$ This is the index for the frequency variable.

$k \cdot \frac{1}{i}$ Generate the points

$f_k := 10^{\frac{k}{i}}$ Define the filter values and compute the impedances as a function of frequency

$$R_L := 600 \quad R_5 := 314 \quad R_7 := 440 \quad R_9 := 565$$

$$L_5 := 100 \cdot 10^{-3} \quad L_7 := L_5 \quad L_9 := L_5$$

$$C_5 := 0.0025 \cdot 10^{-6} \quad C_7 := 0.0013 \cdot 10^{-6} \quad C_9 := 783 \cdot 10^{-12}$$

$$Z_5(f) := R_5 + 2 \cdot \pi \cdot f \cdot L_5 \cdot j + \frac{1}{2 \cdot \pi \cdot f \cdot C_5 \cdot j} \quad \text{Fifth harmonic filter impedance}$$

$$Z_7(f) := R_7 + 2 \cdot \pi \cdot f \cdot L_7 \cdot j + \frac{1}{2 \cdot \pi \cdot f \cdot C_7 \cdot j} \quad \text{Seventh harmonic filter impedance}$$

$$Z_9(f) := R_9 + 2 \cdot \pi \cdot f \cdot L_9 \cdot j + \frac{1}{2 \cdot \pi \cdot f \cdot C_9 \cdot j} \quad \text{Ninth harmonic filter impedance}$$

$$Z_L := R_L \quad \text{Load resistance}$$



Total impedance of the network including the load resistance


$$Z_T(f) := \frac{1}{\left(\frac{1}{Z_5(f)} + \frac{1}{Z_7(f)} + \frac{1}{Z_9(f)} + \frac{1}{Z_L} \right)}$$

Plot the magnitude and phase angle of the total impedance as the frequency changes from 1 Hz to 100 kHz

frequency changes from 1 Hz to 100 kHz

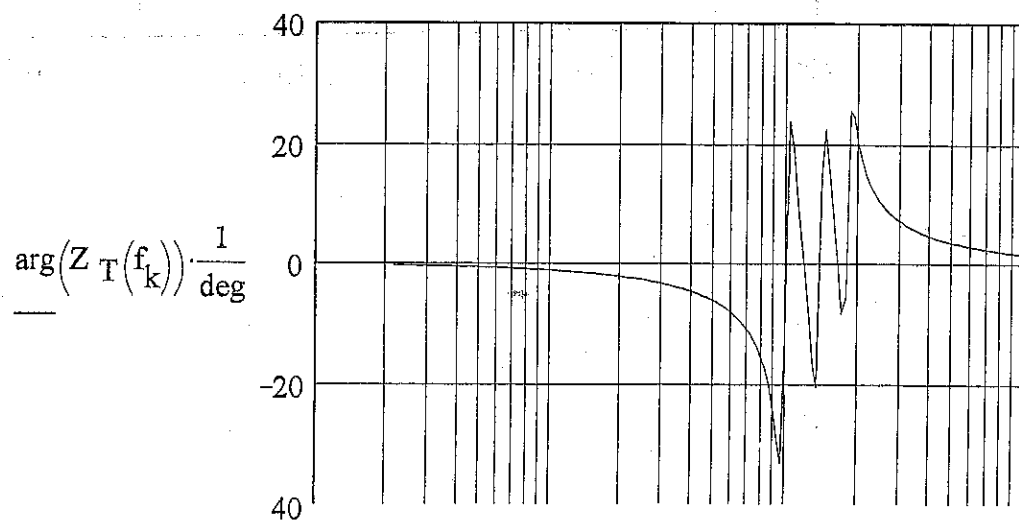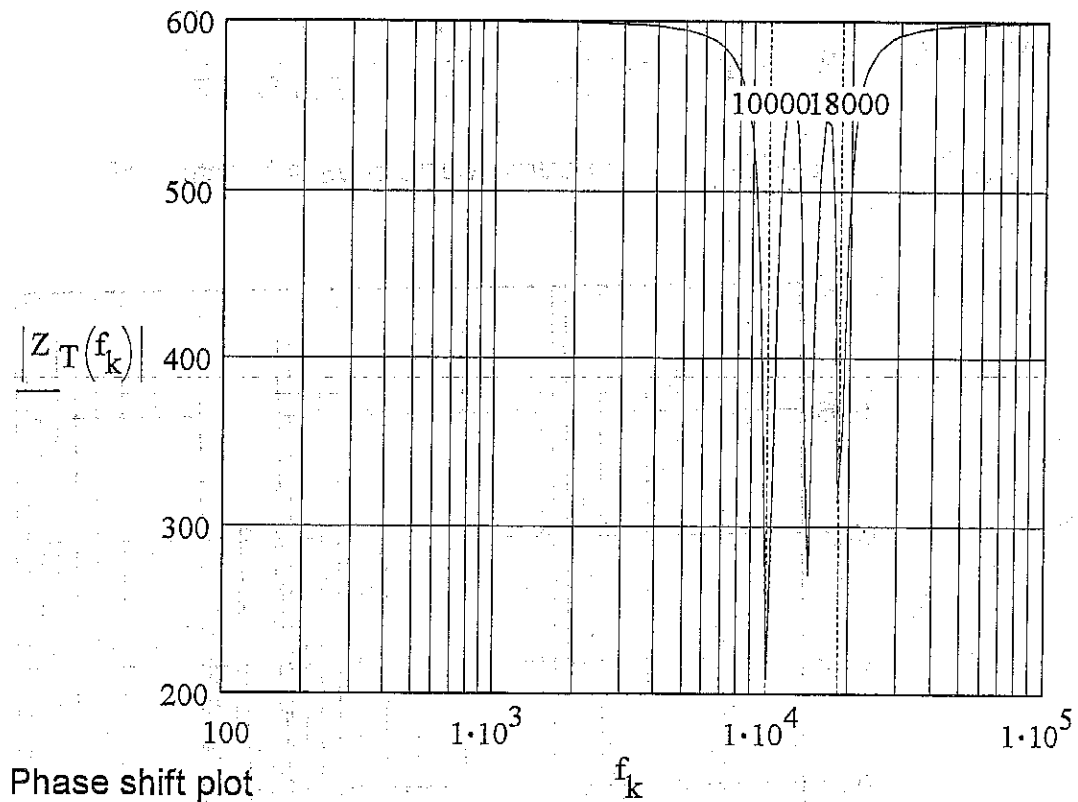Impedance plot for the filter circuit notice that the individual filters interact and reduce the impedance at frequencies beyond the resonance frequency.



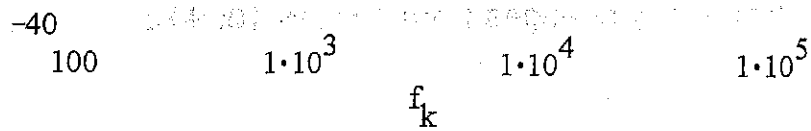

Find the total current as a function of frequency

$$V_s := 7.07 + 0j \quad Y_T(f) := \frac{1}{Z_5(f)} + \frac{1}{Z_7(f)} + \frac{1}{Z_9(f)} + \frac{1}{Z_L}$$

$$I_s(f) := V_s \cdot Y_T(f) \quad \text{The source current as a function of } f$$

