

ET438B Differential Amplifier Homework

In the circuit shown below, R2 is a thermistor. The calibration curve for this device is also shown below. Determine the error voltage that is produced by ignoring the loading effects of the differential amplifier on the sensor circuit when the measured temperature is 60 degrees C.

