

# Lesson 7: Anti-Aliasing Filtering

ET 438b Sequential Control and Data Acquisition  
Department of Technology

Lesson 7\_et438b.pptx

1

## Learning Objectives

After this presentation you will be able to:

- Explain why anti-aliasing filters are used.
- Design a first order anti-aliasing filter using an OP AMP
- Design a 2<sup>nd</sup> order anti-aliasing filter using an OP AMP
- Verify the performance of an anti-aliasing filter using simulation software.

Lesson 7\_et438b.pptx

2

# Anti-Aliasing Filters

Dealing with Aliasing in practical systems

Exact frequency components of a sampled signal are unknown.

Can not determine if signal component is alias or real

Sampling rate limited by hardware selection.

Lab DAQ cards rate is 200 kHz-250 kHz.

$f_{\text{nyquist}} = 100 \text{ kHz} - 125 \text{ kHz}$  sets input frequency limits

Bandwidth limit input signals using anti-aliasing filters to eliminate frequencies above  $f_{\text{nyquist}}$ .


Lesson 7\_et438b.pptx

3


# Anti-Aliasing Filters

**Goal-** reduce amplitude of all frequencies above  $f_{\text{nyquist}}$  to zero level

Ideal low pass filter Bode plot

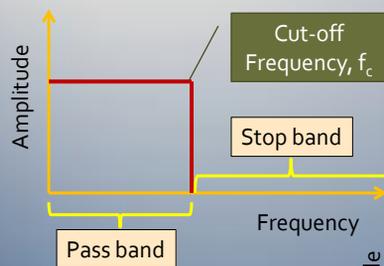

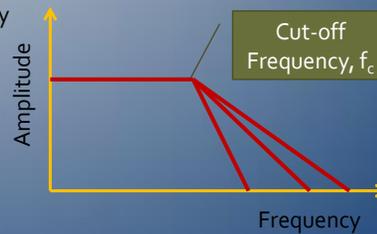Set  $f_c = f_{\text{nyquist}}$  for perfect signal elimination



Practical (Butterworth) filters have sloping characteristics


- 1<sup>st</sup> Order: -20 dB/decade
- 2<sup>nd</sup> Order: -40 dB/decade
- 3<sup>rd</sup> Order: -60 dB/decade

Lesson 7\_et438b.pptx

4

## Anti-Aliasing Filters: OP AMP Circuits

### First order Butterworth filter

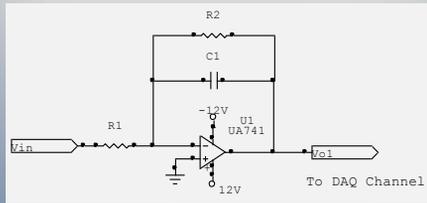

#### Design formulas

$$A_v = \frac{-R2}{R1} \quad \text{Voltage gain in the pass band}$$

$$f_c = \frac{1}{2\pi \cdot R2 \cdot C1} \quad \text{Cut-off frequency (Hz)}$$

#### Design Procedure

- 1.) Determine the acceptable level of signal gain,  $A_v$ , at sampling frequency  $f_s$
- 2.) Use the formula below to determine the value of  $f_c$  based on the designed signal gain

$$f_c = \frac{f_s}{2 \cdot \sqrt{\frac{1-A_v^2}{A_v^2}}} \quad \text{for } A_v < 1$$

3. Select a value of  $C1$  from standard values and compute value of  $R2$

Lesson7\_et438b.pptx

5

## Anti-Aliasing Filters: OP AMP Circuits

### Design Procedure (continued)

- 4.) Set  $R1=R2$  to give pass band gain of -1 (0 dB). Amplify signal after filtering to reduce noise and unwanted signal components. (e.g. 60 Hz)

**Design Example:** A data acquisition system samples an analog signal at  $T_s=0.0004$  seconds. Design a 1<sup>st</sup> order anti-aliasing filter that will reduce the voltage level of all signal above the Nyquist frequency to 0.4

Solution: Determine the sampling frequency from  $T_s$  then find the  $f_{\text{nyquist}}$

$$f_s = \frac{1}{T_s} = \frac{1}{0.0004 \text{ s}} = 2500 \text{ Hz} \quad f_{\text{nyquist}} = \frac{f_s}{2} = \frac{2500 \text{ Hz}}{2} = 1250 \text{ Hz}$$


Find the value of  $f_c$  for the given level of  $A_v$  above  $f_{\text{nyquist}}$

$$f_c = \frac{f_s}{2 \cdot \sqrt{\frac{1-A_v^2}{A_v^2}}} = \frac{2500 \text{ Hz}}{2 \cdot \sqrt{\frac{1-0.4^2}{0.4^2}}} = \frac{2500 \text{ Hz}}{2 \cdot \sqrt{5.25}} = 546 \text{ Hz}$$

Lesson7\_et438b.pptx

6

### Design Example (continued)

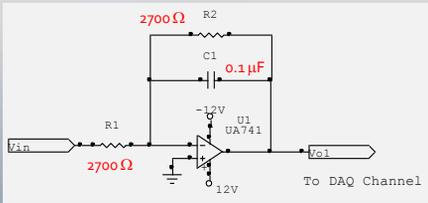

Set  $R_1=R_2$  to give gain of -1

Design complete. Check result with circuit simulation.


Select a capacitor value of  $0.1 \mu\text{F}$ .  
Use larger values for lower  $f_c$ 's to keep values of resistors in range of  $1\text{k}$  to  $82\text{k}\Omega$

$$f_c = \frac{1}{2\pi \cdot R_2 \cdot C_1} \rightarrow R_2 = \frac{1}{2\pi \cdot C_1 \cdot f_c}$$

$$R_2 = \frac{1}{2\pi \cdot 0.1 \times 10^{-6} \cdot 546} = 2916 \Omega$$

Select standard value of  $2700 \text{ ohms}$  and compute value of  $f_c$

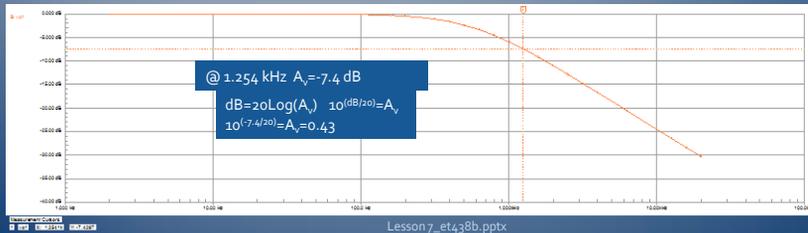
$$C_1 = \frac{1}{2\pi \cdot 0.1 \times 10^{-6} \cdot 2700} = 590 \text{ Hz}$$



Lesson7\_et438b.pptx

## Anti-Aliasing Filters- 2<sup>nd</sup> Order Filters

### Second order Butterworth filter

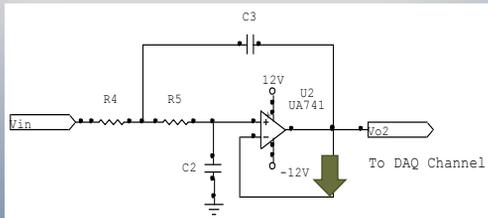

Unity gain is fixed by negative feedback loop in this design.

Use same design procedure as 1<sup>st</sup> order filter but use following formula to find cut-off frequency.

Design formulas

$A_v = 1$  Voltage gain in the pass band

$$f_c = \frac{1}{2\pi \cdot \sqrt{R_4 \cdot R_5 \cdot C_3 \cdot C_2}} \text{ Cut-off frequency (Hz)}$$

With  $R_4 = R_5$  and  $C_3 = 2 \cdot C_2$

$$f_c = \frac{f_s}{2 \cdot \sqrt[4]{\frac{1-A_v^2}{A_v^2}}} \text{ for } A_v < 1$$

2<sup>nd</sup> order filter produces -40 dB/decade rolloff in stop band

Lesson7\_et438b.pptx

## Anti-Aliasing 2<sup>nd</sup> Order Filter Design

**Design Example 2:** Repeat the design of the 1<sup>st</sup> order filter example using a 2<sup>nd</sup> order filter

$T_s=0.0004$  seconds sampling. Design a 2<sup>nd</sup> order anti-aliasing filter that will reduce the voltage level of all signal above the Nyquist frequency to 0.4

Same  $f_s$  and  $f_{\text{nyquist}}$  as previous case

$$f_s = \frac{1}{T_s} = \frac{1}{0.0004 \text{ s}} = 2500 \text{ Hz} \quad f_{\text{nyquist}} = \frac{f_s}{2} = \frac{2500 \text{ Hz}}{2} = 1250 \text{ Hz}$$


Find the value of  $f_c$  for the given level of  $A_v$  using 2<sup>nd</sup> order filter formula

$$f_c = \frac{f_s}{2 \cdot \sqrt{\frac{1-A_v^2}{A_v^2}}} = \frac{2500 \text{ Hz}}{2 \cdot \sqrt{\frac{1-0.4^2}{0.4^2}}} = \frac{2500 \text{ Hz}}{2 \cdot \sqrt{5.25}} = 826 \text{ Hz}$$

Lesson7\_et438b.pptx

9

### Design Example (continued)

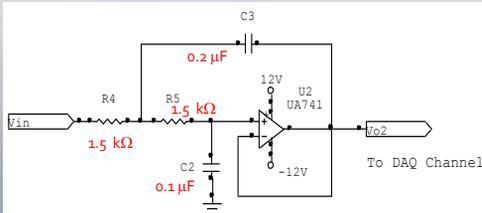

Select value of  $C_2$  and compute  $C_3$ .  
Let  $C_2=0.1 \mu\text{F}$  so.....

$$C_3 = 2 \cdot C_2 = 2 \cdot (0.1 \mu\text{F}) = 0.2 \mu\text{F}$$

Use design formulas to find value of  $R_4=R_5$

$$f_c = \frac{1}{2\pi \cdot \sqrt{R_4 \cdot R_5 \cdot C_3 \cdot C_2}} \quad \text{With } R_4 = R_5 \text{ and } C_3 = 2 \cdot C_2$$

$$f_c = \frac{1}{2\pi \cdot \sqrt{R_4^2 \cdot 2 \cdot C_2^2}} = \frac{1}{2\pi \cdot \sqrt{2} \cdot R_4 \cdot C_2}$$

Solve for  $R_4$  given  $C_2$  and  $f_c$

$$f_c = \frac{1}{2\pi \cdot \sqrt{2} \cdot R_4 \cdot C_2} \quad \Rightarrow \quad R_4 = \frac{1}{2\pi \cdot \sqrt{2} \cdot C_2 \cdot f_c}$$

$$R_4 = \frac{1}{2\pi \cdot \sqrt{2} \cdot C_2 \cdot f_c}$$

$$R_4 = \frac{1}{2\pi \cdot \sqrt{2} \cdot 0.1 \times 10^{-6} \text{ F} \cdot 826 \text{ Hz}}$$

$$R_4 = 1363 \Omega = R_5$$


Use standard value of 1.5k.  
Response very sensitive to R values

Lesson7\_et438b.pptx

10
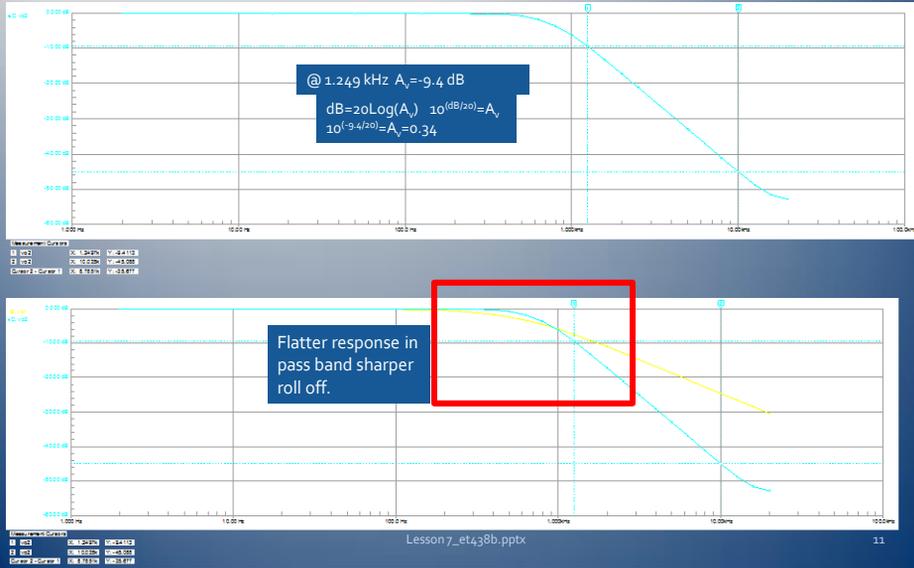
## Design Example (continued)

Design complete. Check result with circuit simulation.



# End Lesson 7: Anti-Aliasing Filtering

ET 438b Sequential Control and Data Acquisition

Department of Technology