

ET 332b  
3 Phase System Homework

For the circuit given below, compute:

- a.) the magnitude of line-to-neutral voltage
- b.) the magnitude of the line current
- c.) the total apparent power absorbed in the circuit
- d.) the apparent power absorbed in one phase
- e.) the power factor of the load

