

Lesson 9: Practical Transformer Model and Calculations

ET 332b Ac Motors, Generators and Power Systems

Lesson 9_et332b.pptx

Lesson 9_et332b.pptx


Learning Objectives

After this presentation you will be able to:


- Identify factors that contribute to non-ideal operation of power transformers
- Draw the schematic model of a non-ideal transformer and include all parameters
- Reflect impedances through a non-ideal transformer
- Identify step-up and step down transformer connections
- Compute transformer voltages and currents using the full circuit model.

Transformer Circuit Model

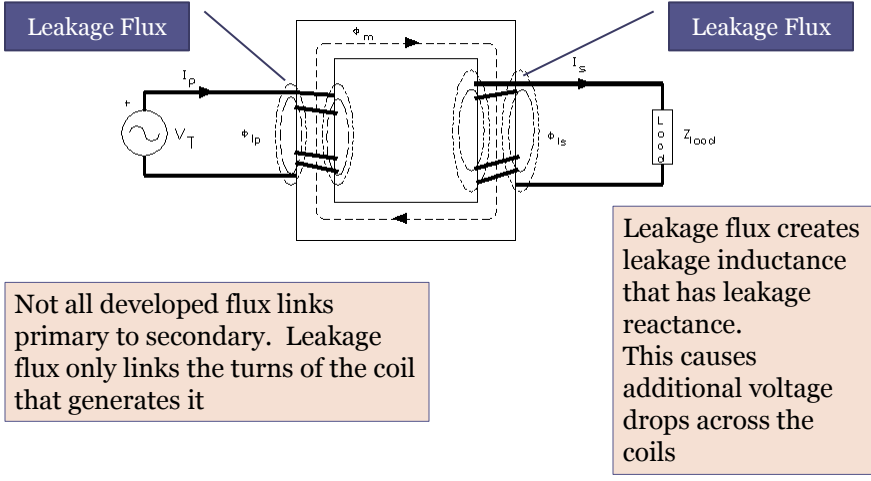Equivalent Circuit Model for Leakage and Coil Resistance




Leakage Reactance and Voltage Drop

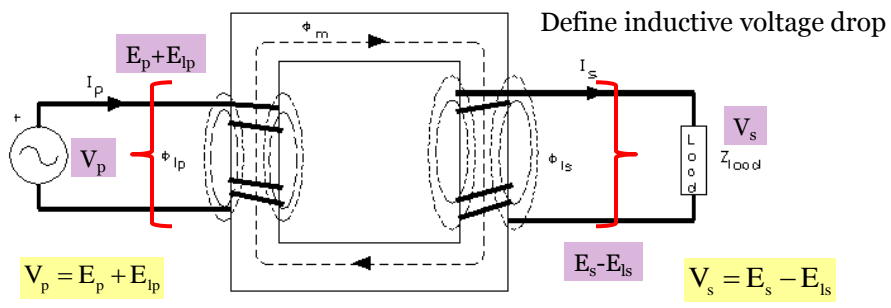

- Where:
- V_p = net voltage induced in primary
 - E_p = voltage induced due to mutual flux
 - E_{lp} = voltage induced in primary due to leakage
 - V_s = net voltage induced in secondary
 - E_s = voltage induced due to mutual flux
 - E_{ls} = voltage induced in the secondary due to leakage

Coil Resistance and Total Voltage Drop

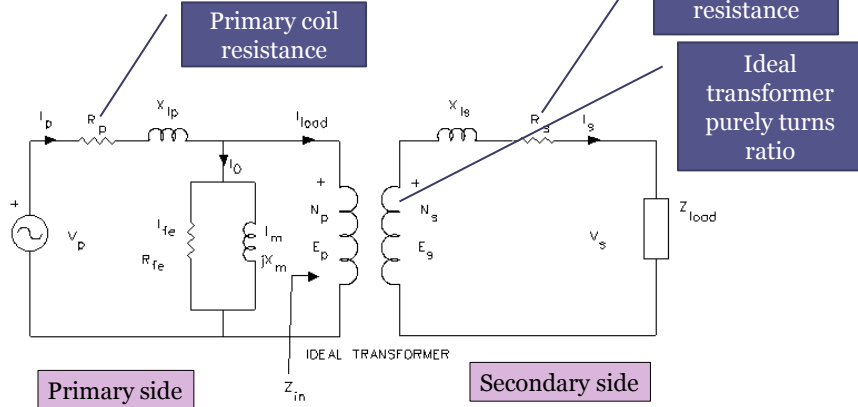Resistance of windings modeled by lumped resistance




Primary side

Secondary side

Circuit Model of Non-ideal Transformers

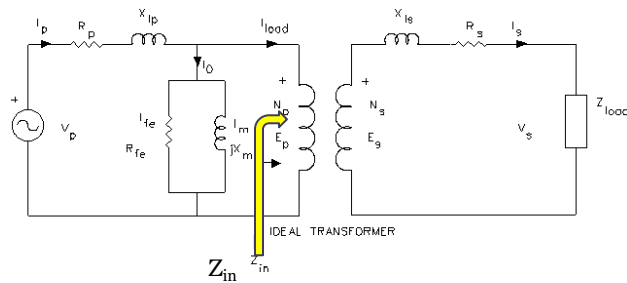Use ideal transformer impedance formulas to get equivalent Z_{in}
 Z_{in} is called the reflected or referred impedance



From ideal transformers

$$Z_{in} = a^2 \cdot \left(\frac{V_s}{I_s} \right) \quad a^2 = \left(\frac{N_p}{N_s} \right)^2$$

Circuit Model of Non-ideal Transformers

From Ohm's Law

$$\left(\frac{V_s}{I_s}\right) = (R_s + j \cdot X_{ls}) + Z_{load}$$

$$Z_{in} = a^2 \cdot (R_s + j \cdot X_{ls}) + a^2 \cdot Z_{load}$$

$$Z_{in} = a^2 \cdot R_s + j \cdot a^2 \cdot X_{ls} + a^2 \cdot Z_{load}$$

Where: $a^2 \cdot R_s$ = secondary R **referred to primary**


$a^2 \cdot X_{ls}$ = secondary X_{ls} **referred to primary**

$a^2 \cdot Z_{load}$ = load impedance **referred to primary**

Referring the secondary impedances to the primary side effectively removes the need for the ideal transformer. The turns ratio captures all the effects

Circuit Model of Non-ideal Transformers

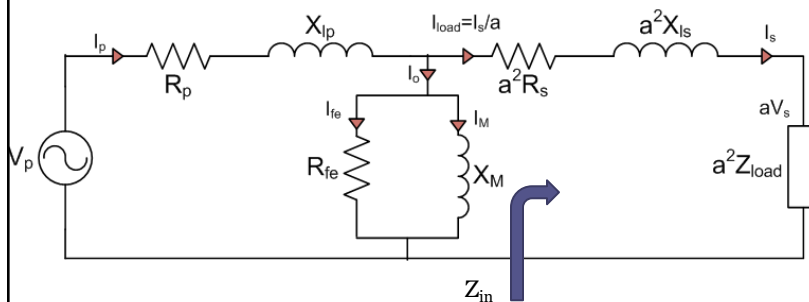
Transformer circuit with ideal turns ratio removed



Can solve this circuit to find anything about non-ideal transformer operation. Voltage drop, power losses, primary and secondary currents and voltages.

Simplified Circuit Model

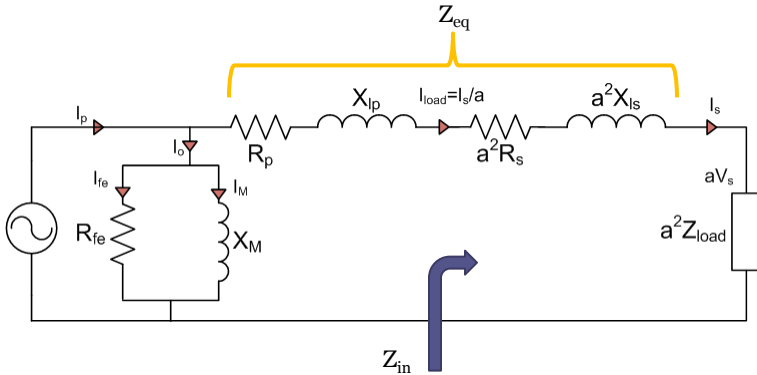
Another simplifying assumption: $I_0 \ll I_{load}$. Combine primary and secondary impedances



Equivalent series impedance referred to primary side $Z_{eq} = (R_p + a^2 \cdot R_s) + j \cdot (X_{lp} + a^2 \cdot X_{ls})$

Simplified Model-Referred to Secondary

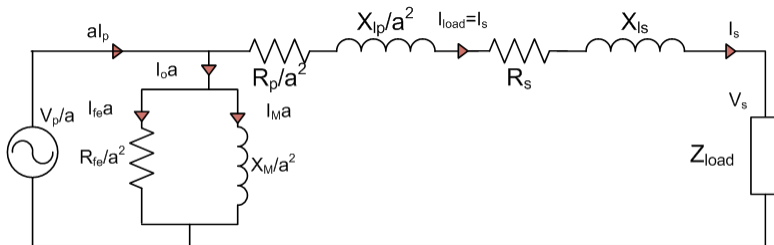The impedance Z_{eq} can be referred to the secondary side instead. Just divide the impedance components by a^2 .



Resistance of the primary winding referred to secondary

Leakage reactance of the primary winding referred to secondary


Equivalent impedance referred to the secondary side

$$Z_{eqs} = \left(\frac{R_p}{a^2} + R_s \right) + j \cdot \left(\frac{X_{lp}}{a^2} + X_{ls} \right)$$

Series Impedance of Transformers

Power transformers are bi-directional devices. They can operate with a V source attached to either primary or secondary winding.

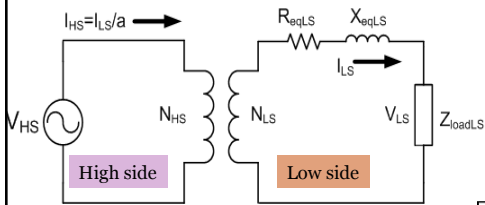Step-down operation: load connected to low voltage coil



Referring Z's to low side

$$Z_{eqLS} = \frac{Z_{eqHS}}{a^2}$$


$$Z_{loadLS} = \frac{Z_{loadHS}}{a^2}$$

Referring Z's to high side

$$Z_{eqHS} = a^2 \cdot Z_{eqLS}$$

$$Z_{loadHS} = a^2 \cdot Z_{loadLS}$$

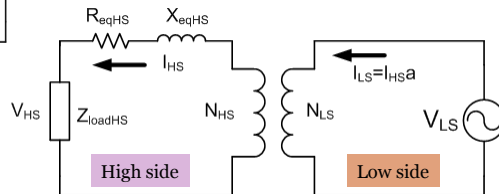Step-up operation: load connected to the high voltage winding



Transformer Problems

Example 9-1: A 100 kVA, 7200 -480 V 60 Hz single phase transformer has the following parameters all given in ohms:

$$R_{LS} = 0.00800 \quad R_{HS} = 1.96 \quad R_{feHS} = 53.2$$


$$X_{LS} = 0.01510 \quad X_{HS} = 4.55 \quad X_{MHS} = 7800$$

This transformer is operated in the step-down mode and delivers 75% of its rated power to a load that has a power factor of 0.93 lagging. Find:

- draw the equivalent circuit model of the transformer with the equivalent series Z's referred to the high voltage side
- find the total Z_{in} of the transformer at the high side
- input Z of the transformer with the load disconnected
- input voltage at 75% load required to maintain rated load voltage
- exciting current with the load disconnected.

Example 9-1 Solution (1)

Draw circuit model and find Z_{eq}

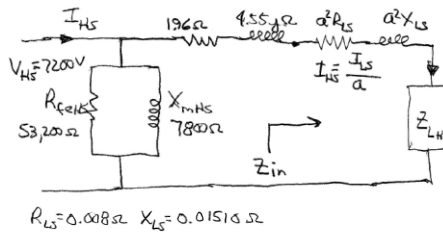

$$R_{LS} = 0.008 \Omega \quad X_{LS} = 0.0151 j \Omega$$

$$\begin{aligned} R_{eq} &= R_{HS} + a^2 R_{LS} & X_{eq} &= X_{HS} + a^2 X_{LS} \\ R_{eq} &= 1.96 + (15)^2 (0.008) & X_{eq} &= 4.55 + (15)^2 (0.0151j) \\ R_{eq} &= 3.76 \Omega & X_{eq} &= 7.9475 \Omega \end{aligned}$$

$$Z_{eq} = 3.76 + j 7.9475 \Omega \quad \leftarrow \text{Ans}$$

$$\begin{aligned} \alpha &= \frac{V_p}{V_s} = \frac{7200V}{480V} \\ \alpha &= 15 \end{aligned}$$

$$\begin{aligned} F_p &= 0.93 & Z_{LHS} &= \alpha^2 Z_{LVS} \\ V_H &= \alpha V_{LS} \end{aligned}$$

Find Load Current

$$\begin{aligned} S_L &= 100 \text{ kVA} (0.75) \\ S_L &= 75 \text{ kVA} \end{aligned}$$

$$\begin{aligned} I_{LS} &= \frac{75 \text{ kVA}}{0.48 \text{ kV}} \\ I_{LS} &= 156.25 \text{ A} \end{aligned}$$

$$\begin{aligned} \theta &= \cos^{-1}(0.93) \\ \theta &= -21.57^\circ \text{ Lagging} \end{aligned}$$

Example 9-1 Solution (2)

b) Find the Z_{in} as seen on the HV side

$$\begin{aligned} \bar{Z}_L &= \frac{\bar{V}_L}{\bar{I}_L} & \bar{Z}_L &= \frac{480 \angle 0^\circ}{156.25 \angle -21.57^\circ} \\ \bar{Z}_L &= 3.072 \angle 21.57^\circ \Omega & \bar{Z}_{LHS} &= \alpha^2 \bar{Z}_L \end{aligned}$$

$$\bar{Z}_{LHS} = (15)^2 (3.072 \angle 21.57^\circ)$$

$$\bar{Z}_{LHS} = 691 \angle 21.57^\circ \Omega$$

$$\bar{Z}_{LHS} = 642.8 + j 254.5 \Omega$$

$$\bar{Z}_{in} = \bar{Z}_{eq} + \bar{Z}_{LHS}$$


$$\bar{Z}_{in} = (3.76 + j 7.9475) + (642.8 + j 254.5)$$

$$\bar{Z}_{in} = 646.6 + j 262.5 \Omega$$

$$\bar{Z}_{in} = 697.7 \angle 22.04^\circ \quad \leftarrow \text{Ans}$$


Example 9-1 Solution (3)

c) Z_{in} with the load disconnected

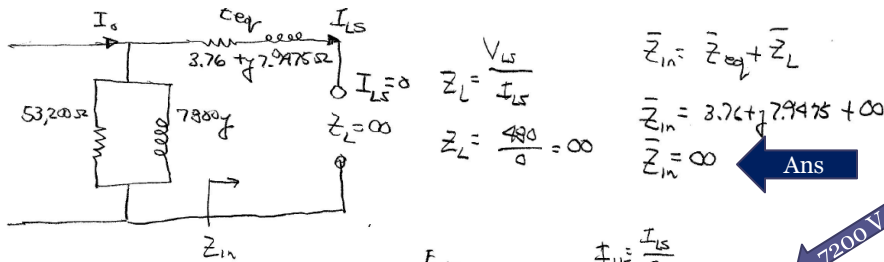

d) Input voltage required at load to maintain $V_s = 480$ V

$V_{HS} = V_{LS} a$
 $V_{HS} = 480 (15)$
 $V_{HS} = 7200$ V

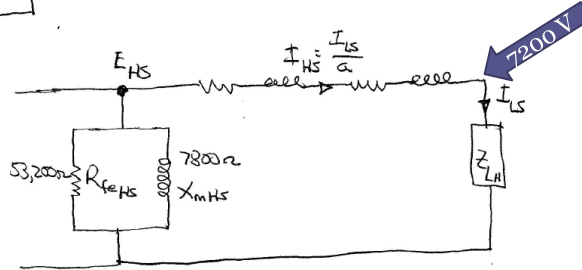


Example 9-1 Solution (4)

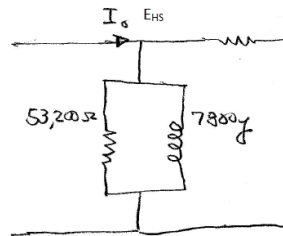e) Exciting current with load disconnected

With load disconnected only current is I_0

$\bar{E}_{HS} = \bar{I}_{HS} \bar{Z}_{in}$
 $\bar{I}_{HS} = \frac{156.25 \angle -21.57^\circ}{15}$
 $\bar{I}_{HS} = 10.42 \angle -21.57^\circ$ A
 $\bar{E}_{HS} = (10.42 \angle -21.57^\circ) (6977.7 \angle 22.06^\circ)$
 $\bar{E}_{HS} = 7270 \angle 0.49^\circ$ V ← Ans



Find $R_{fHS} // X_{mHS} = Z_0$

Remember $I_0 = Y_t E_{HS}$

Example 9-1 Solution (5)

$$Y_T = \frac{1}{R_{\text{feHS}}} + \frac{1}{X_{\text{mHS}}}$$

$$Y_T = \frac{1}{53,200} + \frac{1}{7800j}$$

$$Y_T = 1.8797 \times 10^{-5} - j1.282 \times 10^{-4} \text{ S}$$

$$Y_T = 1.295 \times 10^{-4} \angle -81.7^\circ \text{ S}$$

$$\bar{I}_0 = (1.295 \times 10^{-4} \angle -81.7^\circ) (7270 \angle 0.49^\circ)$$

$$\bar{I}_0 = 0.9415 \angle -81.2^\circ \text{ A} \quad \leftarrow \text{Ans}$$

Find I_0 as percent of rated load I

$$I_{\text{pr}} = \frac{S_{\text{rated}}}{V_{\text{pr}}} = \frac{100,000 \text{ VA}}{7200 \text{ V}} = 13.89 \text{ A}$$

$$I_0\% = \frac{I_0}{I_{\text{pr}}} = \frac{0.9415 \text{ A}}{13.89 \text{ A}} \times 100\%$$

$$I_0\% = 6.8\%$$


Typical values: 3-5% of rated for large power transformers.

Transformer Voltage Drop and Impedance

Example 9-2: The equivalent resistance and reactance of a 50 kVA, 2400-480 V transformer's windings are $R = 2.80 \Omega$ and $X = 6.00 \Omega$ (high side). A load of $10 \angle 20^\circ$ is connected to the low voltage side. Determine:

- equivalent impedance of the transformer and load combined
- primary current if rated voltage is applied to primary
- voltage across the load.

Example 9-2 Solution (1)

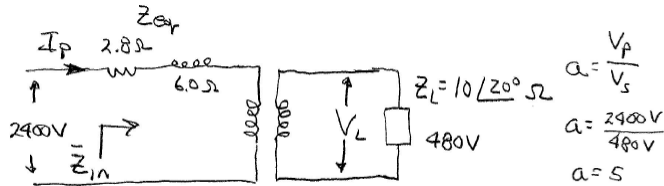

$$a = \frac{V_p}{V_s}$$

$$a = \frac{2400\text{V}}{480\text{V}}$$

$$a = 5$$

Refer Z_L to primary side

$$\bar{Z}_{LHS} = a^2 Z_L$$

$$\bar{Z}_{LHS} = (5)^2 (10\angle 20^\circ)$$

$$\bar{Z}_{LHS} = 250\angle 20^\circ$$

$$\bar{Z}_{in} = \bar{Z}_{eq} + \bar{Z}_{LHS}$$

$$\bar{Z}_{in} = 2.8 + j6.0 + 250\angle 20^\circ$$

$$\bar{Z}_{in} = (2.8 + j6.0) + (234.9 + j85.5)$$

$$\bar{Z}_{in} = 237.7 + j91.5$$

$$\bar{Z}_{in} = 254.7\angle 21.05^\circ \Omega$$

Ans

Example 9-2 Solution (2)

Find the current and voltage on primary

$$\bar{I}_p = \frac{\bar{V}_p}{\bar{Z}_{in}} \quad \bar{I}_p = \frac{2400\angle 0^\circ}{254.7\angle 21.05^\circ} = 9.423\angle -21.05^\circ \text{ A} \quad \bar{Z}_{eq} = 6.62\angle 65^\circ \Omega$$

$$\bar{V}_{LHS} = \bar{V}_p - \bar{I}_p \bar{Z}_{eq}$$

$$\bar{V}_{LHS} = 2400\angle 0^\circ - (9.423\angle -21.05^\circ)(6.62\angle 65^\circ)$$

$$\bar{V}_{LHS} = 2400\angle 0^\circ - 62.4\angle 43.95^\circ$$

$$\bar{V}_{LHS} = 2400 - (44.92 + j43.3)$$

$$\bar{V}_{LHS} = 2355 - j43.2 = 2355\angle -1.05^\circ$$

Ans

$$V_{LW} = \frac{2355\angle -1.05^\circ}{5}$$

Now refer to secondary side

$$V_{LW} = \frac{V_{LHS}}{a}$$

$$V_{LW} = 471\angle -1.05^\circ \text{ V}$$

Ans

End Lesson 9: Practical Transformer Model and Calculations

ET 332b Ac Motors, Generators and Power Systems