ET 332b
Power Factor Calculations

A load is connected to a voltage source operating at 60 Hz and 1320 volts. The load dissipates 100 kW with a power factor of 0.867 lagging. Specifiy the capacitance in microfarads to correct the load power factor to:

a.)   0.895 lagging
b.)   0.95 leading